
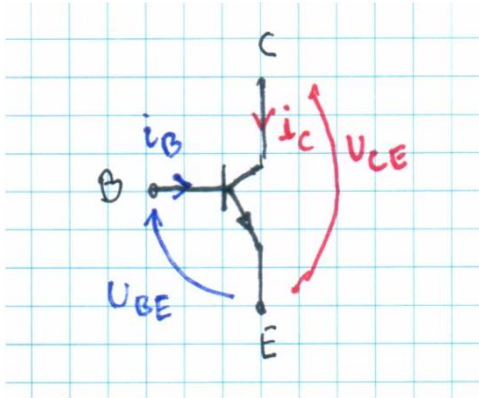


# Charakterystyki tranzystora i jego matematyczny opis (model) zlinearyzowany

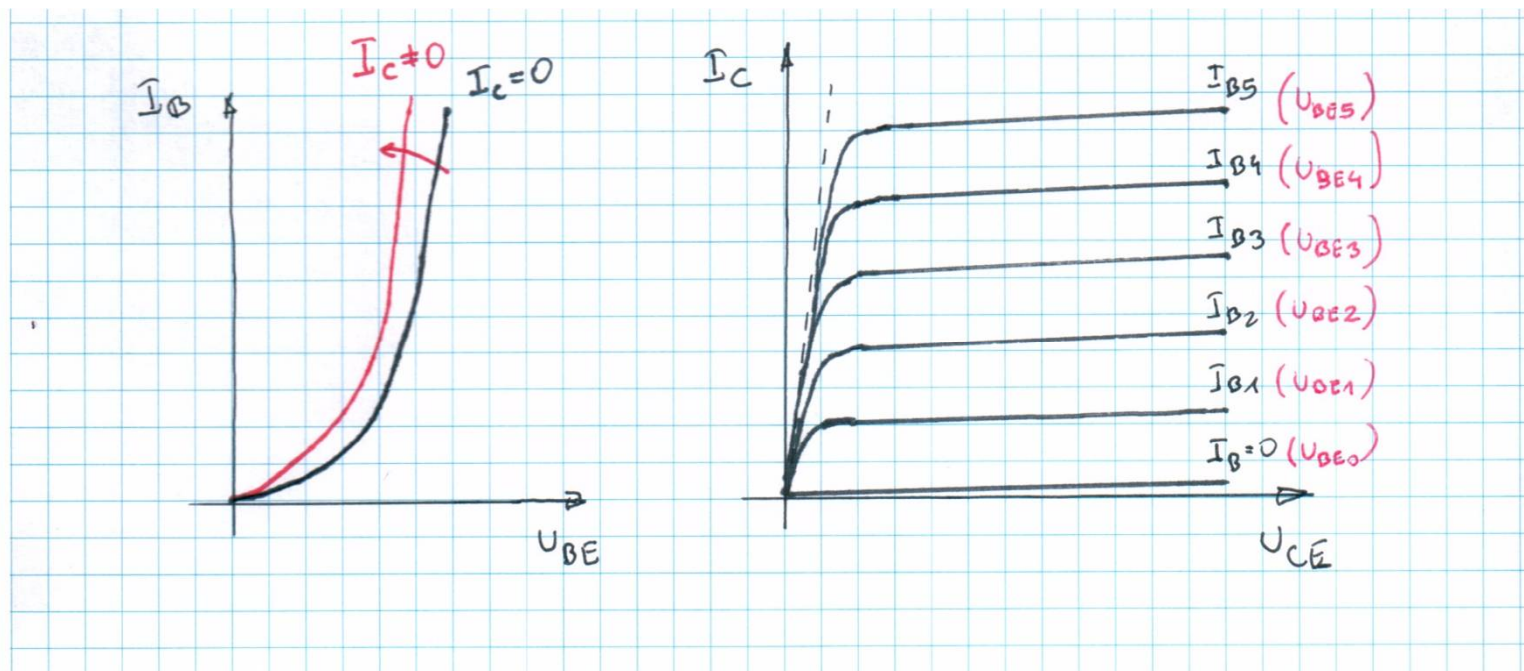
# Charakterystyki tranzystora i jego matematyczny opis (model) zlinearyzowany




Tranzystor n-p-n (npn)



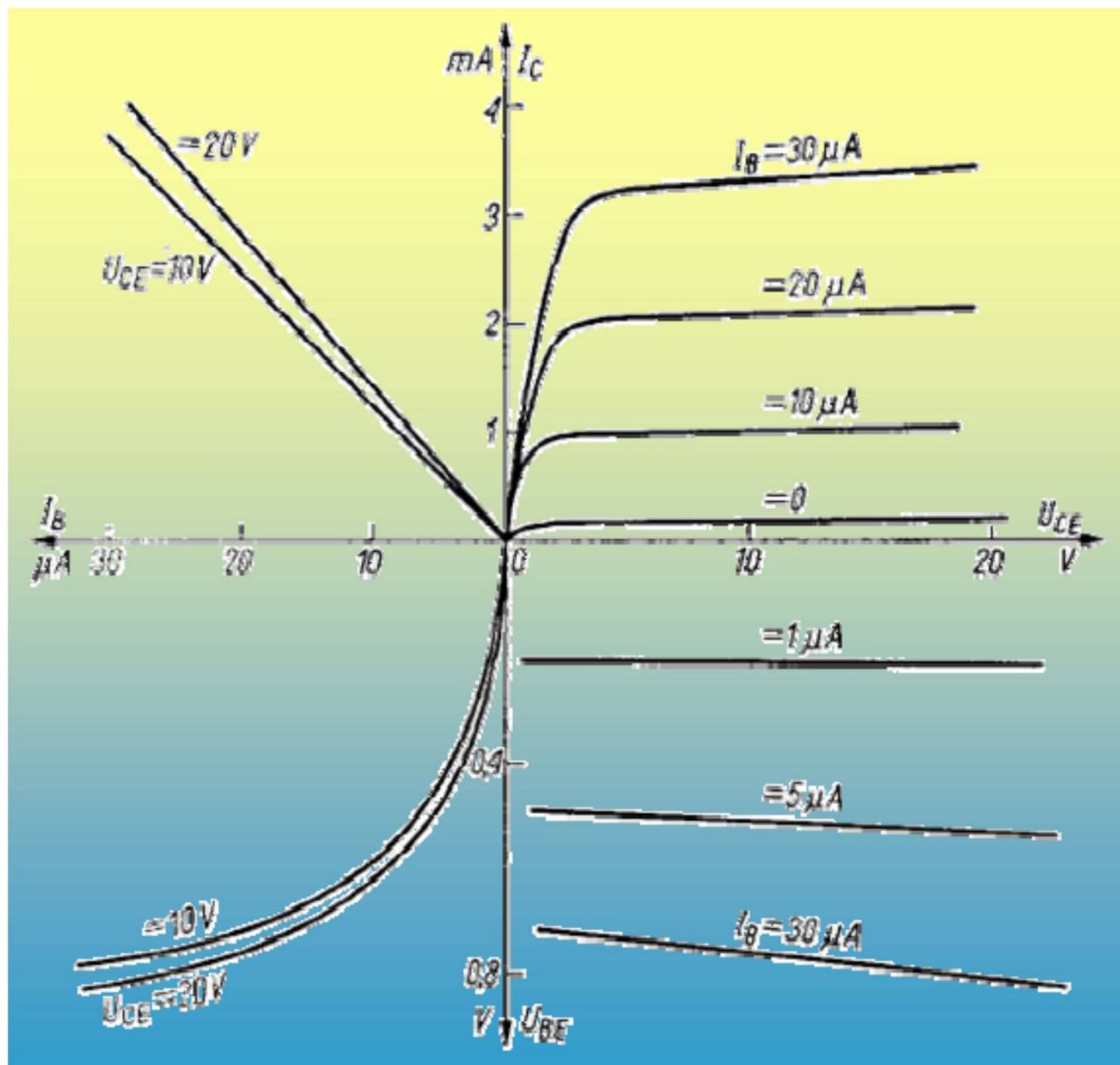
## Charakterystyki katalogowe tranzystora





# Charakterystyki katalogowe tranzystora

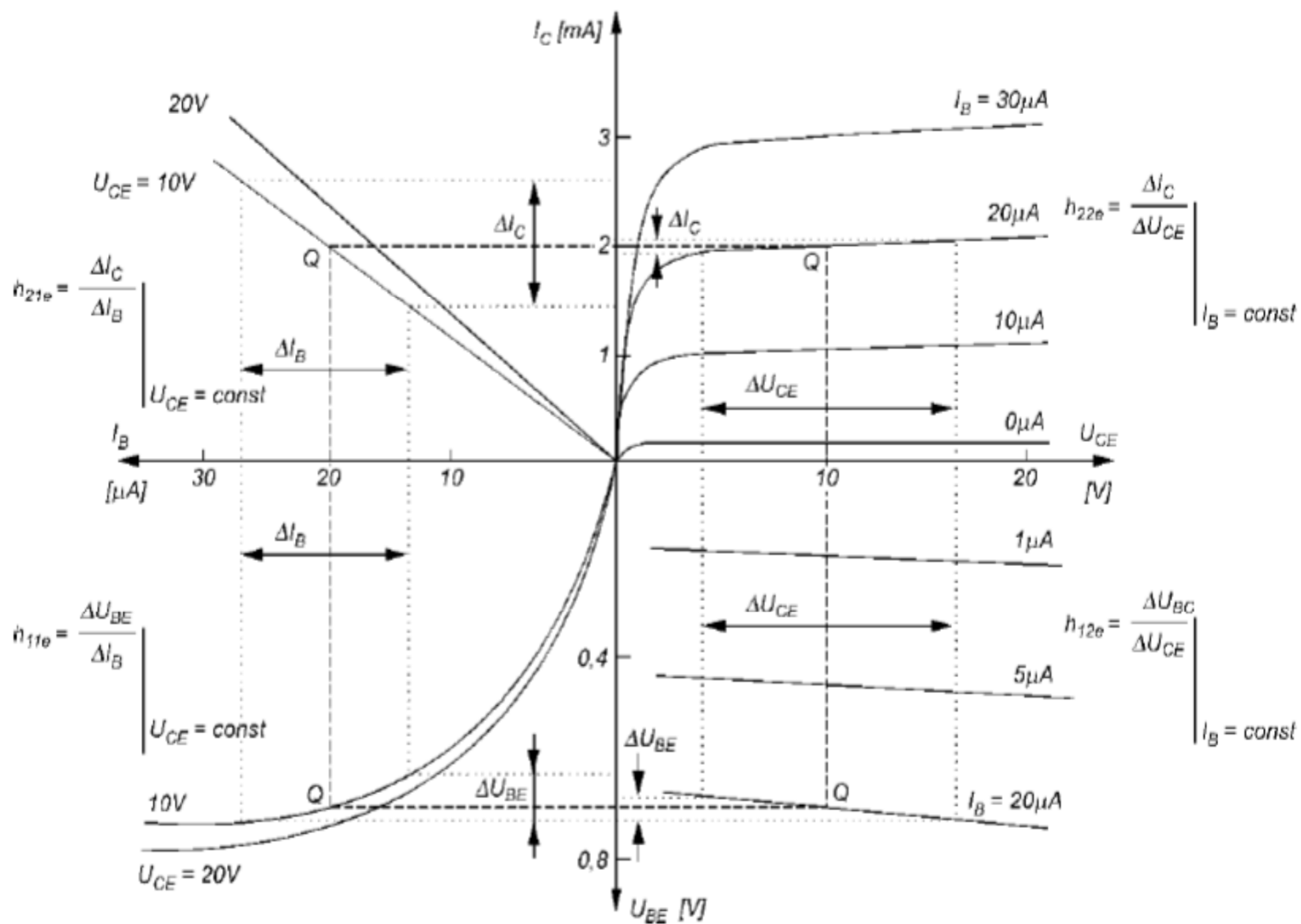


# Linearyzacja charakterystyki diody

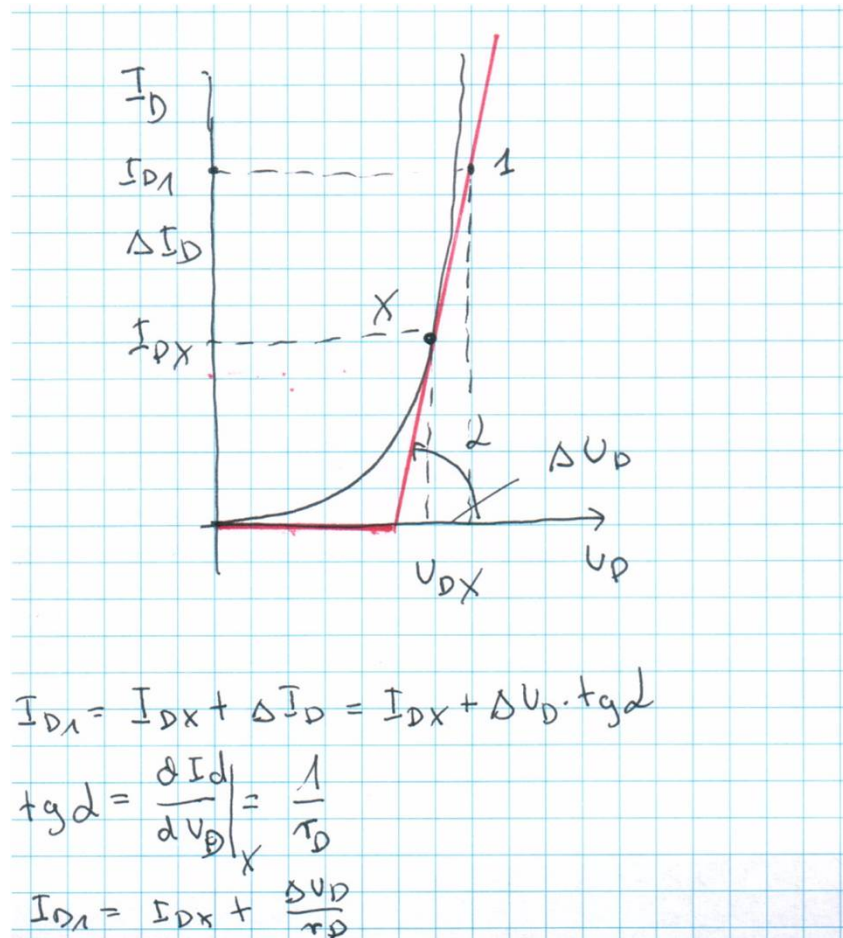
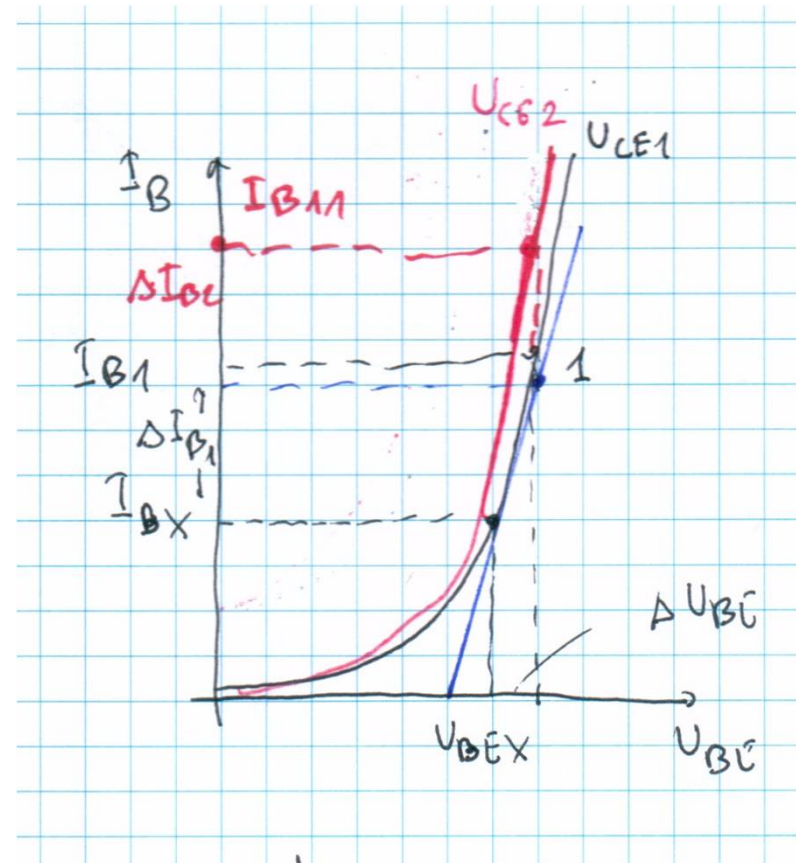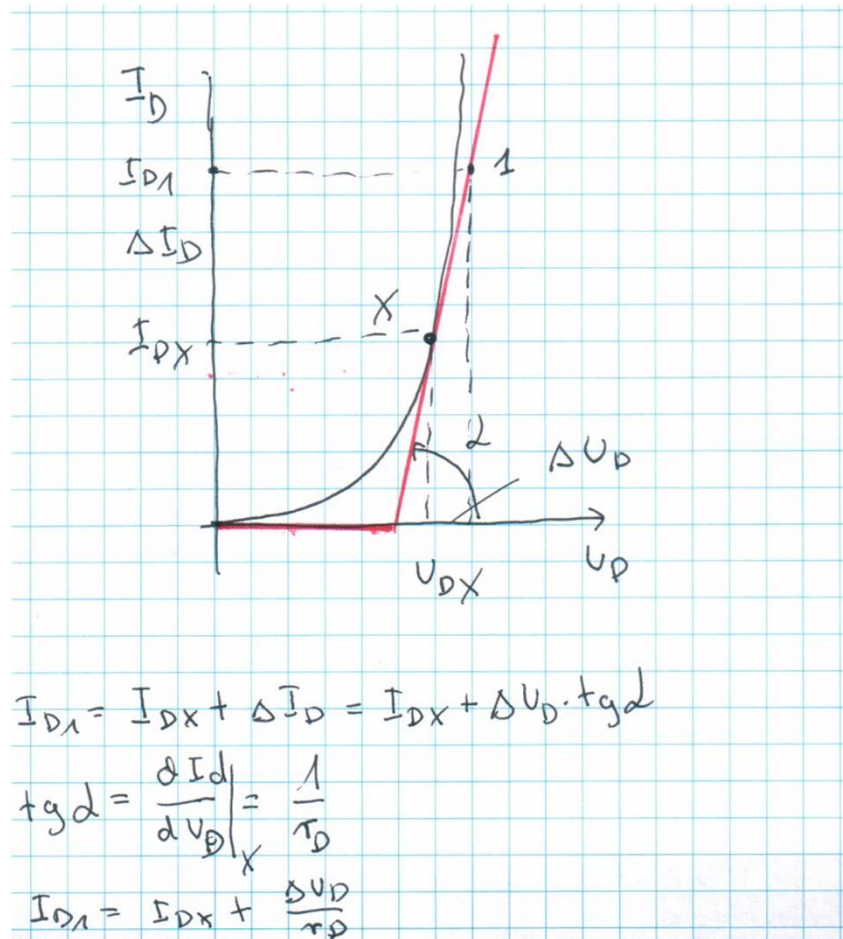
# Linearyzacja charakterystyki diody i tranzystora



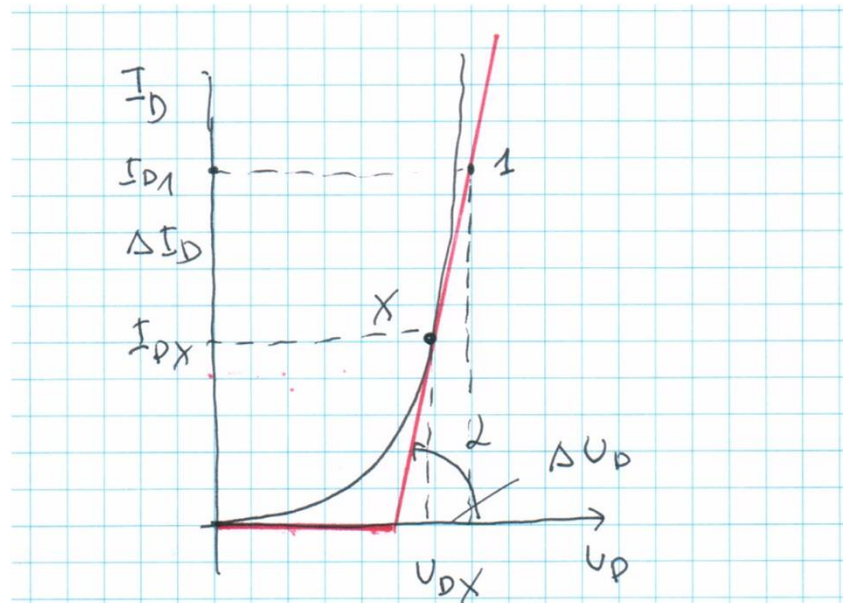
# Linearyzacja charakterystyki diody i tranzystora



$$I_{D1} = I_{DX} + \Delta I_D = I_{DX} + \Delta U_D \cdot \tan \alpha$$

$$\tan \alpha = \left. \frac{dI_D}{dU_D} \right|_X = \frac{1}{r_D}$$
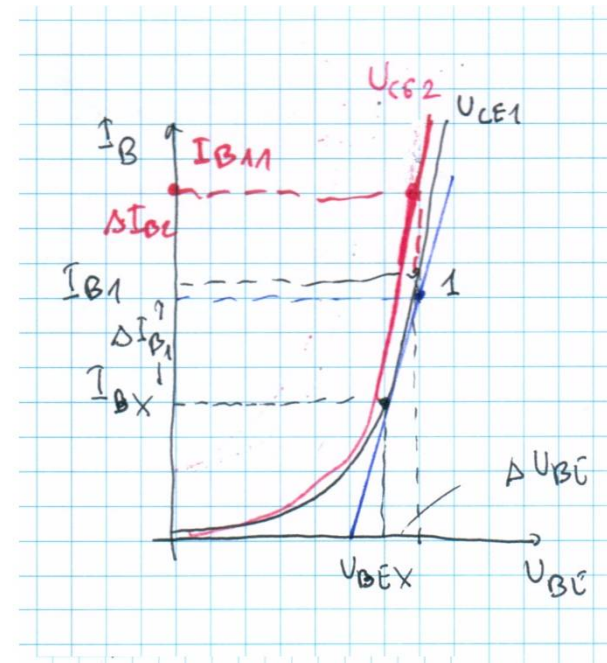
$$I_{D1} = I_{DX} + \frac{\Delta U_D}{r_D}$$



$$I_{B1} = I_{BX} + \Delta I_{B1}$$

$$I_{B1} = I_{BX} + \left. \frac{dI_B}{dU_{BE}} \right|_X \cdot \Delta U_{BE}$$


$$I_B = f(U_{BE}, U_{CE}) =$$

$$I_{B1} = I_{BX} + \Delta I_{B1} + \Delta I_{B2}$$

$$\frac{dI_B}{dU_{BE}} \rightarrow \frac{\partial I_B}{\partial U_{BE}}$$

$$\Delta I_{B1} = \left. \frac{\partial I_B}{\partial U_{BE}} \right|_X \cdot \Delta U_{BE} + \left. \frac{\partial I_B}{\partial U_{CE}} \right|_X \cdot \Delta U_{CE}$$

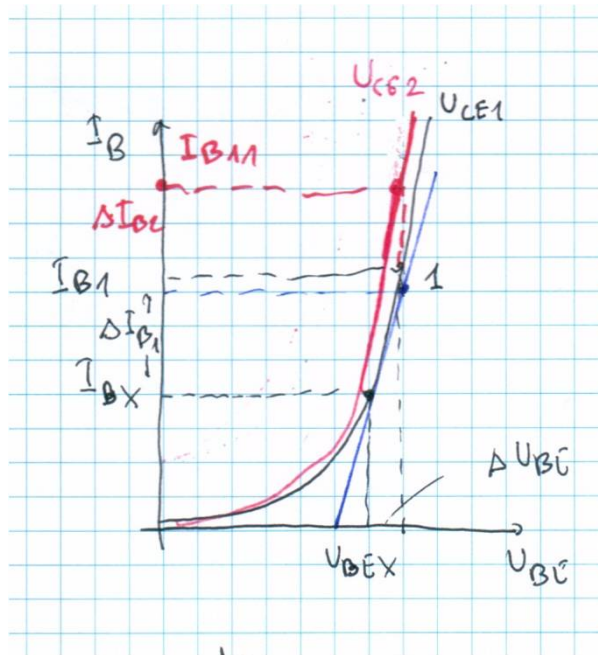
# Linearyzacja charakterystyk tranzystora



$$\frac{dI_B}{dV_{BE}} \rightarrow \frac{\partial I_B}{\partial V_{BE}} \quad \Delta I_{B1} = \left. \frac{\partial I_B}{\partial V_{BE}} \right|_X \cdot \Delta V_{BE} + \left. \frac{\partial I_B}{\partial U_{CE}} \right|_X \cdot \Delta U_{CE}$$

$$y = f(x_1, x_2) \rightarrow y_x + \Delta y = y_x + \frac{\partial f}{\partial x_1} \cdot \Delta x_1 + \frac{\partial f}{\partial x_2} \cdot \Delta x_2 + \dots$$
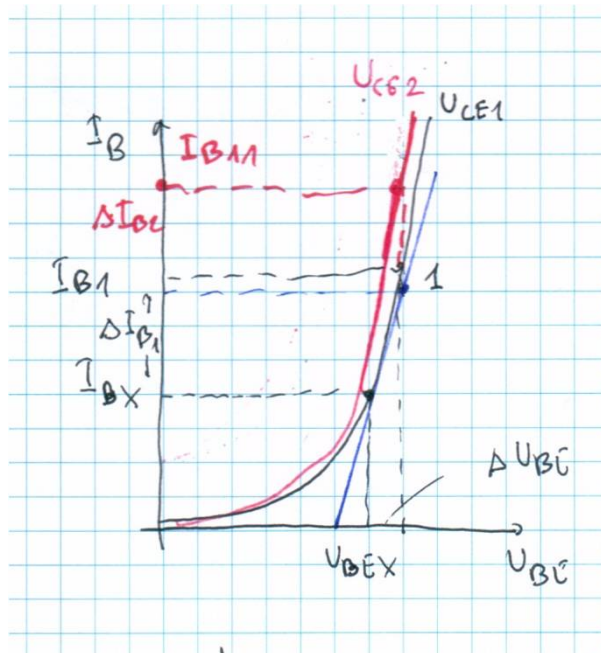
# Linearyzacja charakterystyk tranzystora



$$\frac{dI_B}{dV_{BE}} \rightarrow \frac{\partial I_B}{\partial V_{BE}} \quad \Delta I_{B1} = \left. \frac{\partial I_B}{\partial V_{BE}} \right|_X \cdot \Delta V_{BE} + \left. \frac{\partial I_B}{\partial V_{CE}} \right|_X \cdot \Delta V_{CE}$$

$$y = f(x_1, x_2) \rightarrow y_x + \Delta y = y_x + \frac{\partial f}{\partial x_1} \cdot \Delta x_1 + \frac{\partial f}{\partial x_2} \cdot \Delta x_2 + \dots$$

uproszczenie

$$\frac{\partial I_B}{\partial V_{CE}} \approx 0$$


$$I_B = I_{BX} + \frac{\partial I_B}{\partial V_{BE}} \cdot \Delta V_{BE}$$

$$\Delta I_B = I_B - I_{BX} = \left. \frac{\partial I_B}{\partial V_{BE}} \right|_X \Delta V_{BE}$$

$$\frac{\partial I_B}{\partial V_{BE}} = \frac{1}{r_{BE}}$$


$$\Delta I_B = \frac{1}{r_{BE}} \cdot \Delta V_{BE}$$
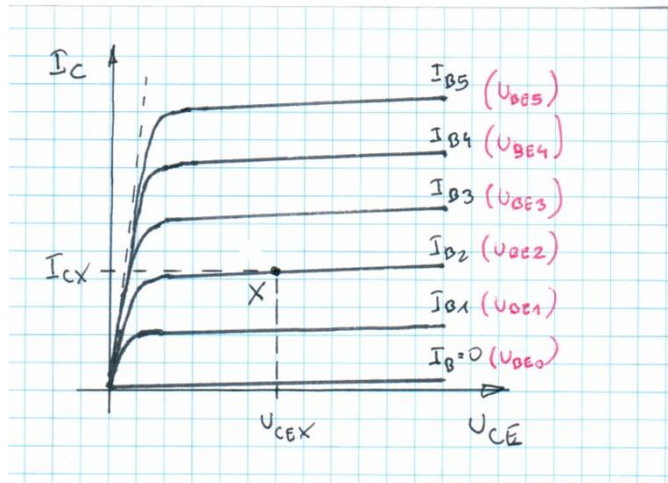
# Linearyzacja charakterystyk tranzystora




$$I_C = f(U_{BE}, U_{CE})$$
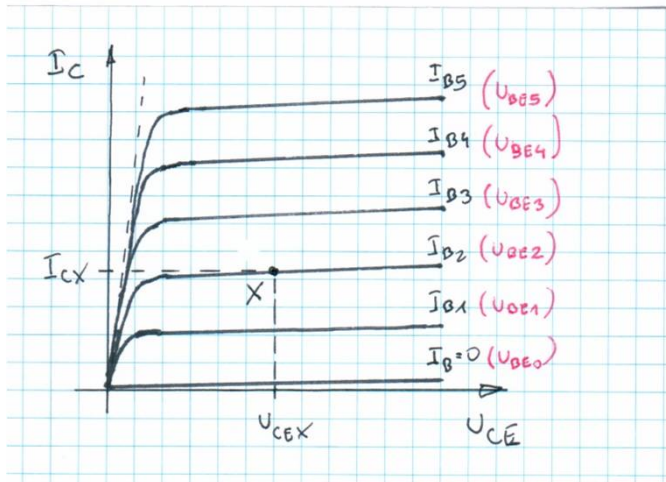
# Linearyzacja charakterystyk tranzystora




$$I_C = f(U_{BE}, U_{CE})$$

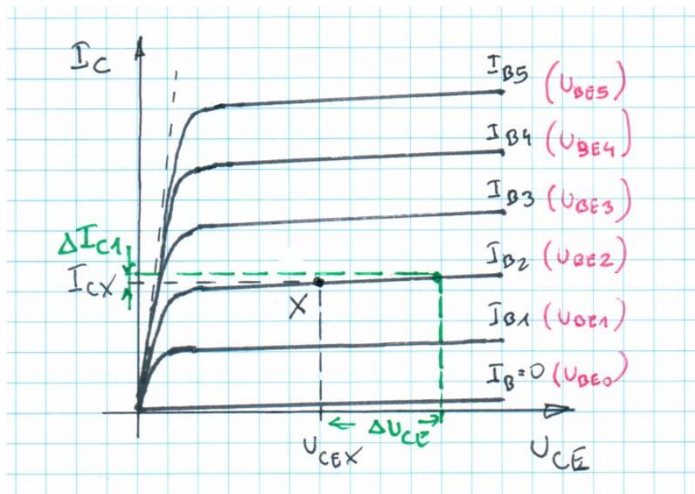


$$\Delta I_{C1} = I_{C1} - I_{CX} = \left. \frac{\partial I_C}{\partial U_{CE}} \right|_X \cdot \Delta U_{CE}$$
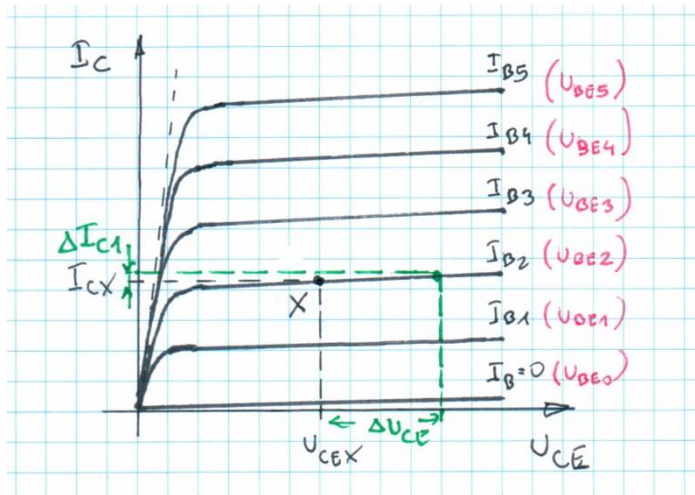
# Linearyzacja charakterystyk tranzystora




$$I_C = f(U_{BE}, U_{CE})$$

$$\Delta I_{C1} = I_{C1} - I_{CX} = \left. \frac{\partial I_C}{\partial U_{CE}} \right|_X \cdot \Delta U_{CE}$$

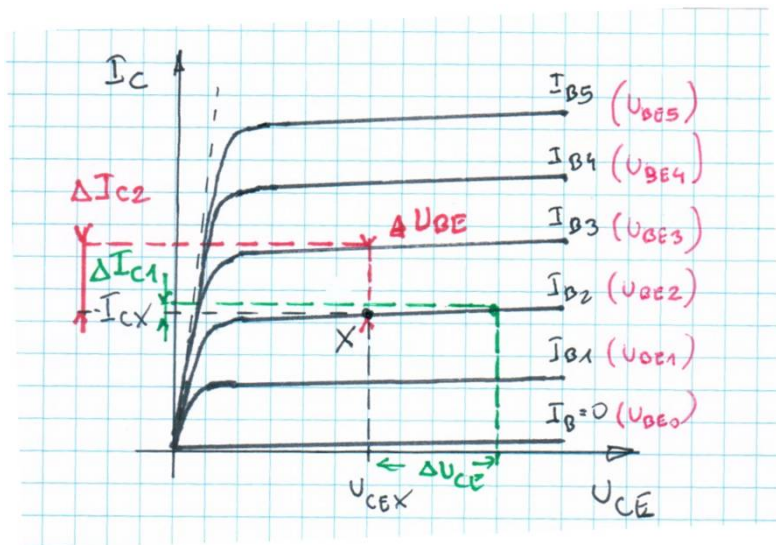


$$\Delta I_{C2} = I_{C2} - I_{C1} = \left. \frac{\partial I_C}{\partial U_{BE}} \right|_X \cdot \Delta U_{BE}$$
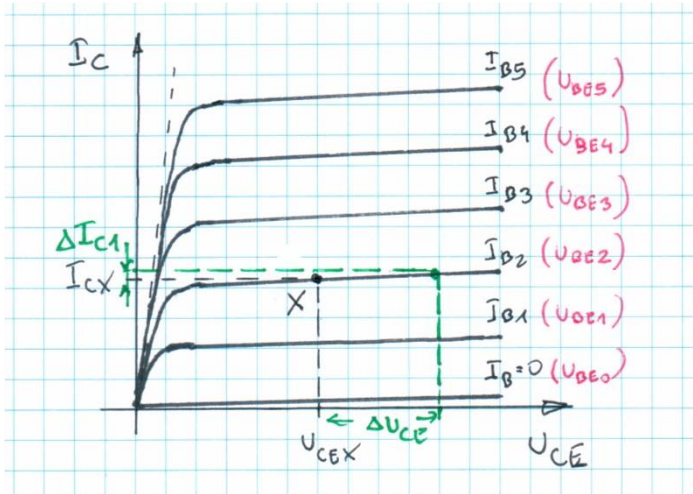
# Linearyzacja charakterystyk tranzystora



$$I_C = f(U_{BE}, U_{CE})$$

$$\Delta I_{C1} = I_{C1} - I_{CX} = \left. \frac{\partial I_C}{\partial U_{CE}} \right|_X \cdot \Delta U_{CE}$$

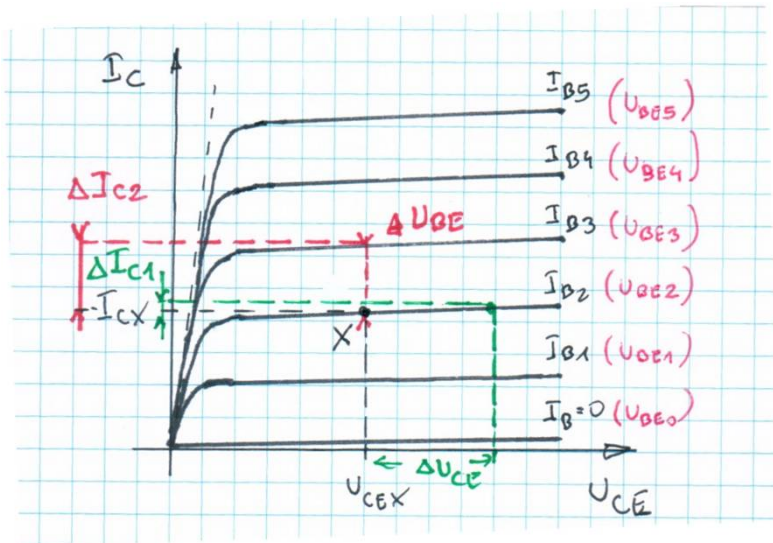

$$\Delta I_{C2} = I_{C2} - I_{CX} = \left. \frac{\partial I_C}{\partial U_{BE}} \right|_X \cdot \Delta U_{BE}$$

$$\Delta I_C = \left. \frac{\partial I_C}{\partial U_{BE}} \right|_X \cdot \Delta U_{BE} + \left. \frac{\partial I_C}{\partial U_{CE}} \right|_X \cdot \Delta U_{CE}$$

$$\frac{\partial I_C}{\partial U_{BE}} = g_m$$

$$\frac{\partial I_C}{\partial U_{CE}} = \frac{1}{r_{CE}}$$

# Linearyzacja charakterystyk tranzystora

Zapis konduktancyjny  
(przewodnościowy)

$$\Delta I_B = \frac{1}{r_{BE}} \cdot \Delta V_{BE}$$

$$\Delta I_C = g_m \cdot \Delta V_{BE} + \frac{1}{r_{CE}} \cdot \Delta V_{CE}$$

$$\begin{bmatrix} \Delta I_B \\ \Delta I_C \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} \Delta V_{BE} \\ \Delta V_{CE} \end{bmatrix}$$

$$g_{11} = \frac{1}{r_{BE}} \quad g_{12} \approx 0$$

$$g_{21} = g_m \quad g_{22} = \frac{1}{r_{CE}}$$

# Linearyzacja charakterystyk tranzystora

Zapis konduktancyjny  
(przewodnościowy)

$$\Delta I_B = \frac{1}{r_{BE}} \cdot \Delta V_{BE}$$

$$\Delta I_C = g_m \cdot \Delta V_{BE} + \frac{1}{r_{CE}} \cdot \Delta V_{CE}$$

$$\begin{bmatrix} \Delta I_B \\ \Delta I_C \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} \Delta V_{BE} \\ \Delta V_{CE} \end{bmatrix}$$

$$g_{11} = \frac{1}{r_{BE}}$$

$$g_{12} \approx 0$$

$$g_{21} = g_m$$

$$g_{22} = \frac{1}{r_{CE}}$$

Zapis hybrydowy

$$\Delta V_{BE} = r_{BE} \cdot \Delta I_B$$

$$\Delta I_C = r_{BE} g_m \cdot \Delta I_B + \frac{1}{r_{CE}} \cdot \Delta V_{CE}$$

$$\frac{\Delta I_C}{\Delta I_B} = \beta$$

$$\Delta I_C = \beta \cdot \Delta I_B$$

$$\beta = r_{BE} g_m$$

$$\Delta V_{BE} = r_{BE} \cdot \Delta I_B$$

$$\Delta I_C = \beta \cdot \Delta I_B + \frac{1}{r_{CE}} \cdot \Delta V_{CE}$$

$$\begin{bmatrix} \Delta V_{BE} \\ \Delta I_C \end{bmatrix} = \begin{bmatrix} h_{11} \cdot \Delta I_B + h_{12} \cdot \Delta V_{CE} \\ h_{21} \cdot \Delta I_B + h_{22} \cdot \Delta V_{CE} \end{bmatrix}$$

$$h_{11} = r_{BE}$$

$$h_{12} \approx 0$$

$$h_{21} = \beta$$

$$h_{22} = \frac{1}{r_{CE}}$$