



# Energoelektronika

## 3. Prostowniki Niesterowane



Dr inż. Dariusz Janiszewski

# Prostowniki niesterowane



---

- ▶ Wprowadzenie do koncepcji prostowania
- ▶ Jednofazowy prostownik diodowy
- ▶ Jednofazowy prostownik mostkowy
- ▶ Podwajacz napięcia
- ▶ Prostowniki trójfazowe
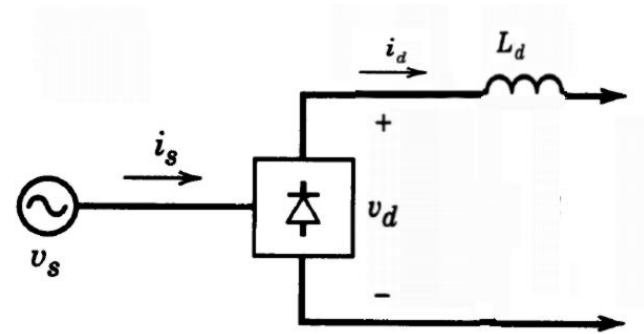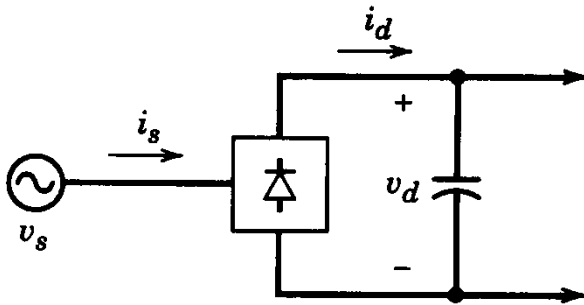
# Diode Rectifier Block Diagram


---

- Uncontrolled utility interface (ac to dc)




# A Simple Circuit

## ► Resistive load

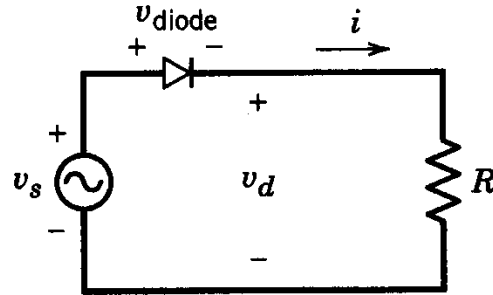

(a)

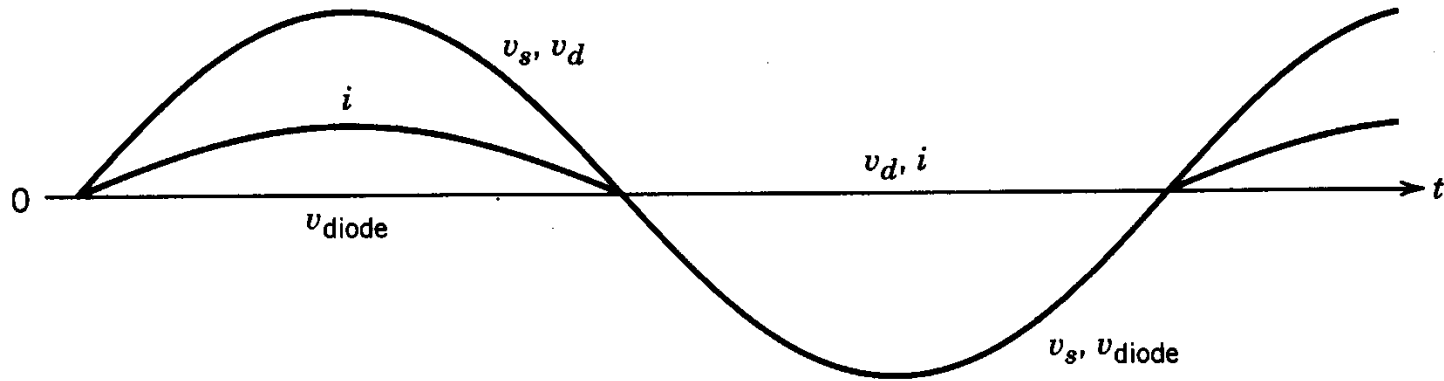

(b)

**Figure 5-2** Basic rectifier with a load resistance.

# A Simple Circuit ( $R$ - $L$ Load)

- ▶ Current continues to flow for a while even after the input voltage has gone negative



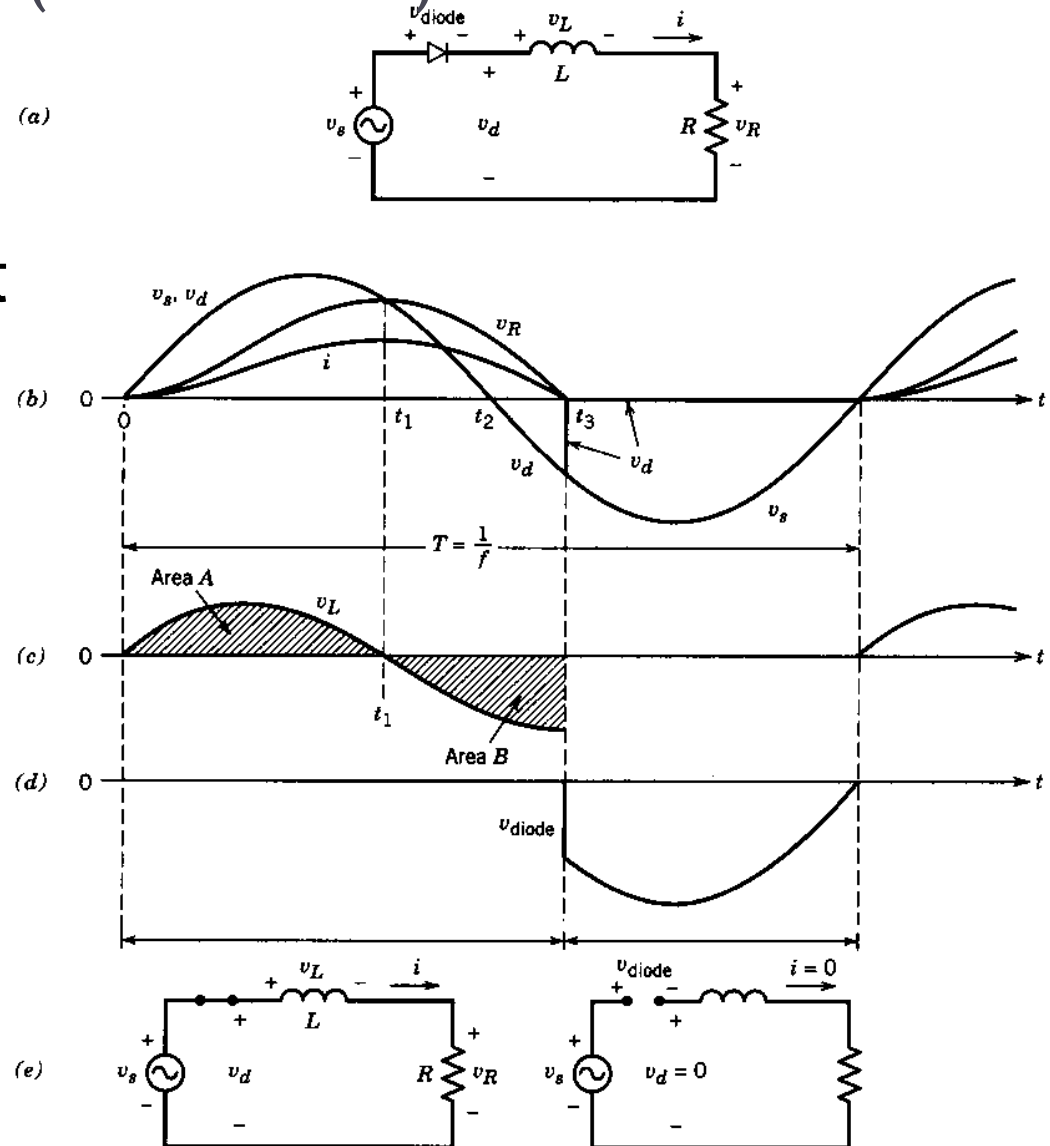


Figure 5-3 Basic rectifier with an inductive load.

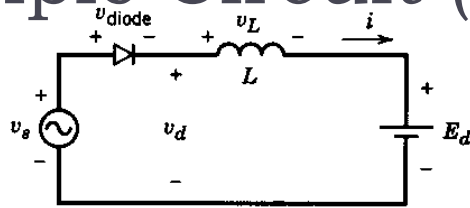
# A Simple Circuit (Load has a dc back-emf)




(a)

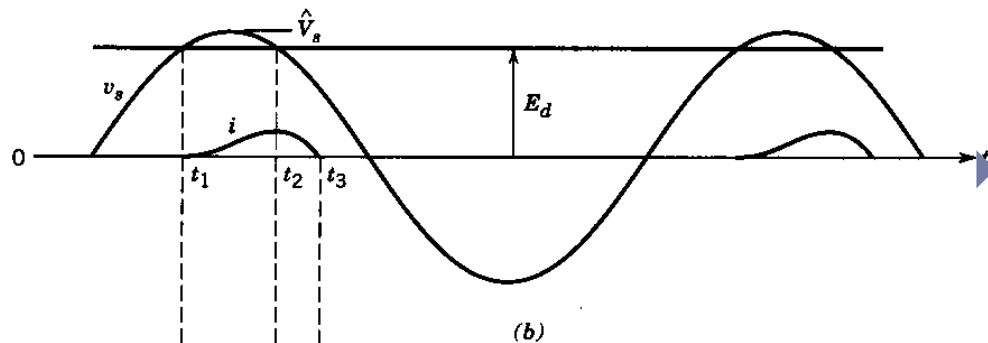

(b)

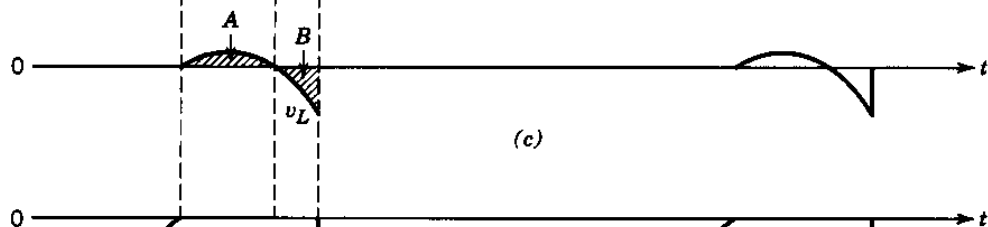

(c)

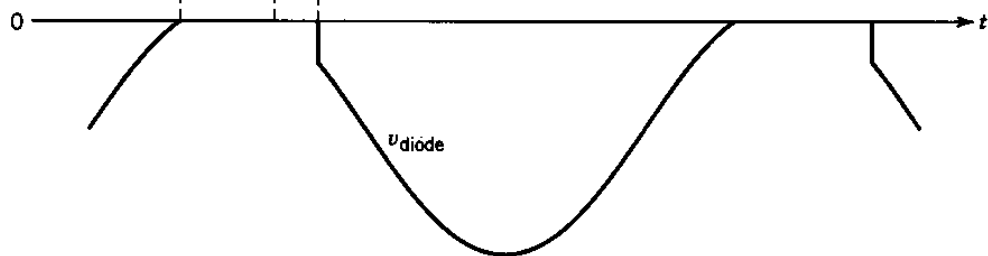

(d)


► Current begins to flow when the input voltage exceeds the dc back-emf

Current continues to flow for a while even after the input voltage has gone below the dc back-emf

Figure 5-4 Basic rectifier with an internal dc voltage.

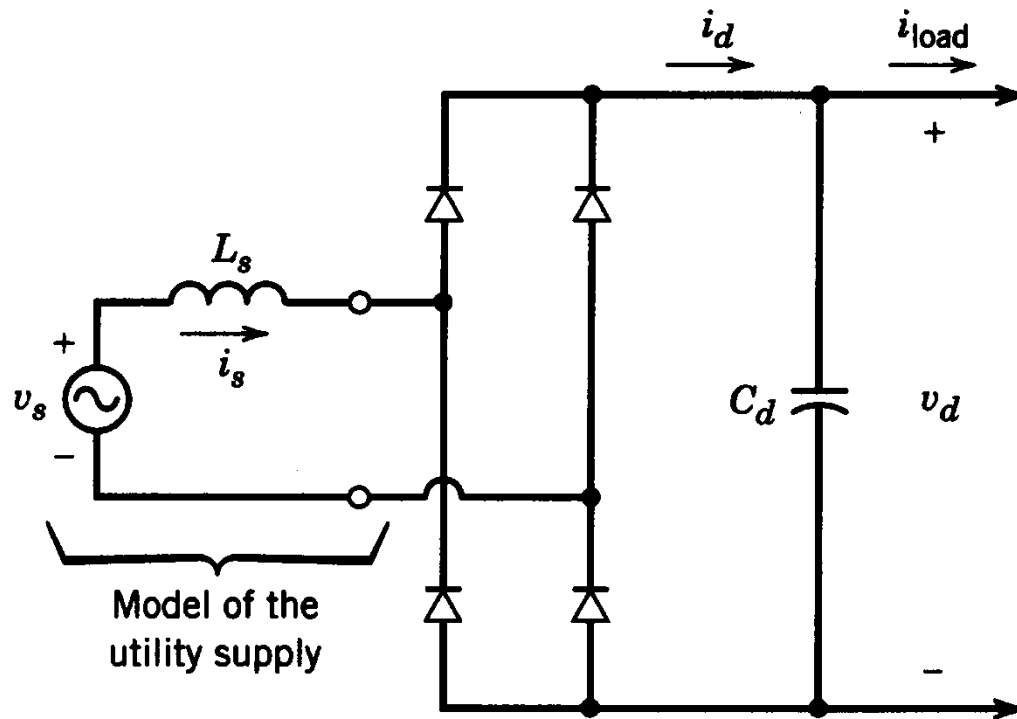
# Single-Phase Diode Rectifier Bridge

- ▶ Large capacitor at the dc output for filtering and energy storage



# Redrawing Diode-Rectifier Bridge


- ▶ Two groups, each with two diodes

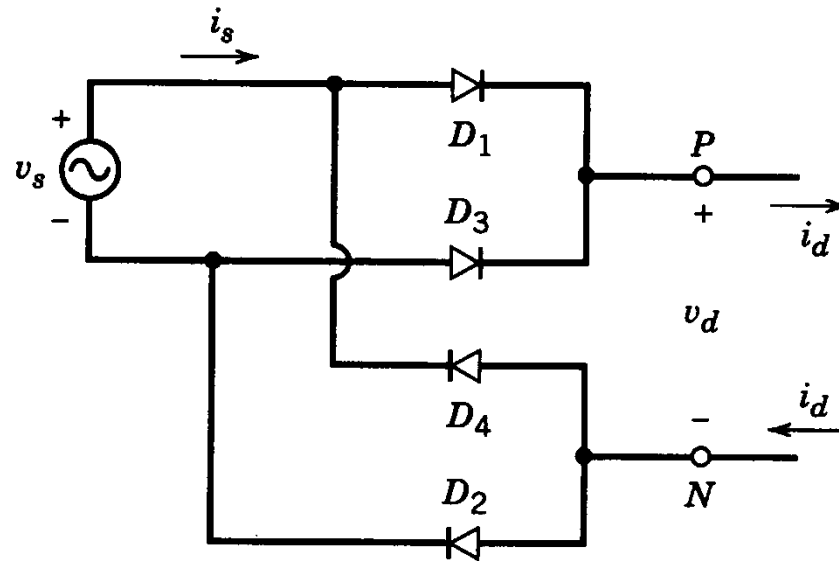



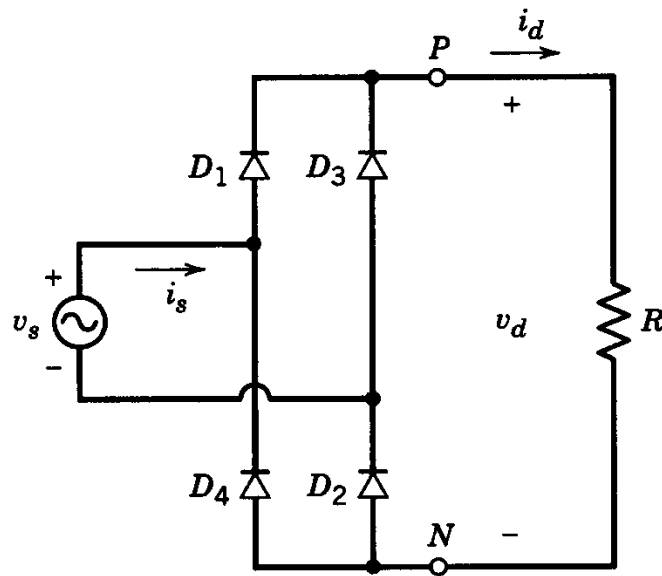
# Diode-Rectifier Bridge Analysis

- ▶ Two simple (idealized) cases to begin with



(a)


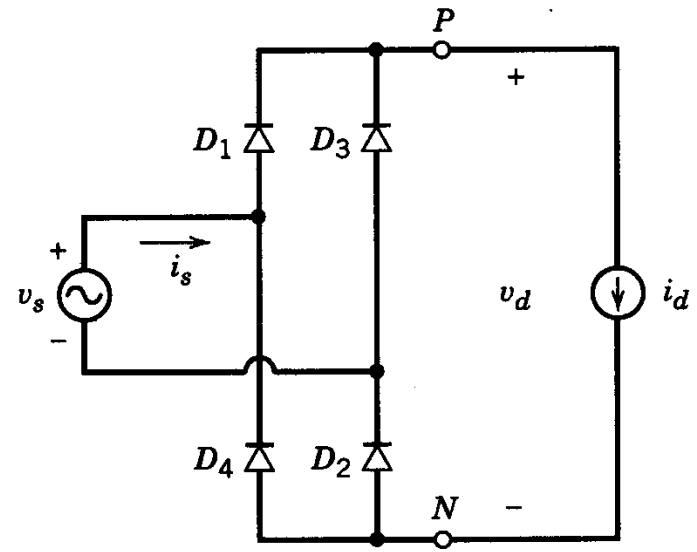


(b)

**Figure 5-6** Idealized diode bridge rectifiers with  $L_s = 0$ .

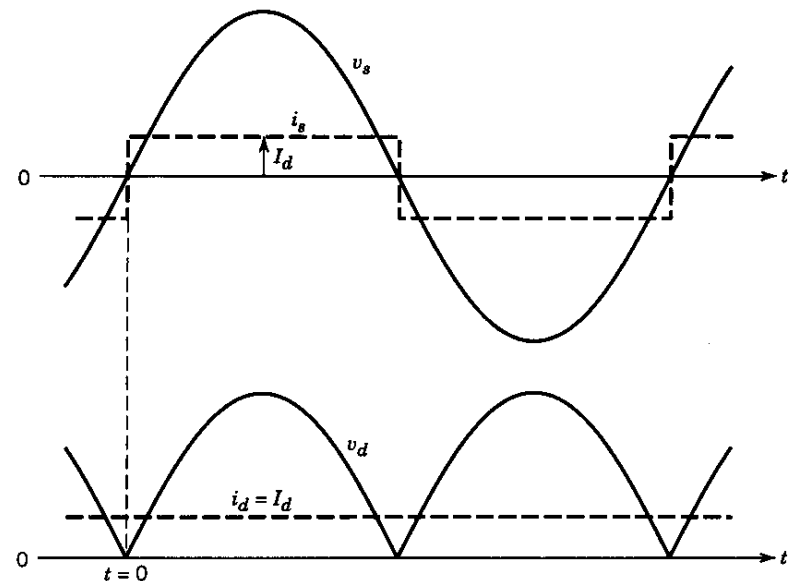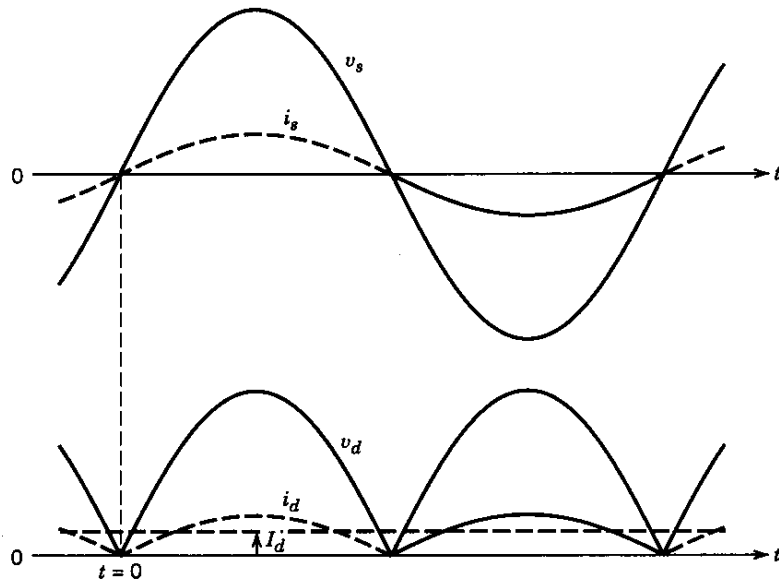
# Waveforms with a purely resistive load and a purely dc current at the output

- In both cases, the dc-side voltage waveform is the same



# Diode-Rectifier Bridge Input Current

- Idealized case with a purely dc output current

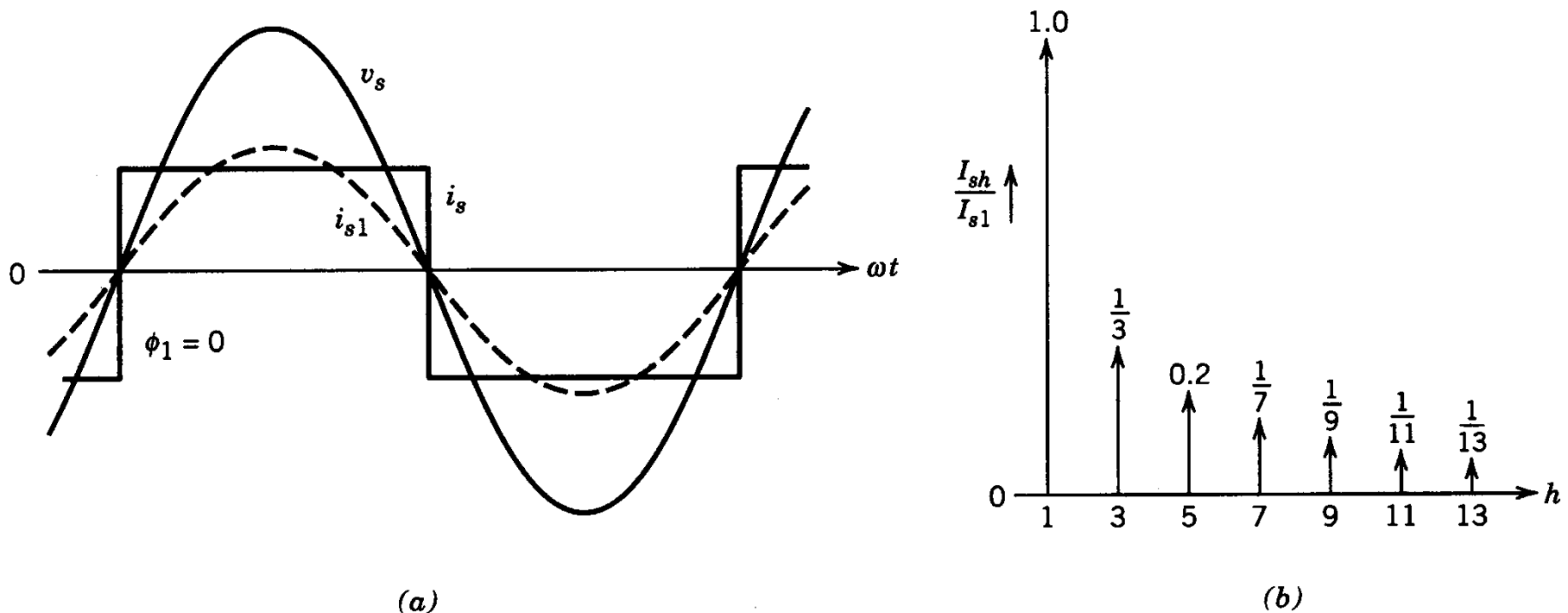


**Figure 5-9** Line current  $i_s$  in the idealized case.
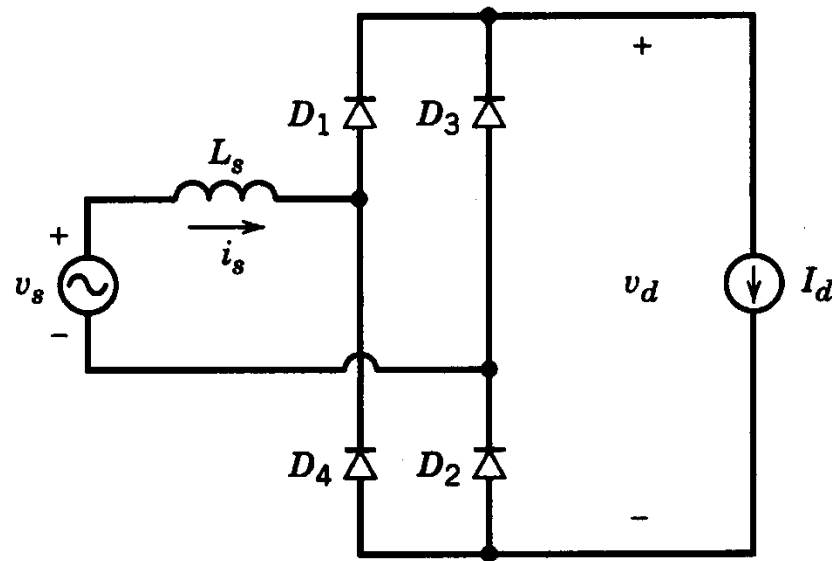
# Diode-Rectifier Bridge Analysis with AC-Side Inductance


---

- ▶ Output current is assumed to be purely dc



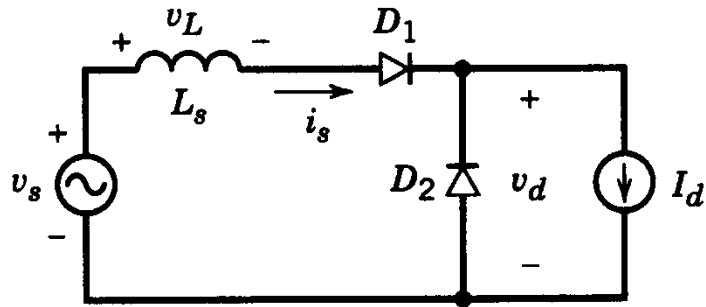
# Understanding Current Commutation

- ▶ Assuming inductance in this circuit to be zero





(a)

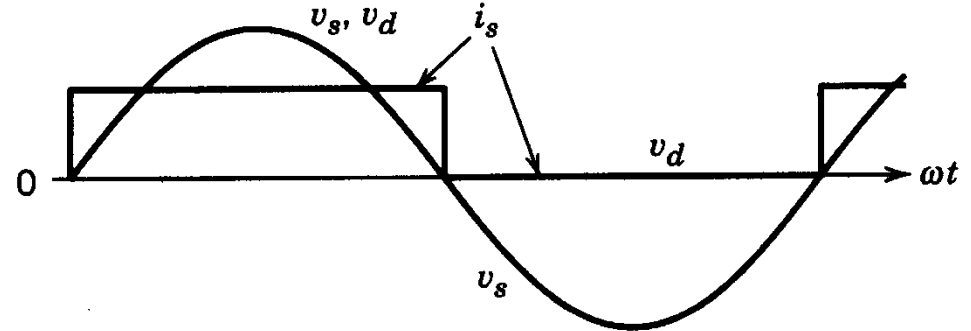

(b)



**Figure 5-11** Basic circuit to illustrate current commutation. Waveforms assume  $L_s = 0$ .
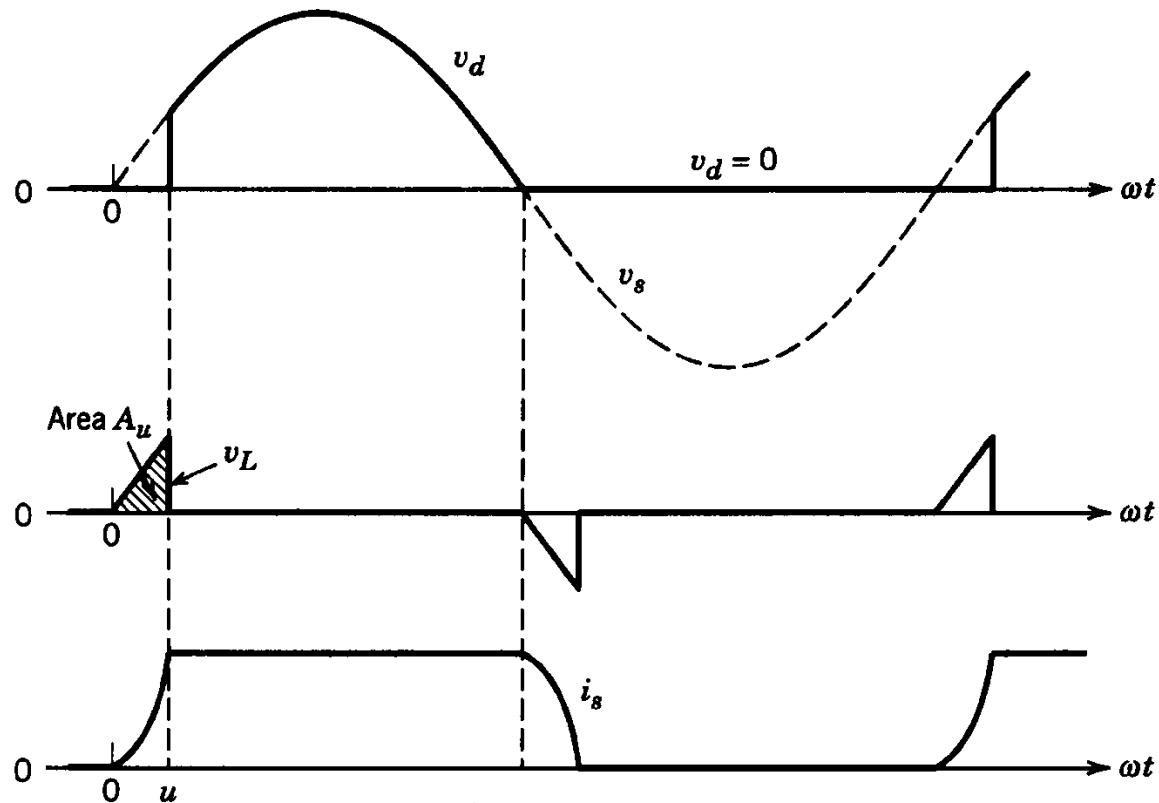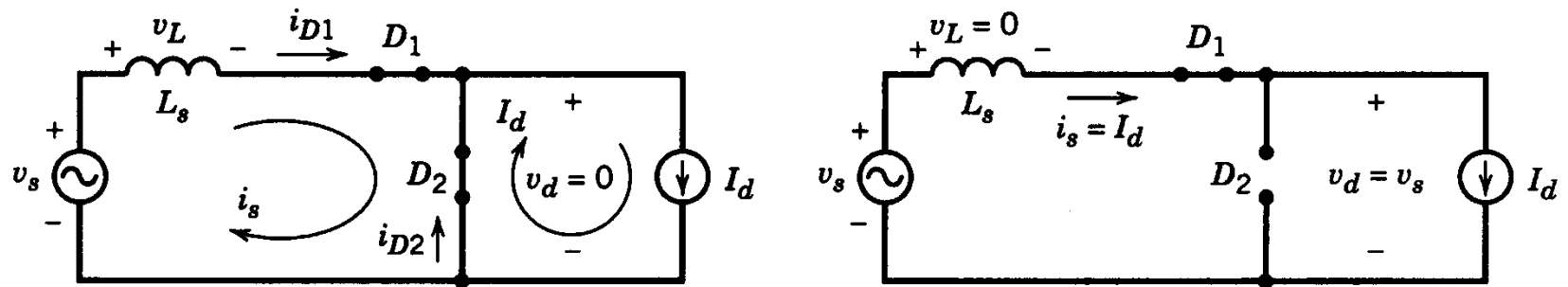
# Understanding Current Commutation (cont.) – inductance is included




# Current Commutation in Full-Bridge Rectifier

- Shows the necessary volt-seconds

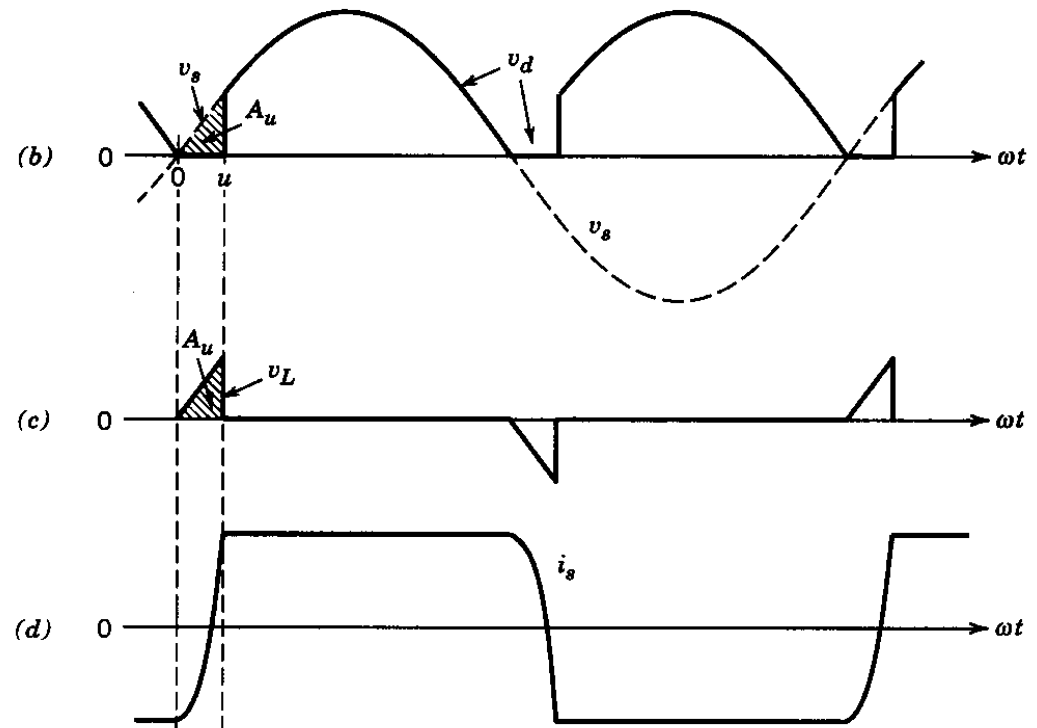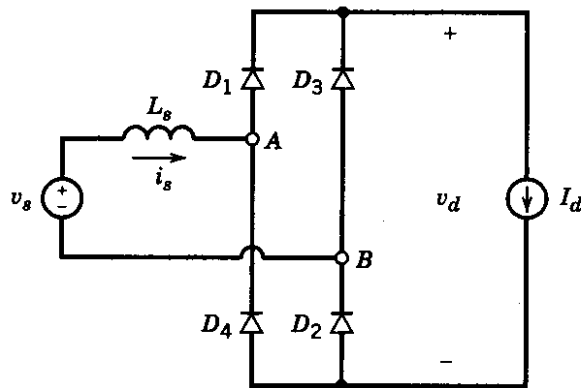

# Understanding Current Commutation




- Note the current loops for analysis

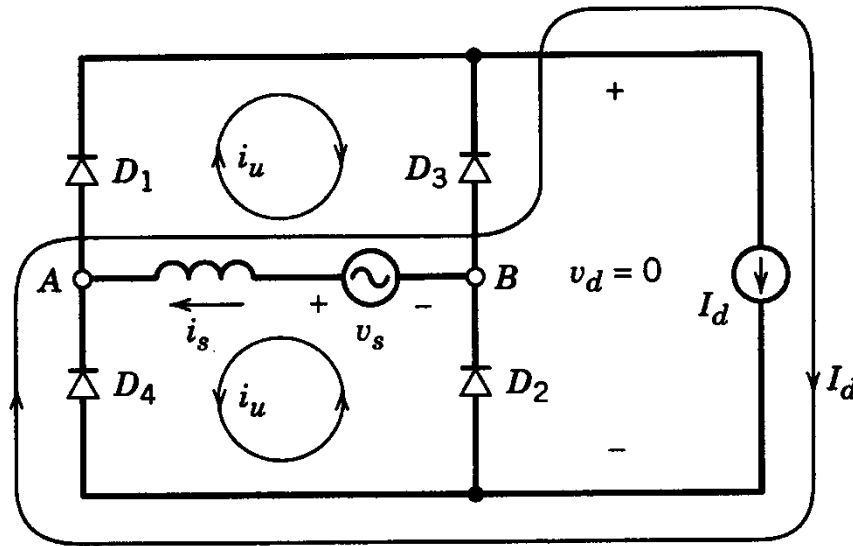

**Figure 5-15** Redrawn circuit of Fig. 5-14a during current commutation.




# Rectifier with a dc-side voltage

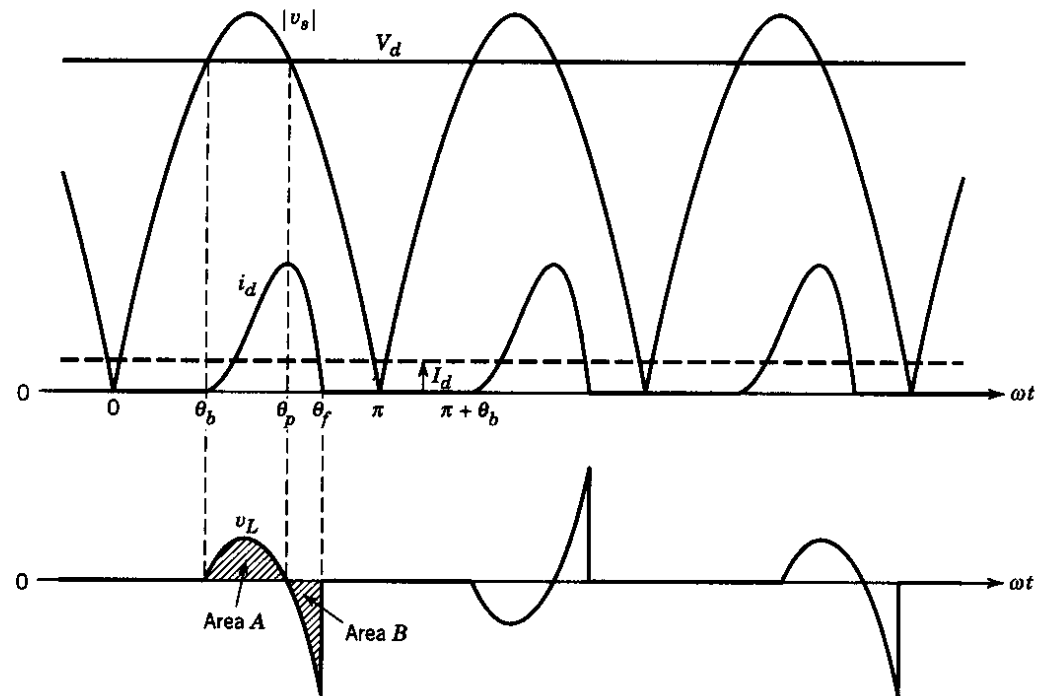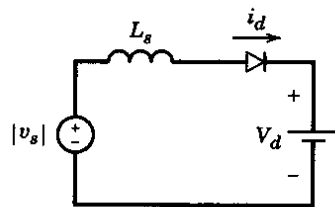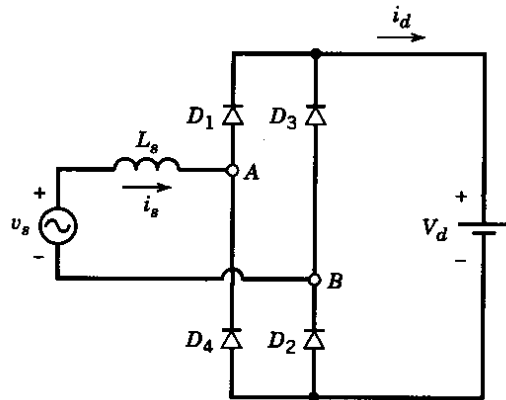

# DC-Side Voltage and Current Relationship


- ▶ Zero current corresponds to dc voltage equal to the peak of the input ac voltage

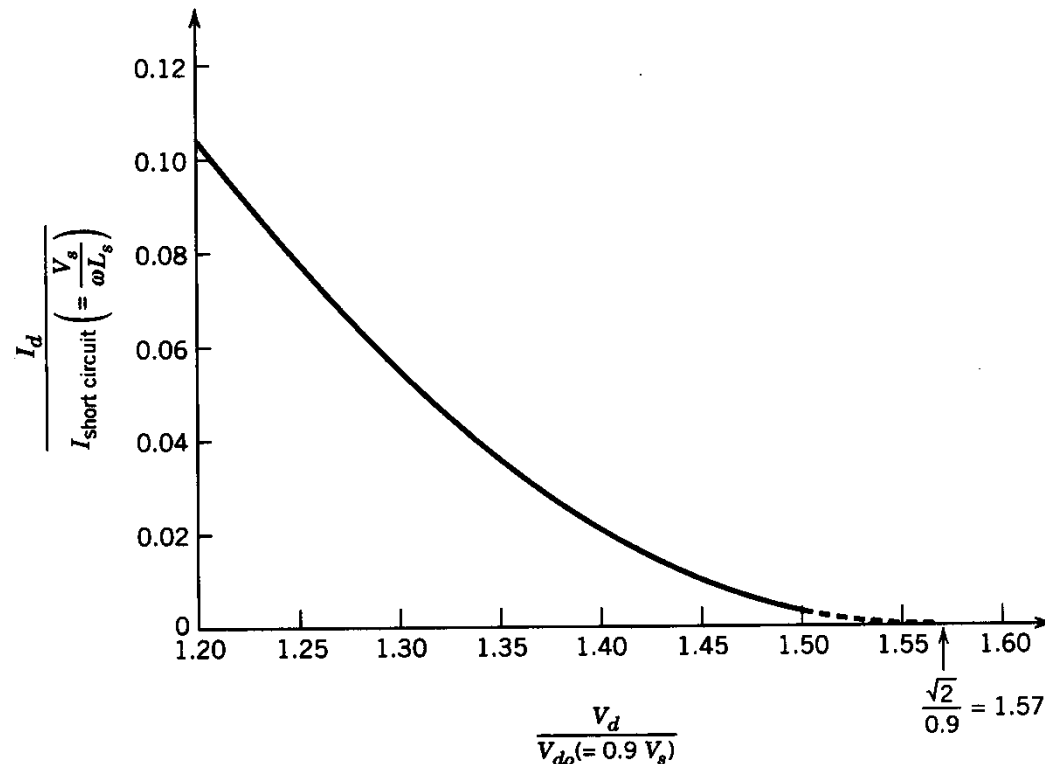

**Figure 5-17** Normalized  $I_d$  versus  $V_d$  in the rectifier of Fig. 5-16a with a constant dc-side voltage.

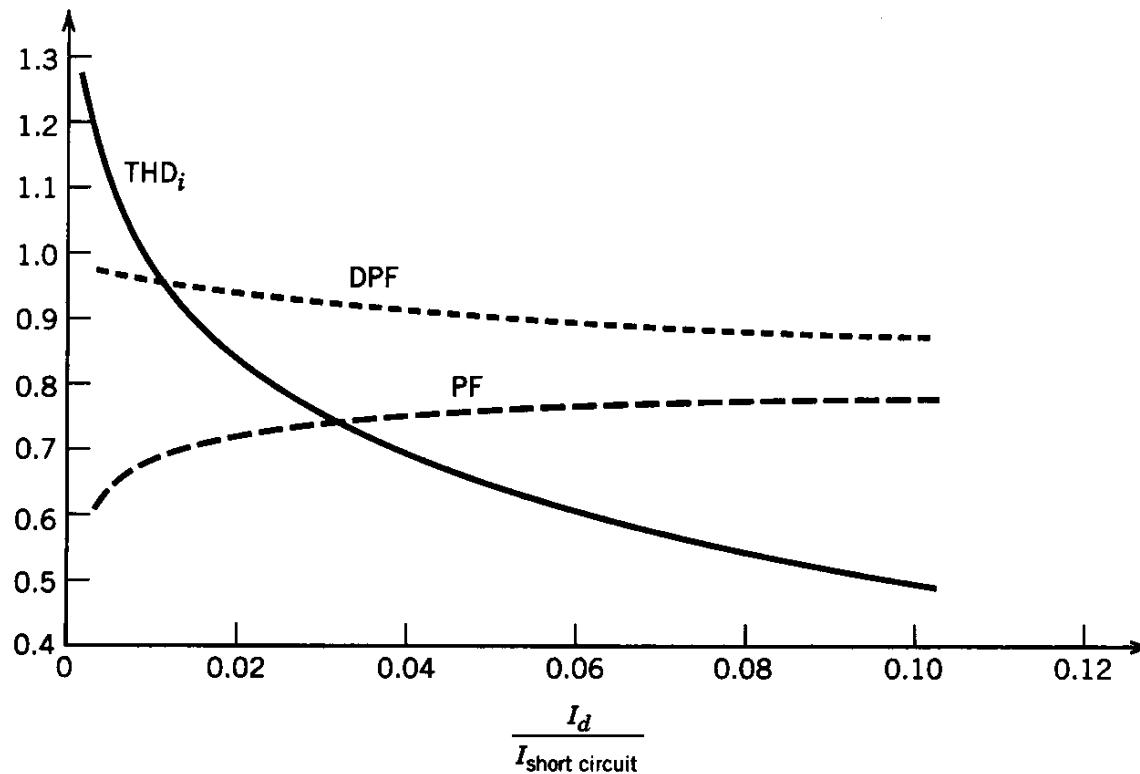
# Effect of DC-Side Current on THD, PF and DPF

- Total Harmonic Distortion (very high at small currents)
- Power Factor ( $\cos\theta$ )
- Displacement Power Factor




# Crest Factor versus the Current Loading

- ▶ The Crest Factor is very high at low values of current

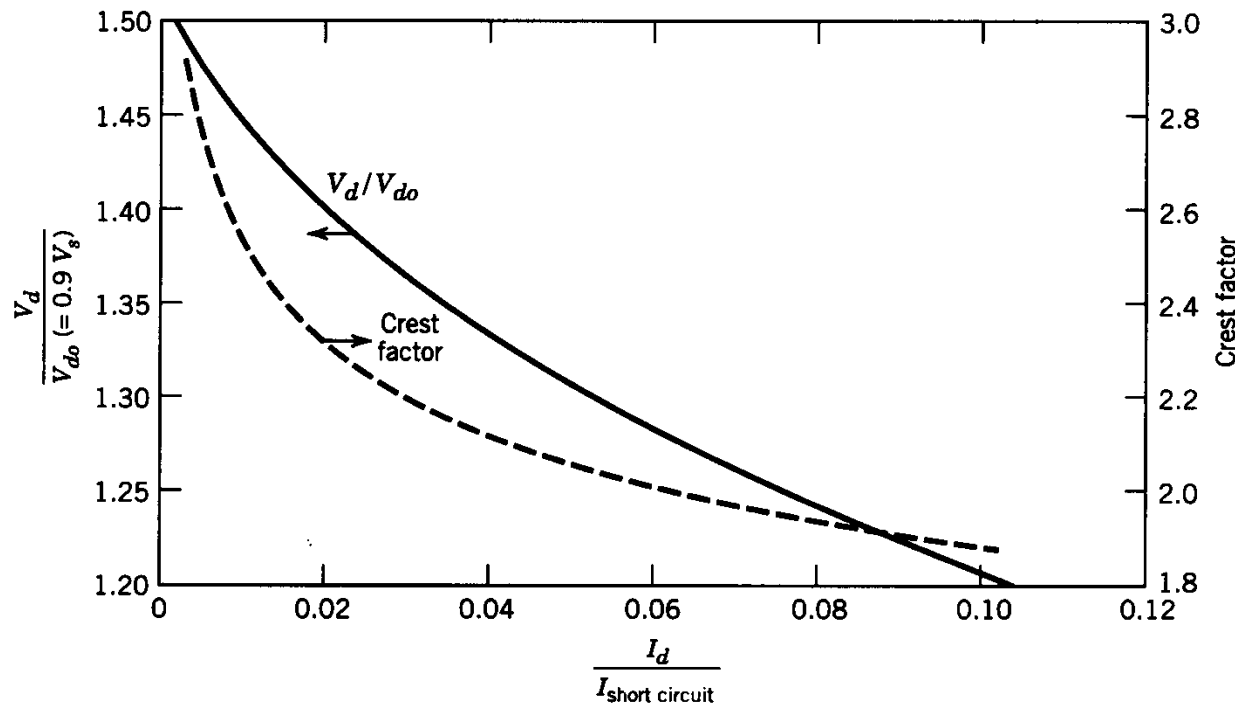

**Figure 5-19** Normalized  $V_d$  and the crest factor in the rectifier of Fig. 5-16a with a constant dc-side voltage.



# Diode-Rectifier with a Capacitor Filter

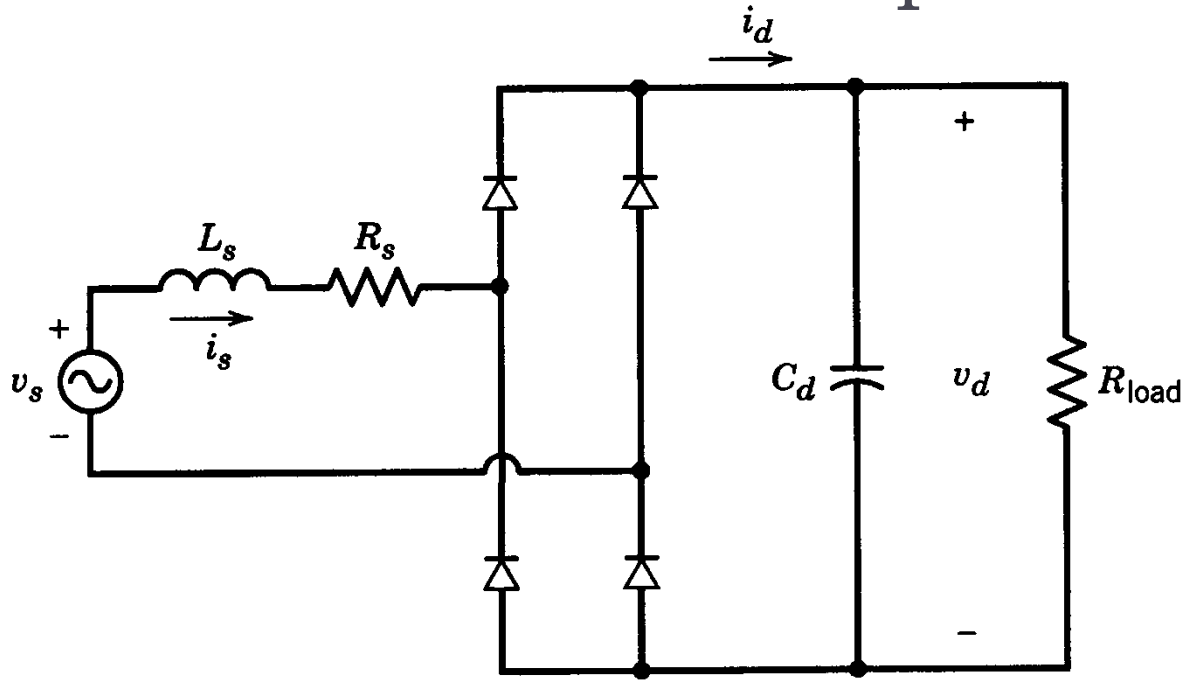


**Figure 5-20** Practical diode-bridge rectifier with a filter capacitor.
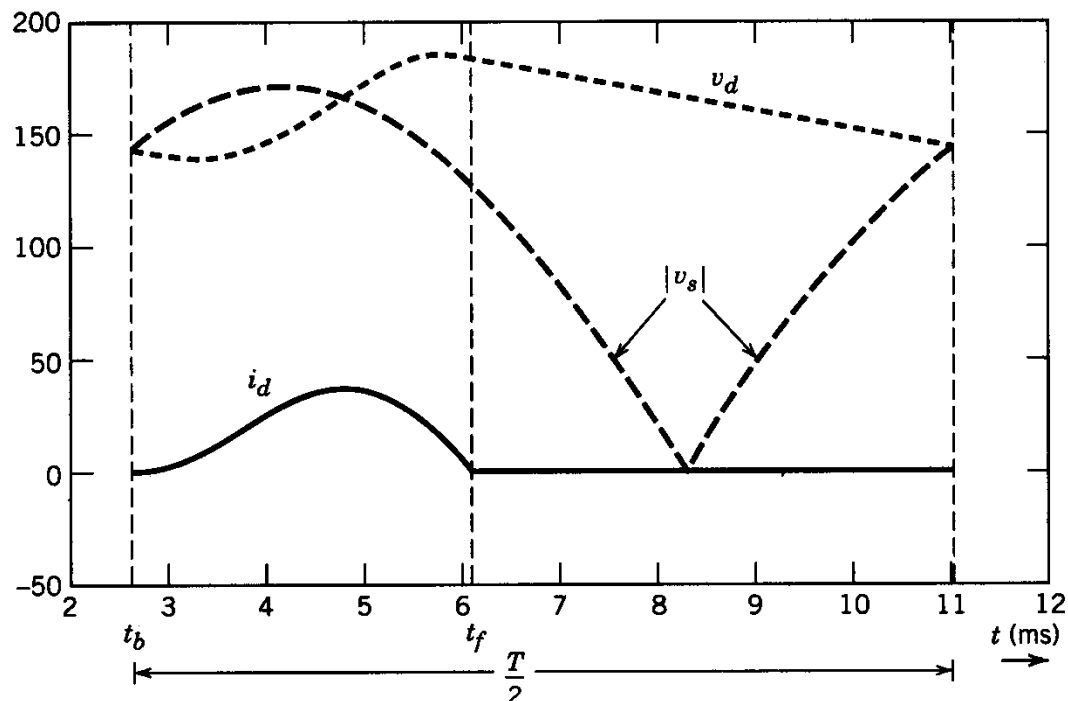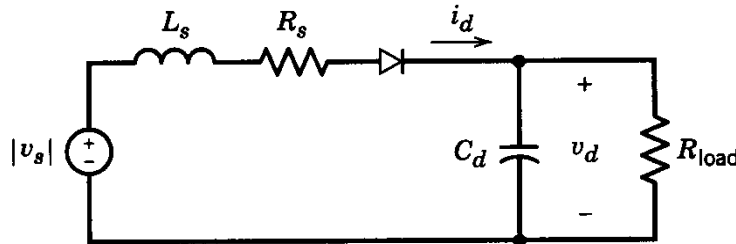
# Diode Rectifier Bridge

- Equivalent circuit for analysis on one-half cycle basis




# Diode-Bridge Rectifier: Waveforms

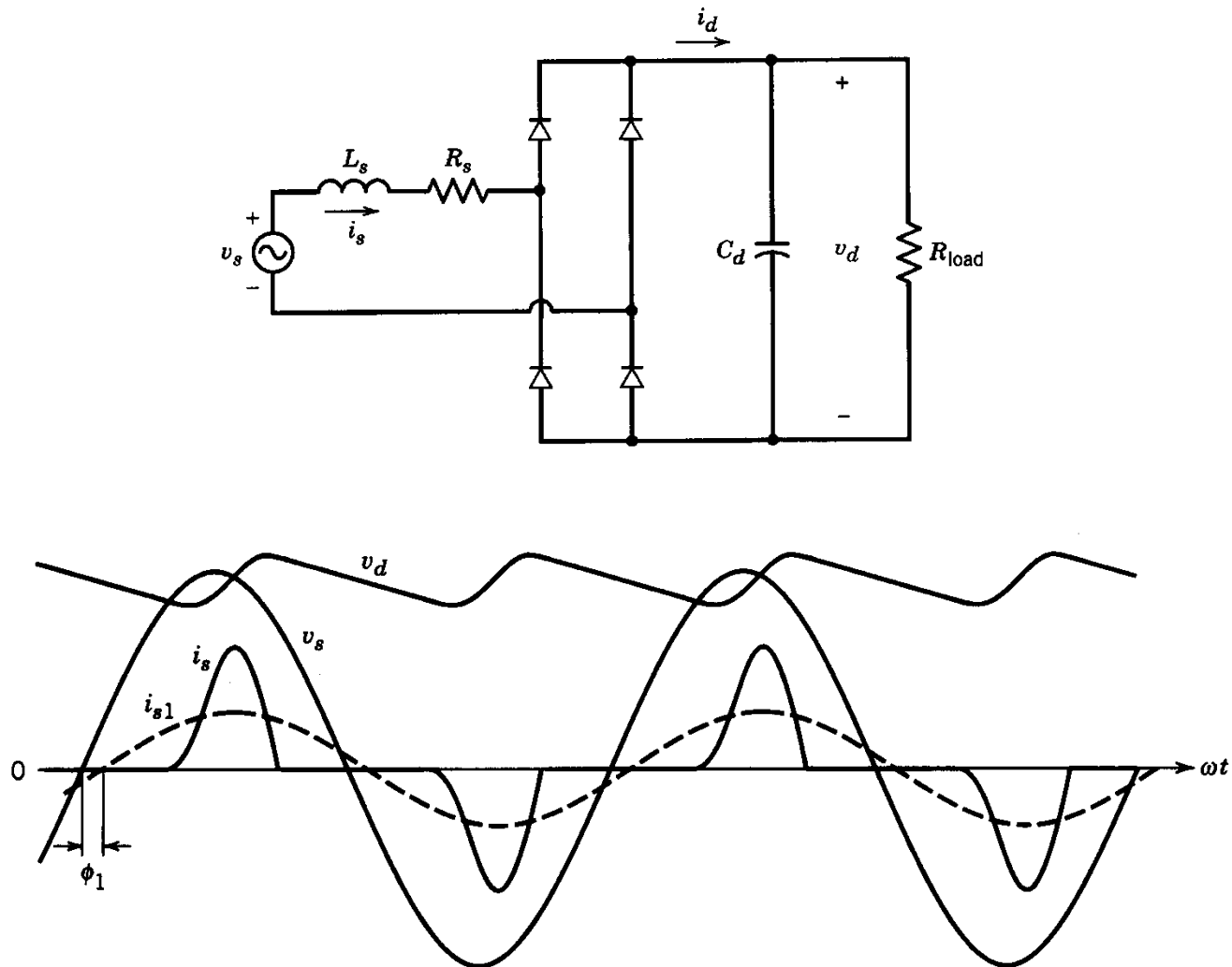

# Input Line-Current Distortion

## – harmonics analysis

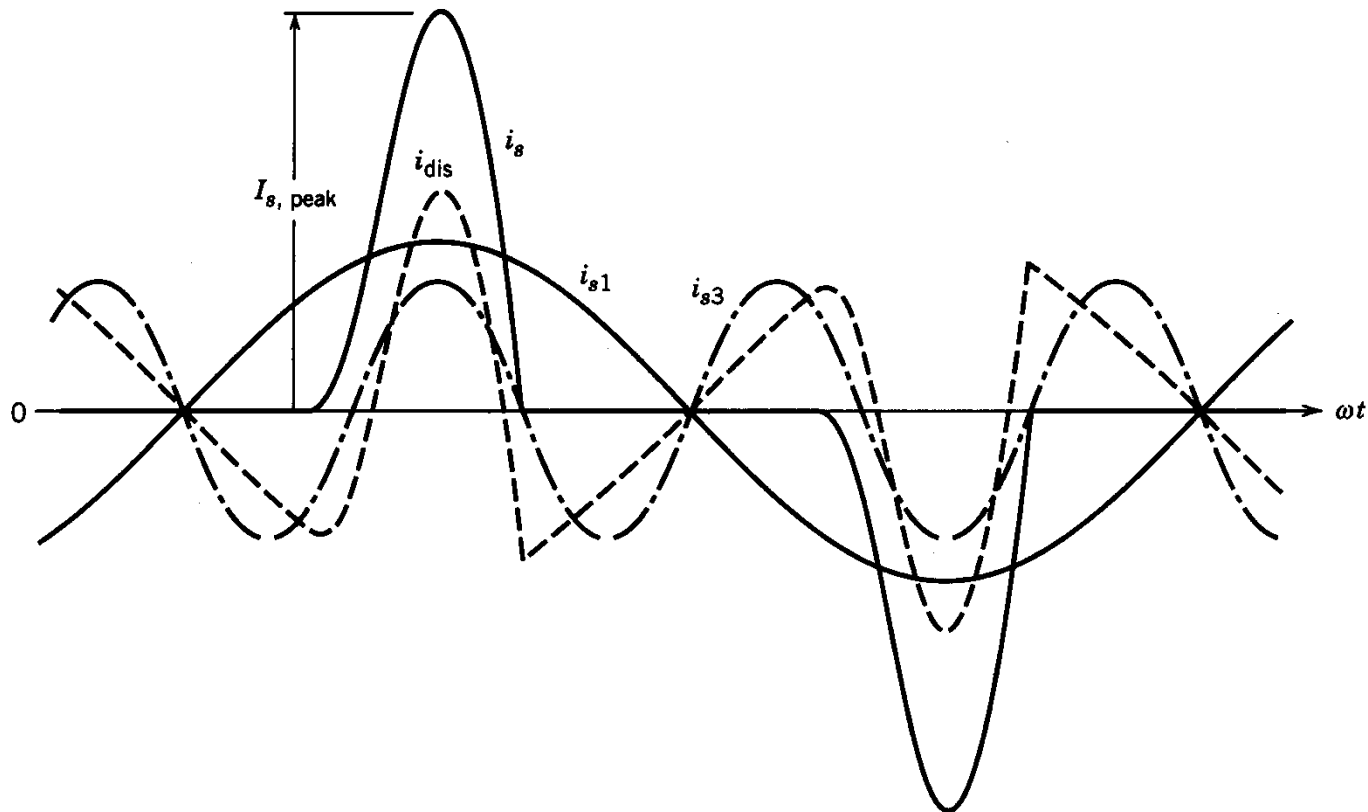---


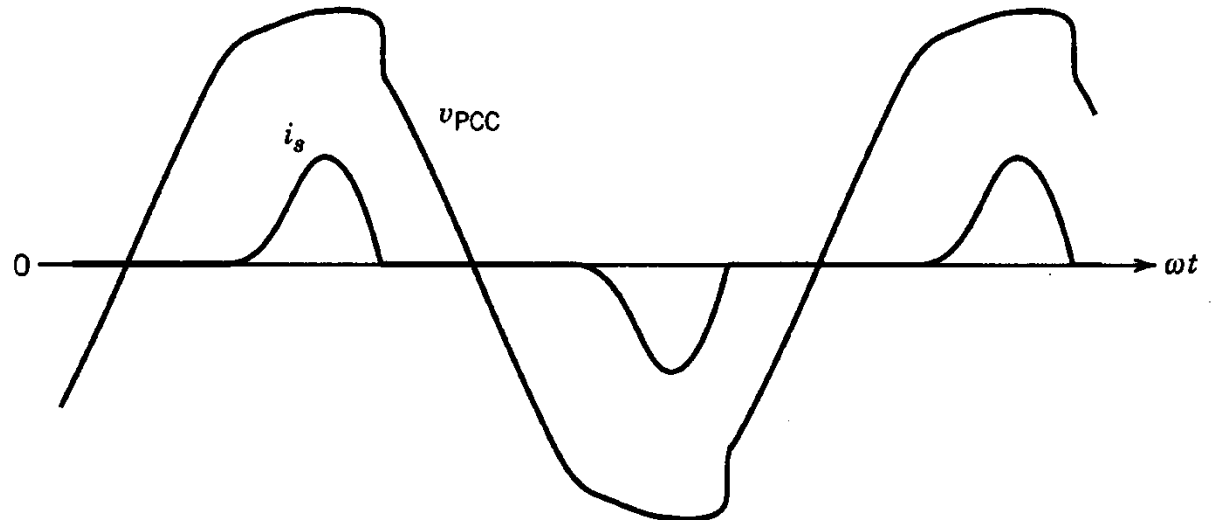


**Figure 5-24** Distorted line current in the rectifier of Fig. 5-20.

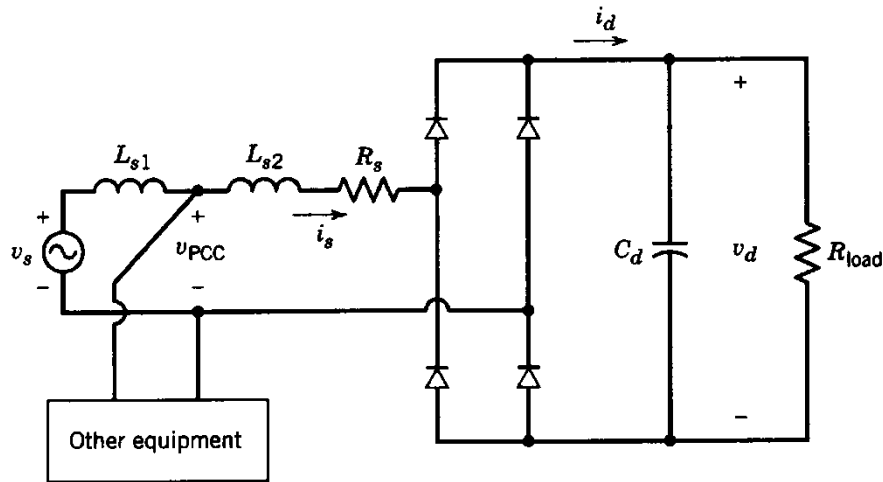


# Line-Voltage Distortion

- PCC is the point of common coupling




# Voltage Doubler Rectifier

- ▶ In 115-V position, one capacitor at-a-time is charged from the input.

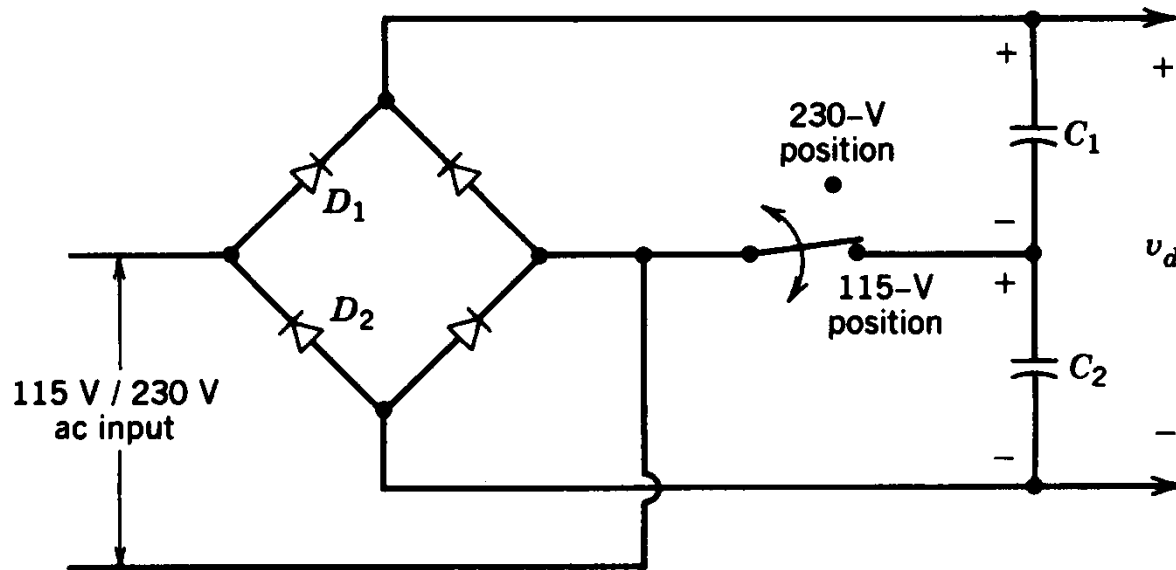


**Figure 5-27** Voltage-doubler rectifier.
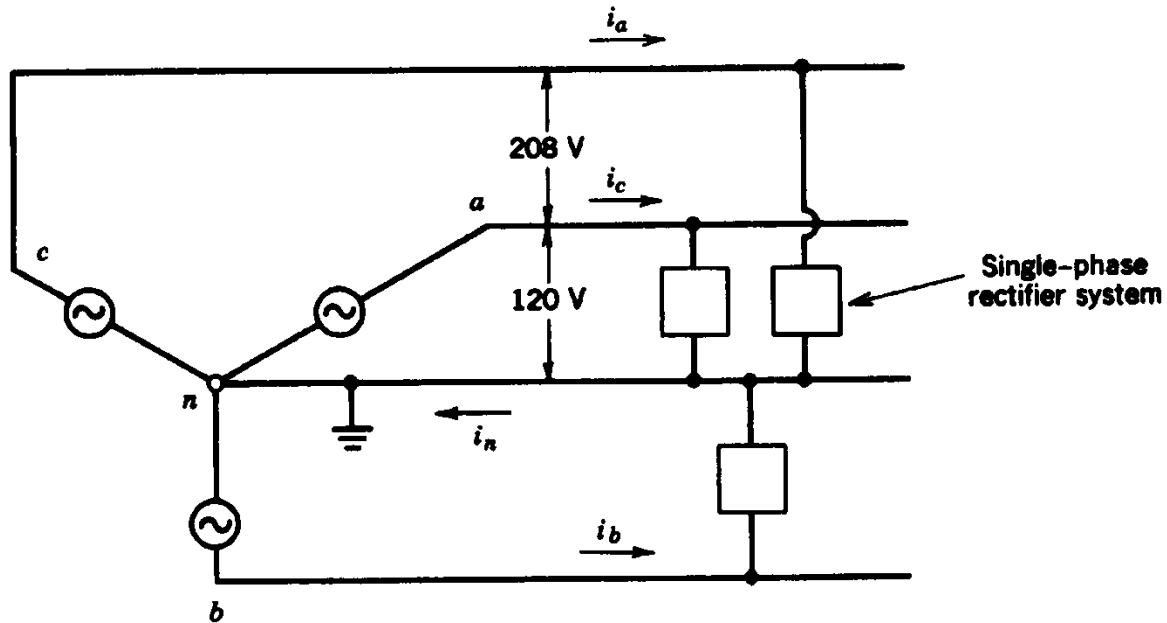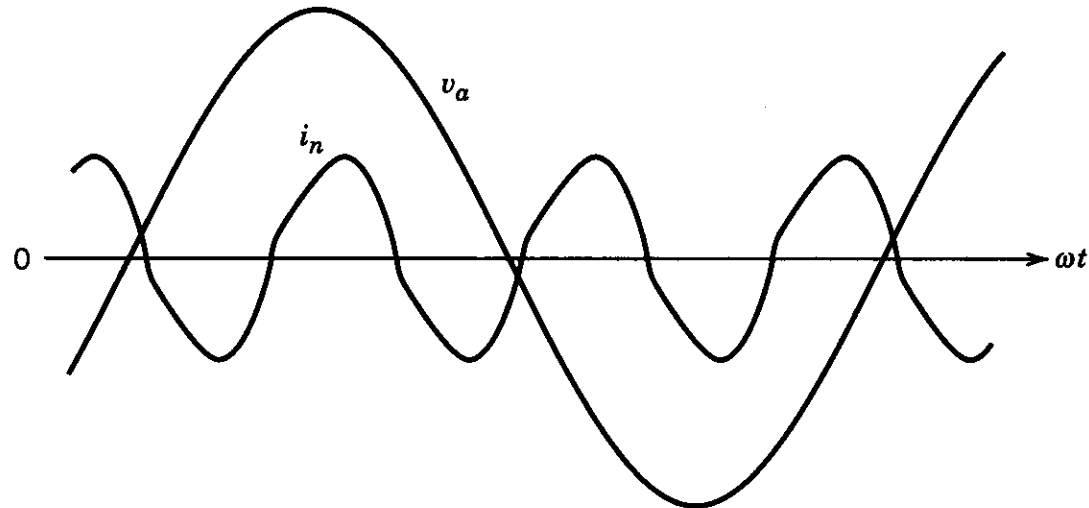
# A Three-Phase, Four-Wire System




- ▶ A common neutral wire is assumed




# Three-Phase, Full-Bridge Rectifier

- ▶ Commonly used

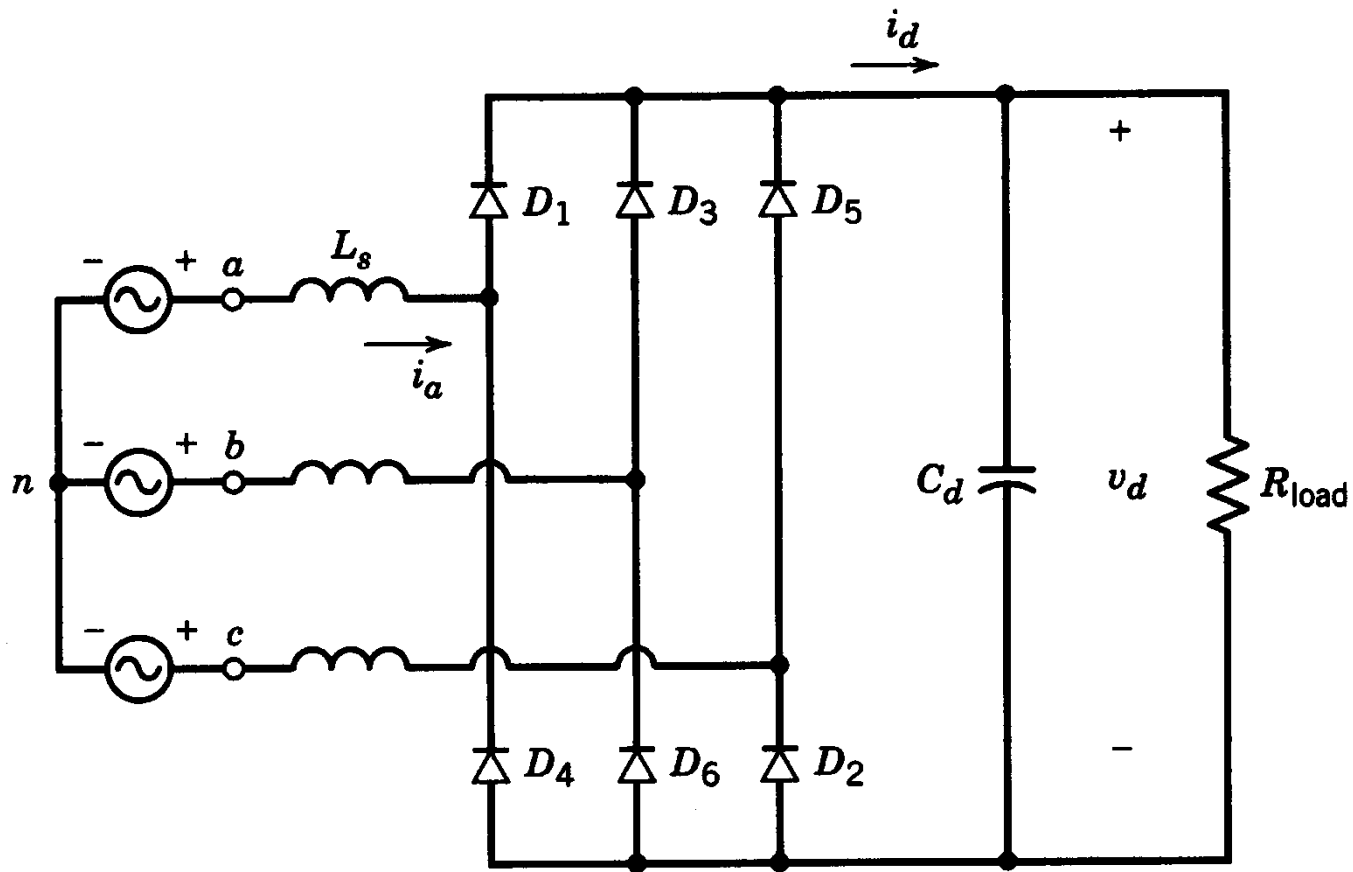


# Three-Phase, Full-Bridge Rectifier: Redrawn

- Two groups with three diodes each

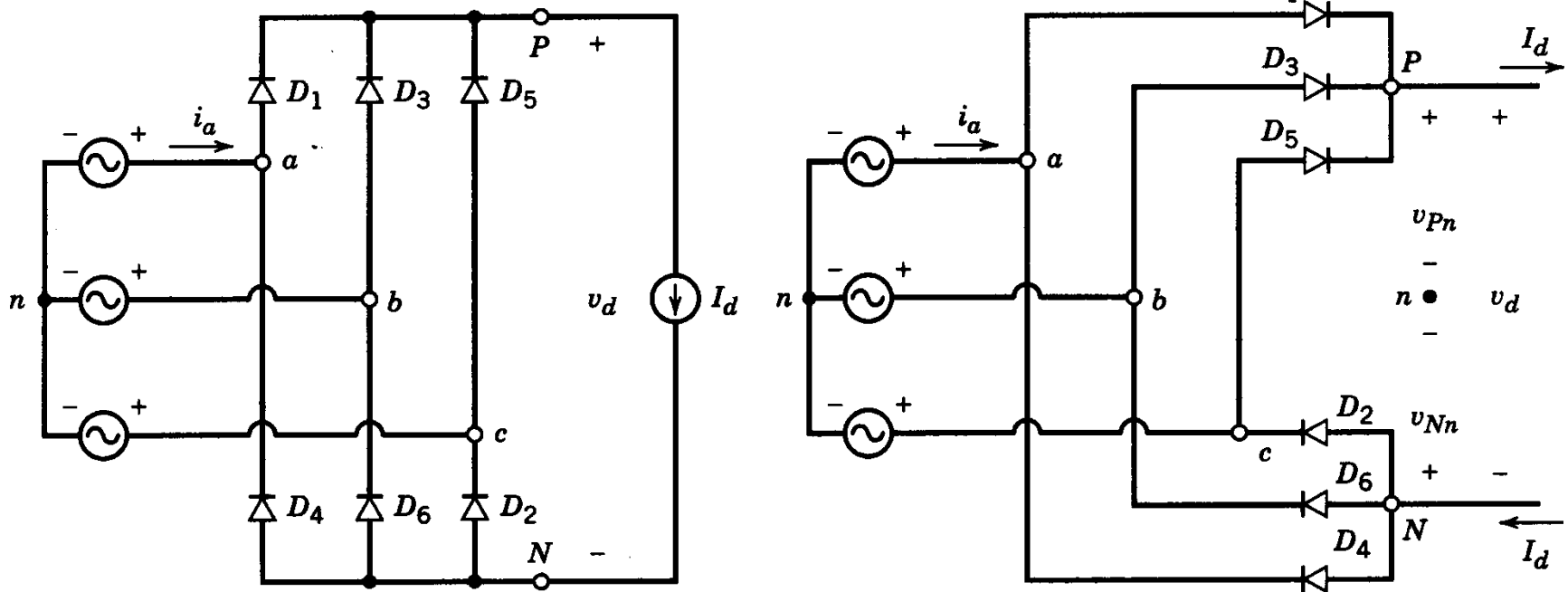


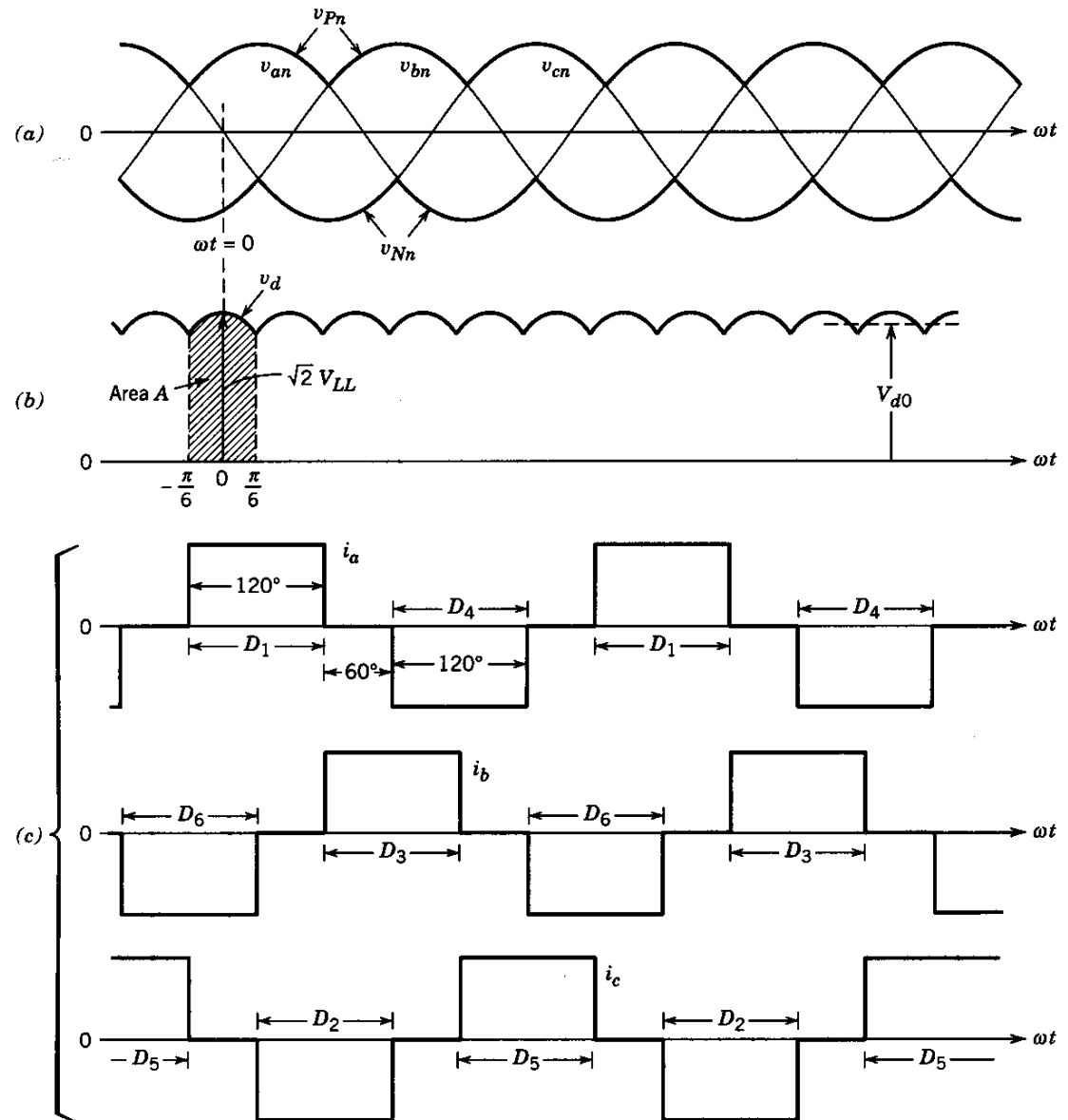
# Three-Phase, Full-Bridge Rectifier Waveforms



- Output current is assumed to be dc

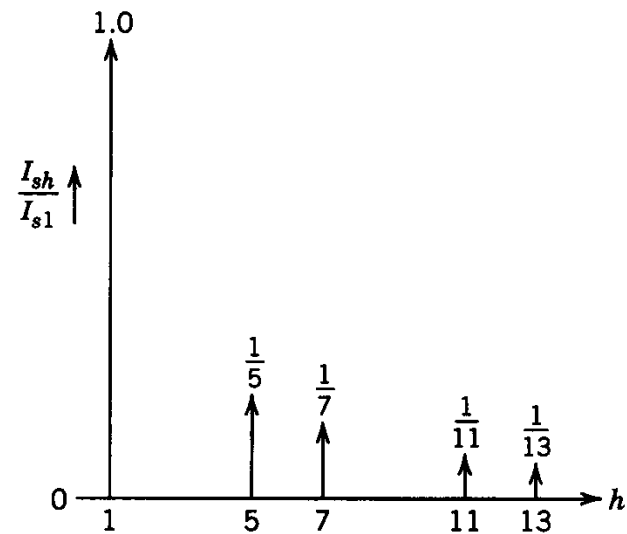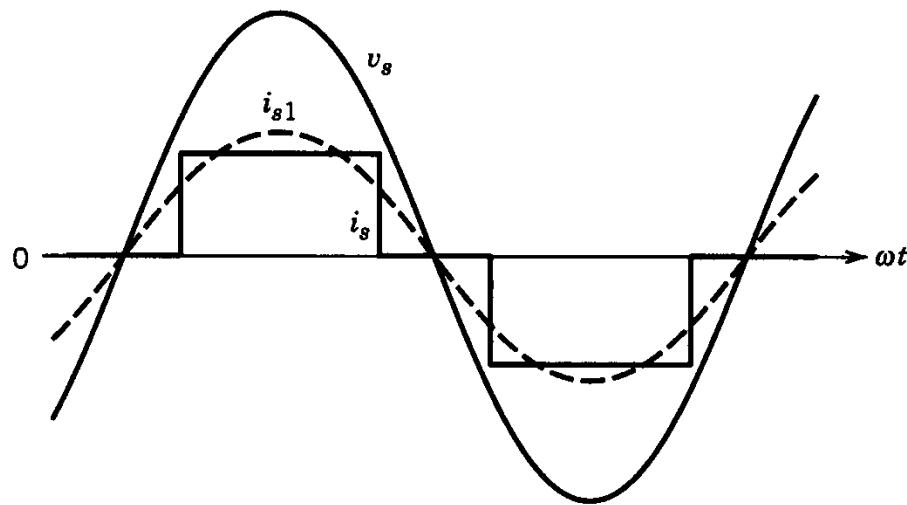
# Three-Phase, Full-Bridge Rectifier: Input Line-Current

- Assuming output current to be purely dc and zero ac-side inductance



# Three-Phase, Full-Bridge Rectifier




- ▶ Including the ac-side inductance

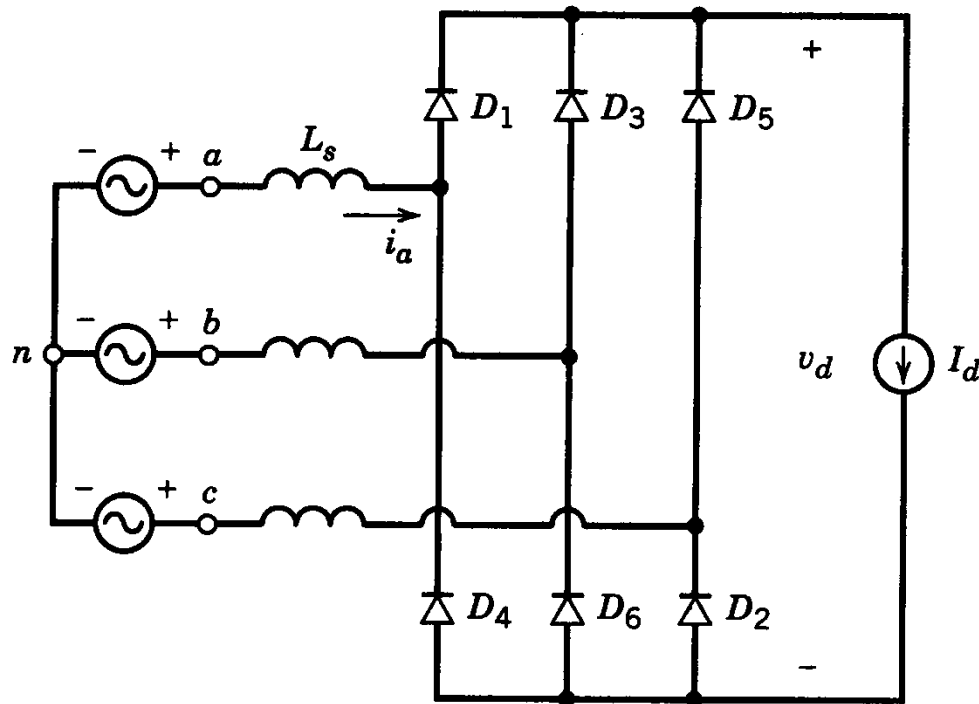



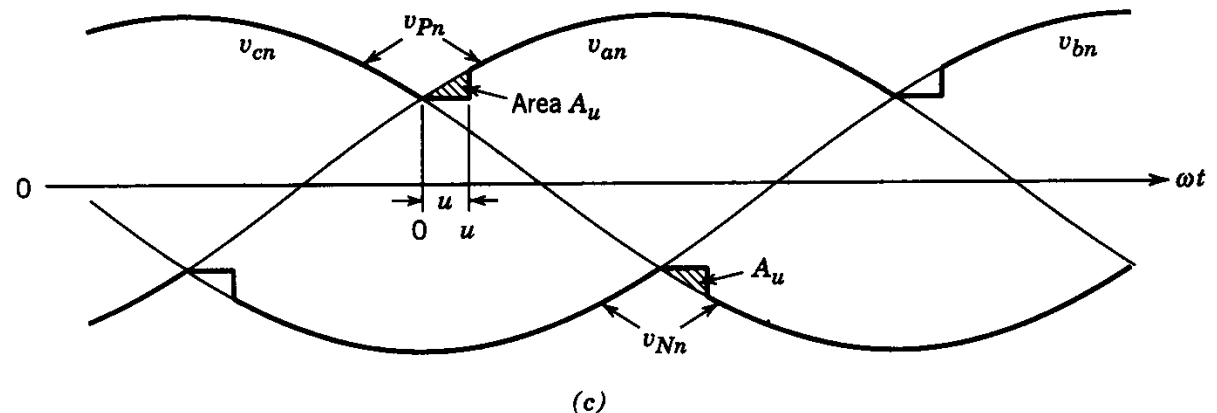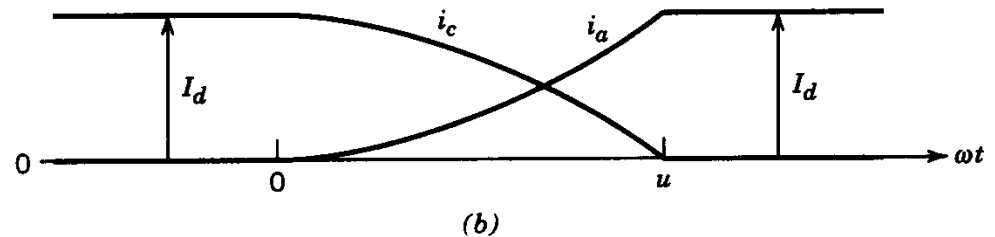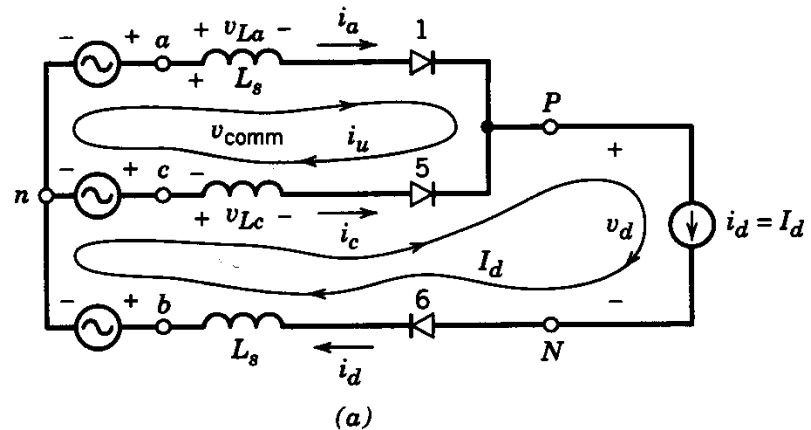
# 3-Phase Rectifier: Current Commutation

- ▶ output current is assumed to be purely dc



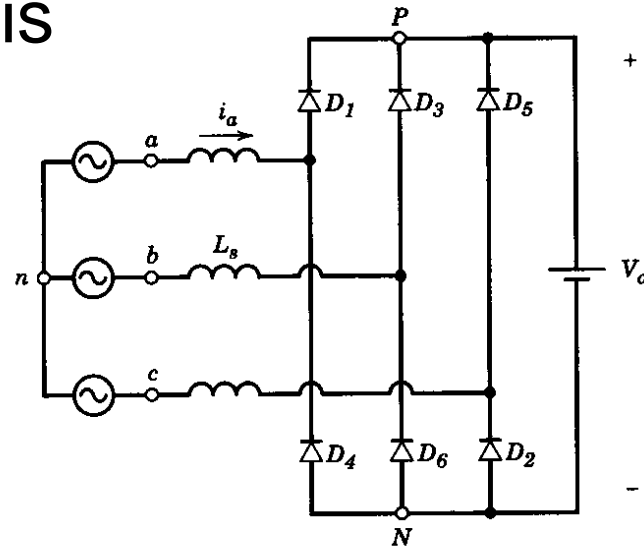
# Rectifier with a Large Filter Capacitor


- ▶ Output voltage is assumed to be purely dc



(a)

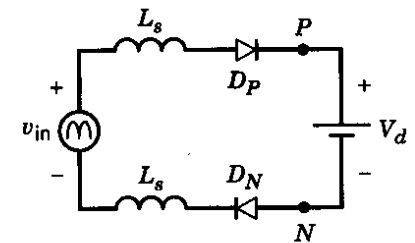


(b)

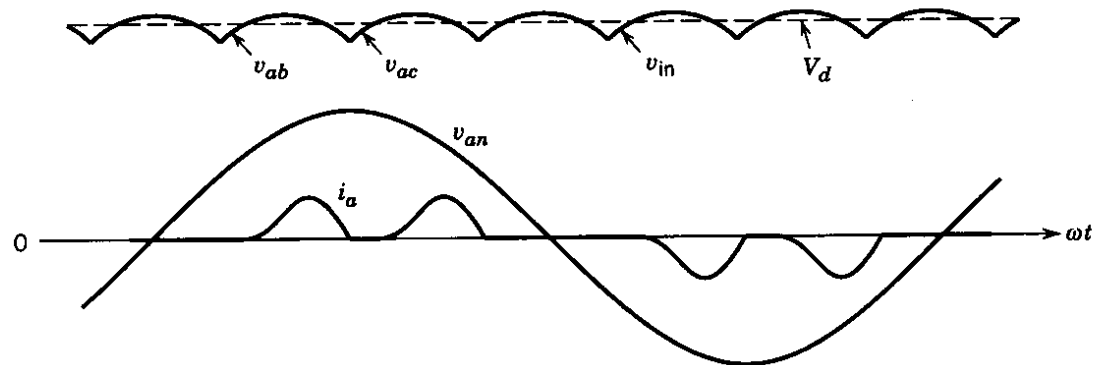

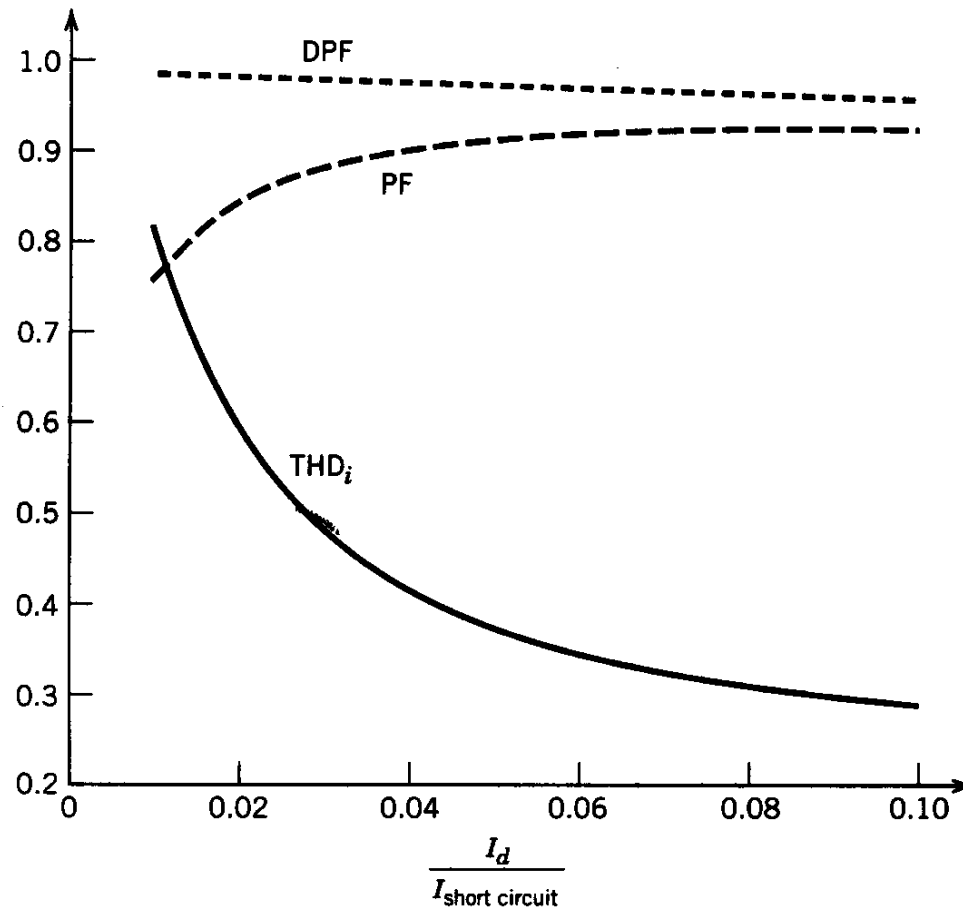
# Three-Phase, Full-Bridge Rectifier

- ▶ THD, PF and DPF as functions of load current



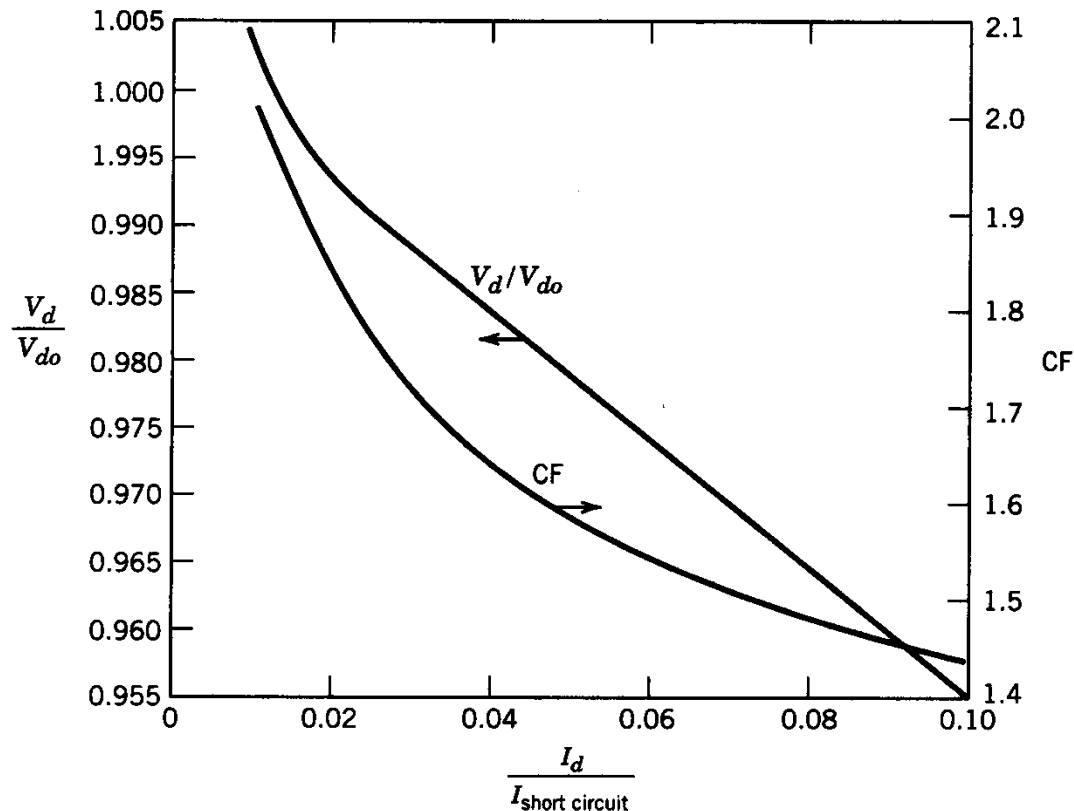
# Crest Factor versus the Current Loading


- ▶ The Crest Factor is very high at low values of current



# Three-Phase Rectifier Waveforms

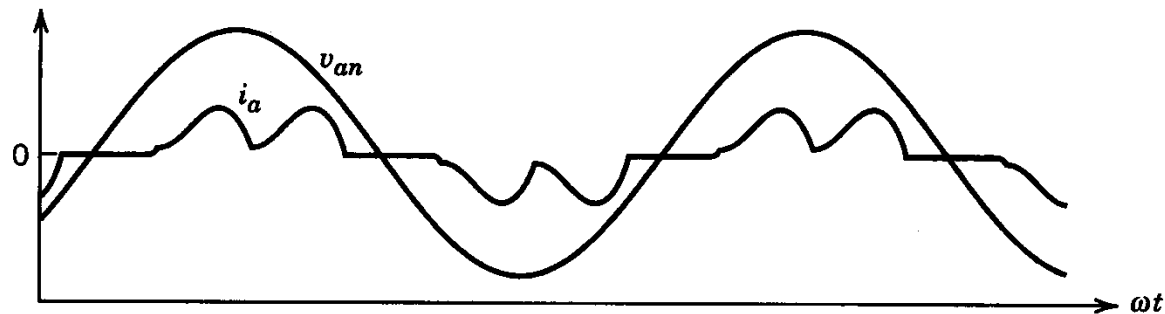

(a)

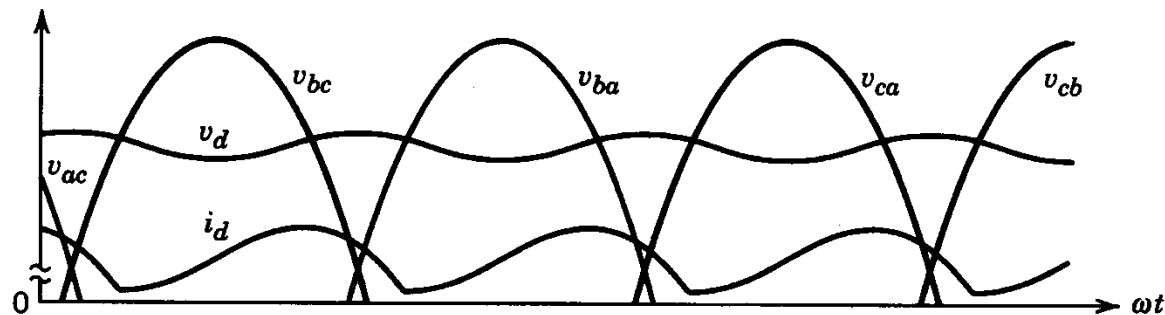

**Figure 5-39** Waveforms in the rectifier of Fig. 5-30, obtained in Example 5-7.