



Power Electronics

5. DC-DC Converters




Dr inż. Dariusz Janiszewski

Plan wykładu

- ▶ Wprowadzenie do przetwarzania DC-DC
- ▶ Idea PWM
- ▶ Step-down Converter – Buck
- ▶ Step-up Converter – Boost
- ▶ Buck-Boost Converter
- ▶ Cuk Converter
- ▶ SEPIC Converter
- ▶ ZETA Converter



Block Diagram of DC-DC Converters

- Functional block diagram


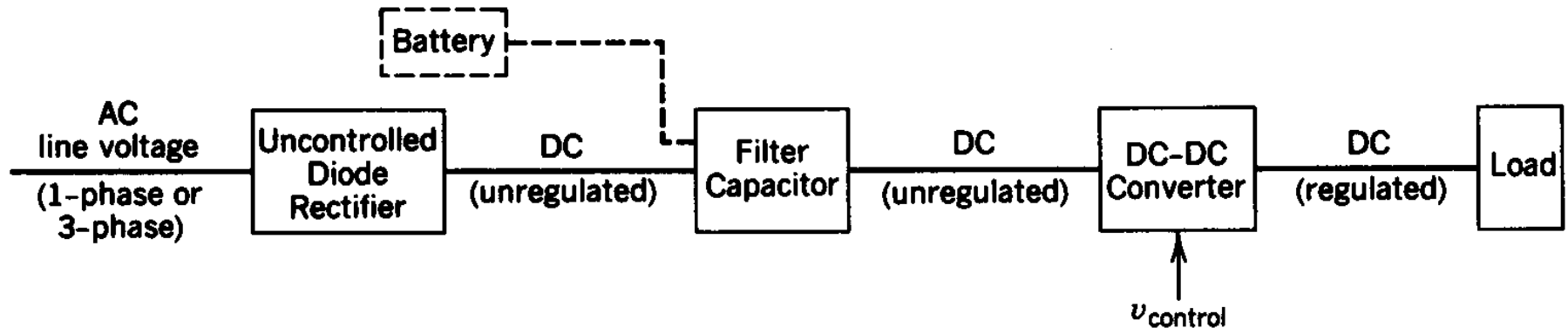


Stepping Down a DC Voltage – Idea

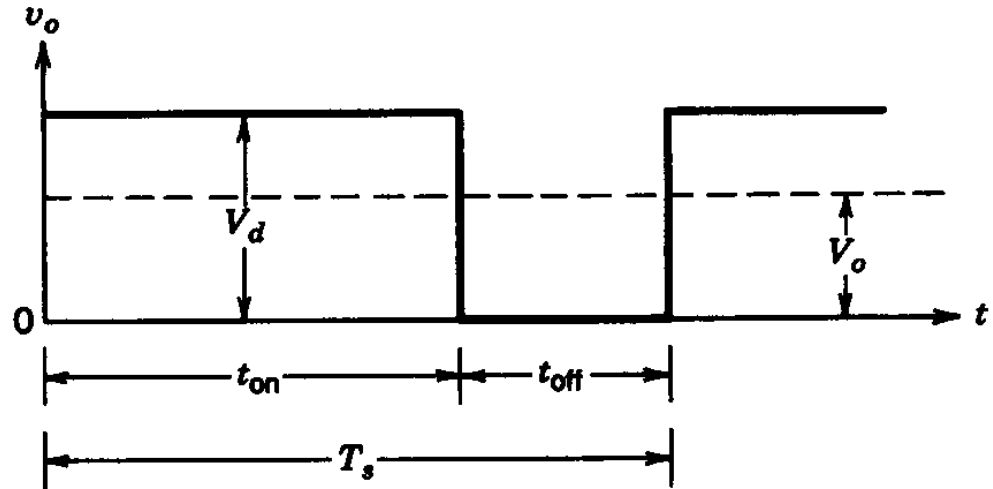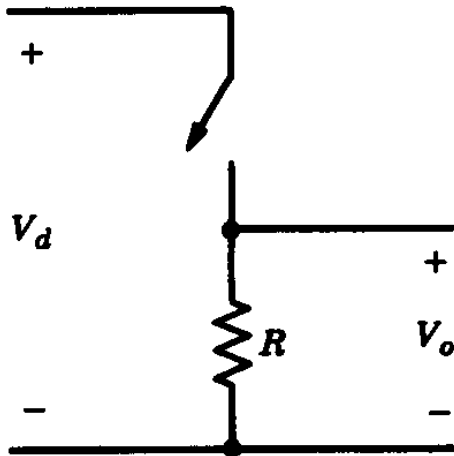- ▶ A simple approach that shows the evolution



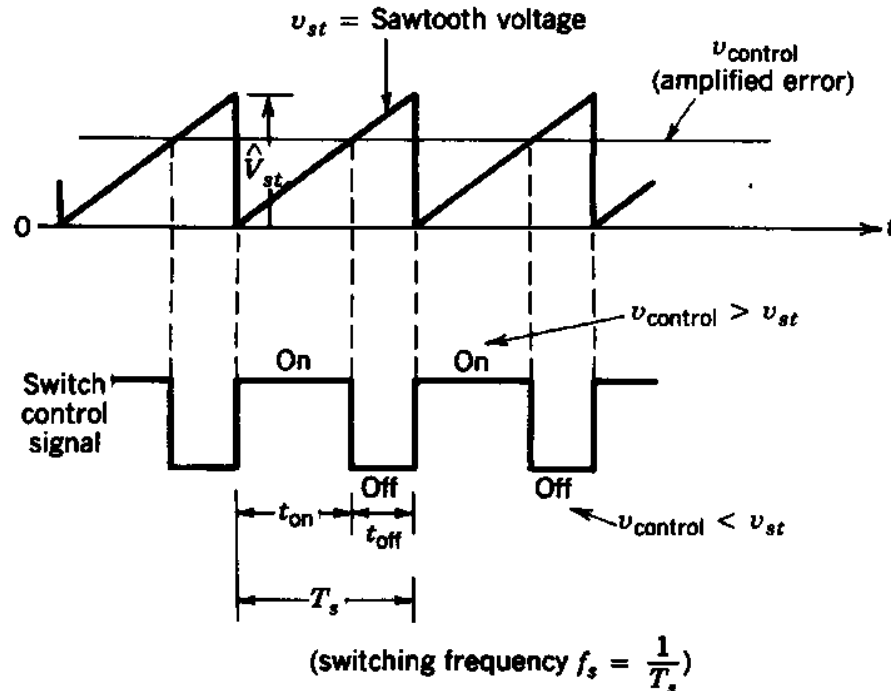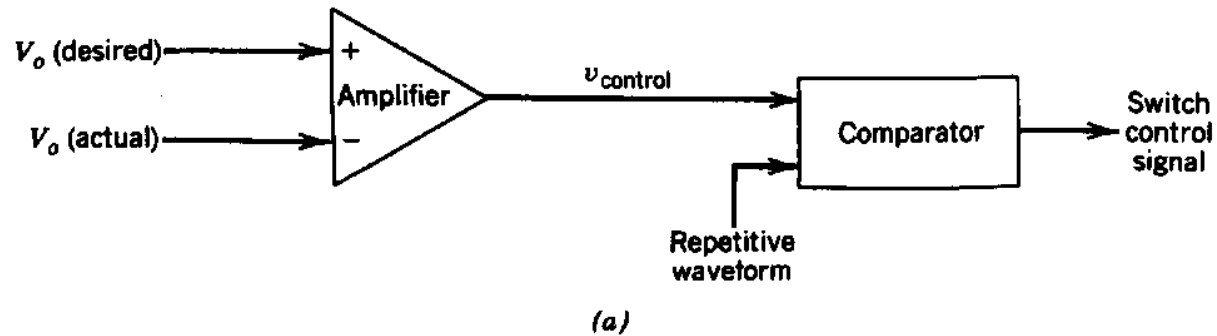
Pulse-Width Modulation in DC-DC Converters



Step-Down DC-DC Converter



– buck converter

► Pulsating input to the low-pass filter

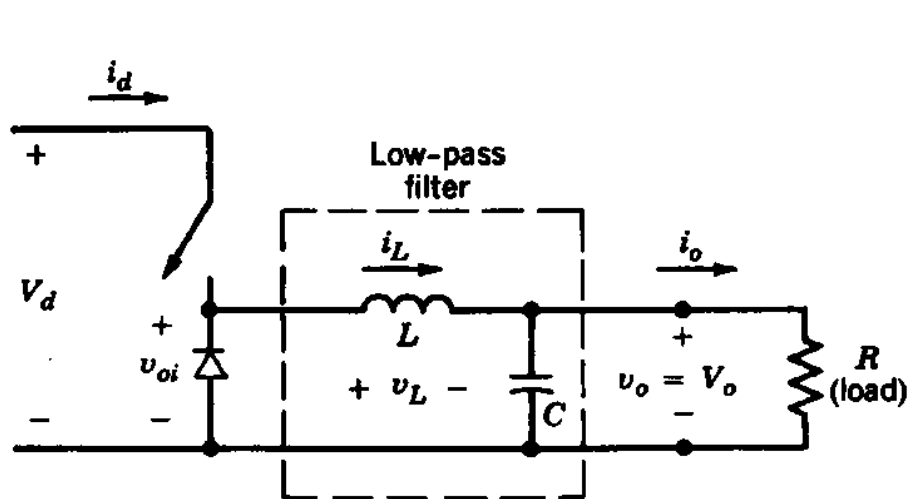


$$\frac{V_o}{V_d} = D$$

$$D = \frac{t_{on}}{T_s}$$

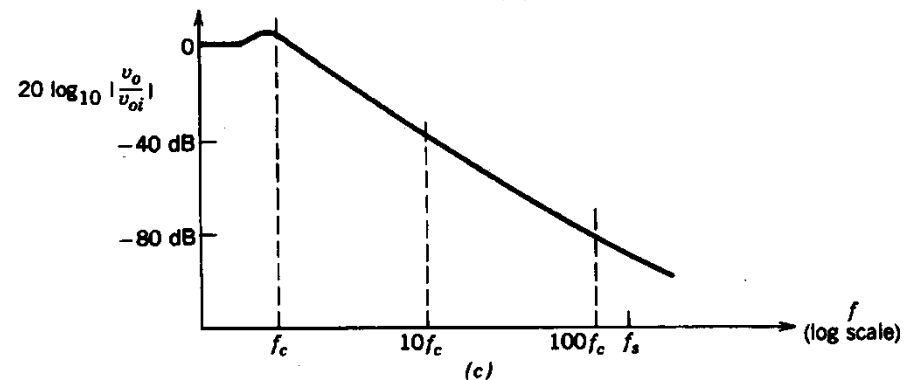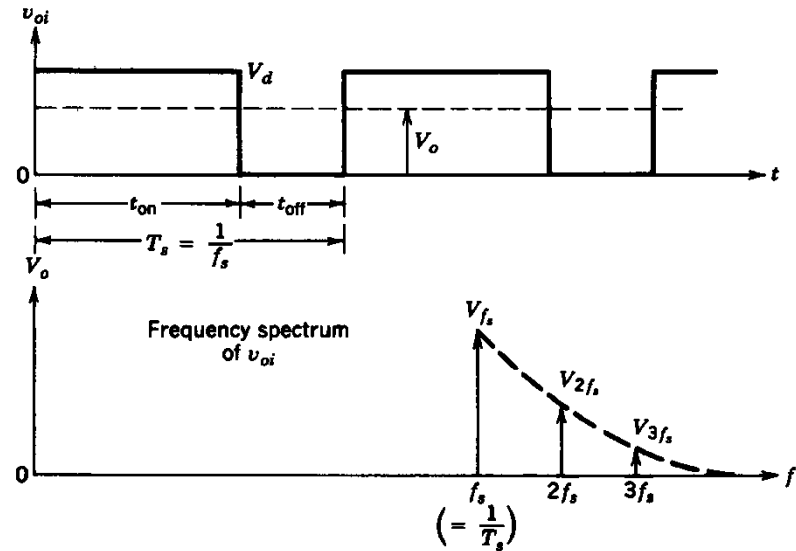



Step-Down DC-DC Converter Waveforms

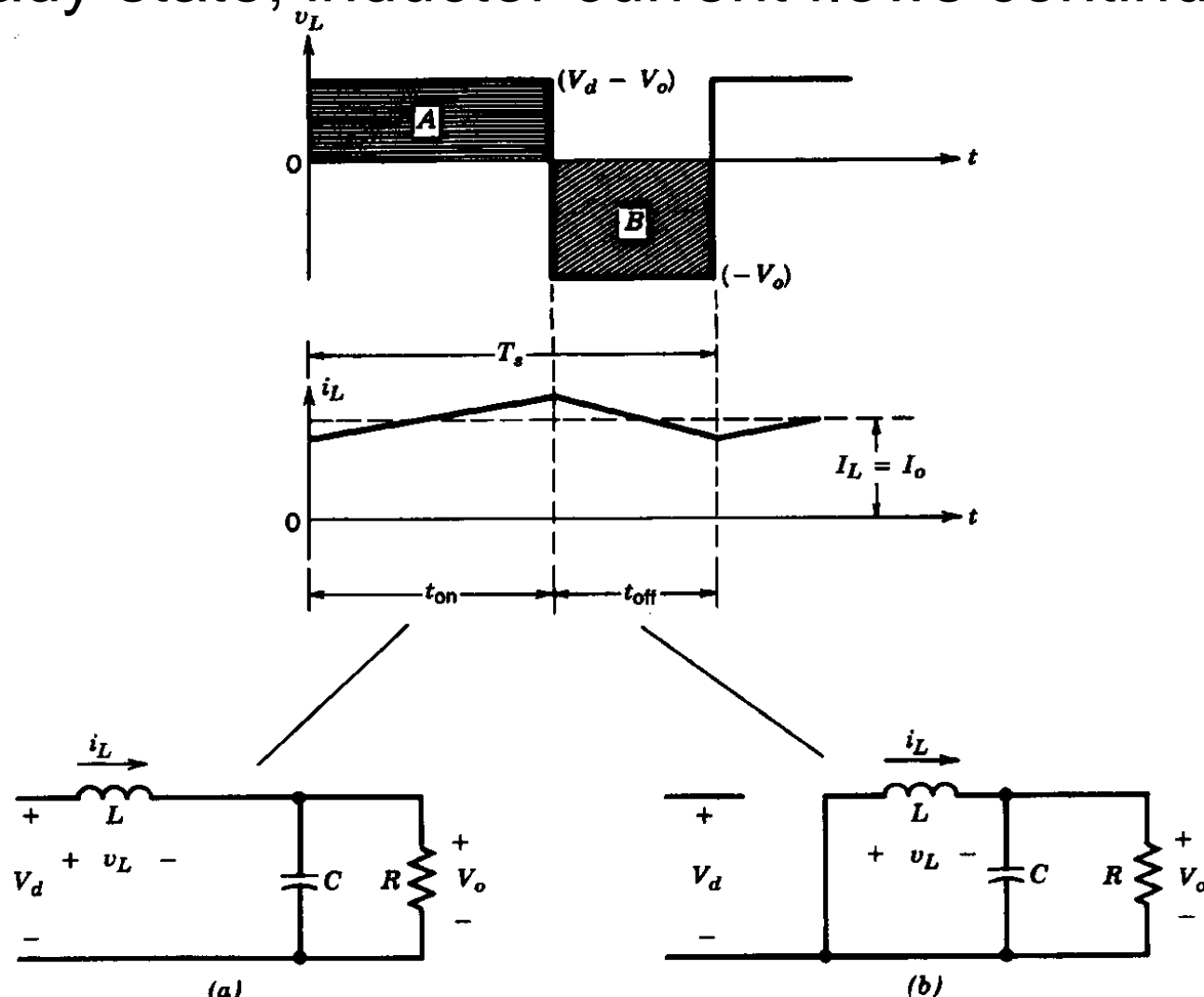- ▶ Steady state; inductor current flows continuously






Step-Down DC-DC Converter: Waveforms at the boundary of Cont./Discont. Conduction

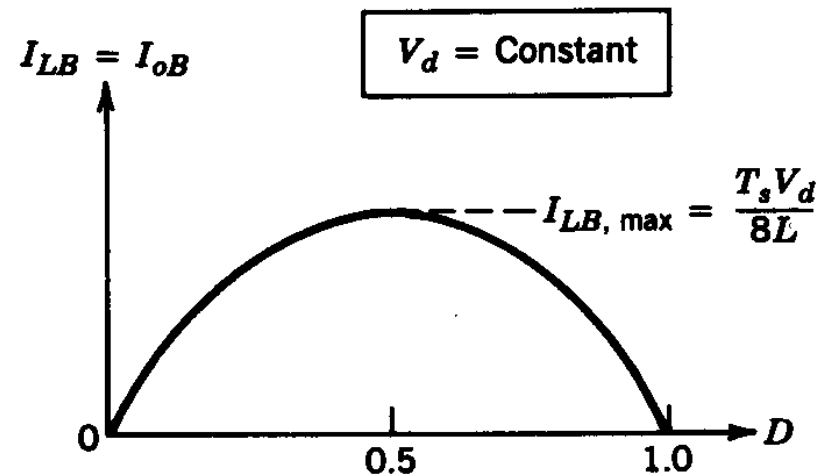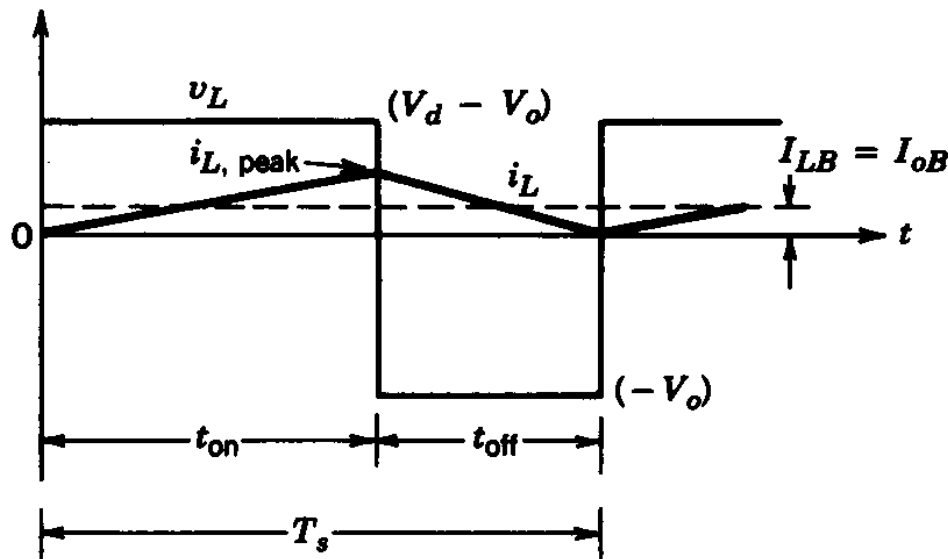- ▶ Critical current below which inductor current becomes discontinuous




Step-Down DC-DC Converter: Discontinuous Conduction Mode

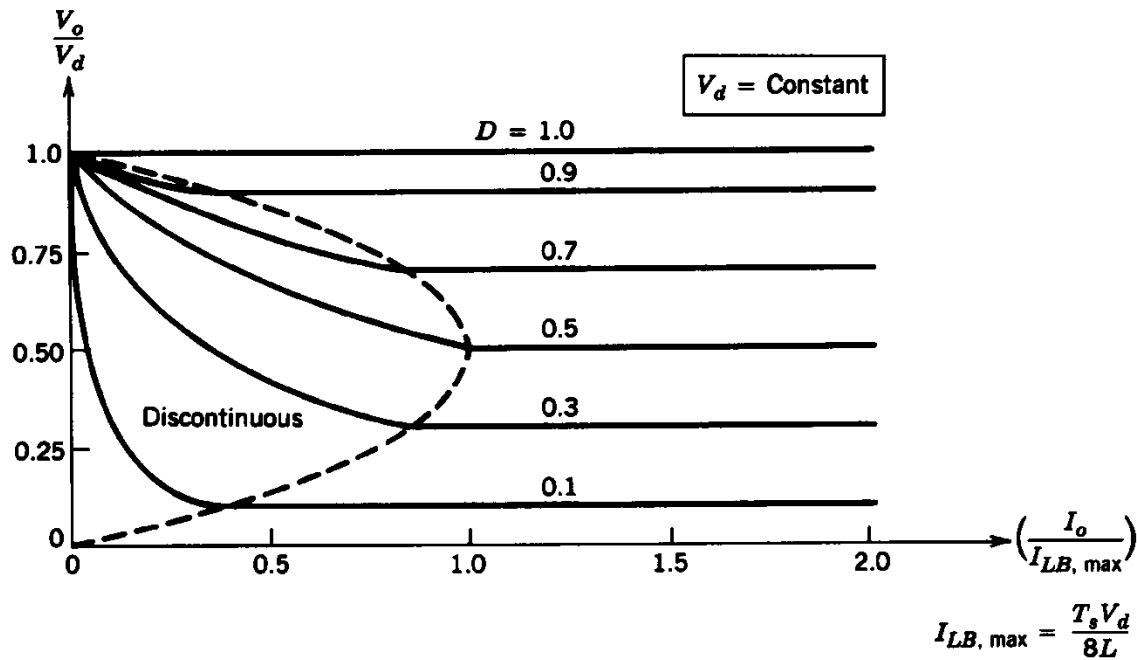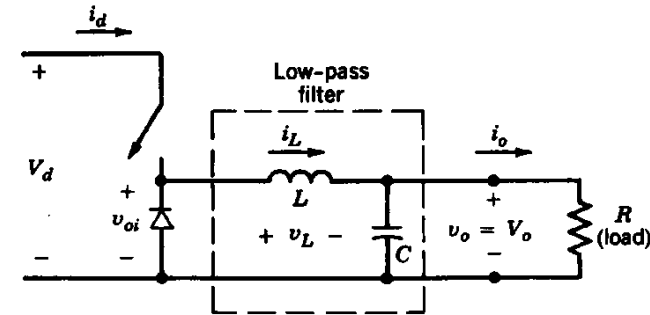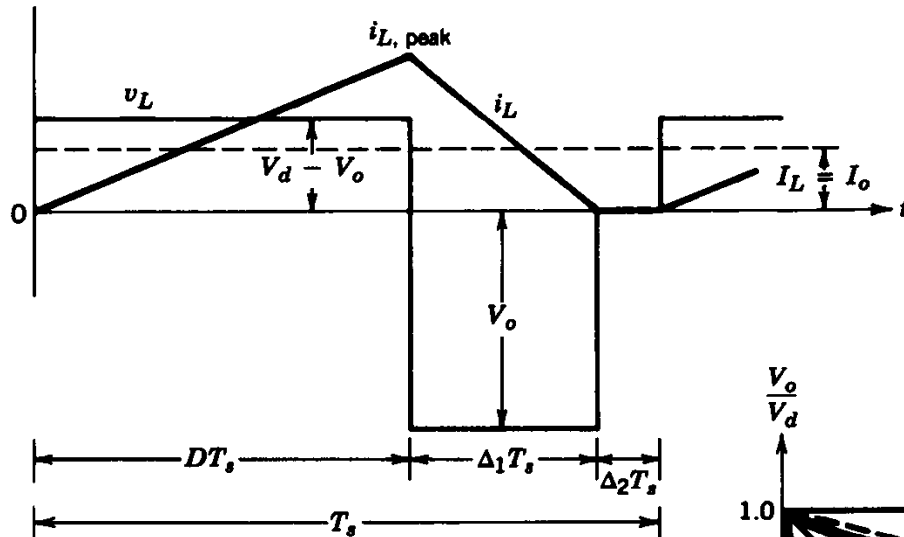- Steady state; inductor current discontinuous







Step-Down DC-DC Converter: Limits of Cont./Discont. Conduction

- Output voltage is kept constant

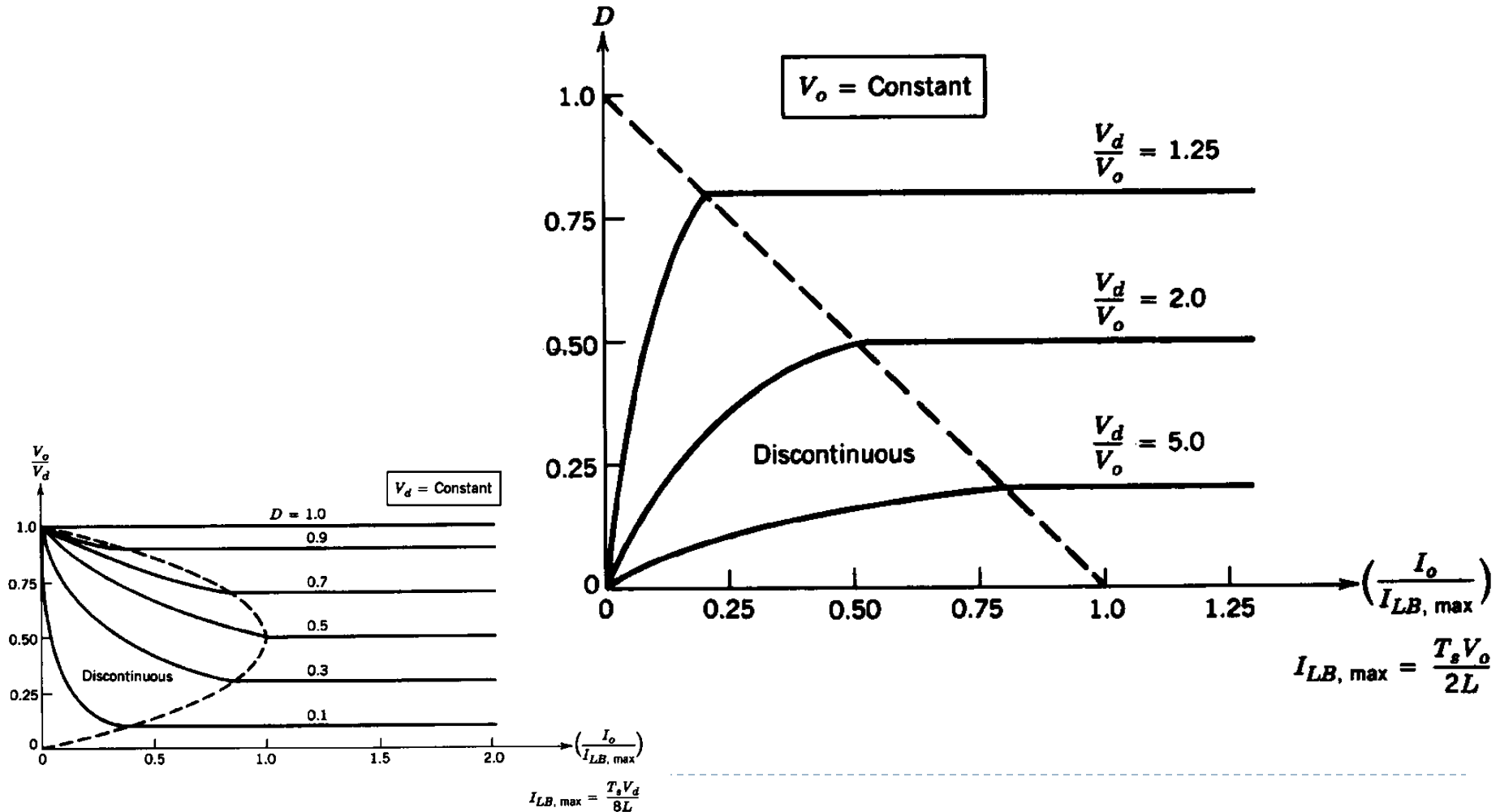

Step-Down Conv.: Output Voltage Ripple


- ESR is assumed to be zero

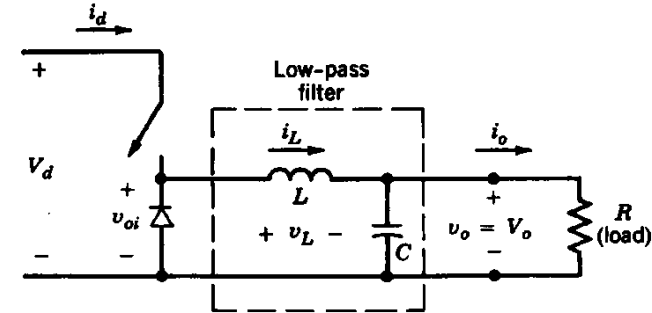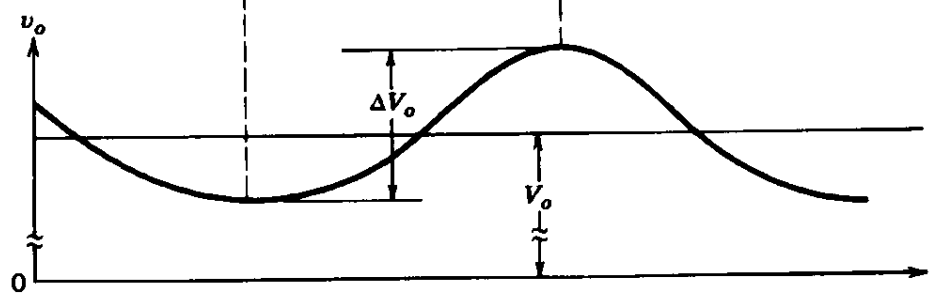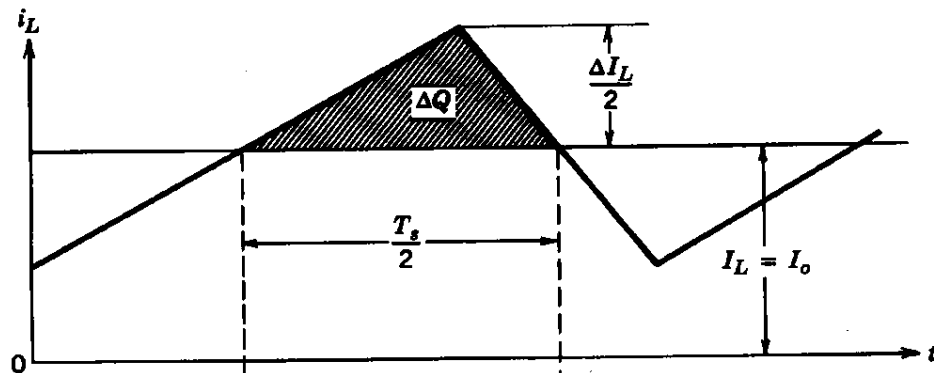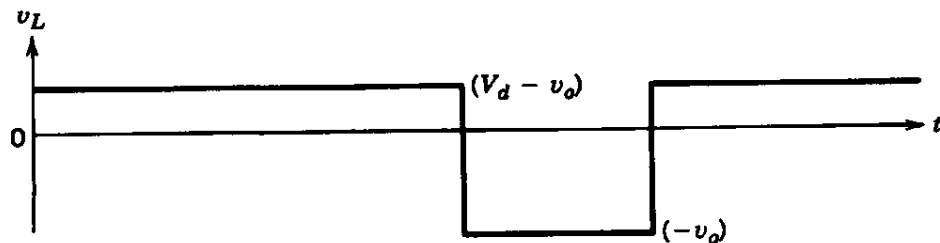

Step-Up DC-DC Converter

– Boost Converter

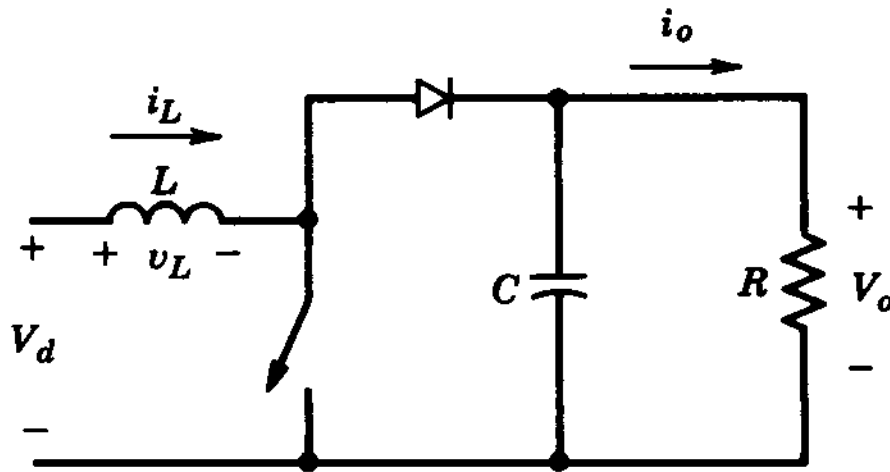- ▶ Output voltage must be greater than the input




$$D = \frac{t_{on}}{T_s}$$

$$\frac{V_o}{V_d} = \frac{1}{1 - D}$$




Step-Up DC-DC Converter Waveforms

Continuous current conduction mode

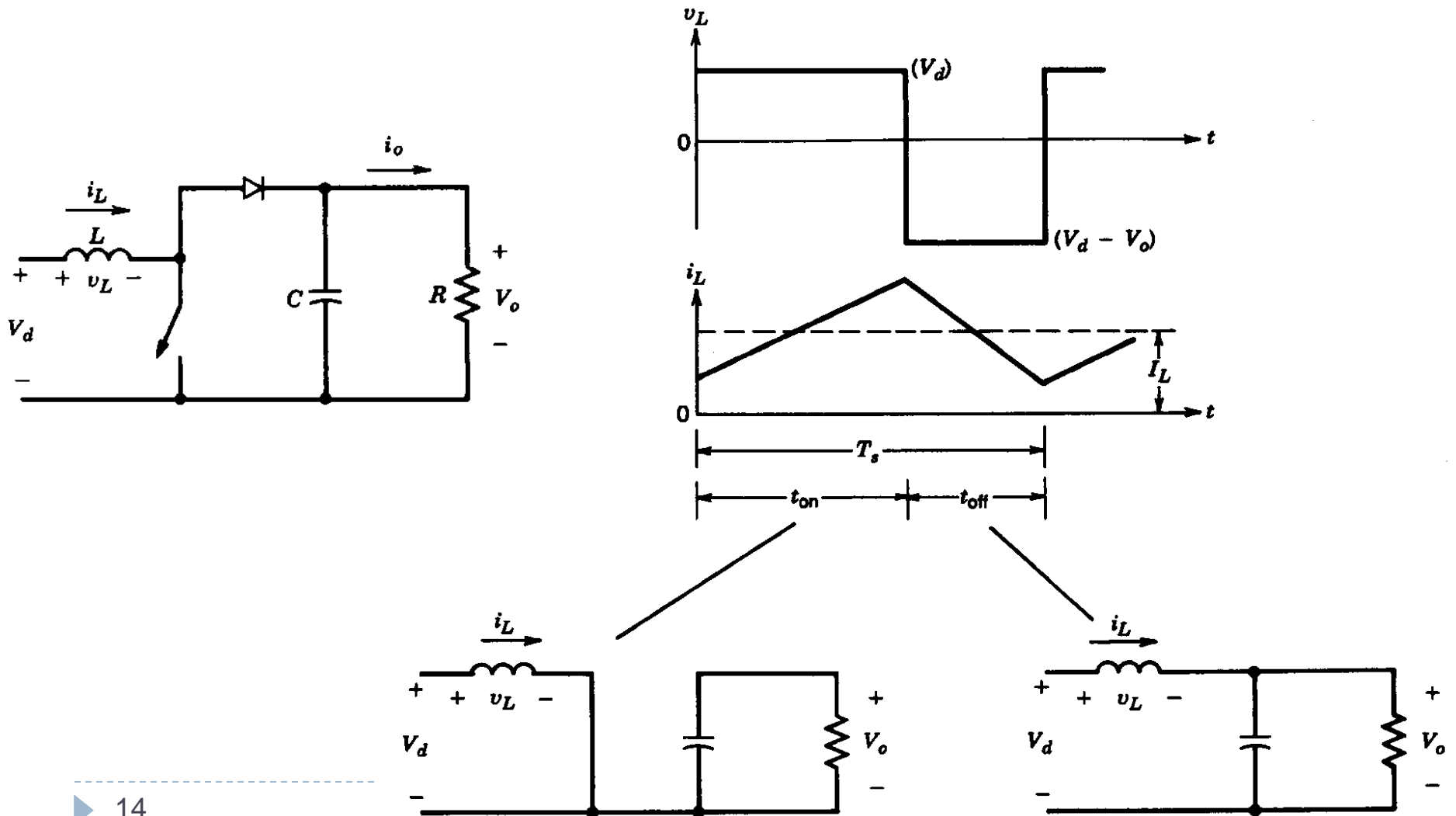



Step-Up DC-DC Converter: Limits of Cont./Discont. Conduction

- ▶ The output voltage is held constant

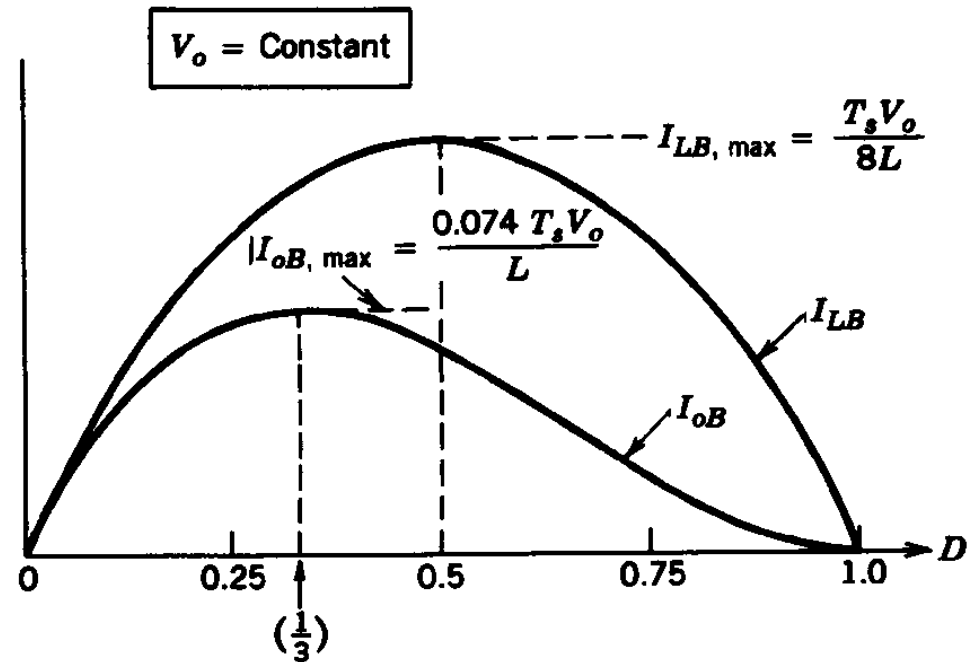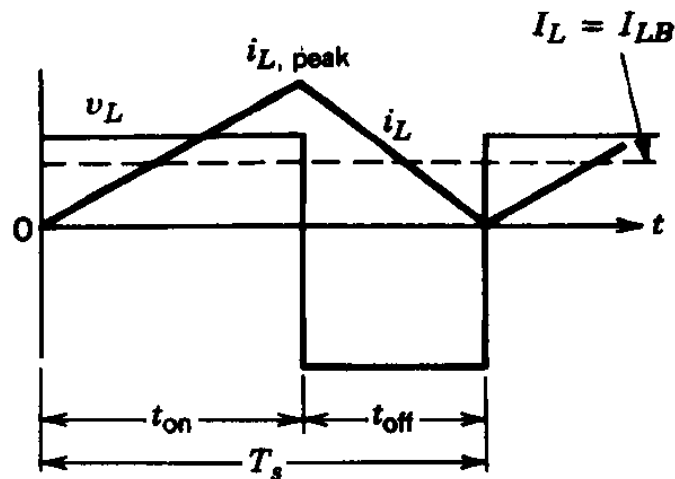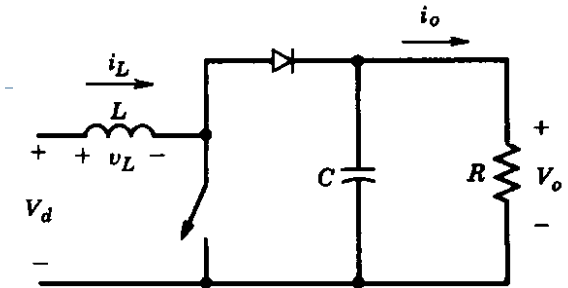

Step-Up DC-DC Converter: Discont. Conduction Mode



- Occurs at light loads

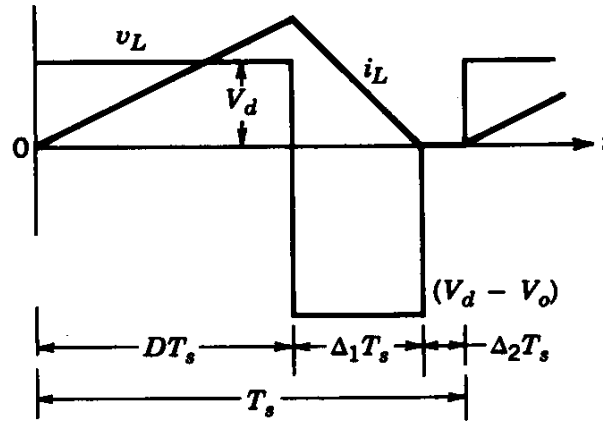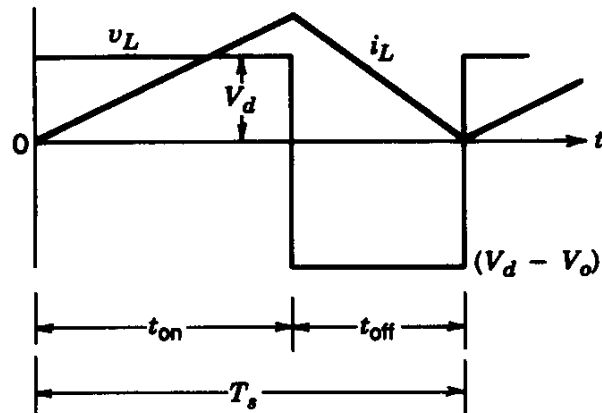

Step-Up DC-DC Converter: Limits of Cont./Discont. Conduction

- ▶ The output voltage is held constant



$$\frac{V_o}{V_d} = \frac{1}{1-D}$$

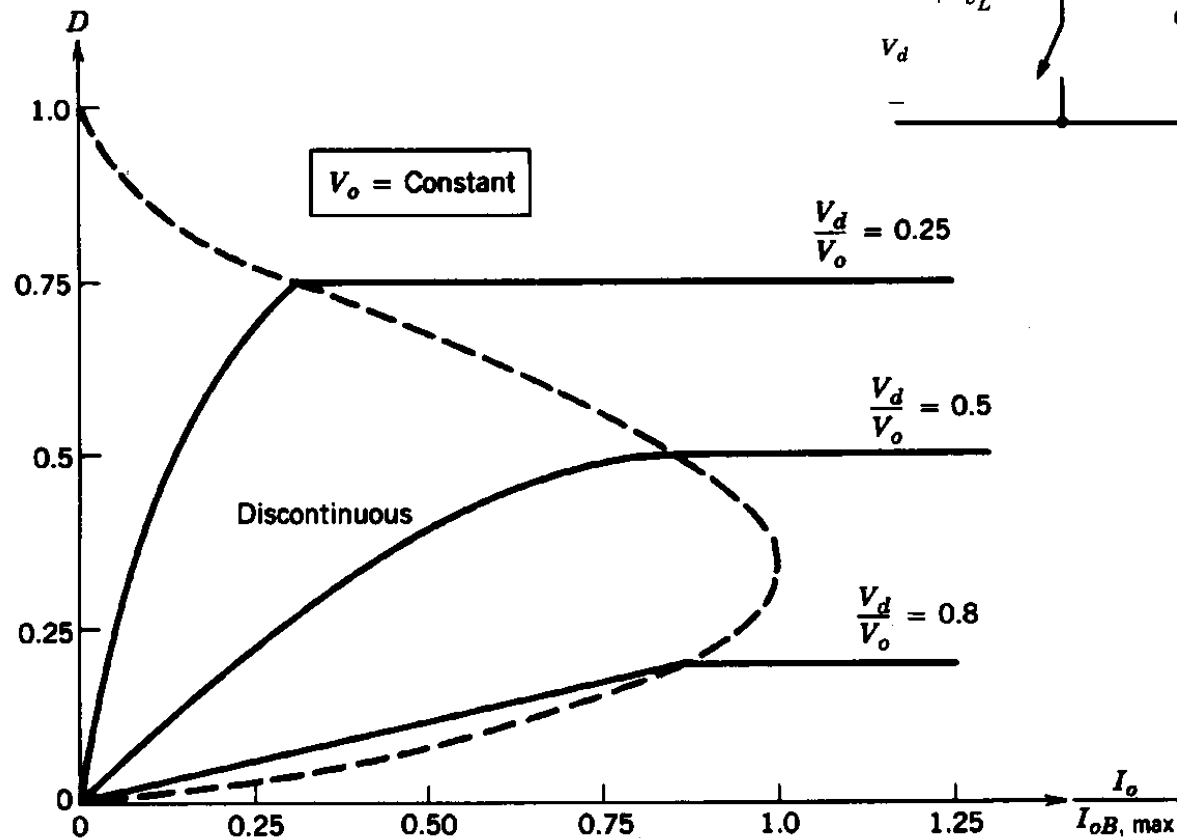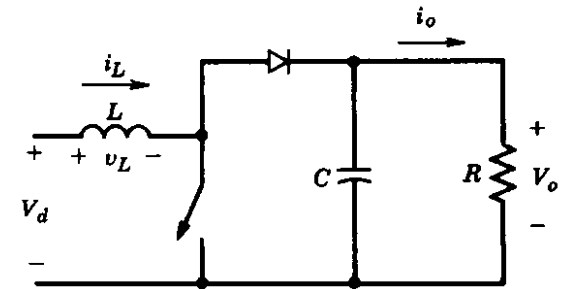

$$I_{oB, \max} = 0.074 \frac{T_s V_o}{L}$$


Step-Up DC-DC Converter Output Ripple

- ESR is assumed to be zero

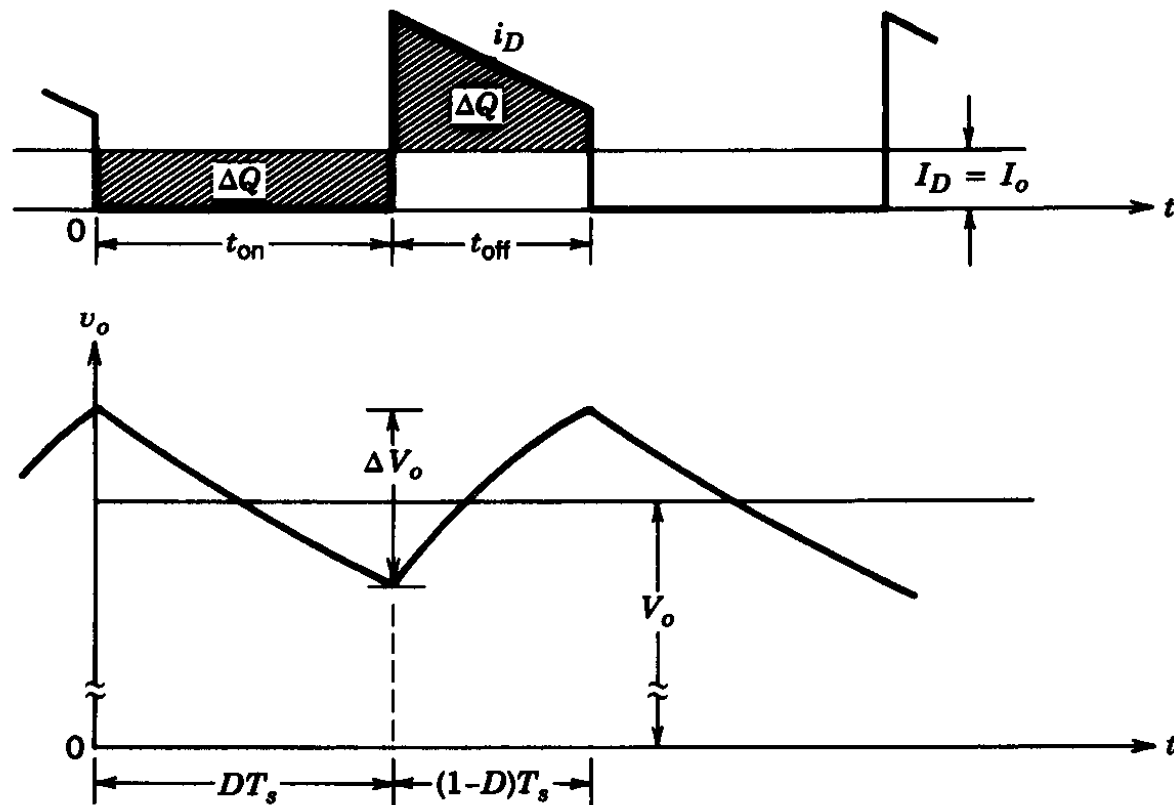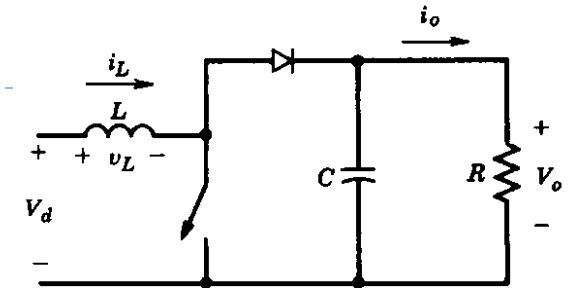


Step-Up DC-DC Converter: Effect of Parasitics

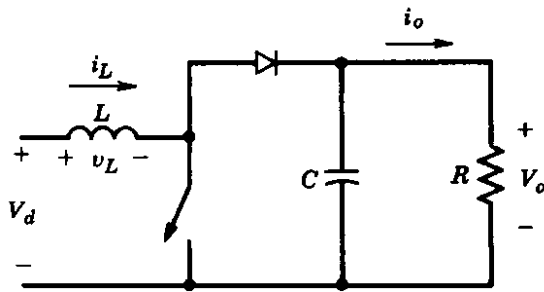- ▶ The duty-ratio is generally limited before the parasitic effects become significant




$$\frac{V_o}{V_d} = \frac{1}{1 - D}$$

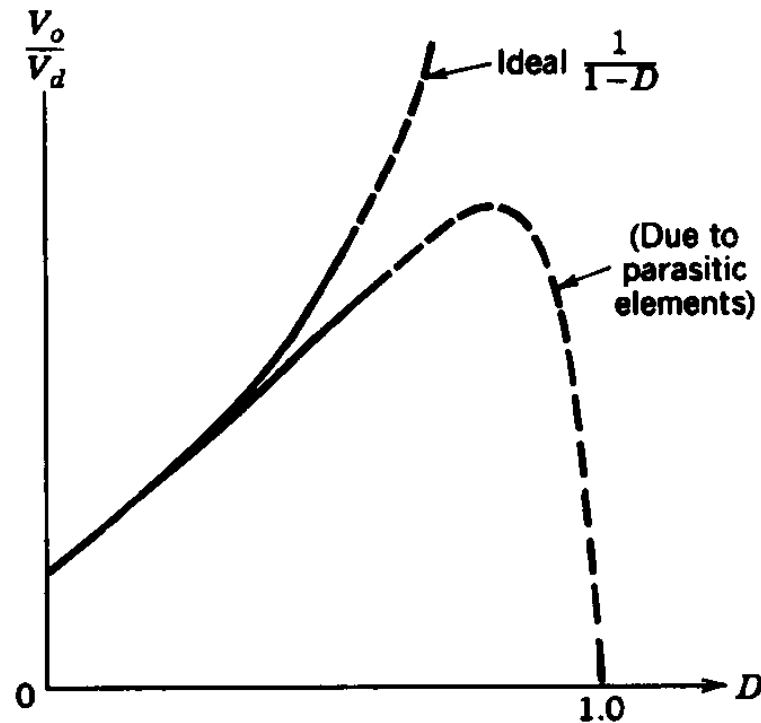

Step-Down/Up DC-DC Converter Buck-boost Converter




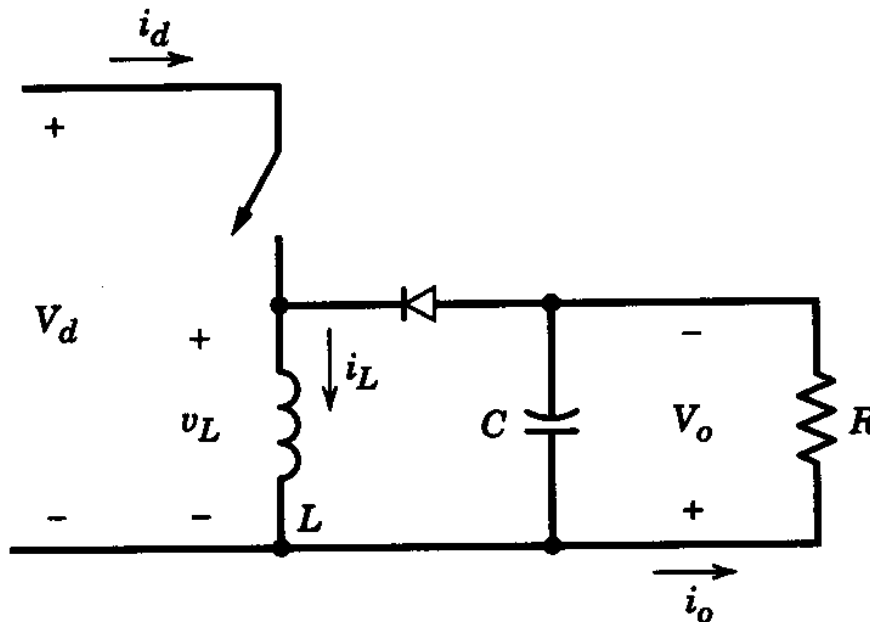
- ▶ The output voltage can be higher or lower than the input voltage



$$\frac{V_o}{V_d} = D \frac{1}{1 - D}$$



Step-Down/Up DC-DC Converter Waveforms

► Continuation conduction mode

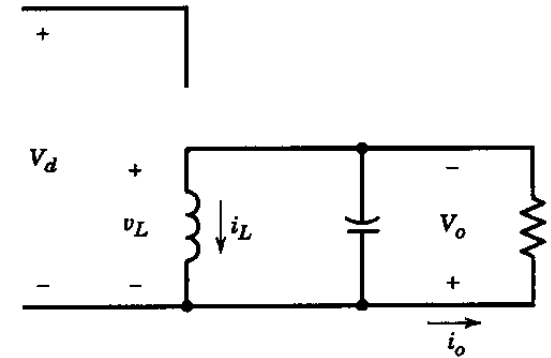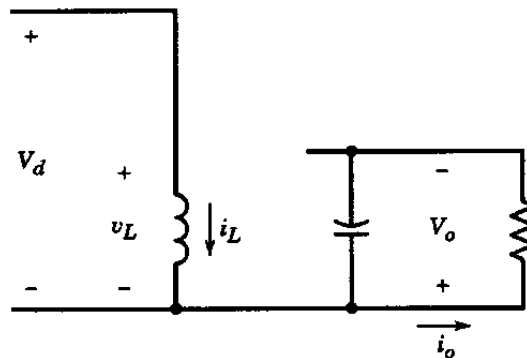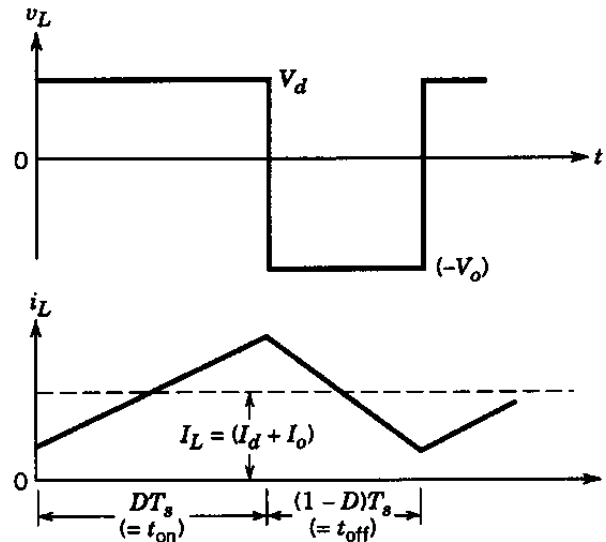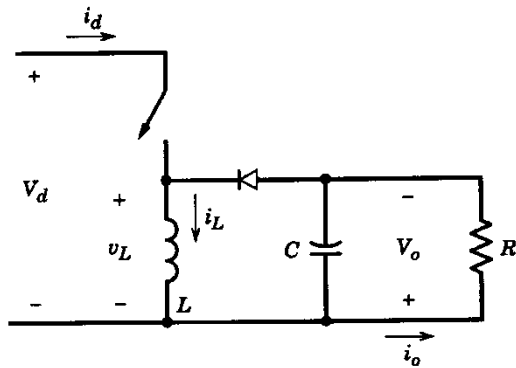



Step-Down/Up DC-DC Converter Limits of Cont./Discont. Conduction

- ▶ The output voltage is held constant

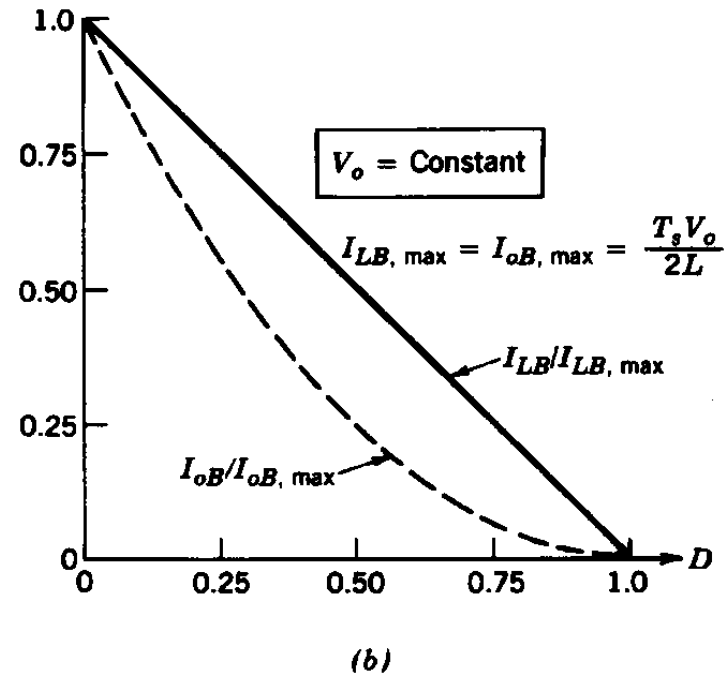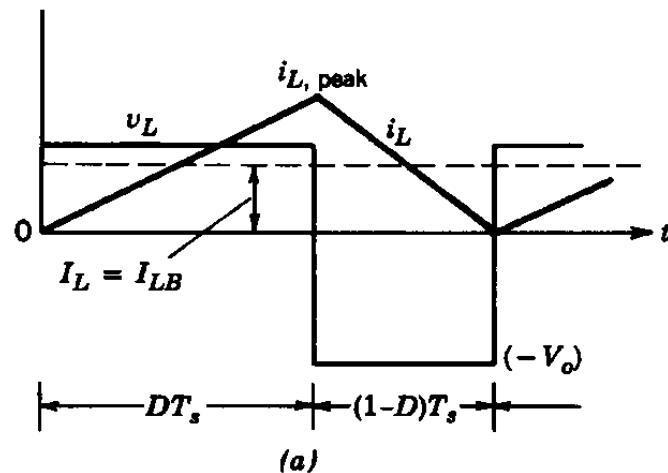

Step-Down/Up DC-DC Converter: Discontinuous Conduction Mode



- This occurs at light loads

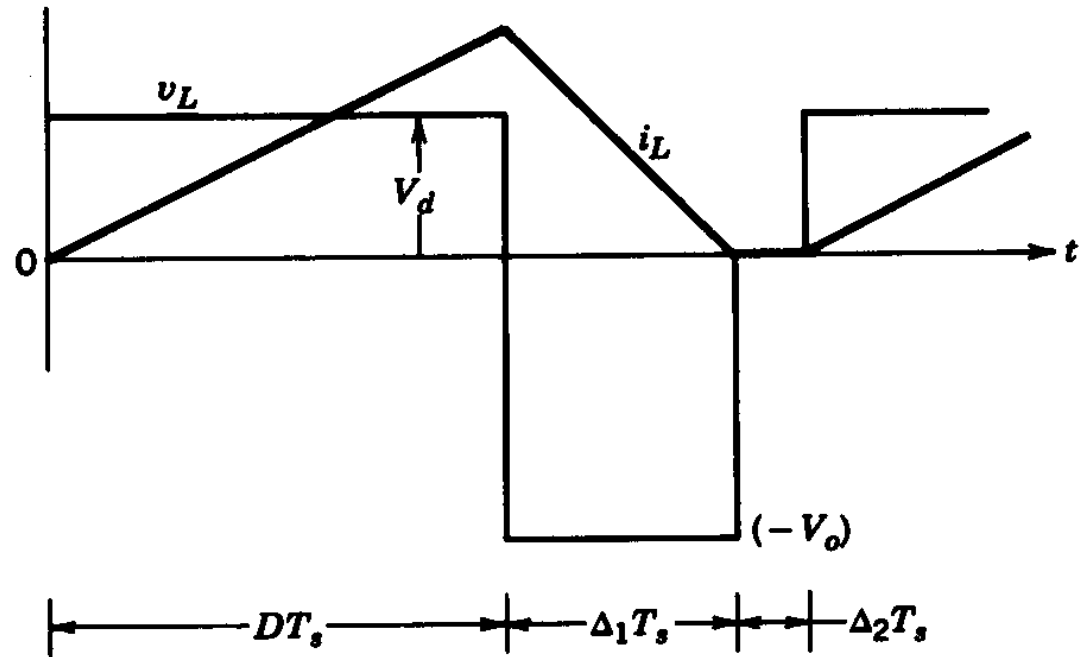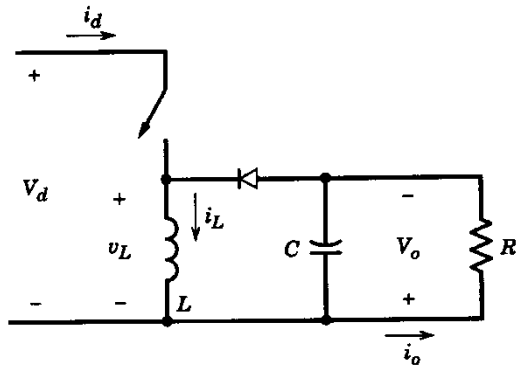

Step-Up DC-DC Converter

Limits of Cont./Discont. Conduction

- ▶ The output voltage is held constant

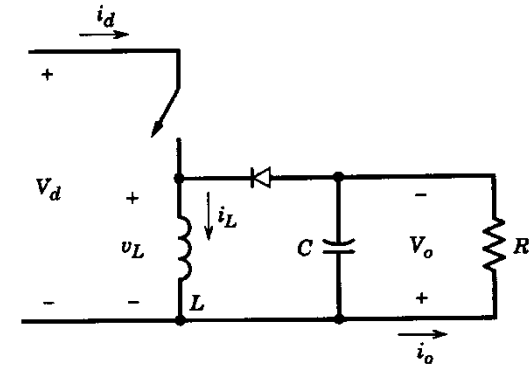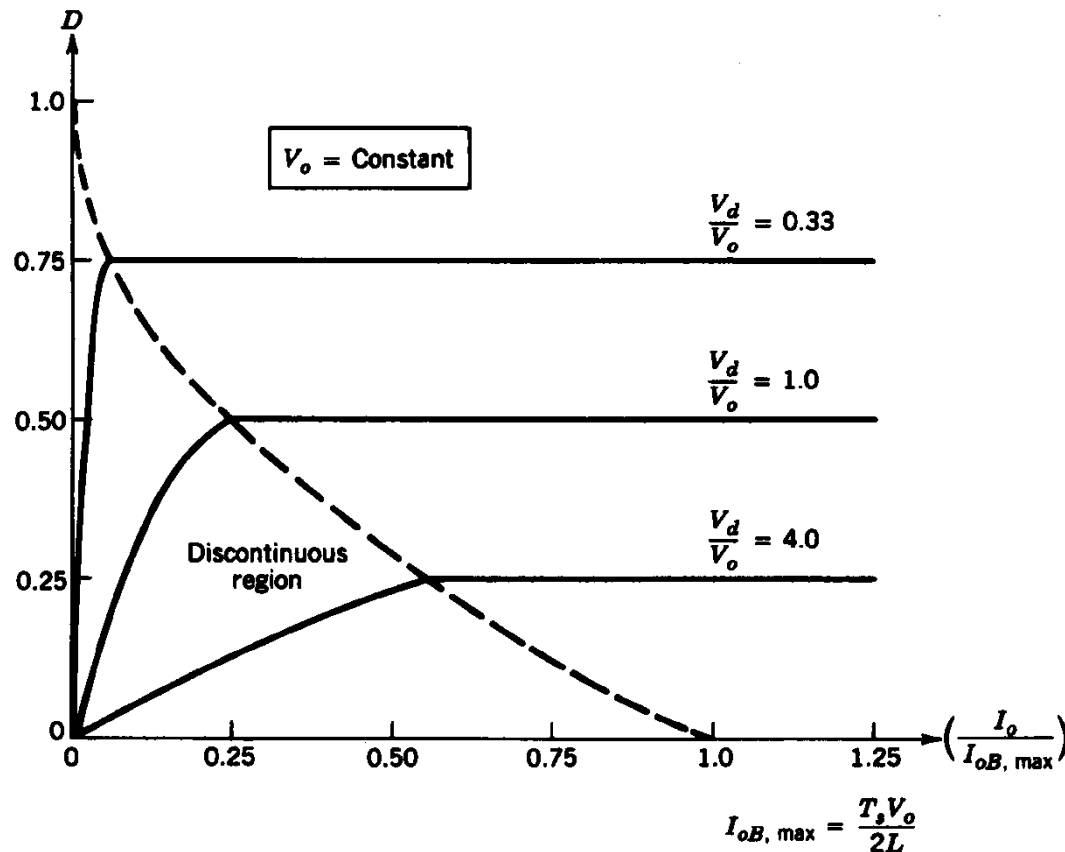


$$\frac{V_o}{V_d} = D \frac{1}{1 - D}$$

Step-Up DC-DC Converter

Output Voltage Ripple



- ESR is assumed to be zero

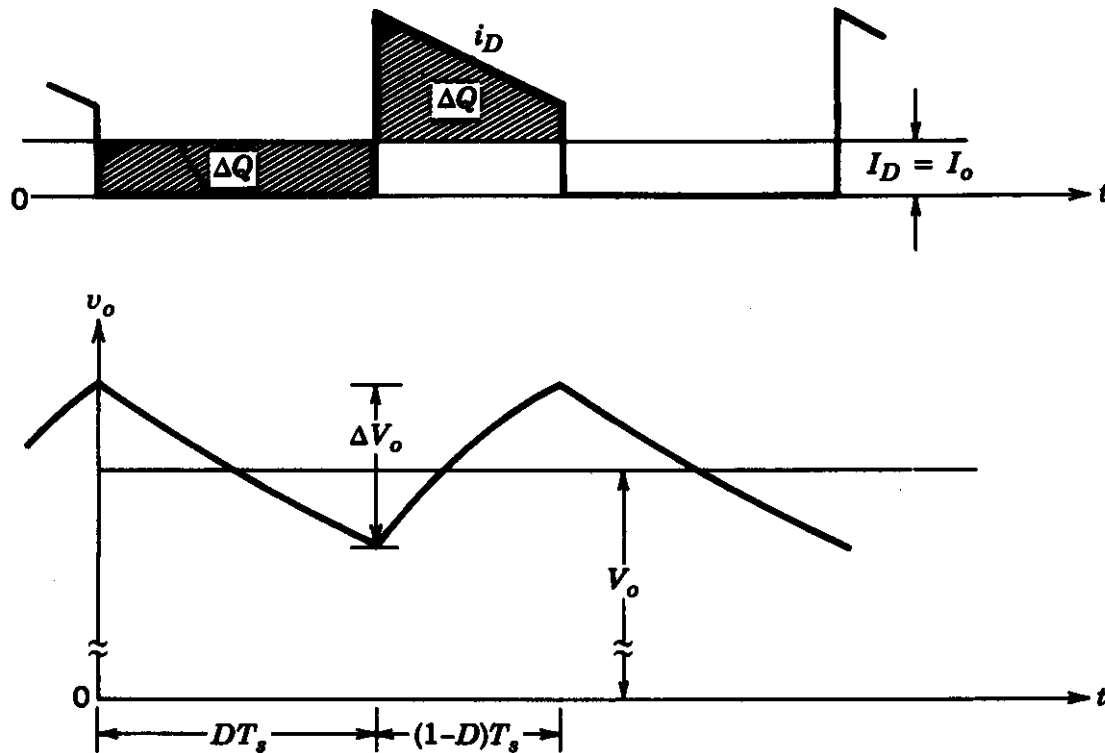

Cuk DC-DC Converter

- ▶ The output voltage can be higher or lower than the input voltage








$$\frac{V_o}{V_d} = \frac{-D}{1-D}$$

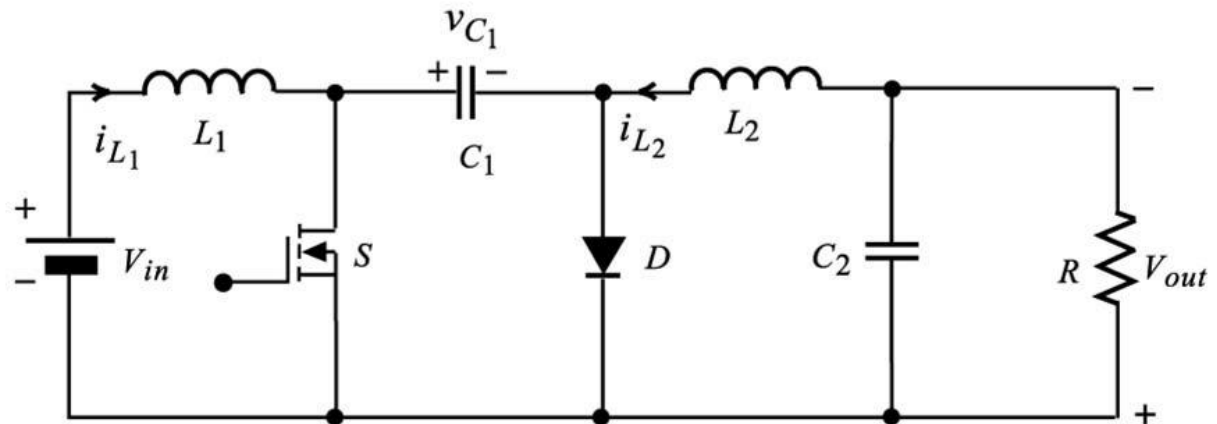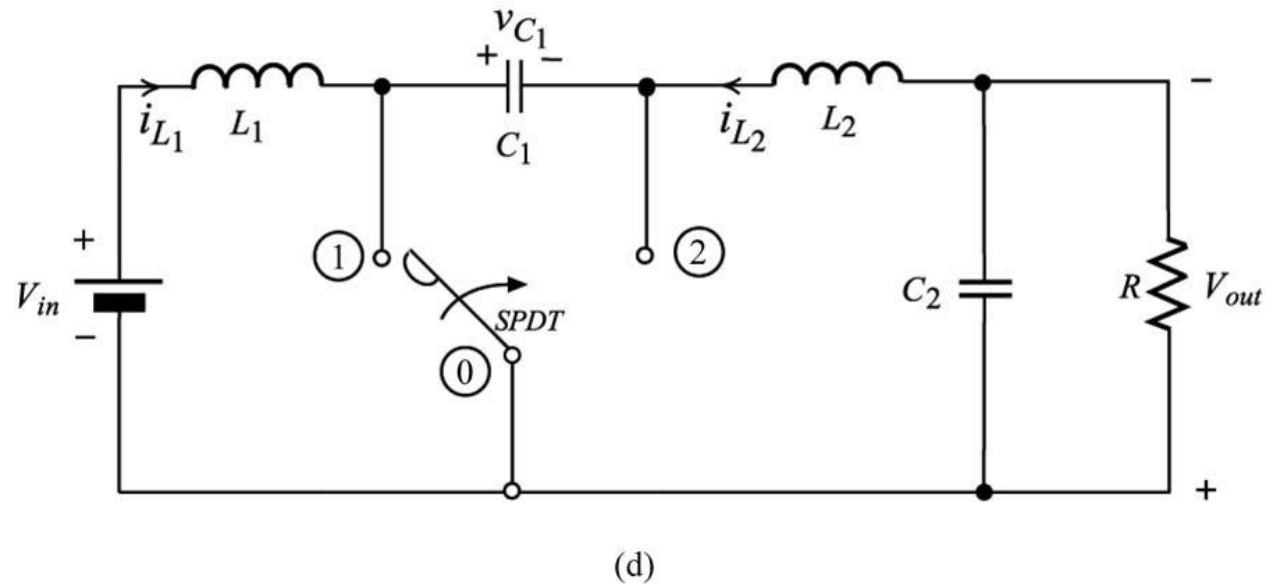

Cuk DC-DC Converter Waveforms





- ▶ The capacitor voltage is assumed constant

$$\frac{V_o}{V_d} = \frac{-D}{1-D}$$

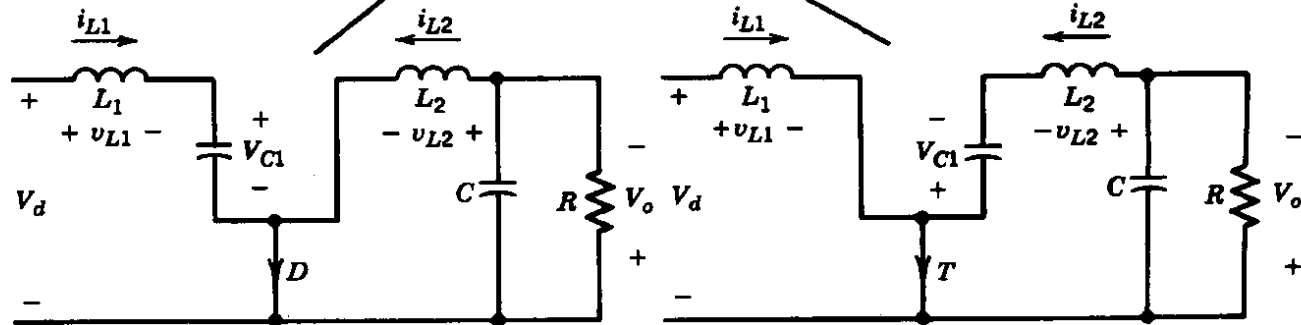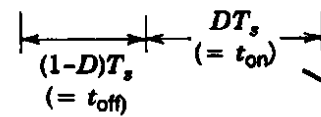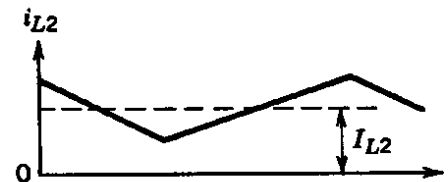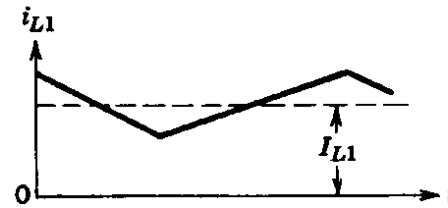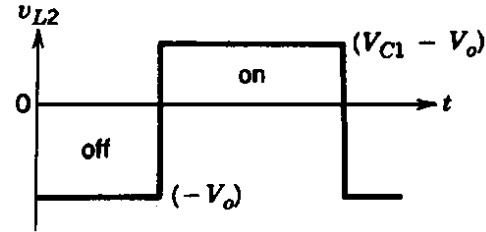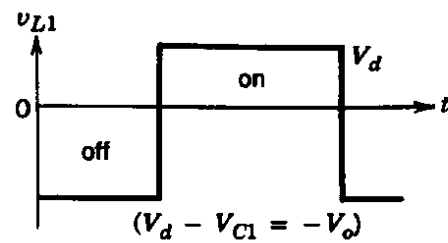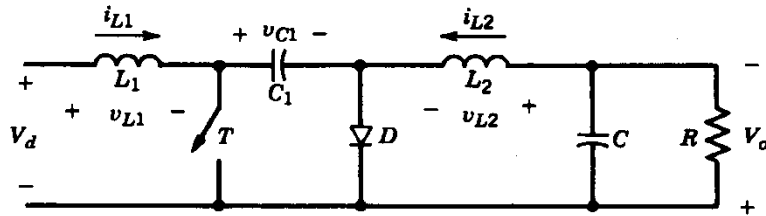



Cuk DC-DC Converter

Discontinuous Conduct

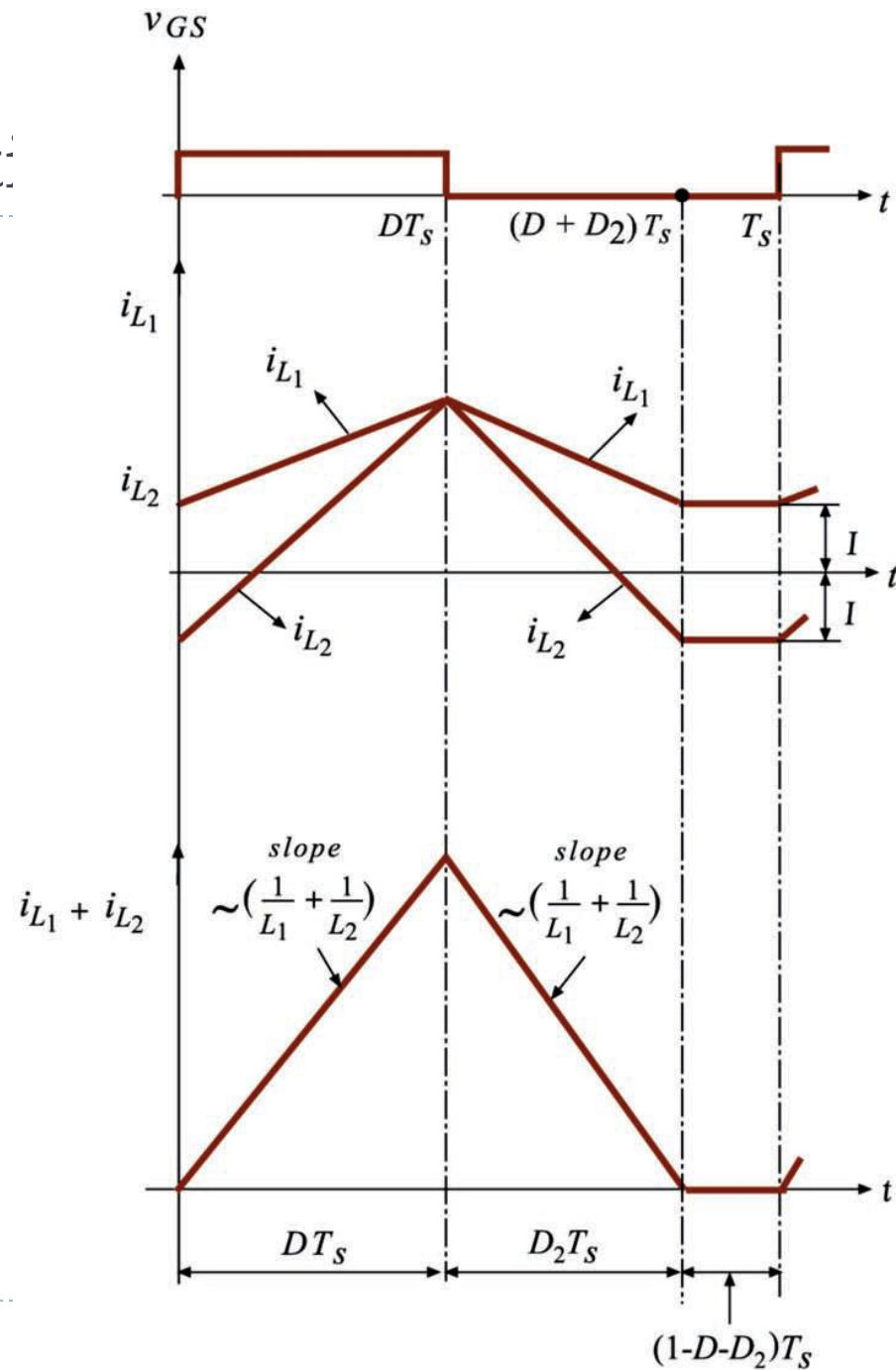
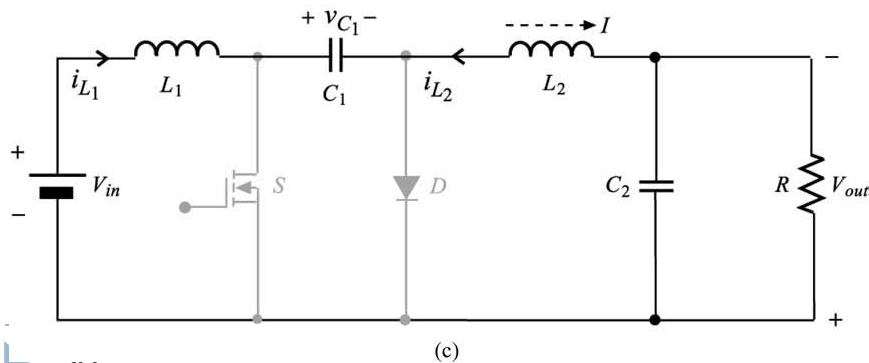
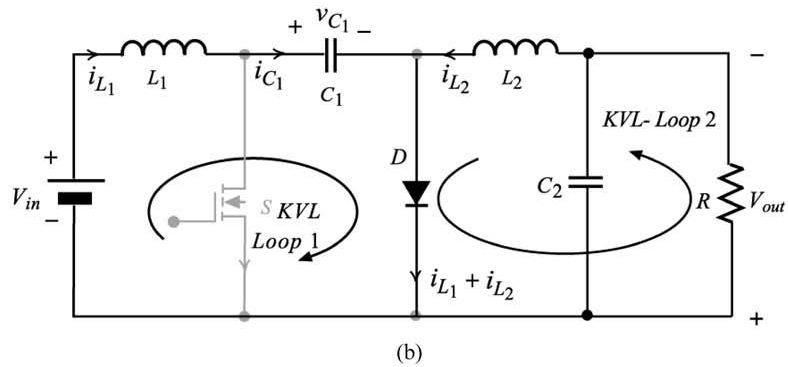
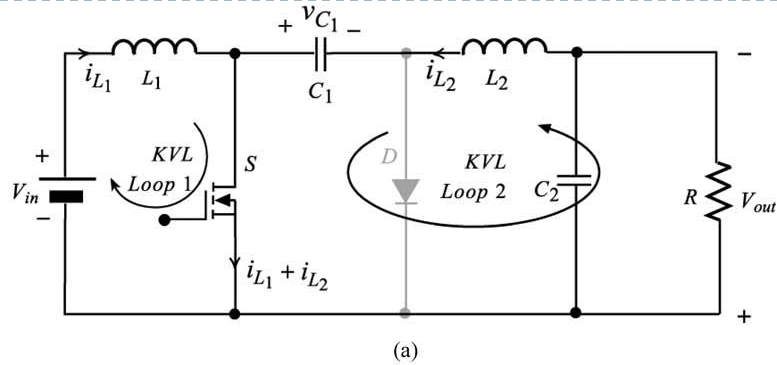


Cuk DC-DC Converter


Effect of Parasitics

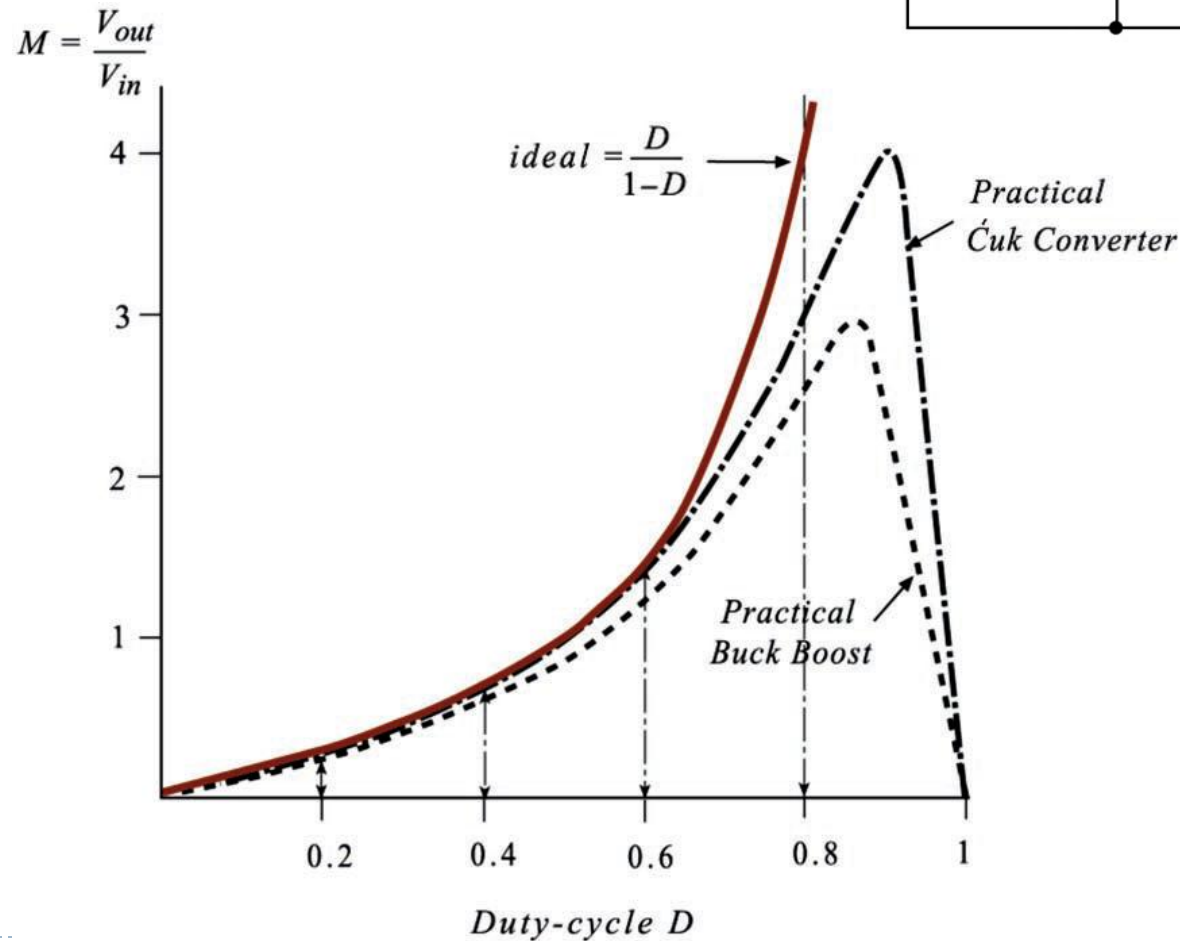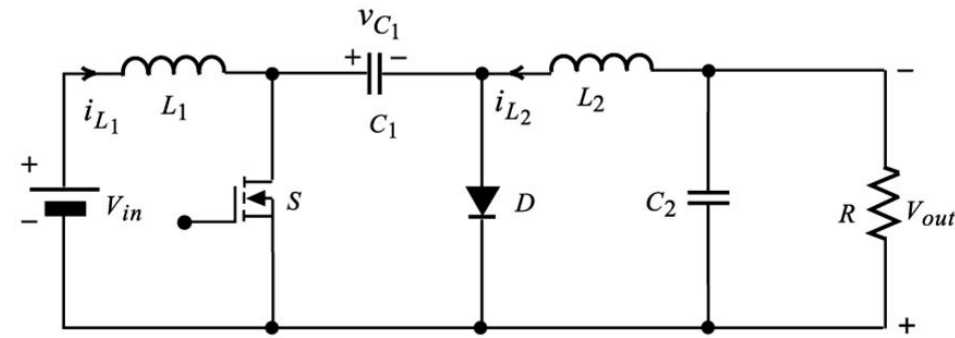

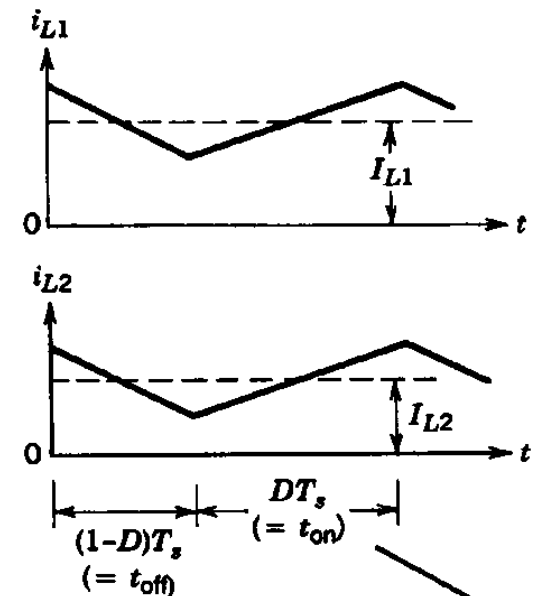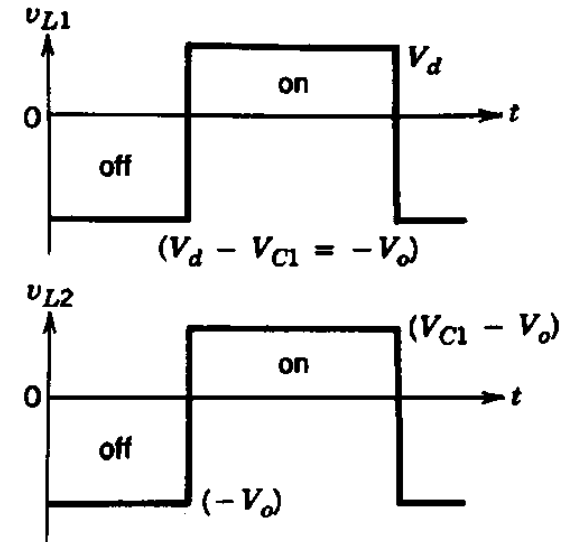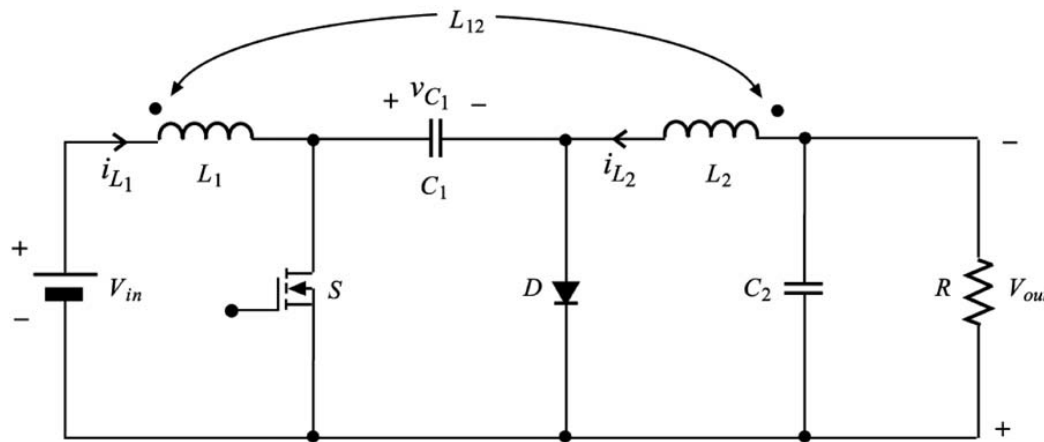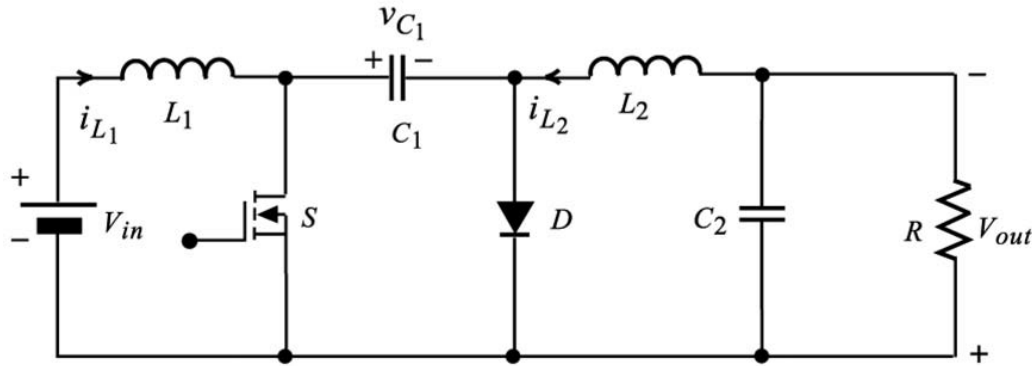
Cuk converter with coupled inductor for reducing the inductor currents ripple



Isolated Cuk converter

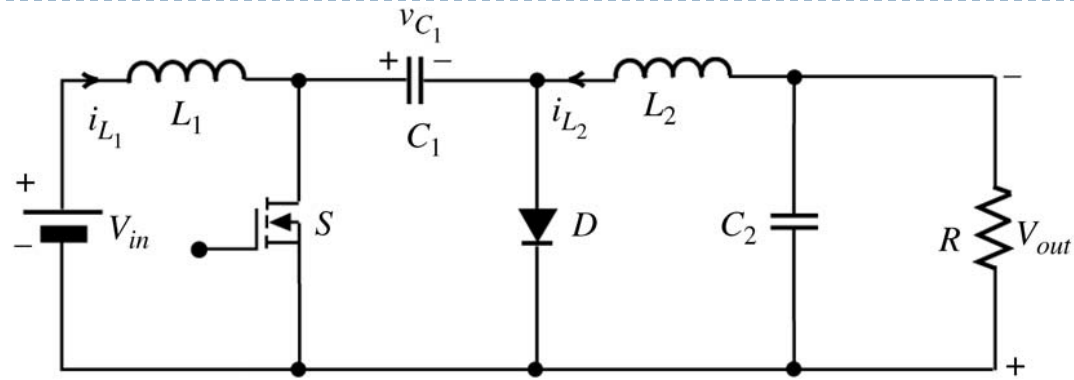


(a)

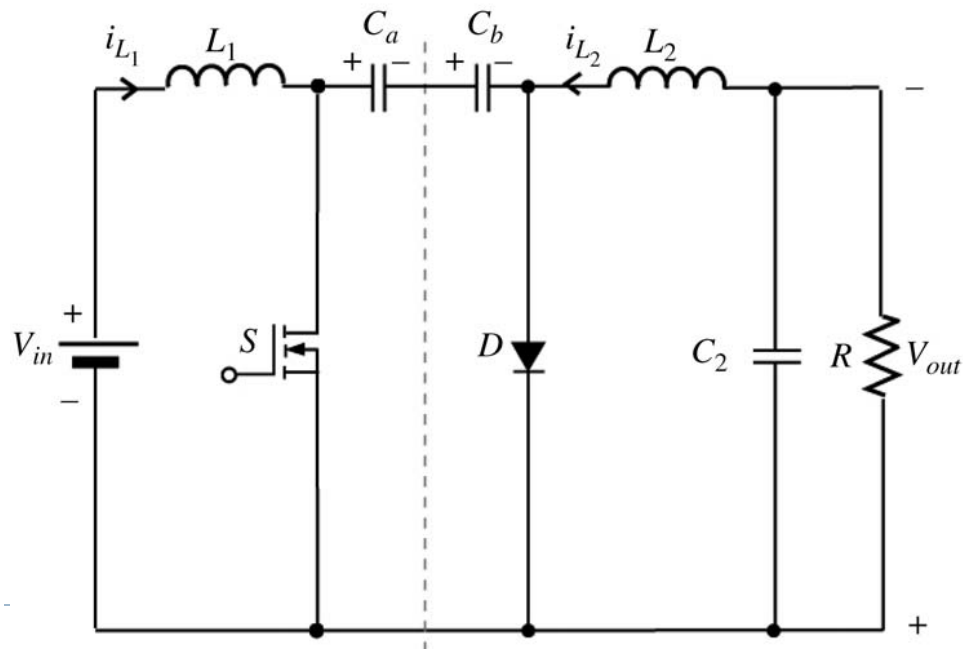


(b)


Isolated Cuk converter (2)

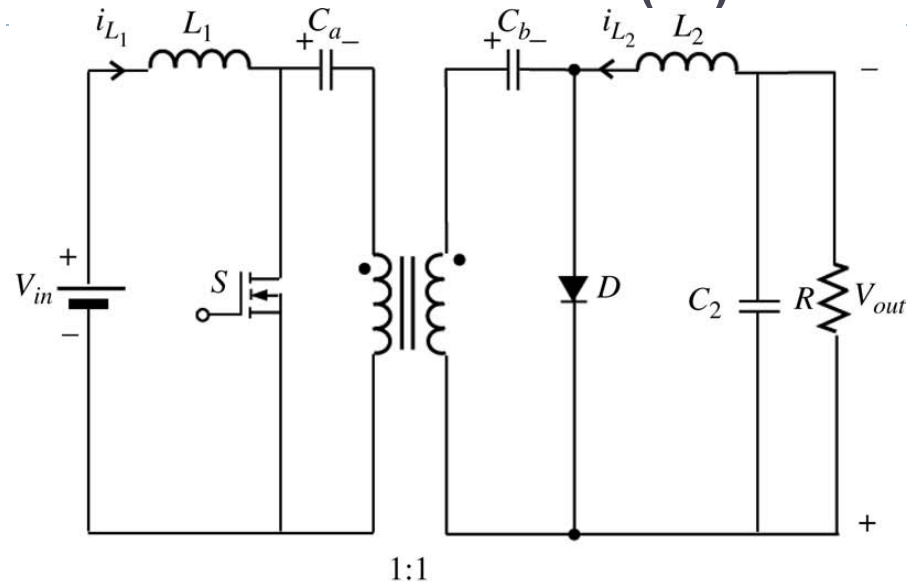


(c)

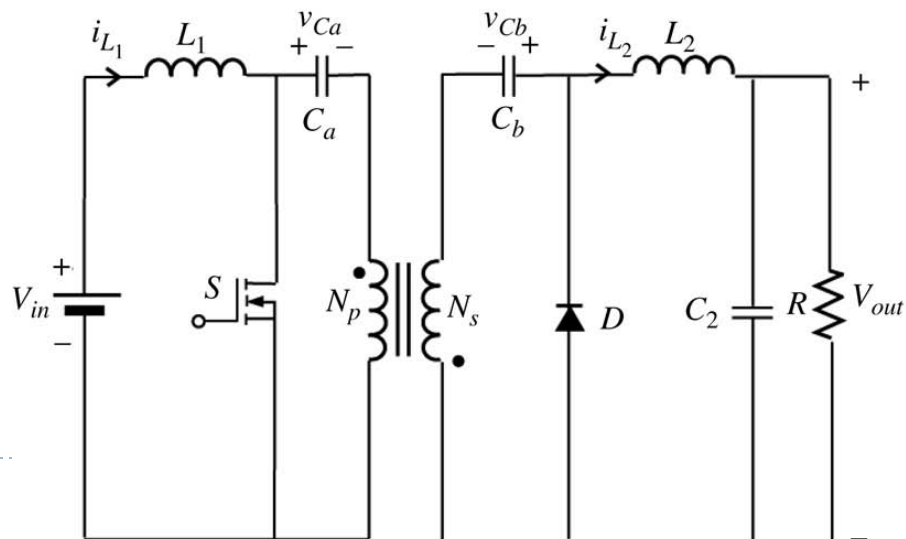


Isolated Cuk converter (3)

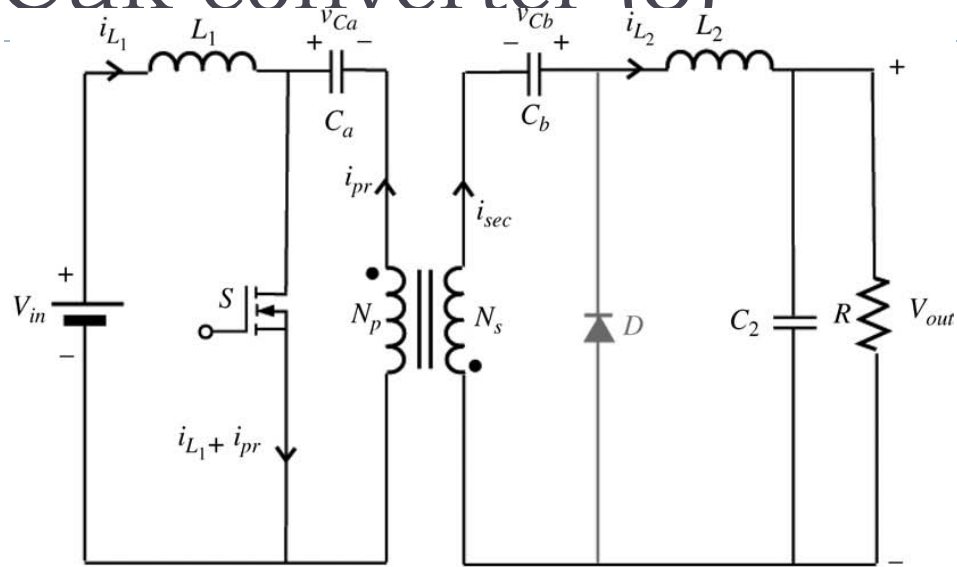

(a)

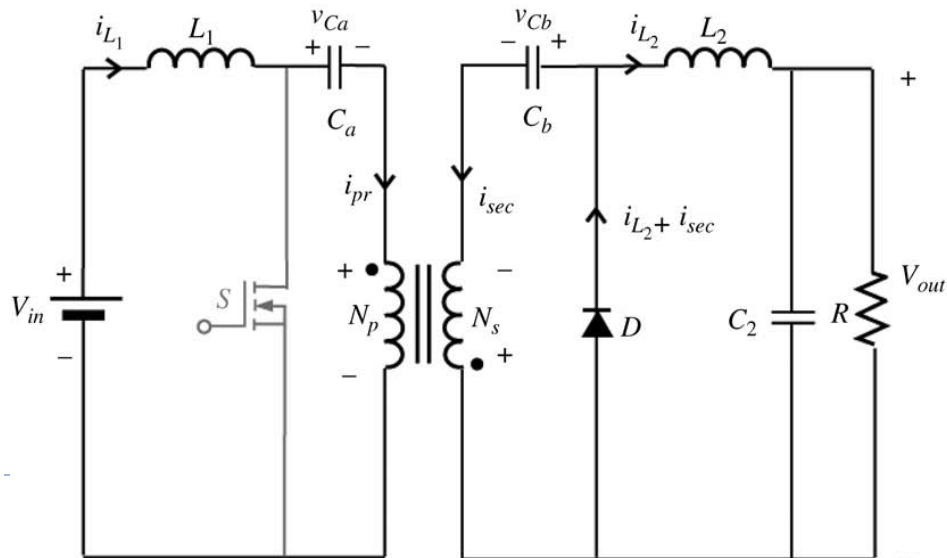


Homework!!!

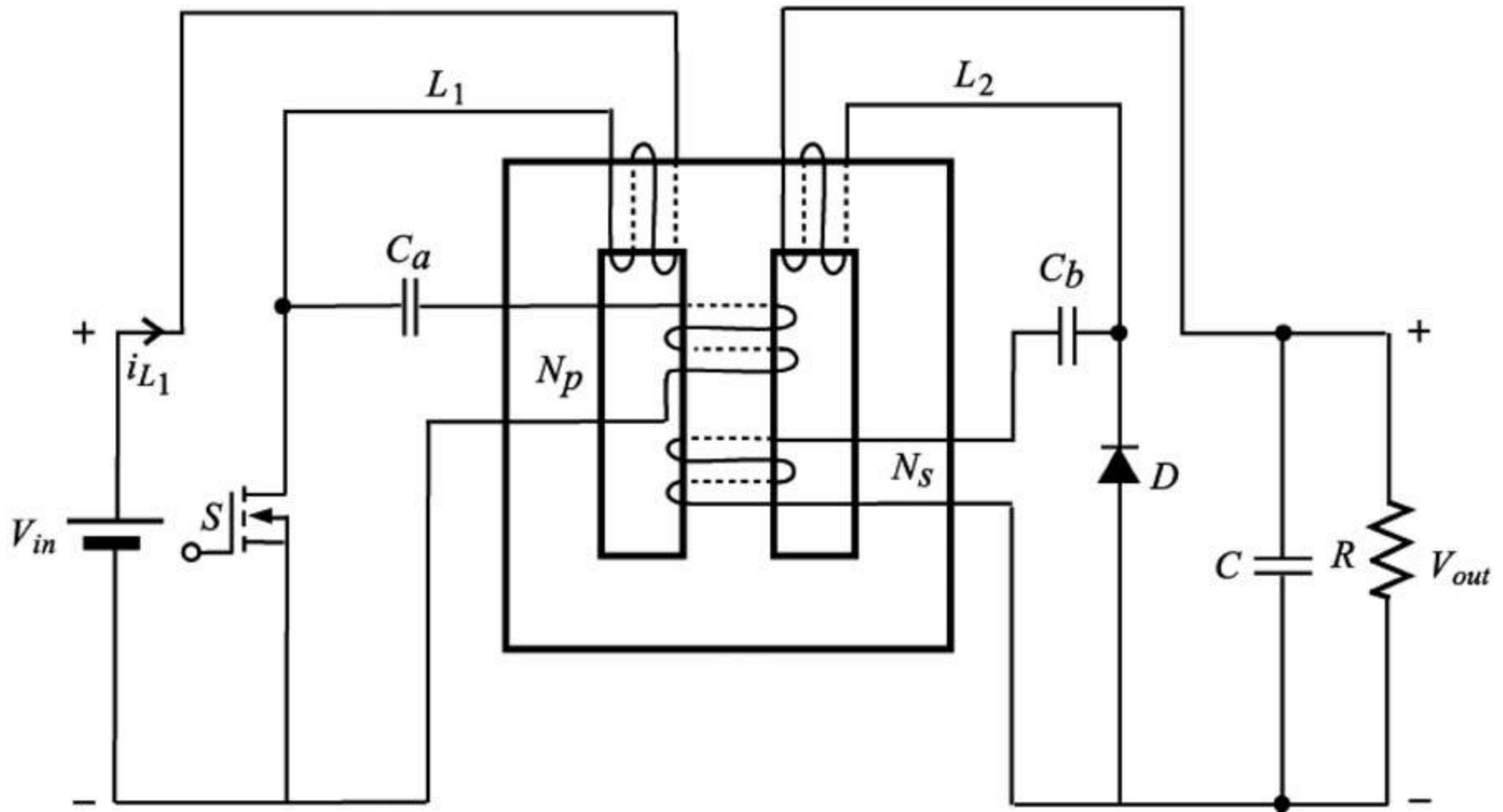

SEPIC



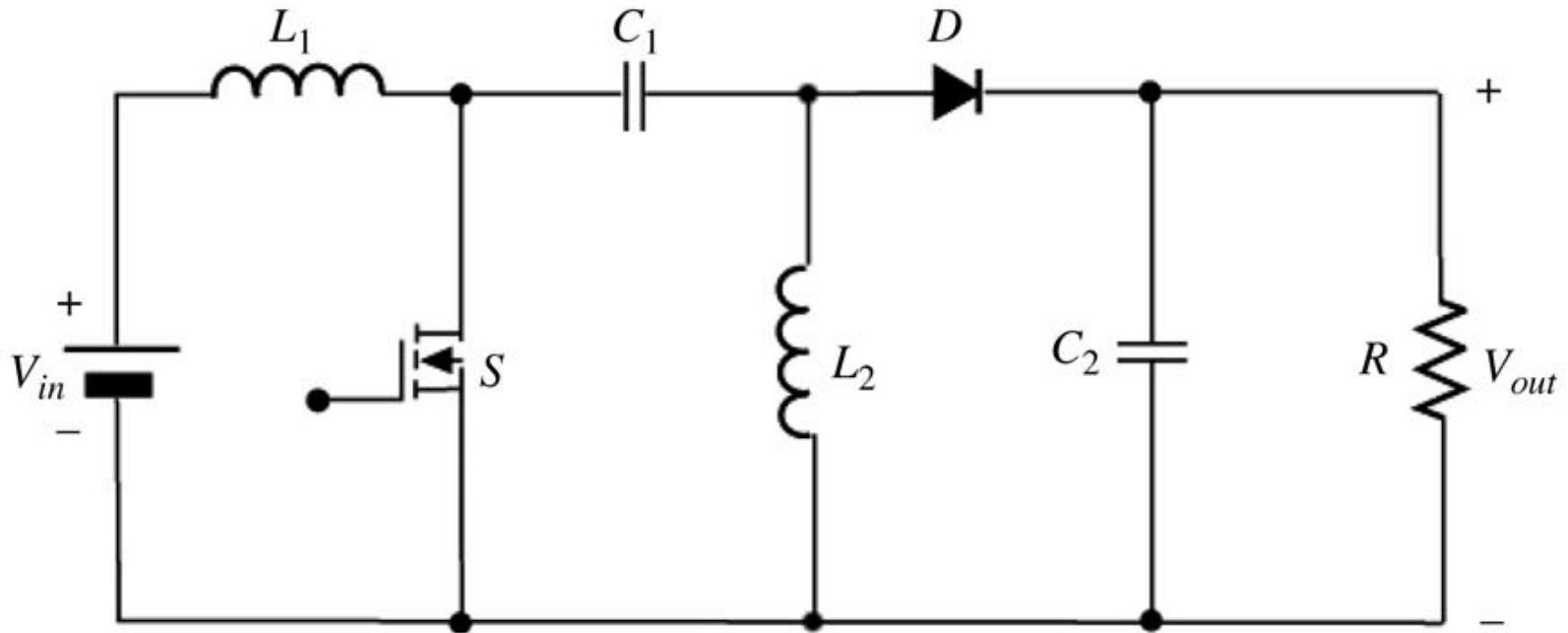
(Single-Ended Primary Inductance Converter)



$$\frac{V_o}{V_d} = \frac{D}{1 - D}$$


SEPIC

Waveform

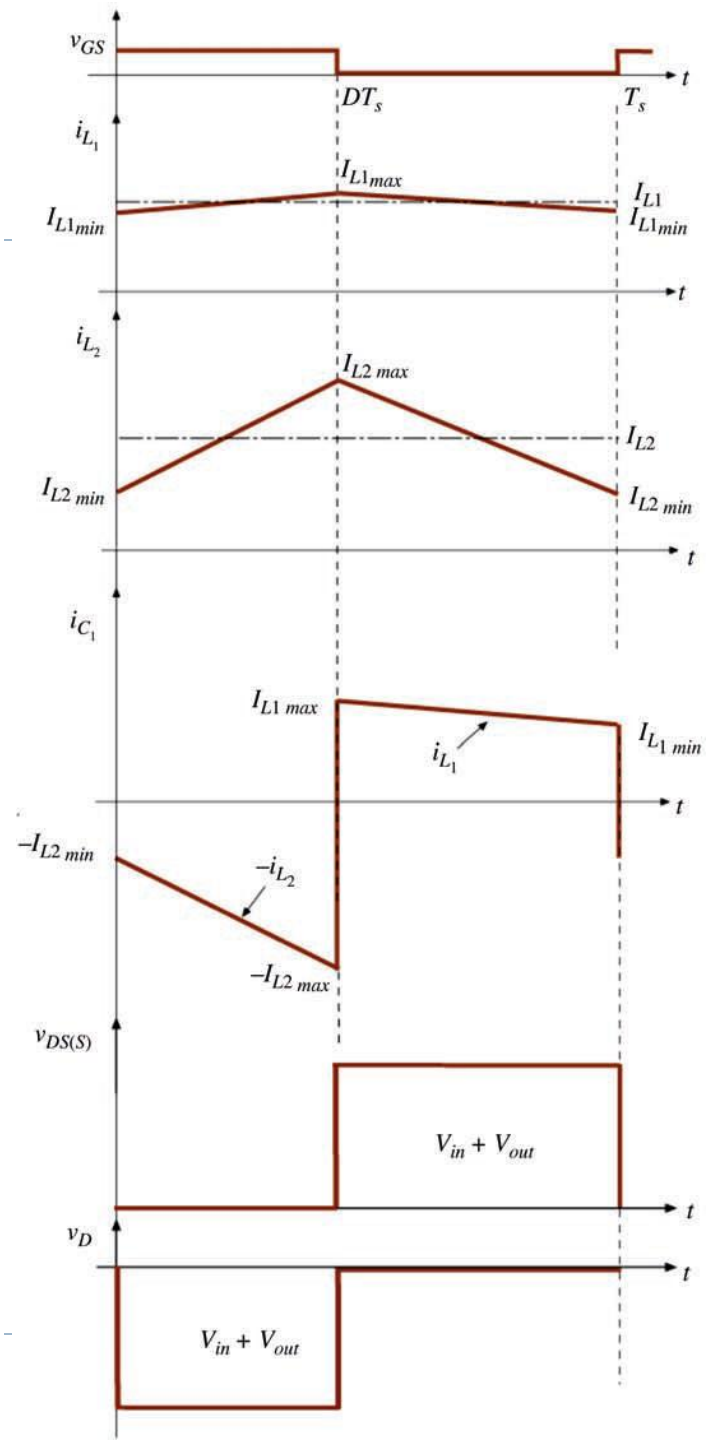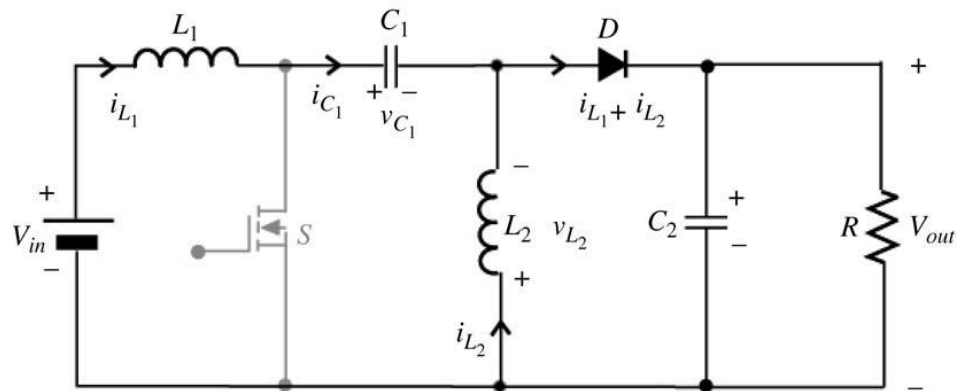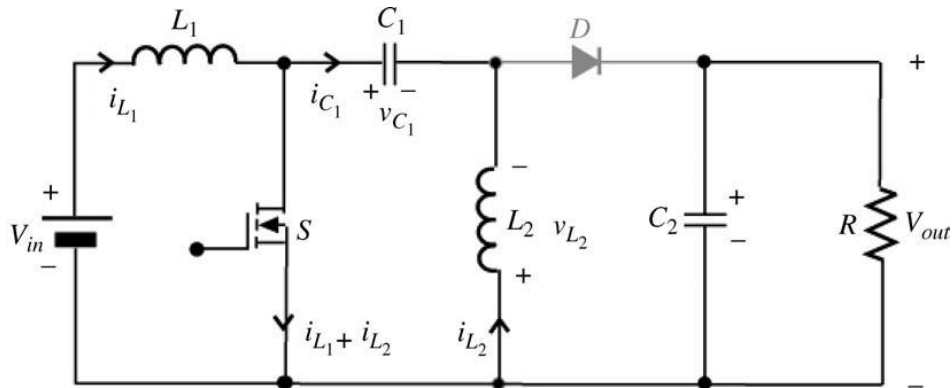


SEPIC


Discontinuous Conduction Mode

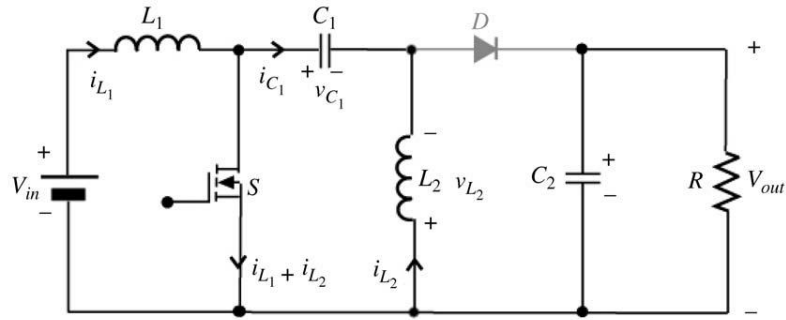


(a)

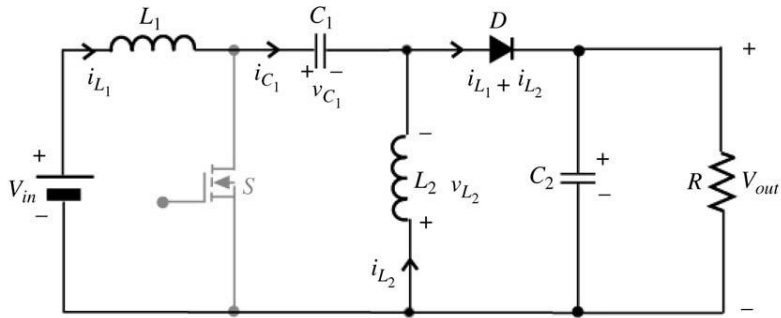

(b)


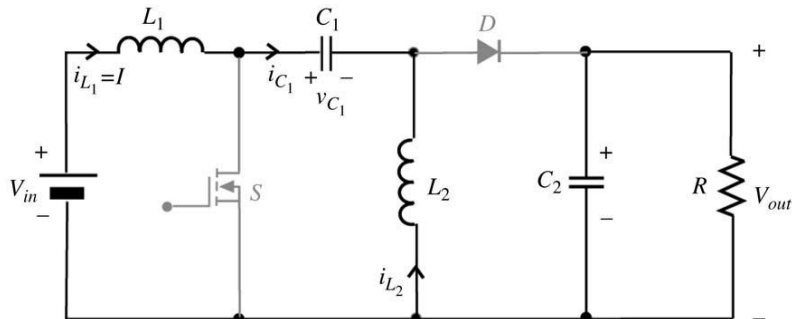


(c)


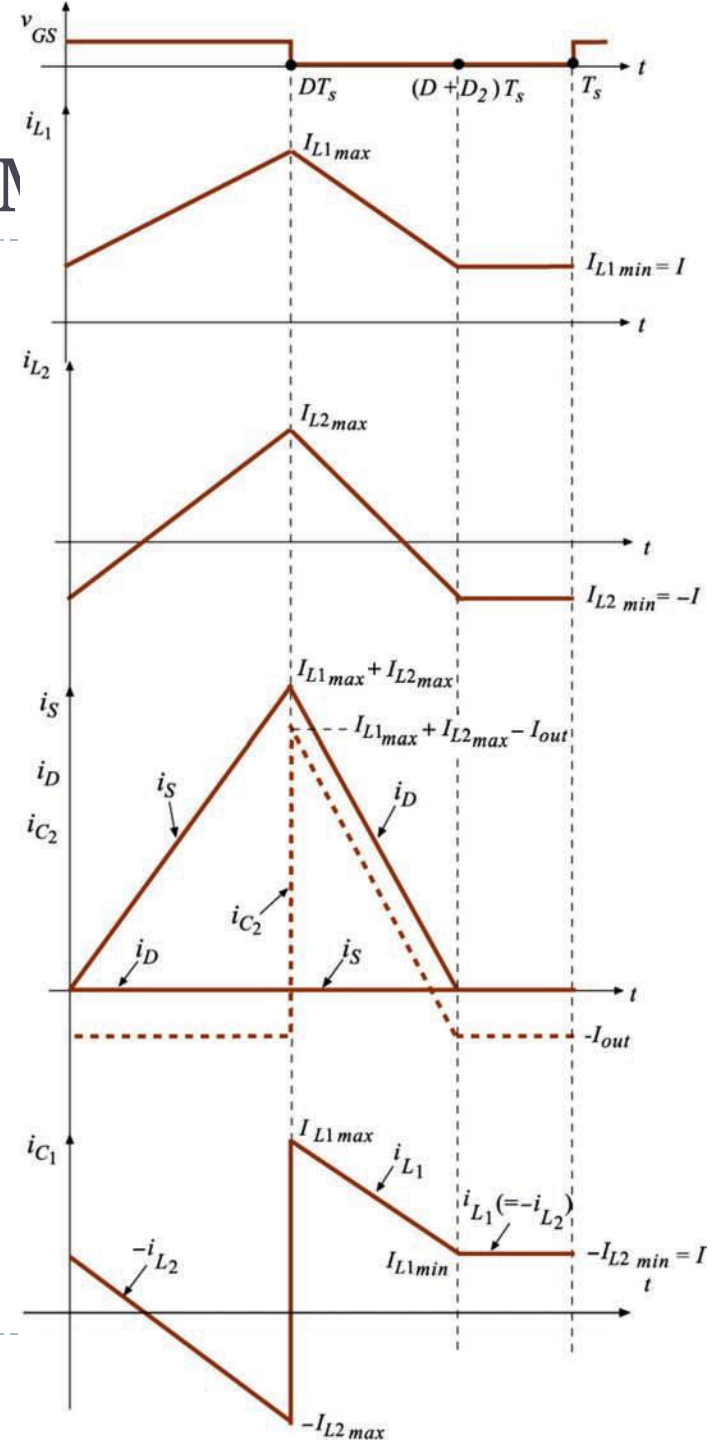


SEPIC Converter


Limits of Cont./Discont. Conduction

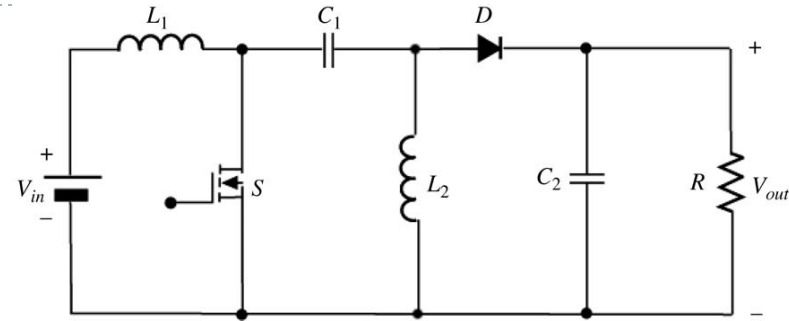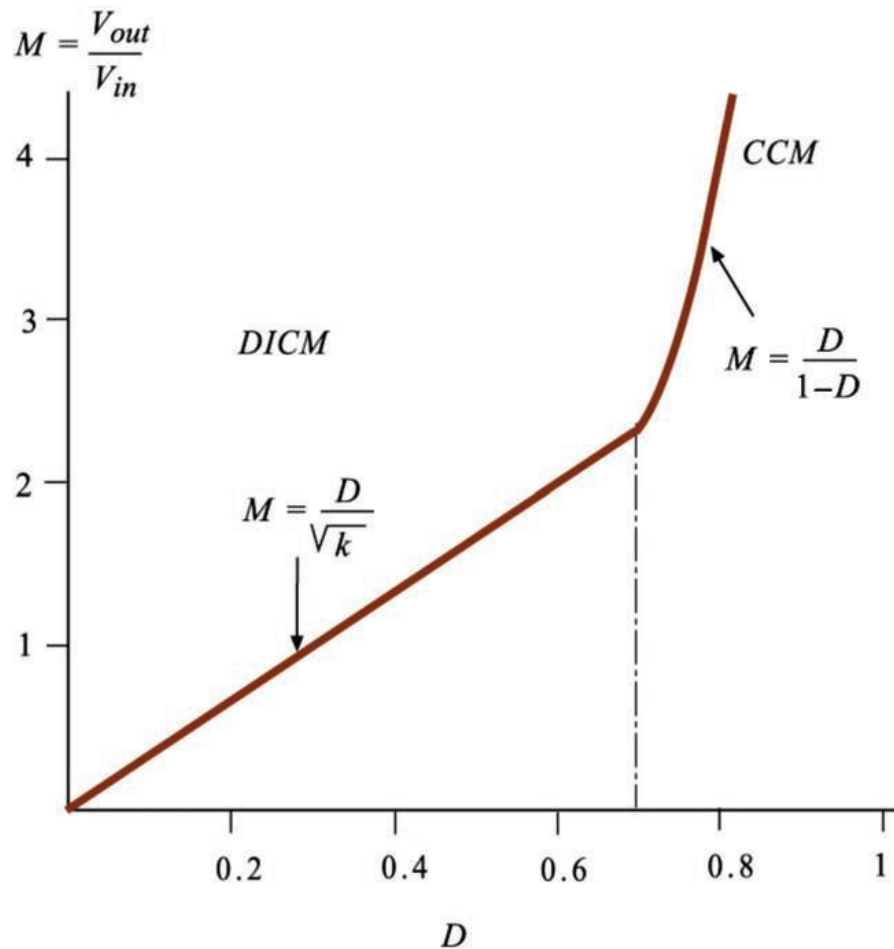

Isolated version of the SEPIC converter

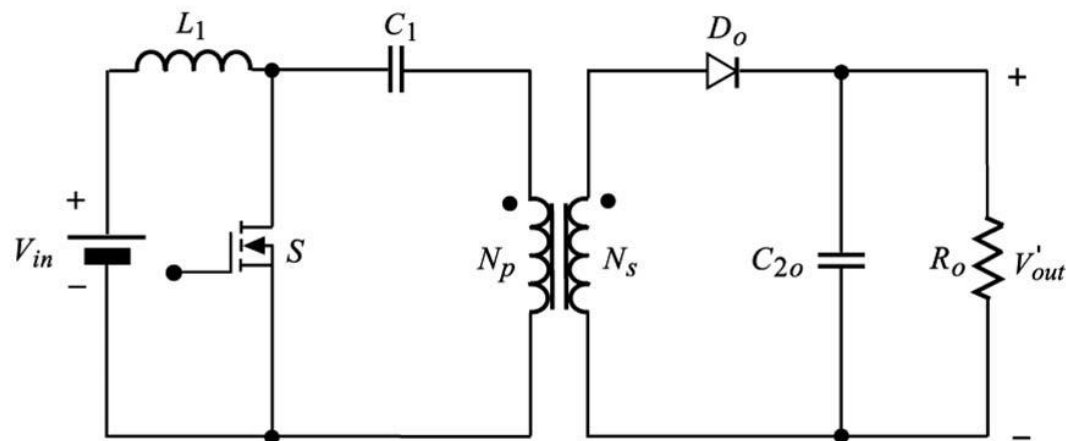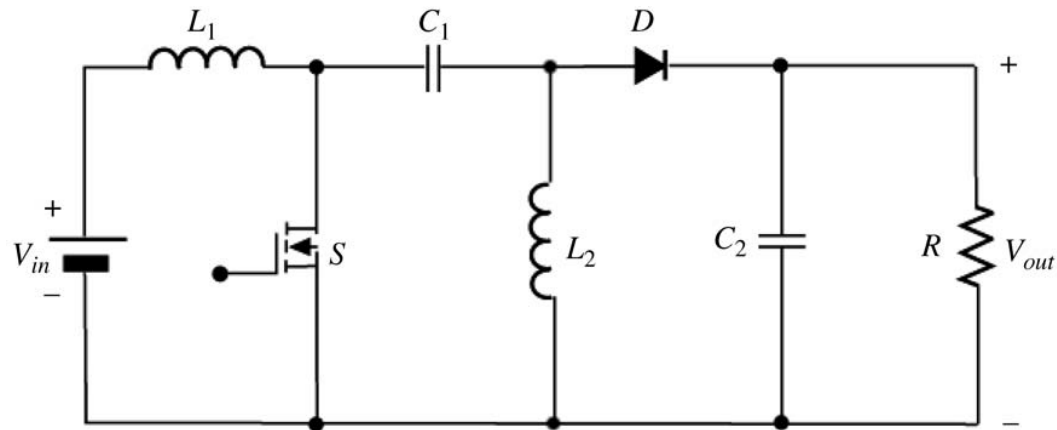

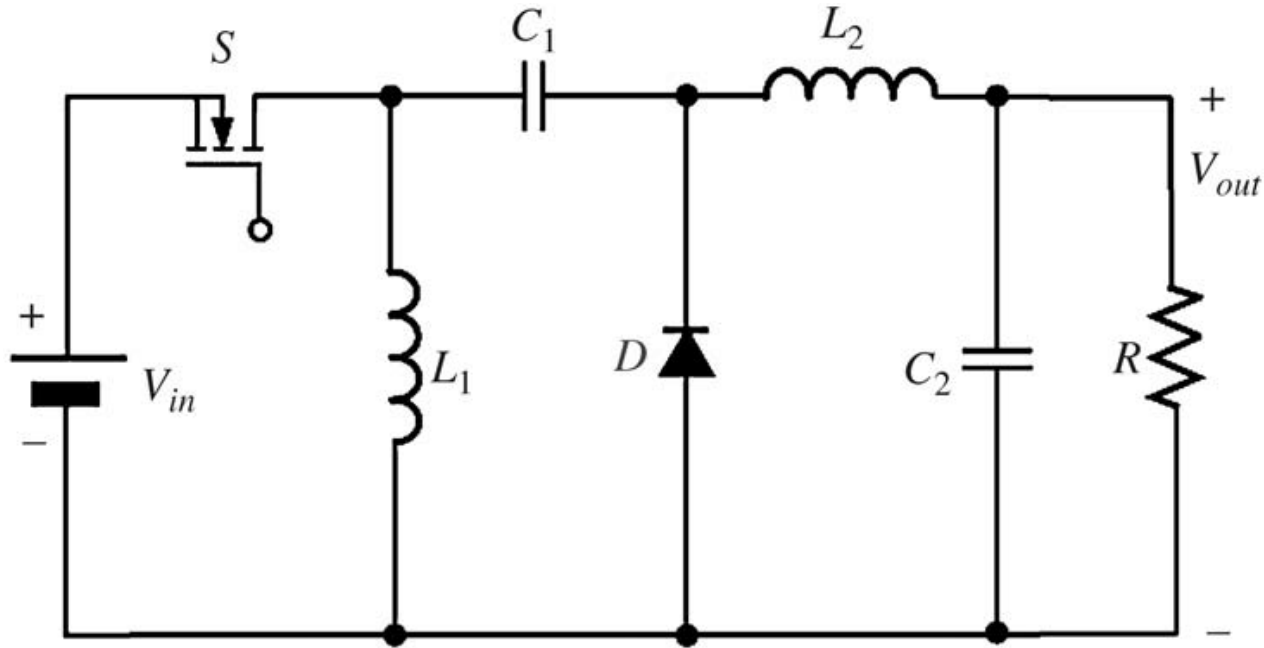
Zeta (Inverse SEPIC) DC-DC Converter (Kazimierczuk/Barbi)





$$\frac{V_o}{V_d} = \frac{D}{1 - D}$$

ZETA


Waveform

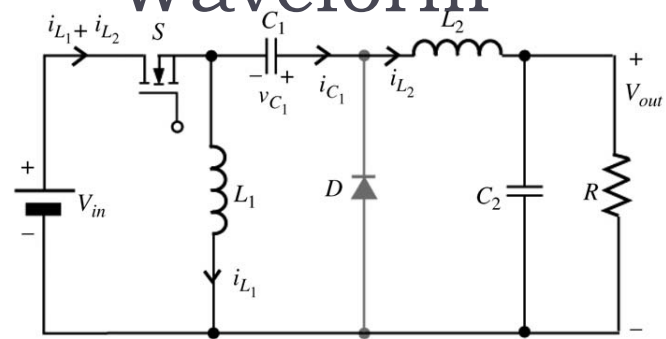


(a)

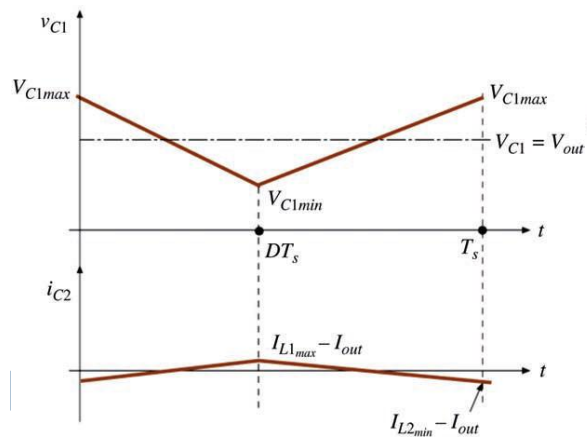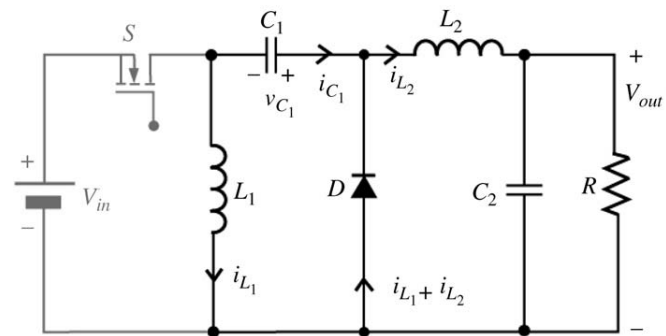

(c)

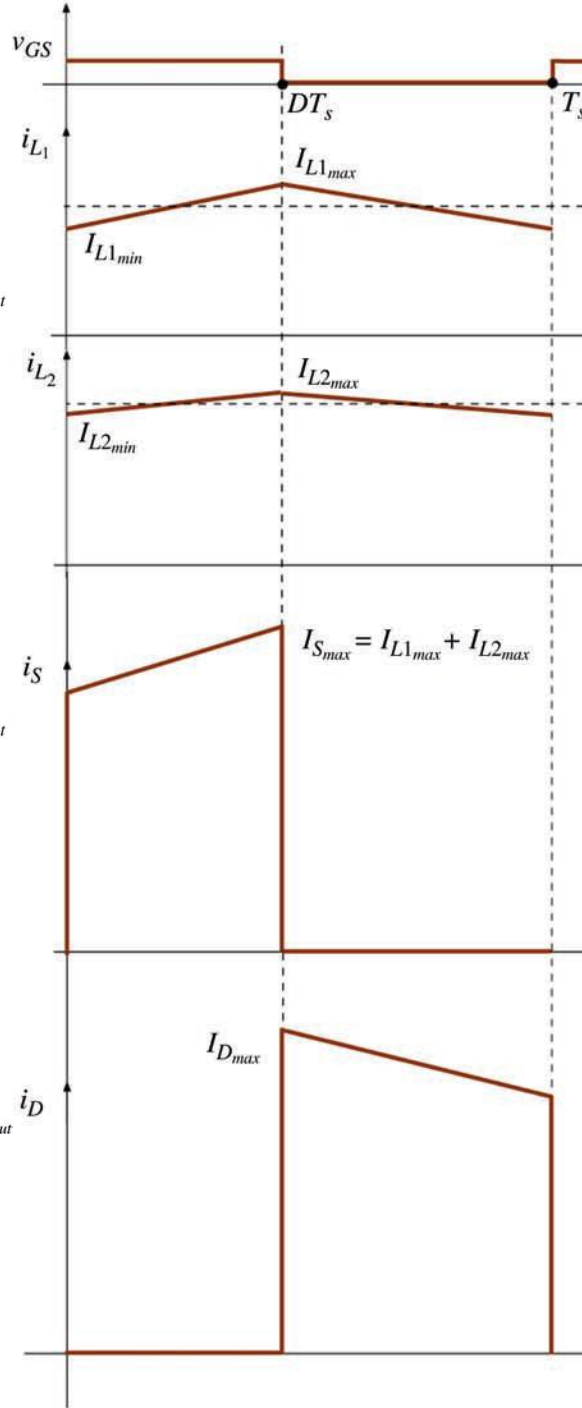


(a)

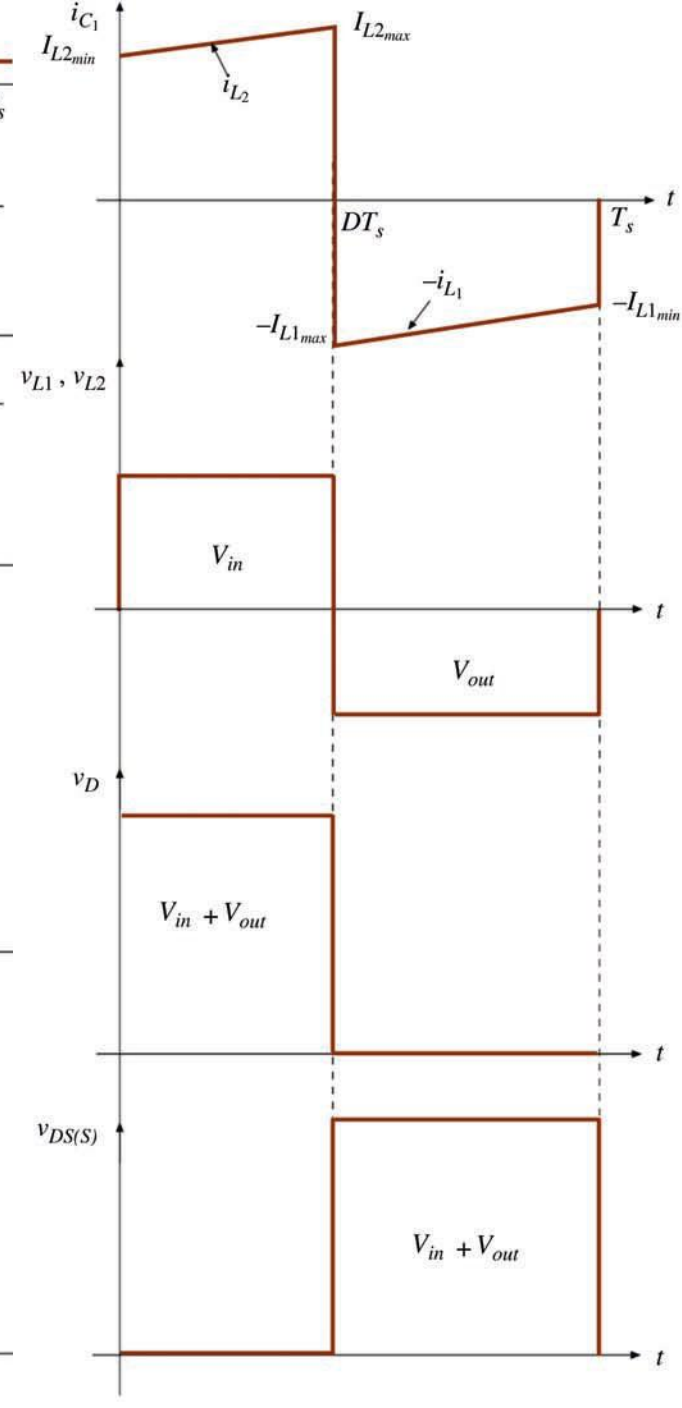


(b)

ZETA


Discontinuous Conduction

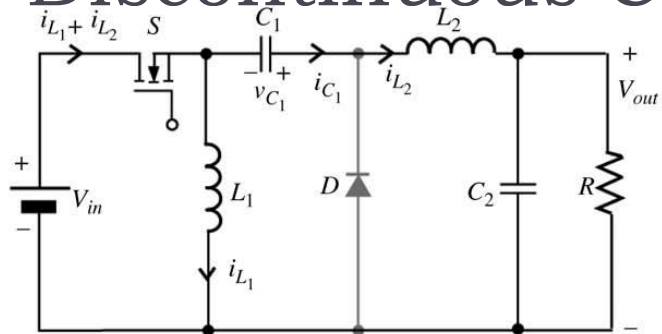


(a)

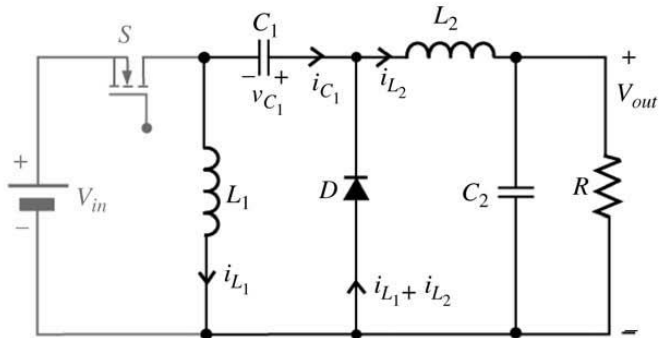

(b)

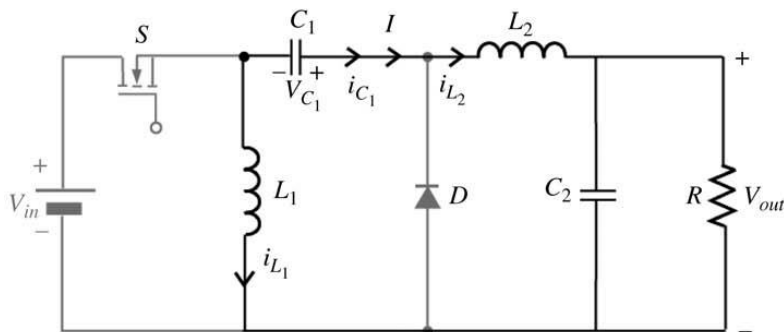


(c)

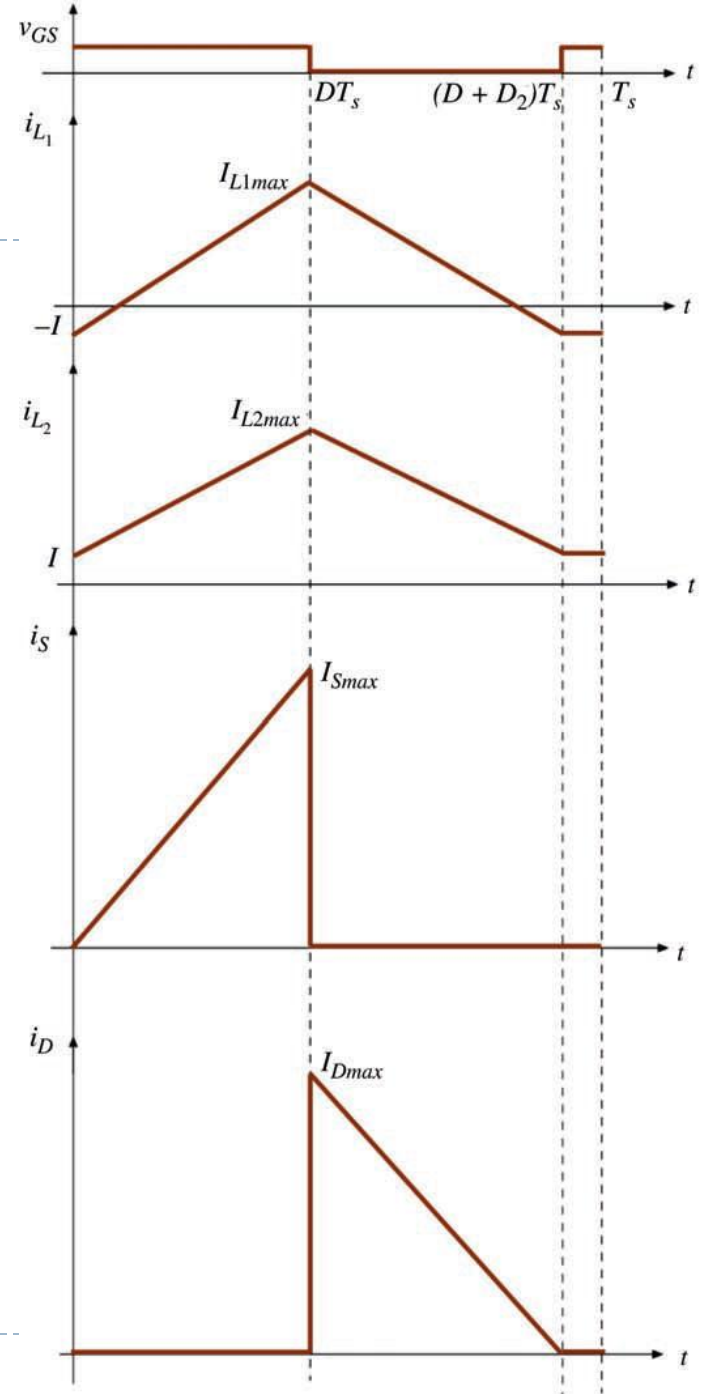

ZETA Converter

Limits of Cont./Discont. Conduction

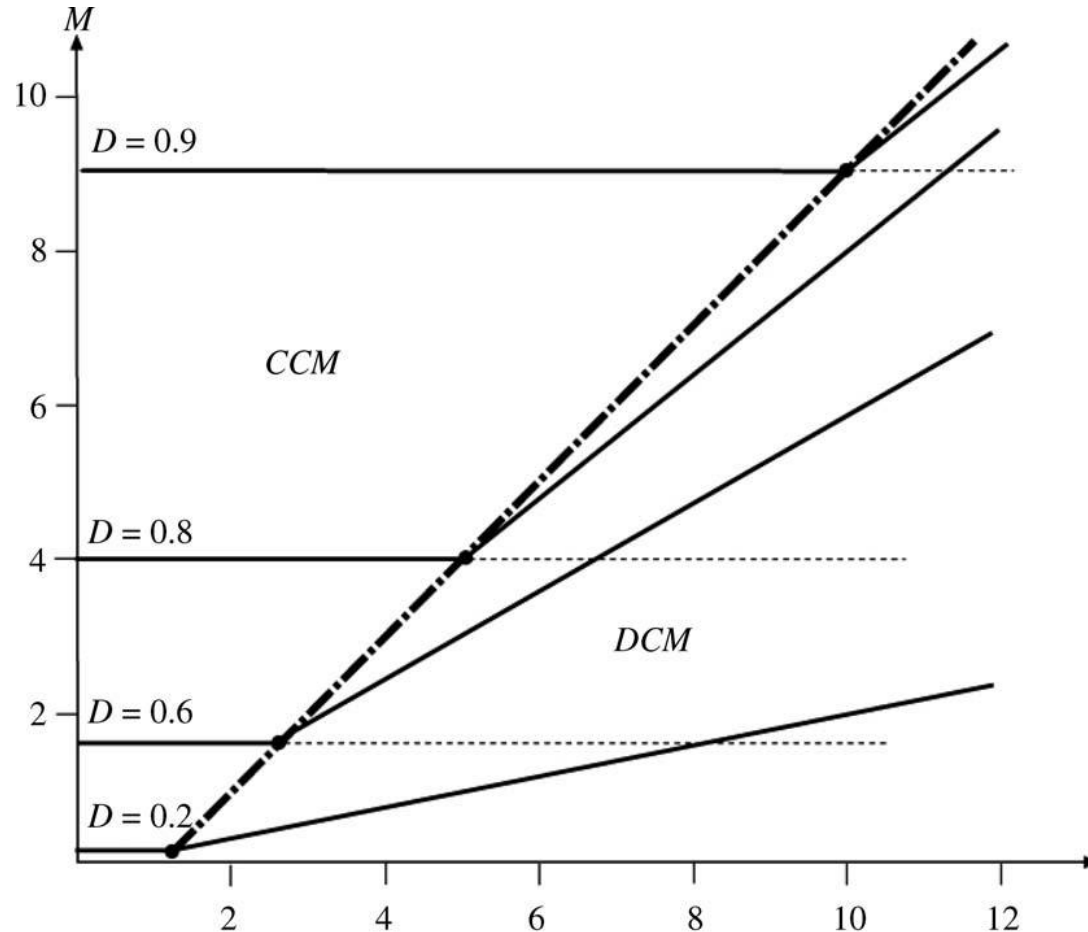


$$\frac{V_o}{V_d} = \frac{D}{1-D}$$



$$\frac{V_o}{V_d} = \frac{D}{D_2}$$

$$\frac{I}{\sqrt{\frac{2Lf_s}{R}}}$$

Isolated ZETA Converter

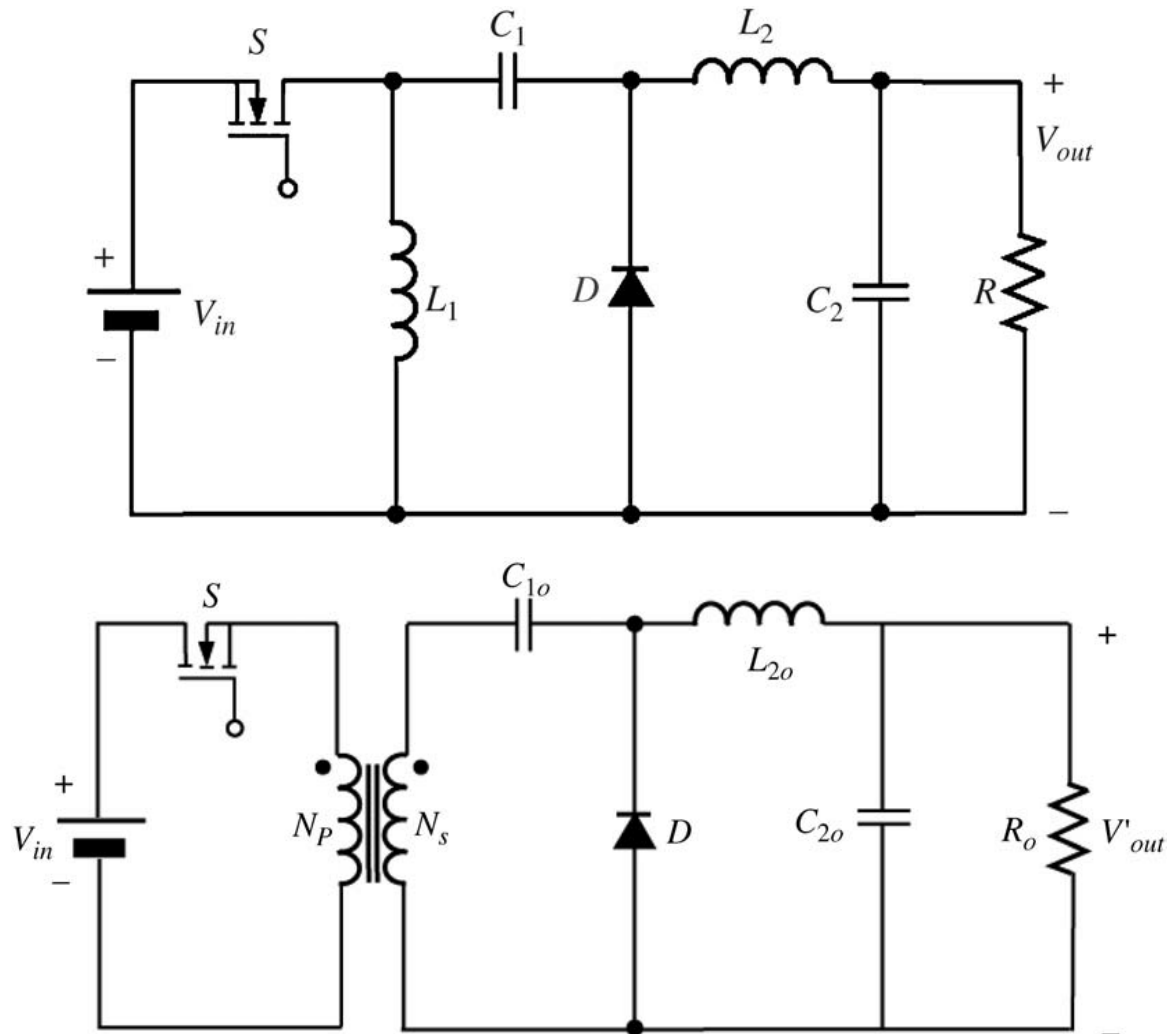

Isolated transformer

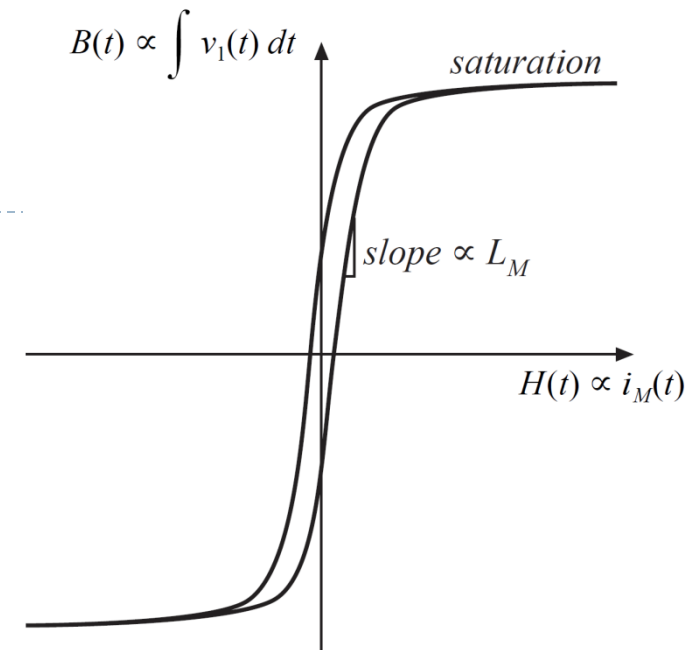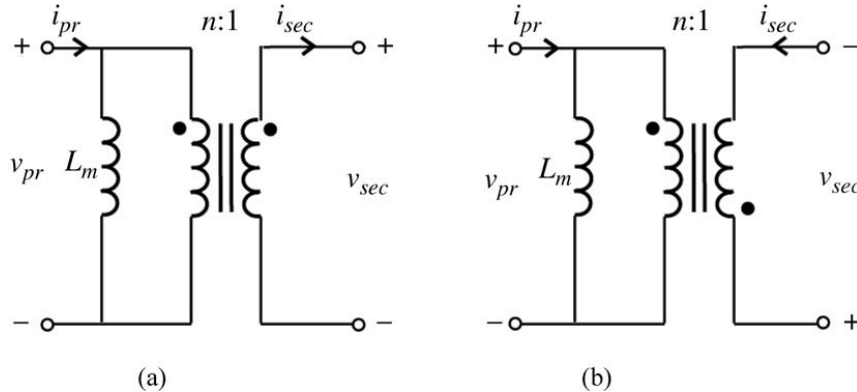


$$n = \frac{N_p}{N_s} \quad v_1 = n \cdot v_2$$

$$i_2 = n \cdot i_1$$

$$v_{pr} = L_m \frac{d \left(i_{pr} + i_{sec} \cdot \frac{1}{n} \right)}{dt}$$

$$v_{sec} = L_m \frac{d(n \cdot i_{pr} + i_{sec})}{dt}$$

47

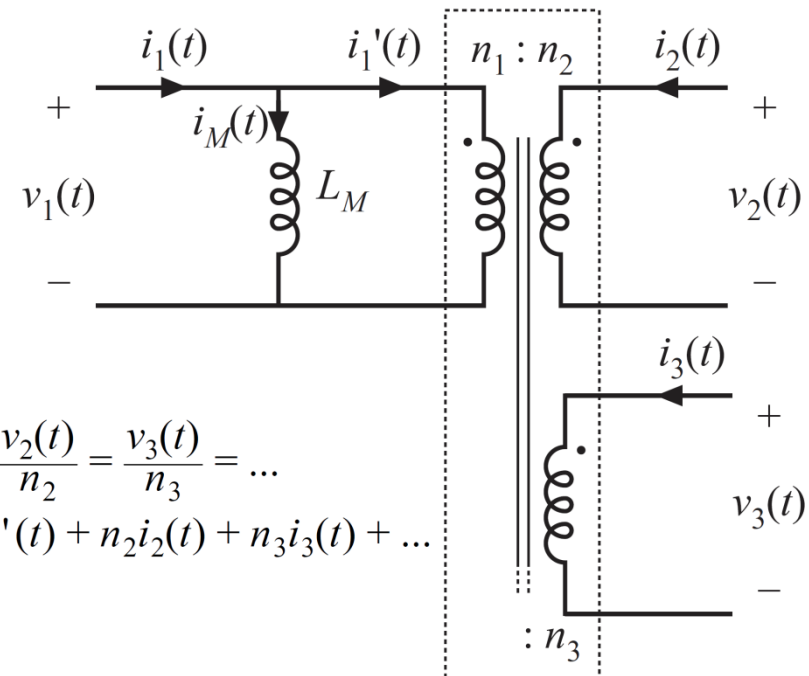


$$\frac{v_1(t)}{n_1} = \frac{v_2(t)}{n_2} = \frac{v_3(t)}{n_3} = \dots$$

$$0 = n_1 i_1'(t) + n_2 i_2(t) + n_3 i_3(t) + \dots$$





Forward Converters

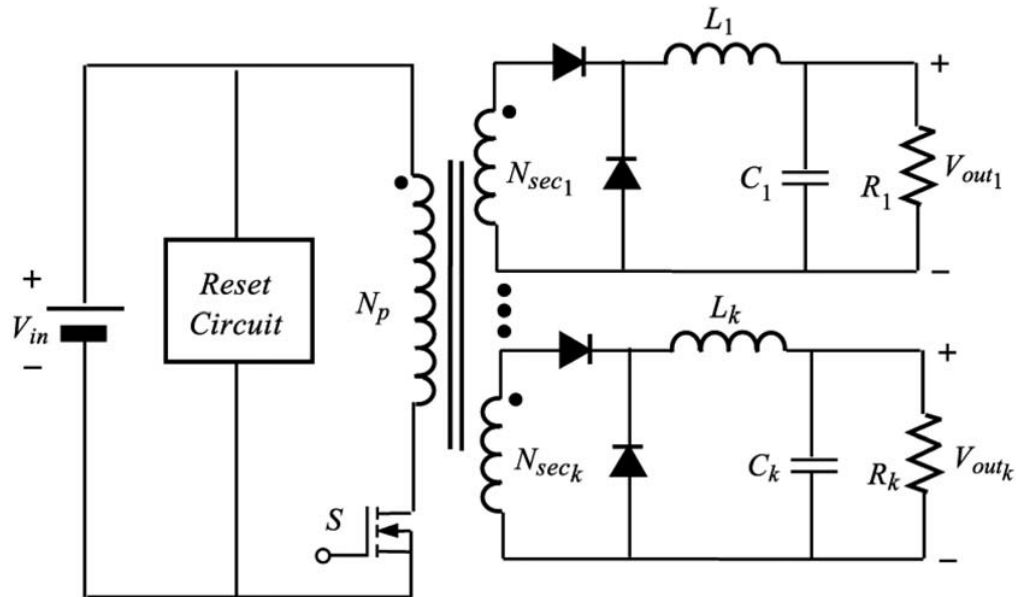- ▶ High frequency transformers
 - ▶ With multiple outputs





Forward Converter


► Buck converter with input filter

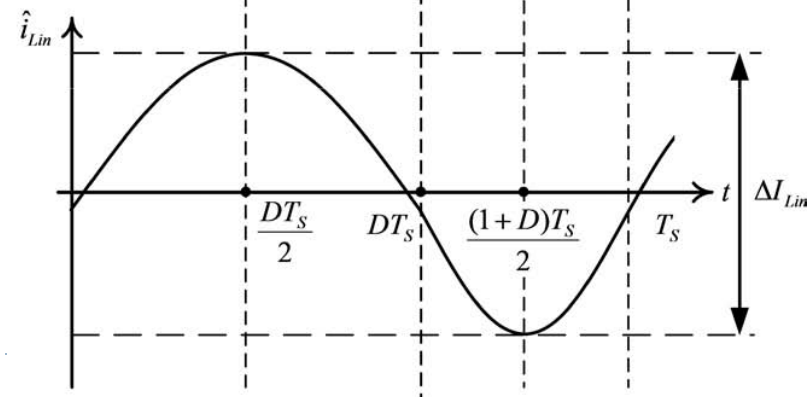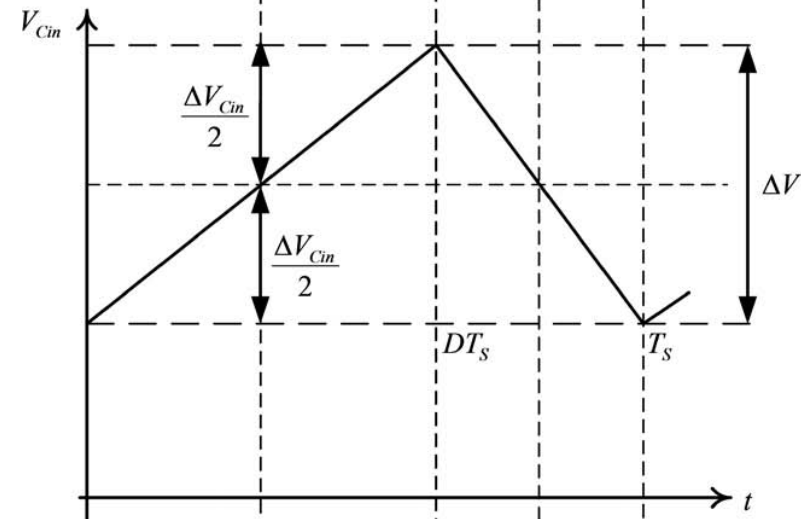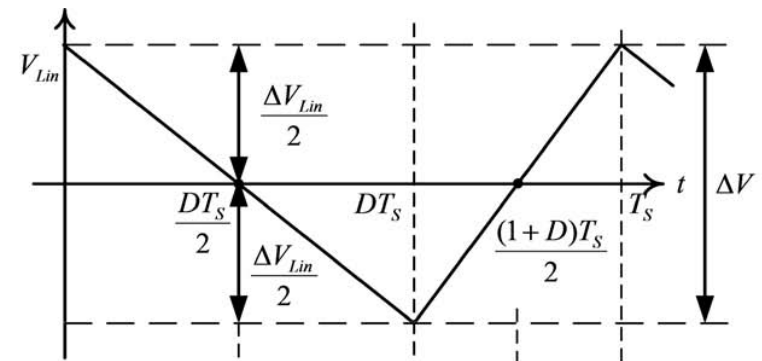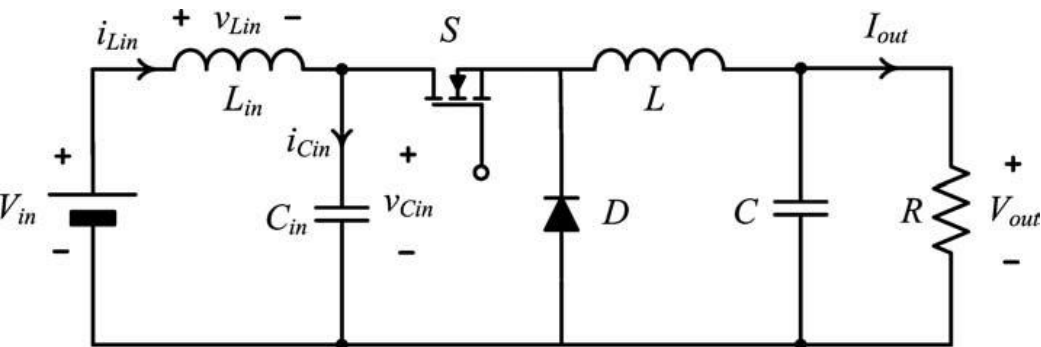


Forward Converter

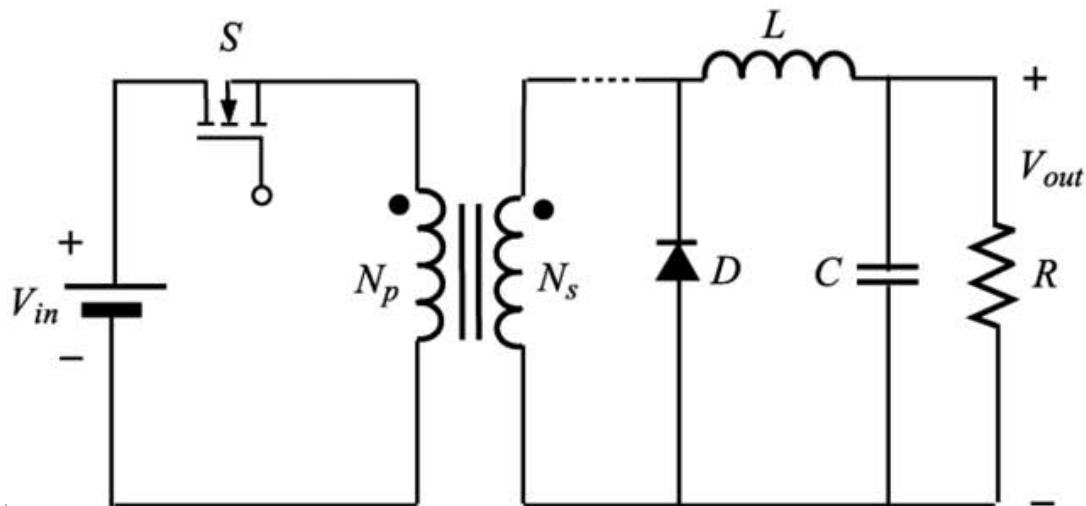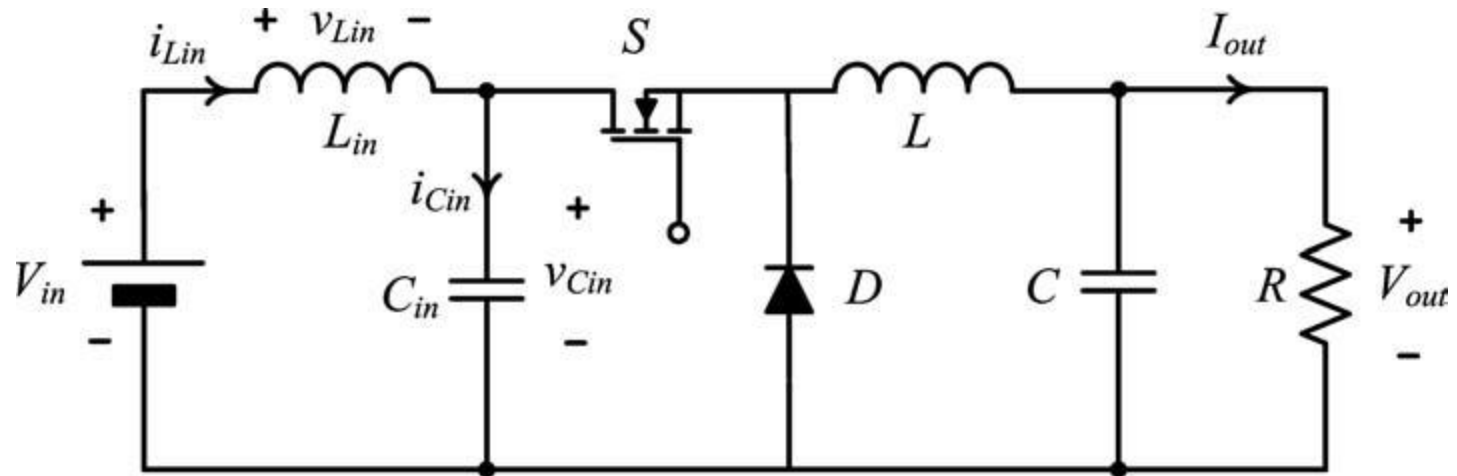

Forward Converter


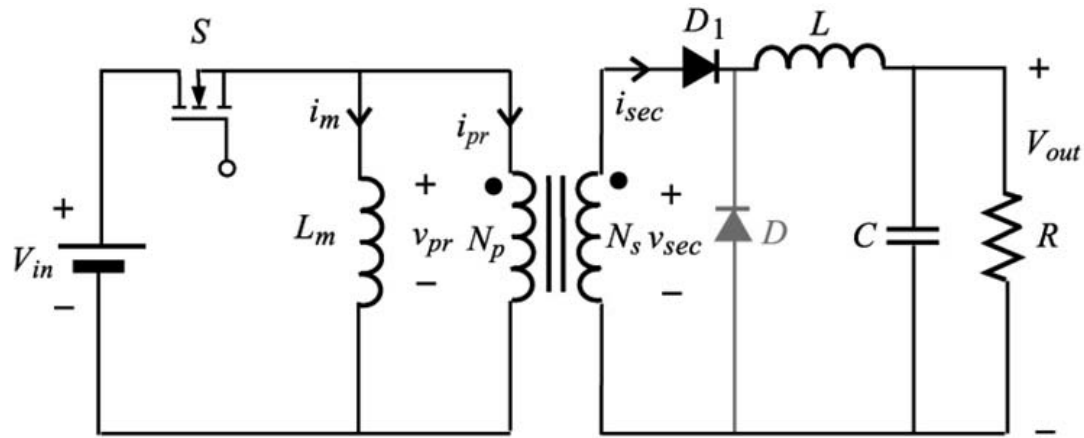


(d)

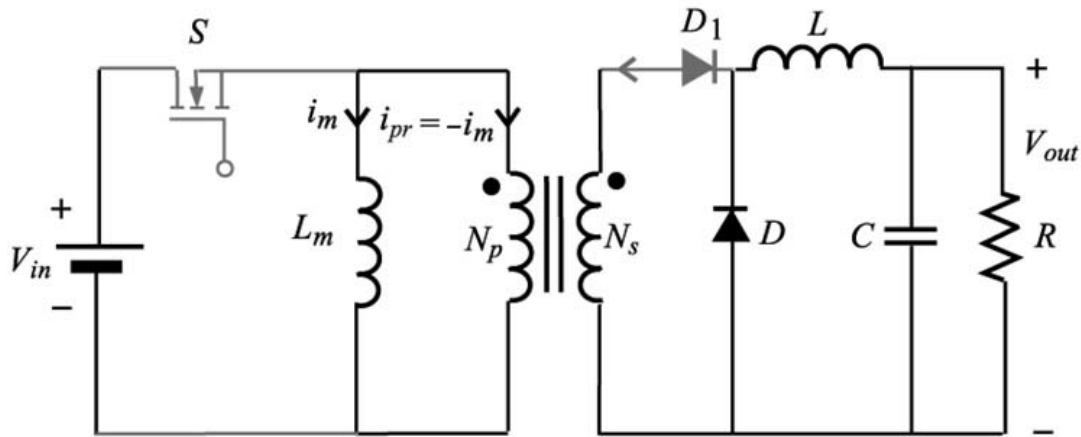






(e)

Forward Converter

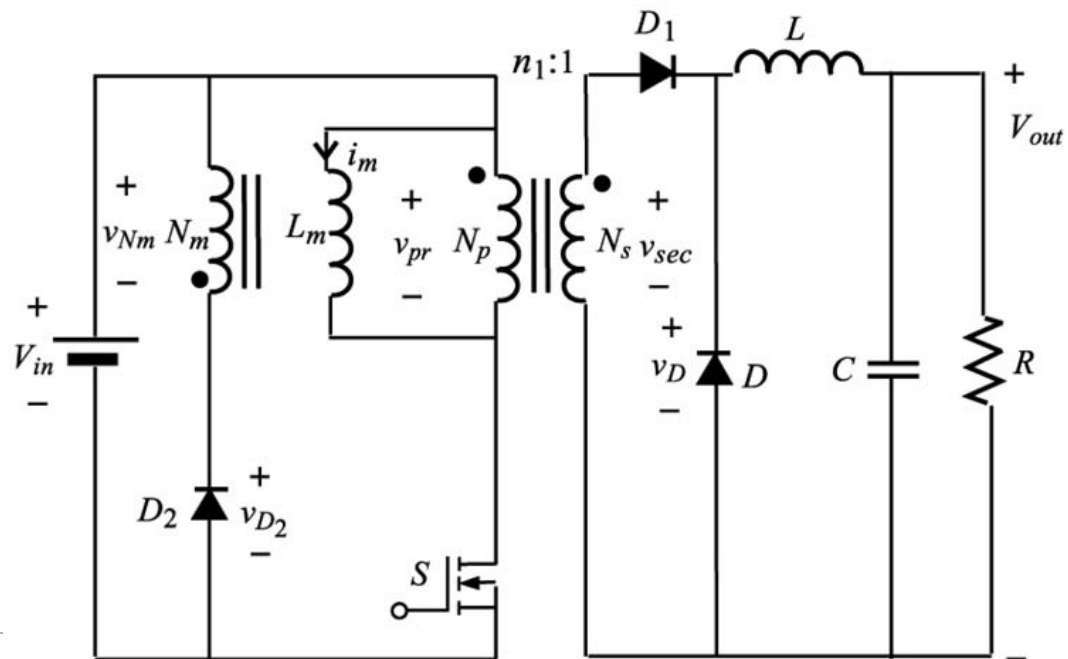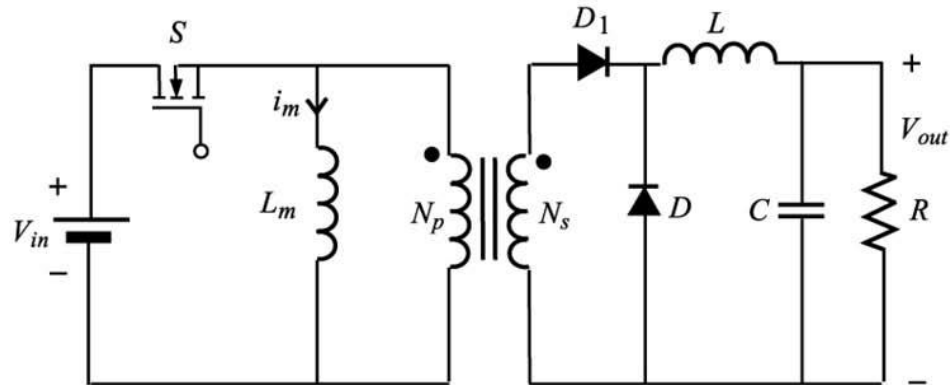


(f)


Continuous mode

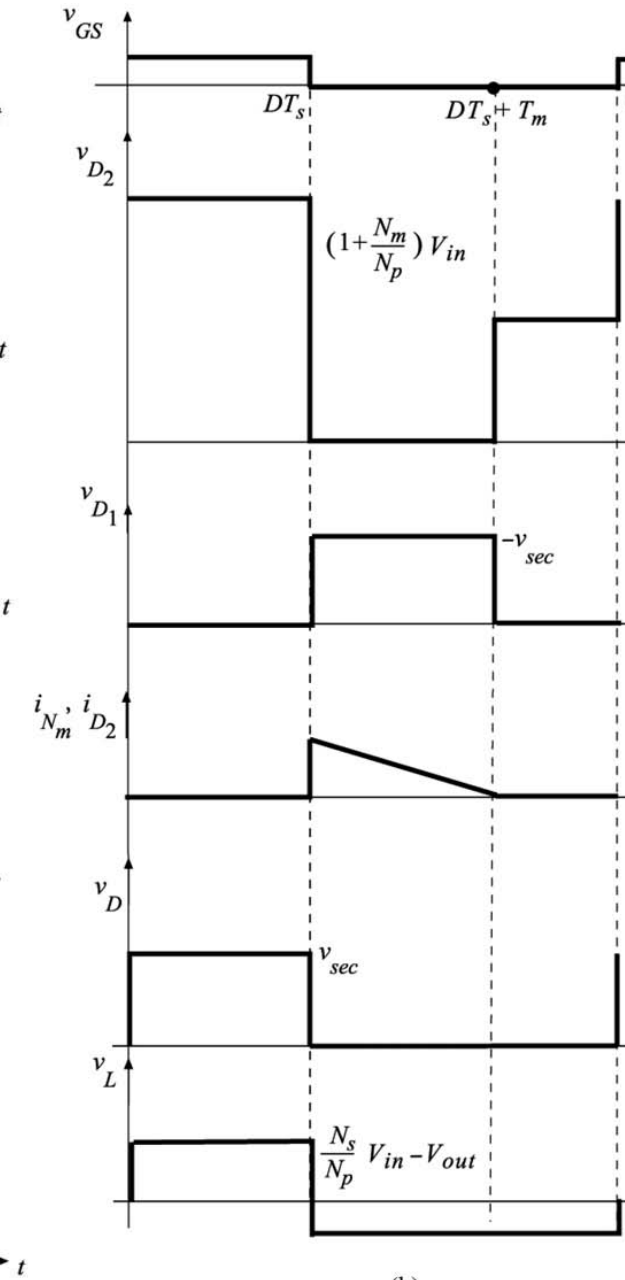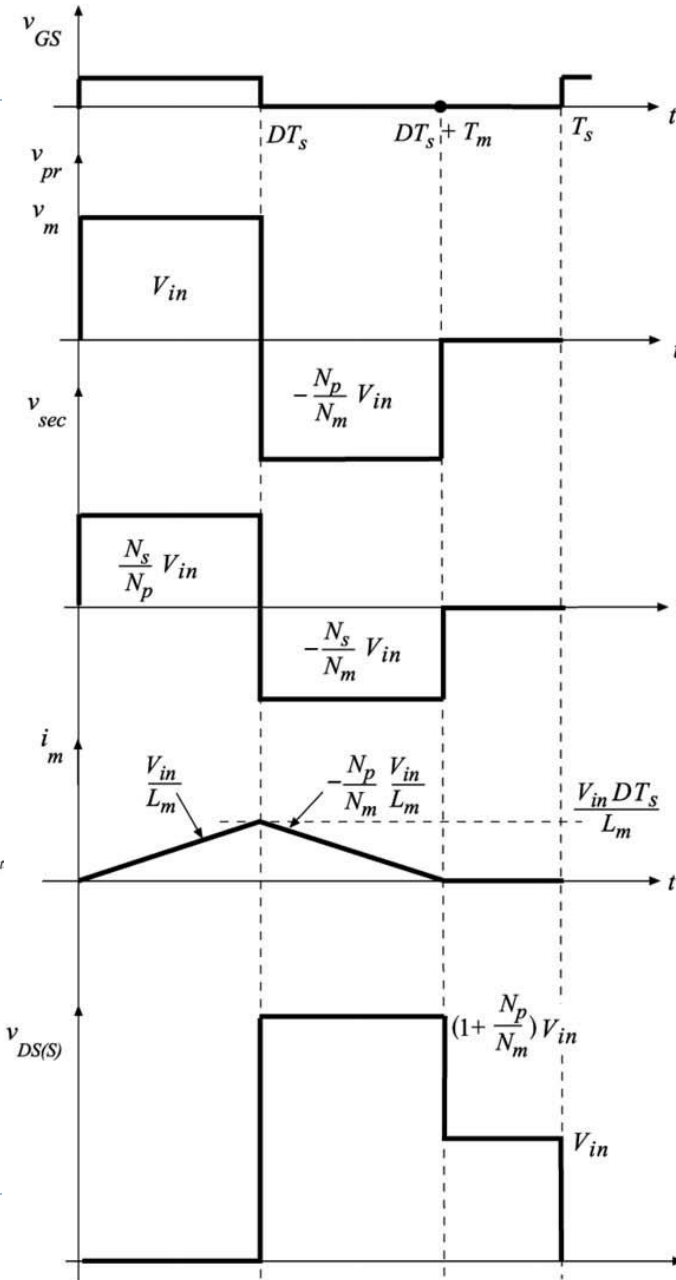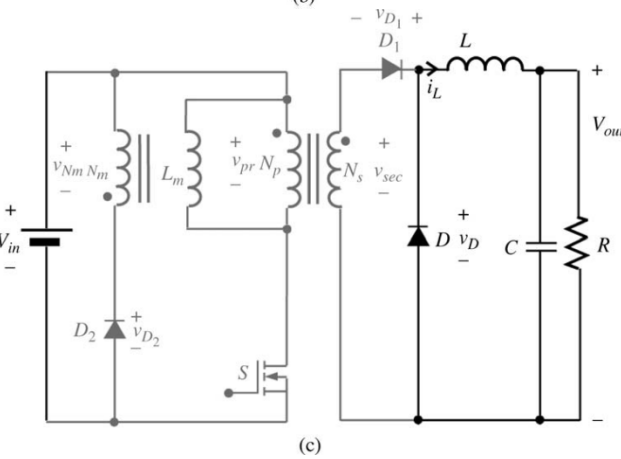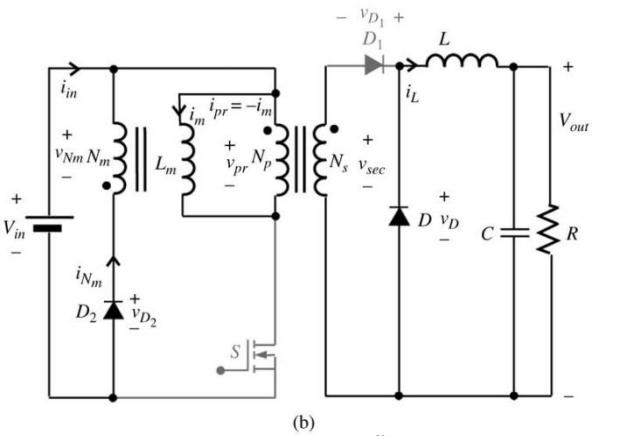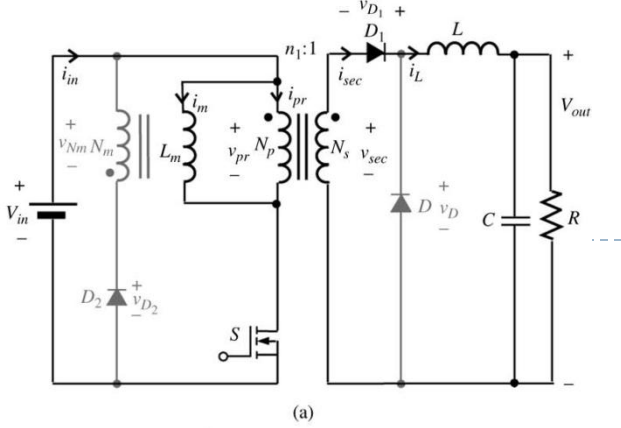



Diconctinuous mode

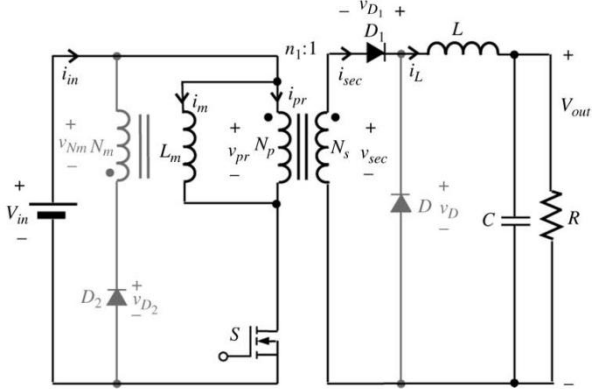


(a)

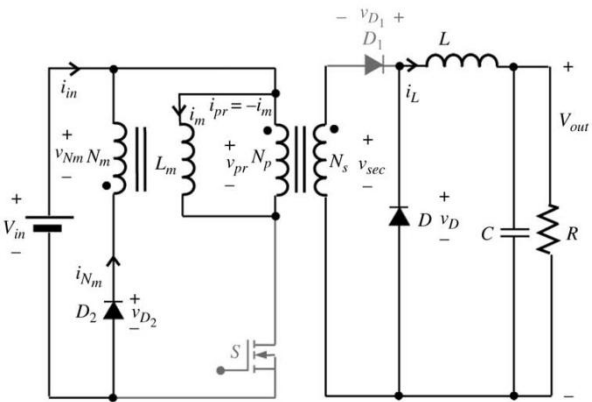


(b)

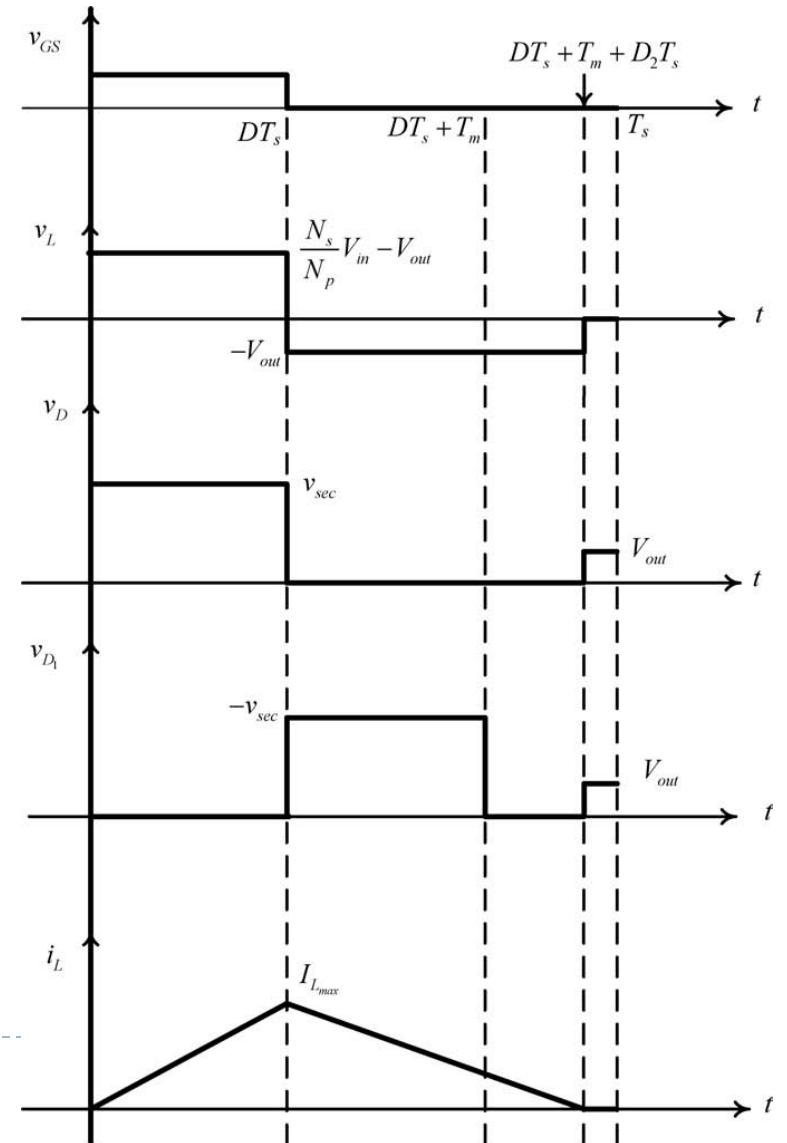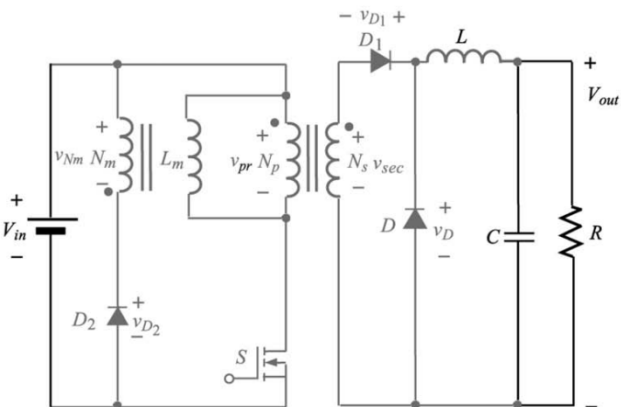

Multiple output forward converter

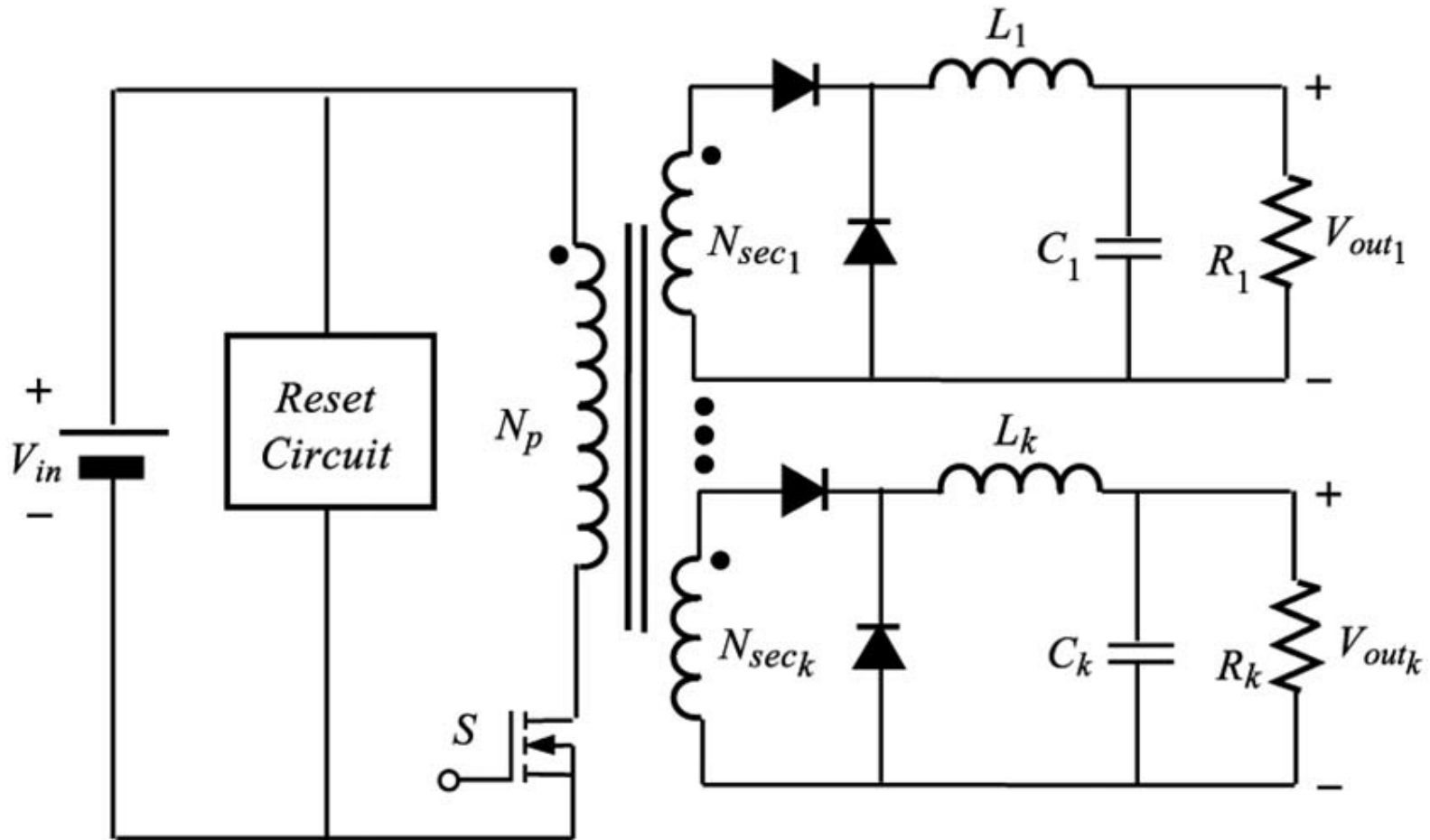


Two transistor forward converter

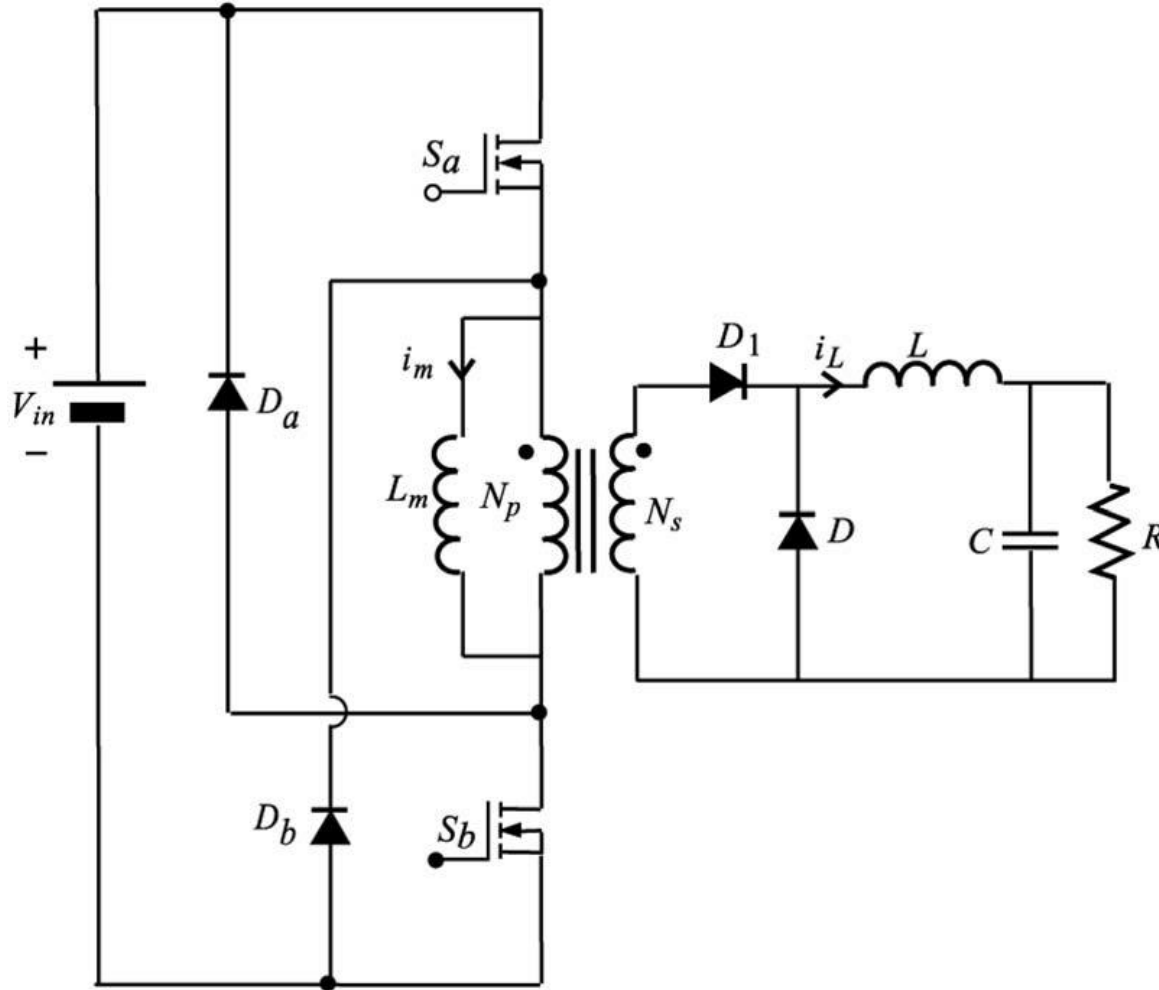


Flyback converter

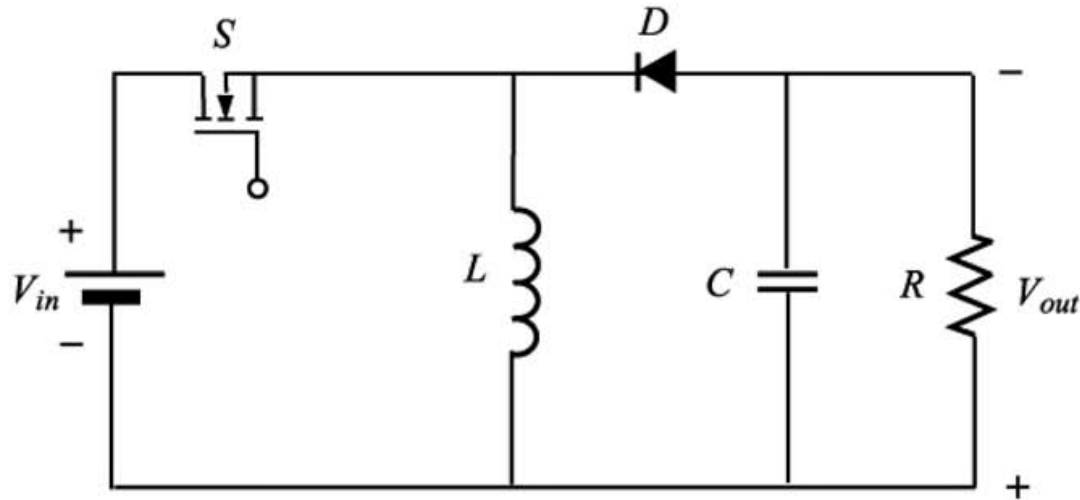- ▶ one of the oldest converters, Hertz effect
- ▶ Buck-boost




- ▶ Isolation „not transformer”


Flyback buck-boost

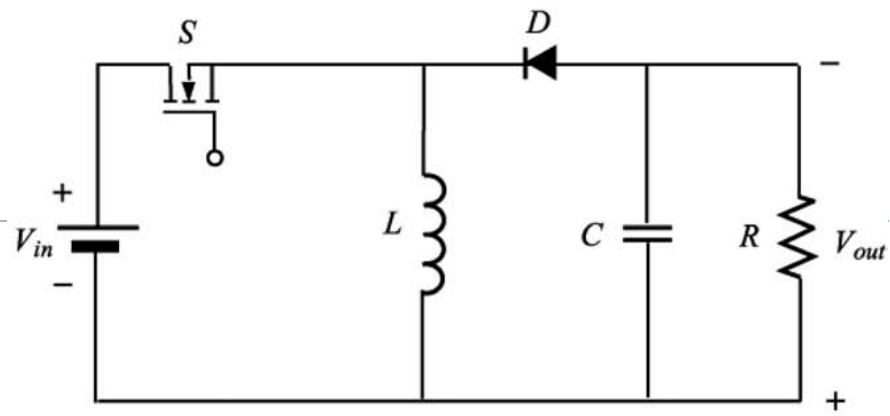


(a)

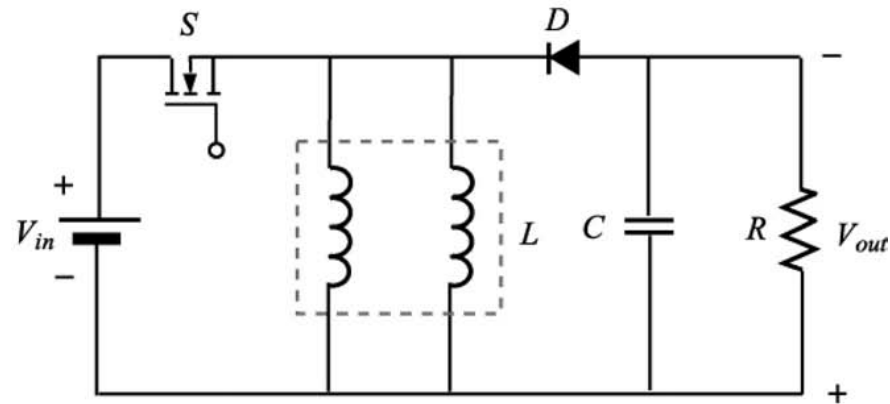


(b)

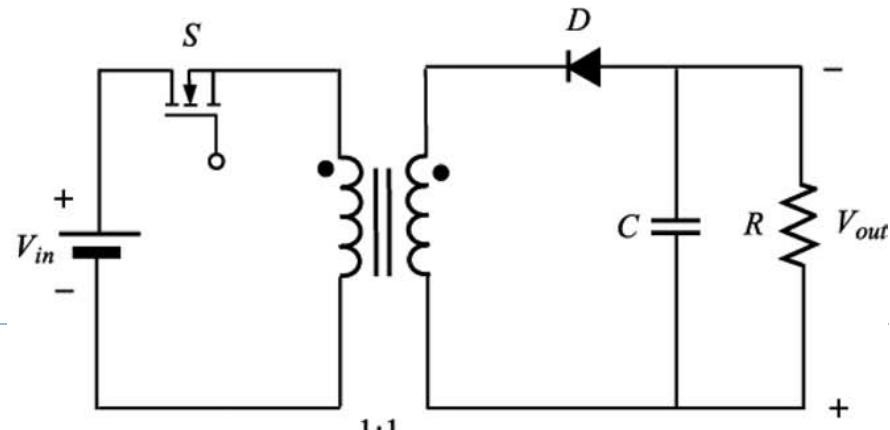

Flyback buck-boost

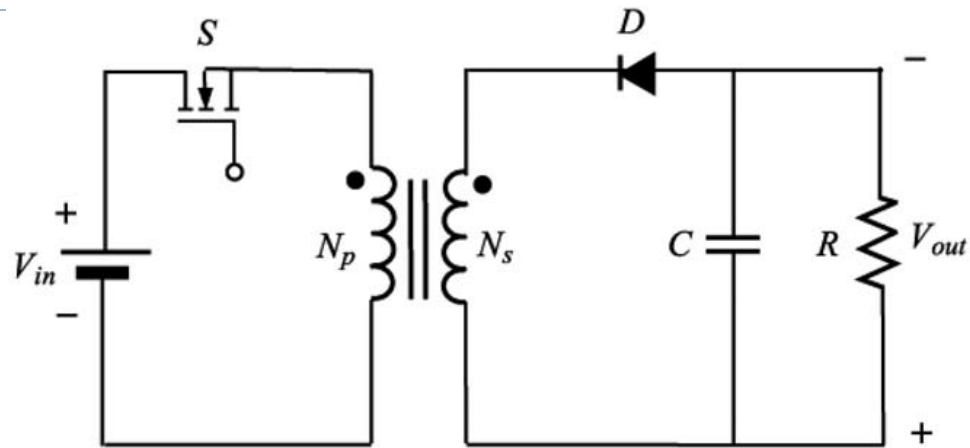


(d)

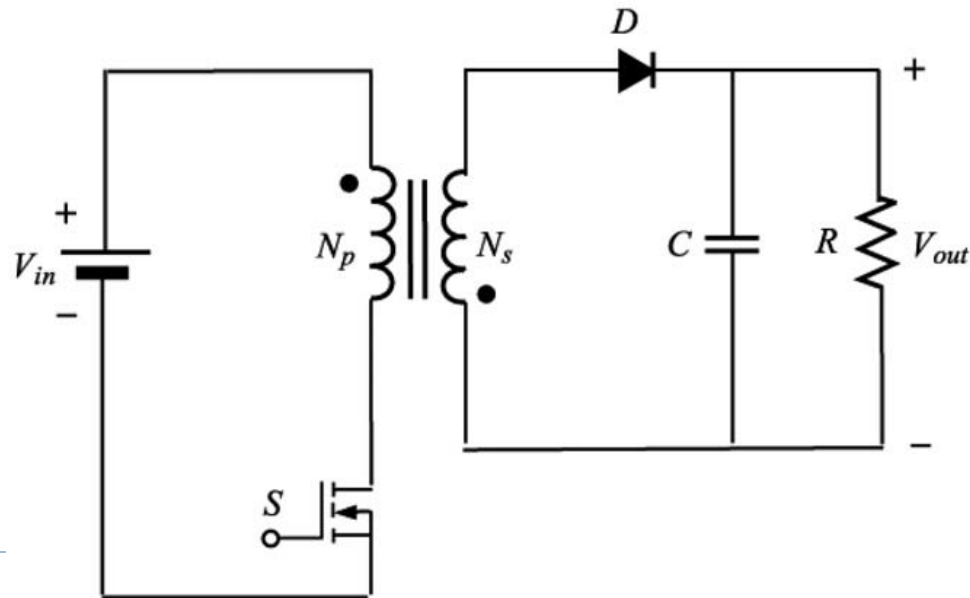


(e)


Flyback Waveform CCM

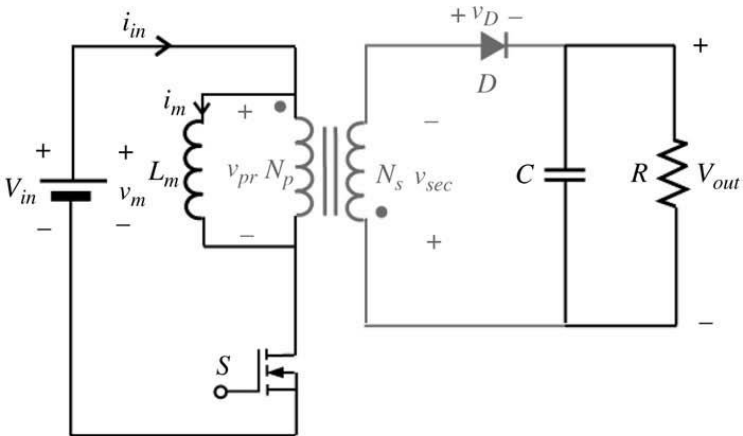


(a)

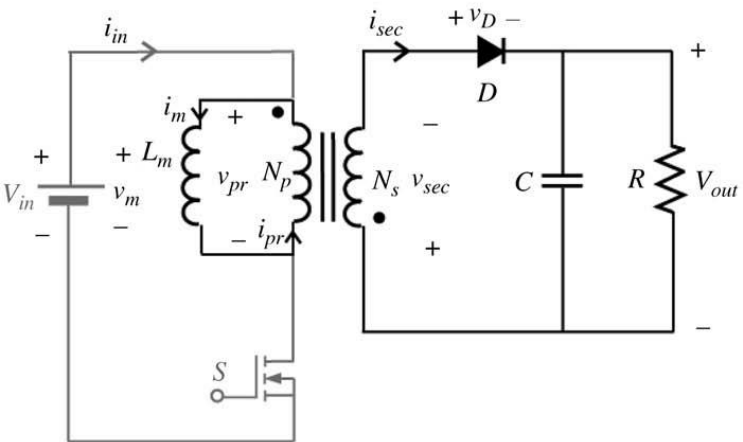

(b)

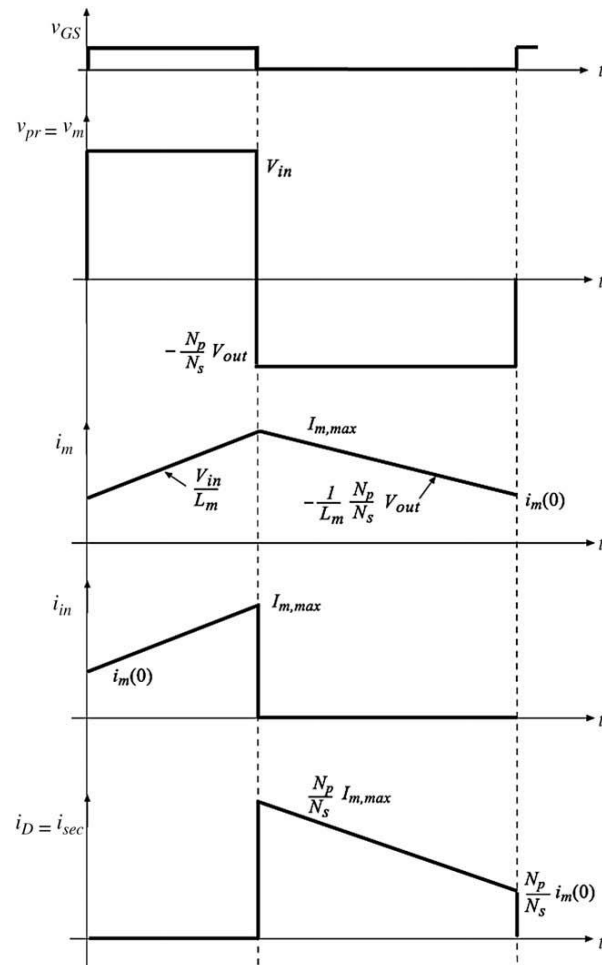


(a)

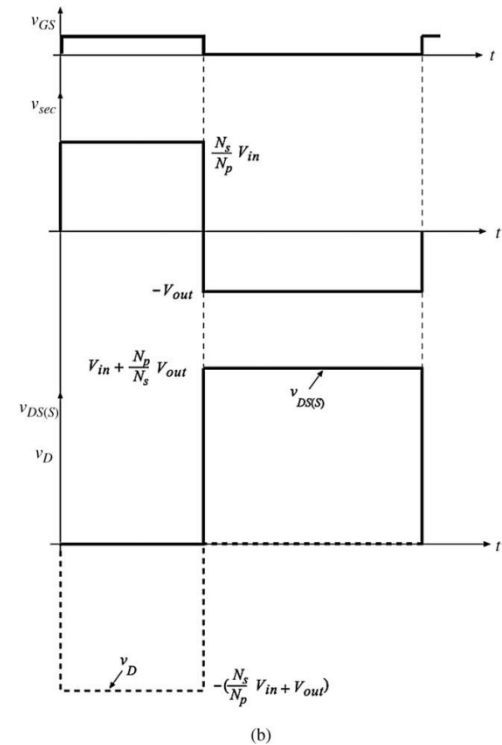


(b)

Flyback


Waveform DCM

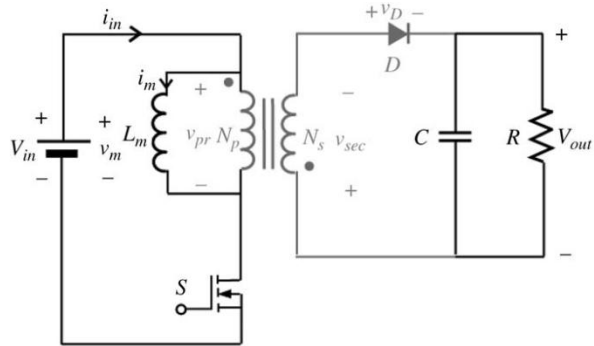

(a)


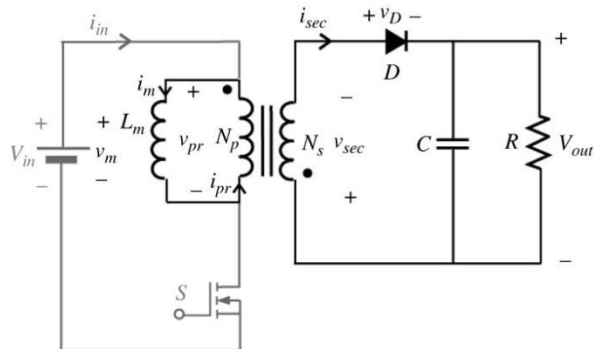


(b)

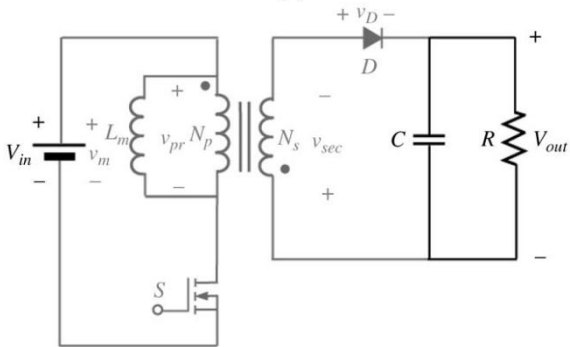


(c)

Flyback with realed transformer

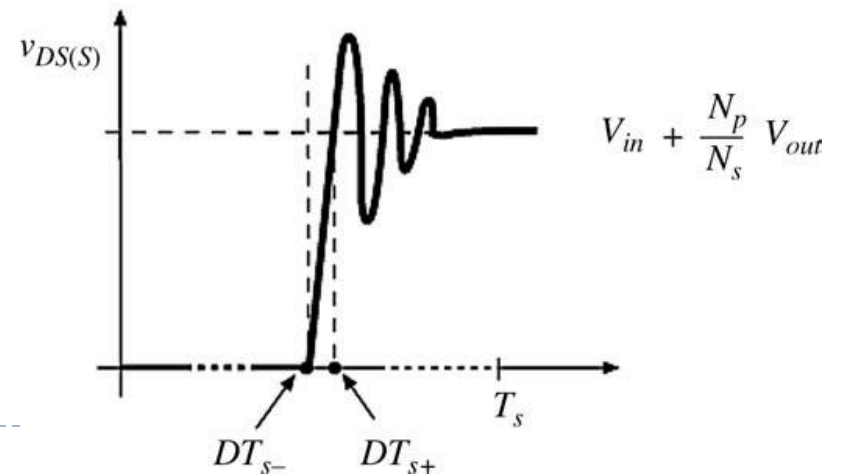
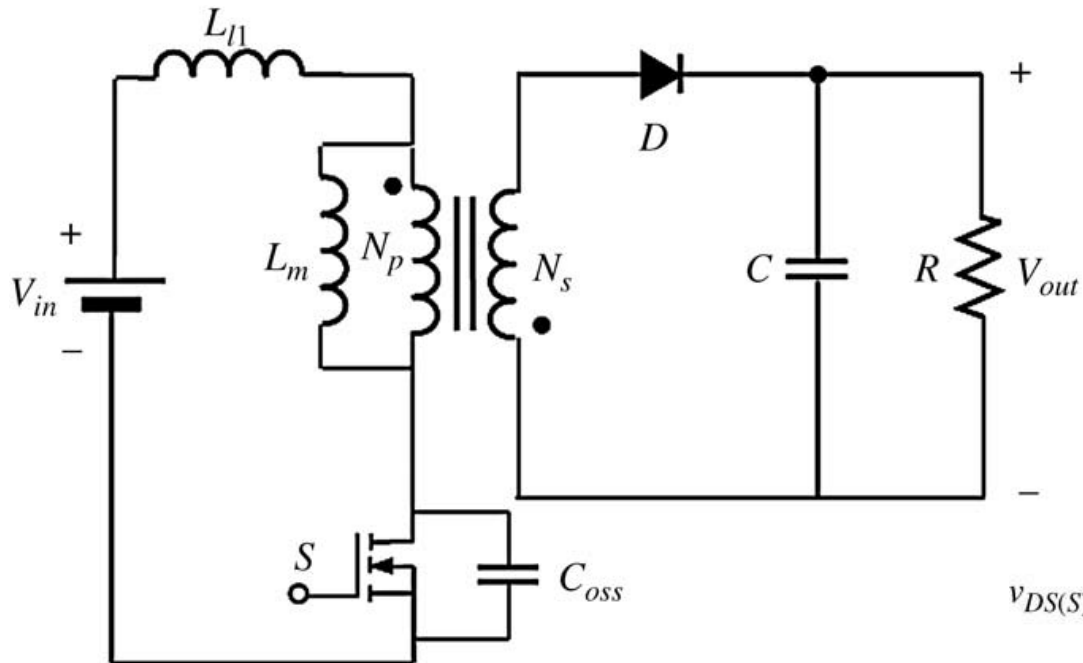


Two transistor flyback



- ▶ Input voltage very high

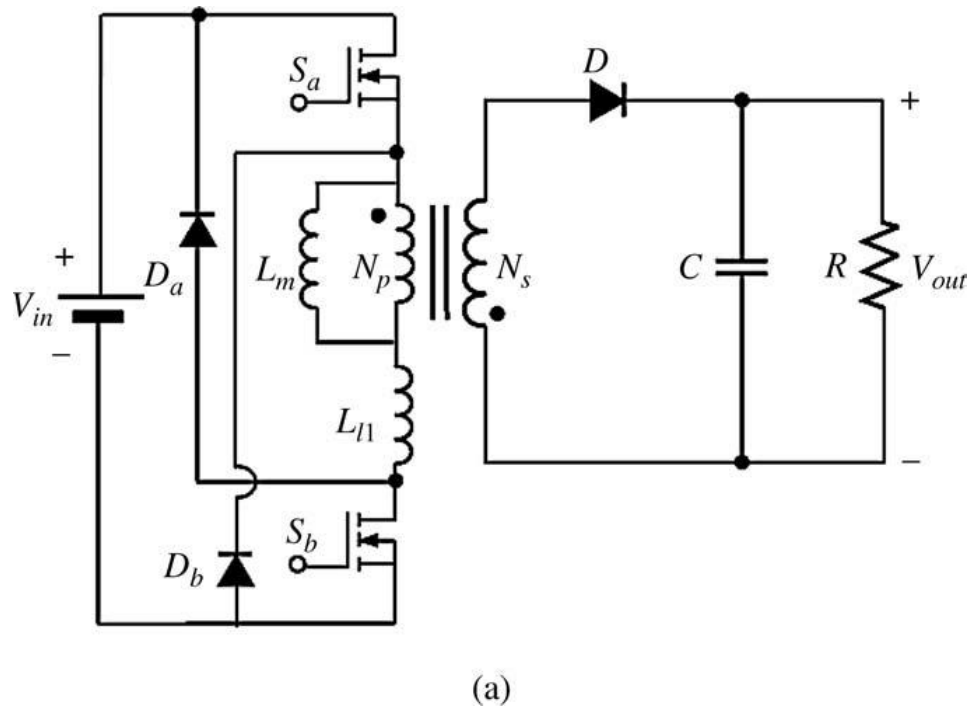

Two transistor flyback

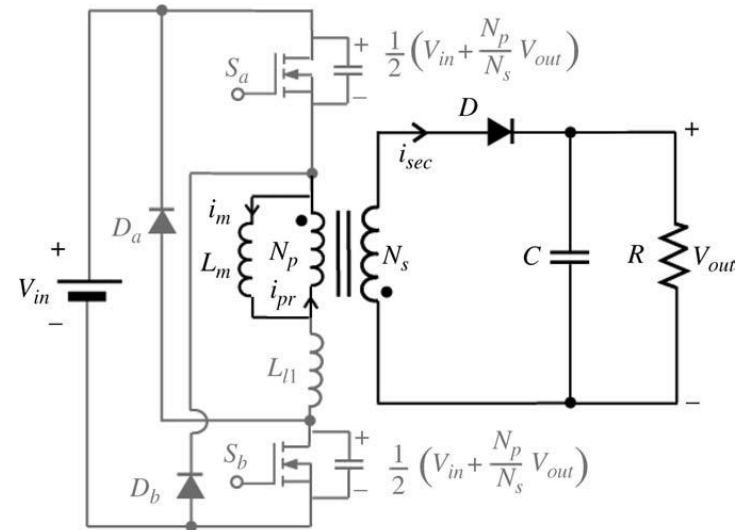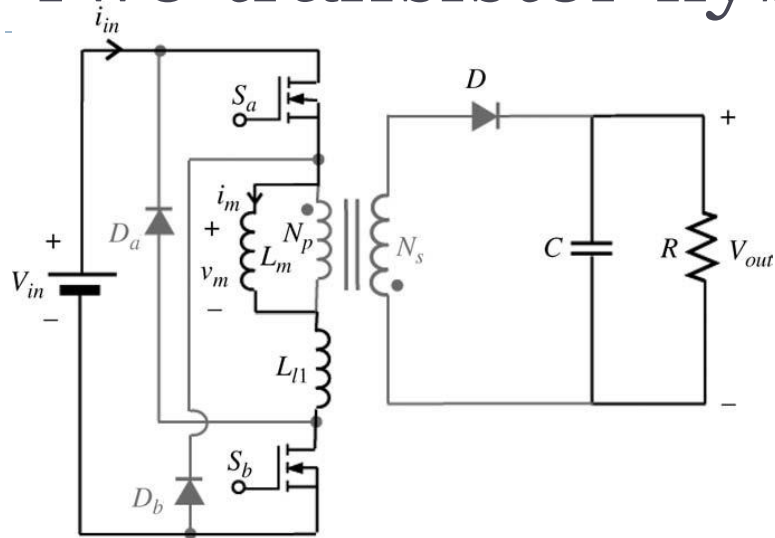


(d)

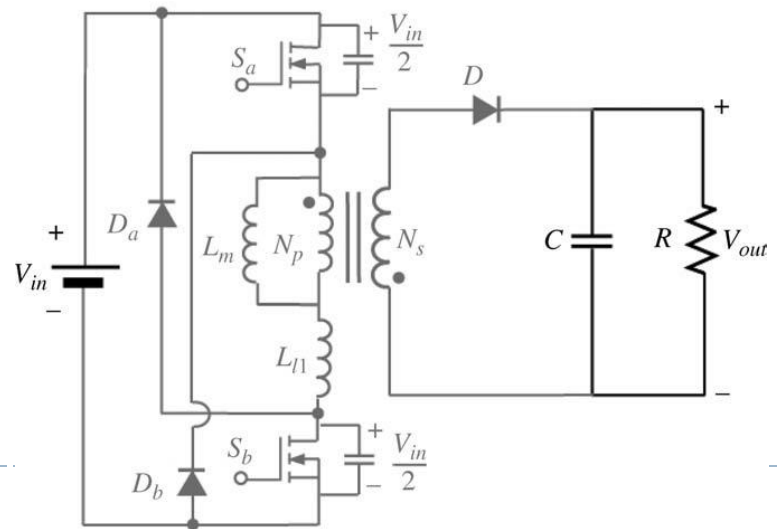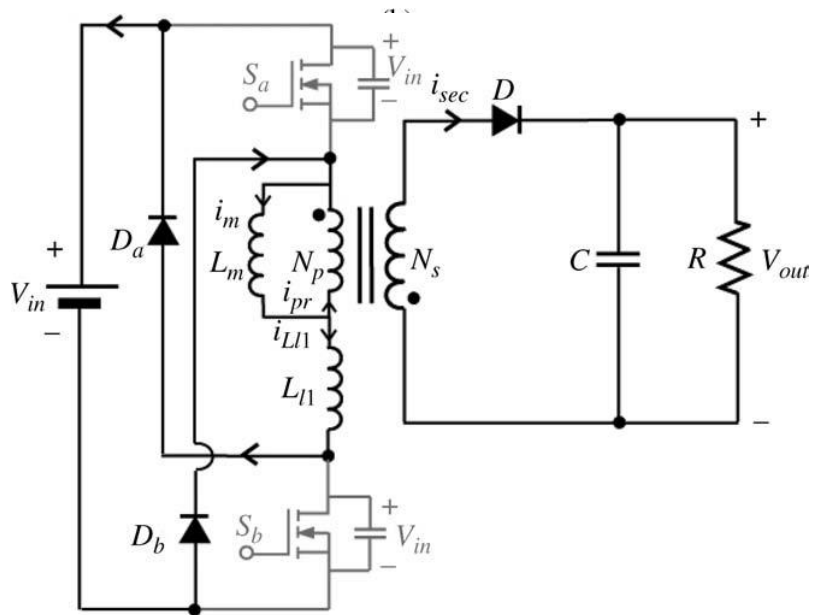


(e)

Equivalent Circuits in DC-DC Converters

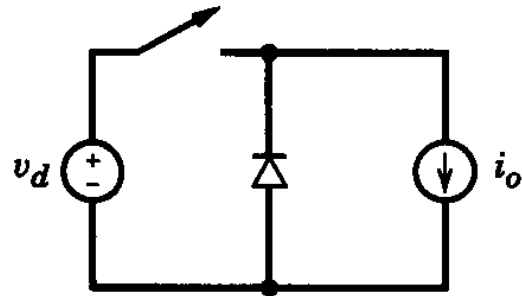
replacing inductors and capacitors by current and voltage sources, respectively




(a)

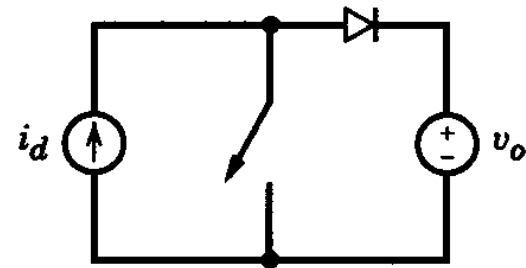

(b)

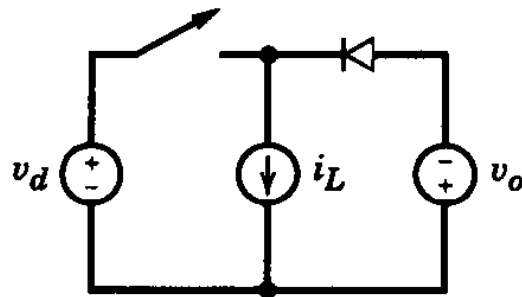



(c)

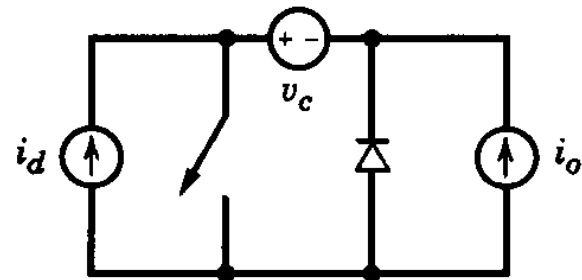

(d)

Reversing the Power Flow in DC-DC Conv.

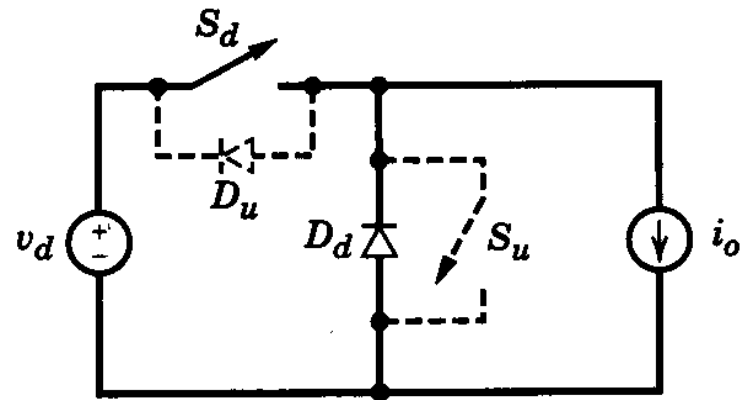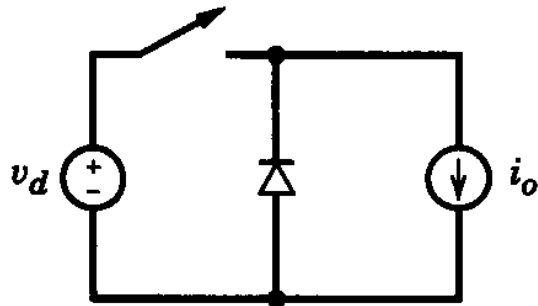- ▶ For power flow from right to left, the input current direction should also reverse



Homework

- ▶ Prześledzić obwody mocy znalezionych w sieci zasilaczy
 - ▶ AT
 - ▶ ATX
 - ▶ viper12