

Energoelektronika





8. Resonant Converters

dr inż. Dariusz Janiszewski

Plan



- ▶ Idea of Resonant Converter
- ▶ Zero Current Switch
- ▶ Zero Voltage Switch
- ▶ Resonant Filter
- ▶ Quasi Resonant Converters
 - ▶ ZC
 - ▶ ZV
- ▶ Full Resonant Converter
- ▶ Tank network
- ▶ Series Resonant Converter
- ▶ *Parallel Resonant Converter*

Idea

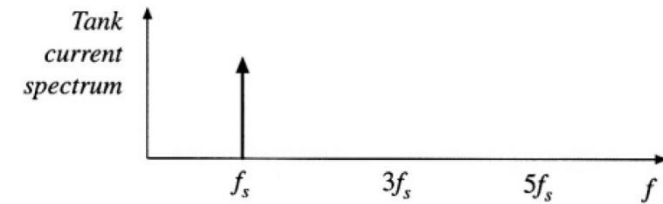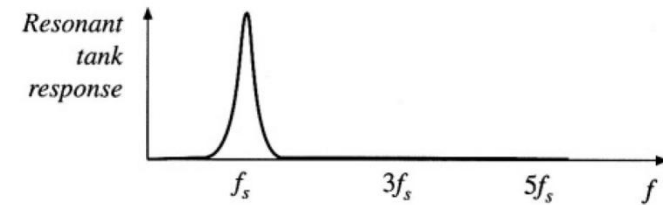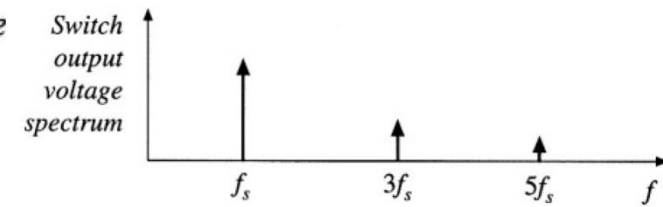
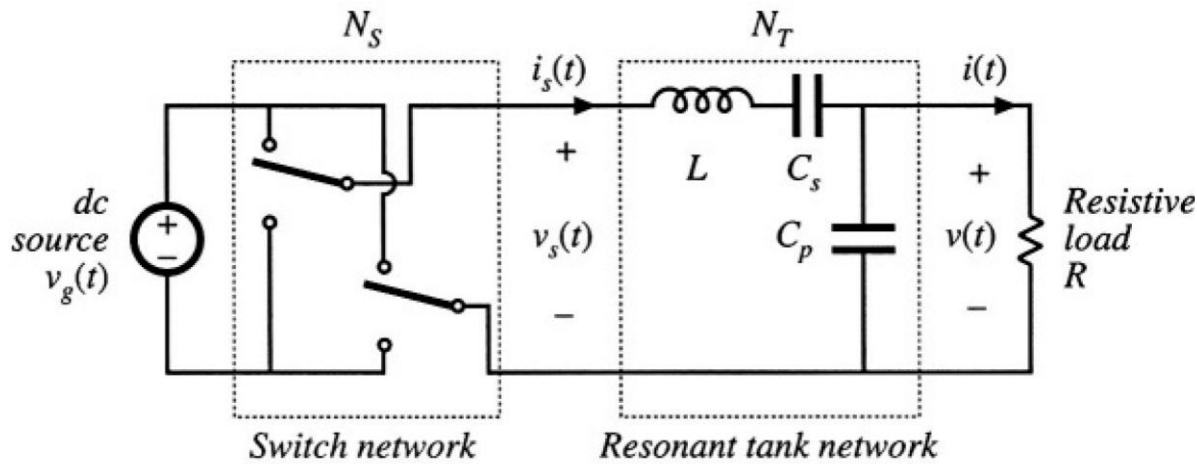


IDEAL



PRACTICAL

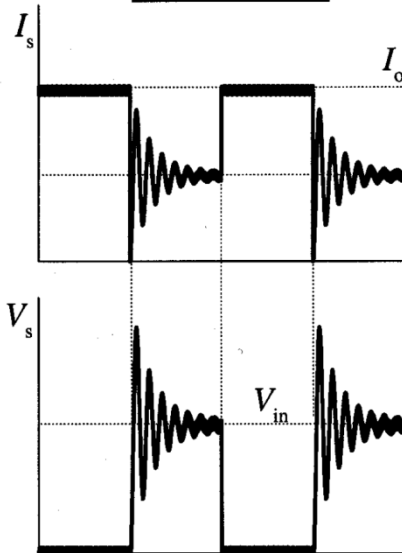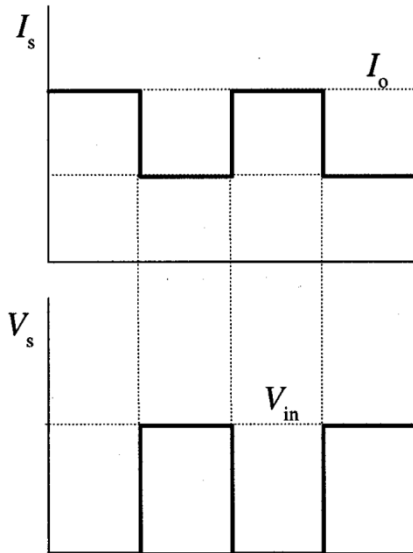



Small capacitor

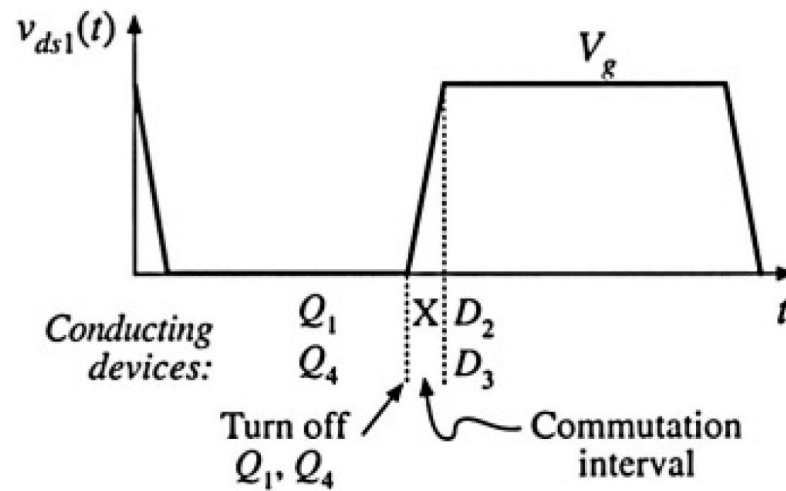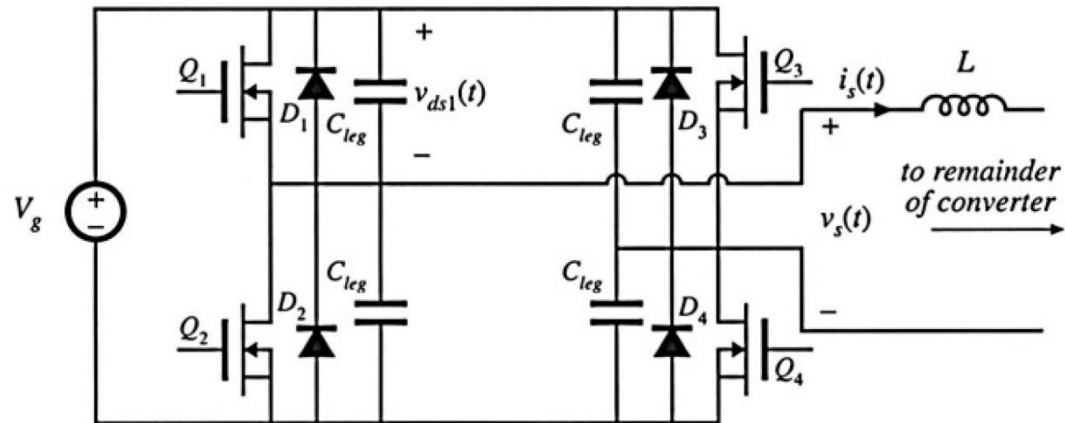







Zero Current Switch

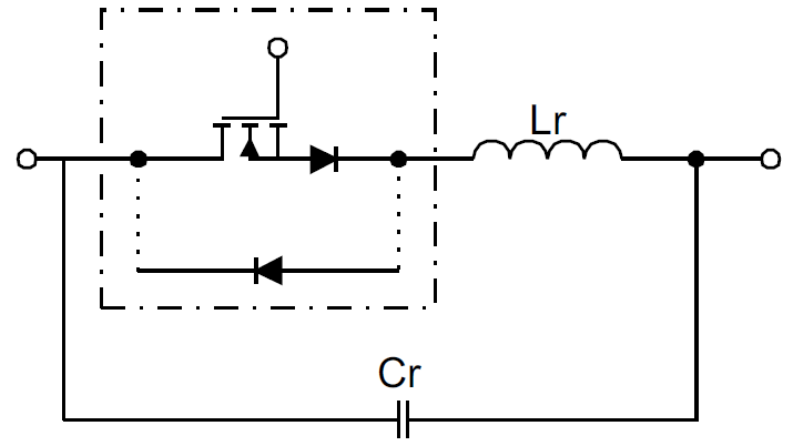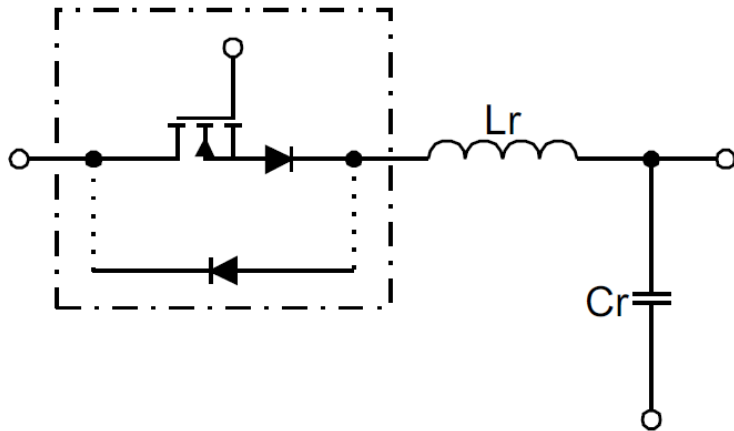



Zero Voltage Switch

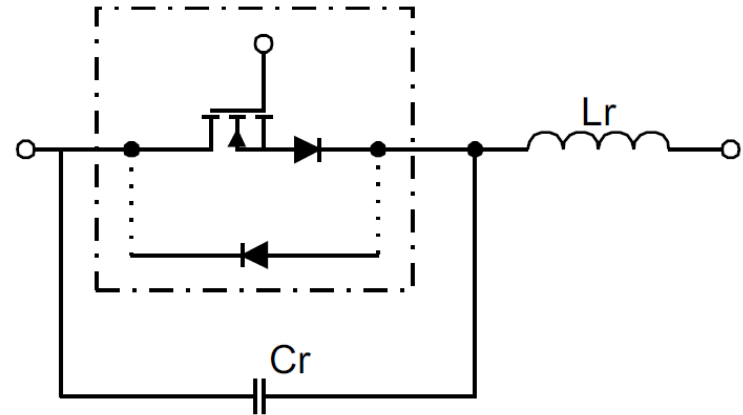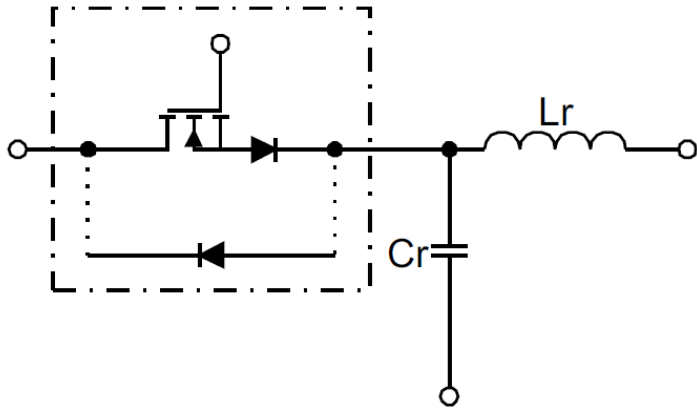


Resonant Filters

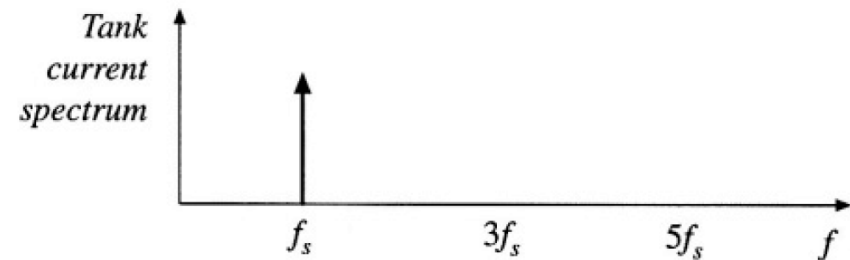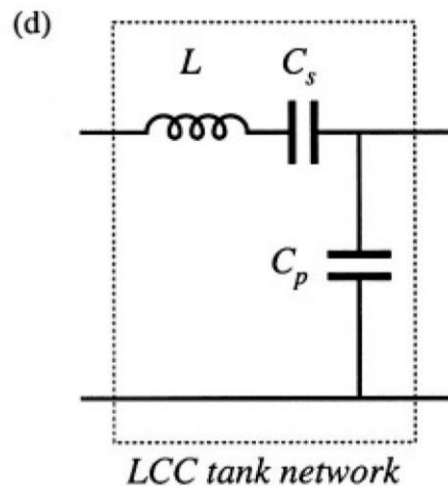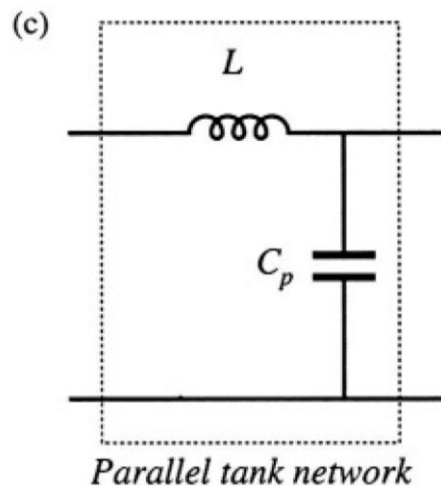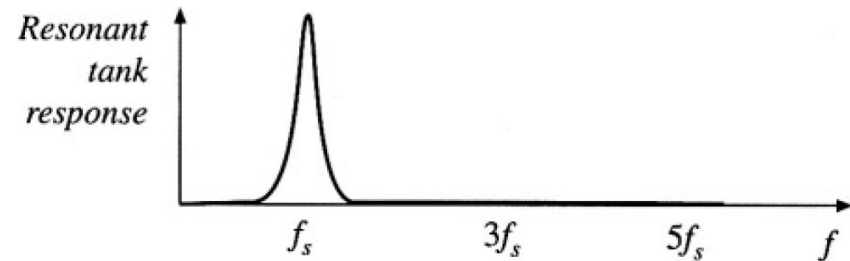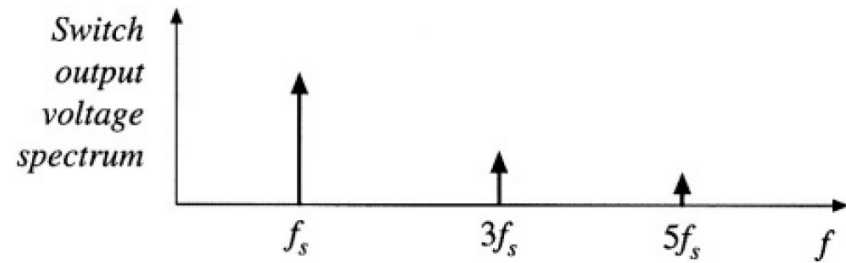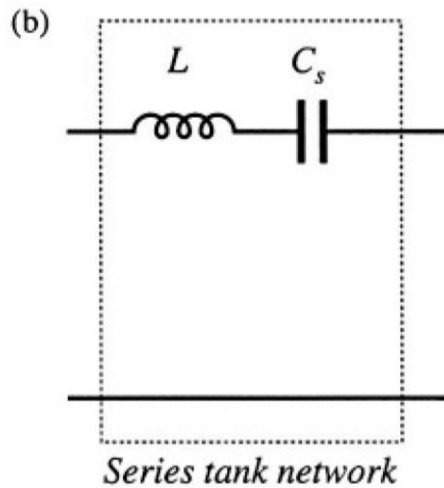

Quasi Resonant ZC

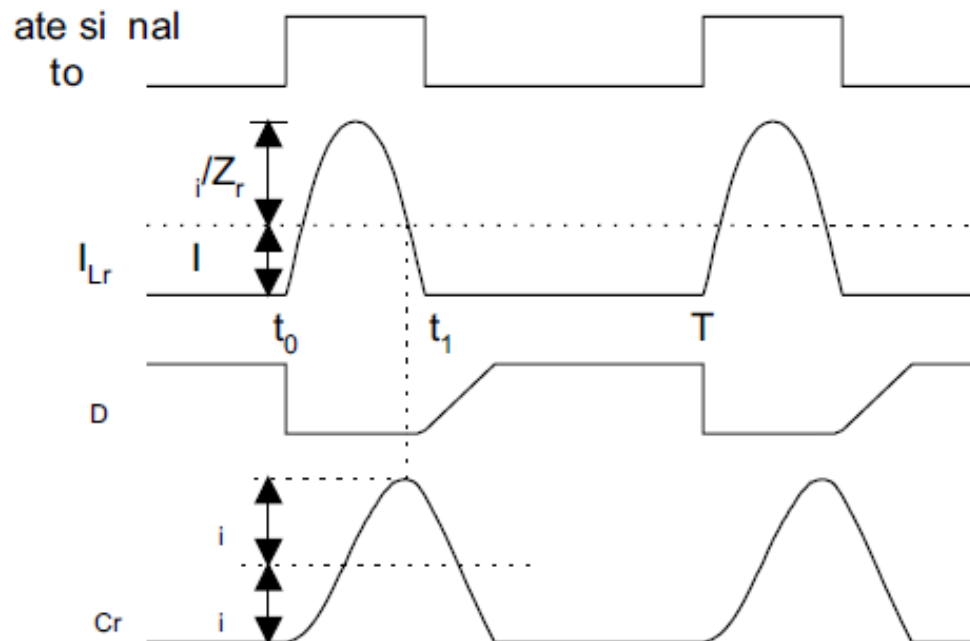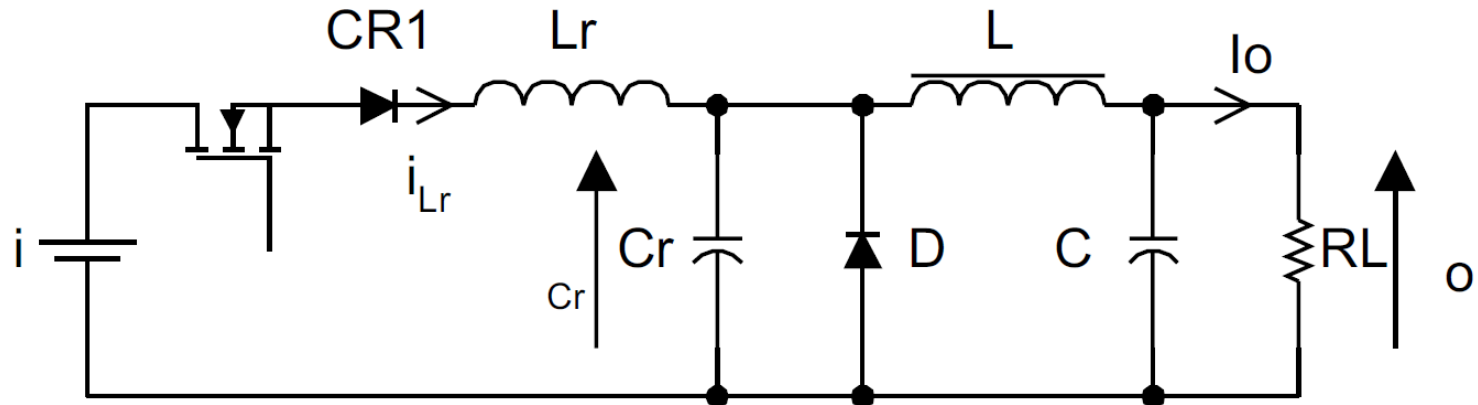

Quasi Resonant ZC


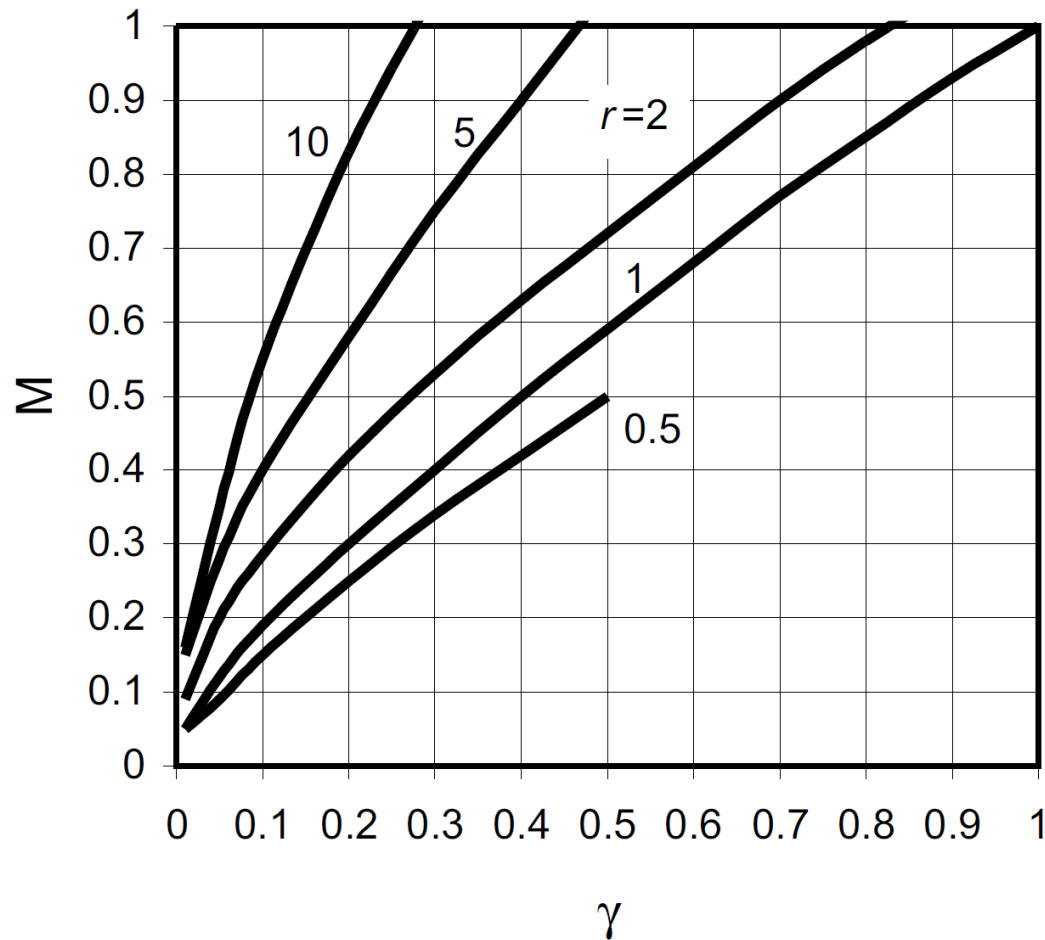


$$M = \frac{V_o}{V_i}$$


$$r = \frac{R_L}{Z_r}$$

$$\gamma = \frac{f_s}{f_r}$$

Quasi Resonant ZV

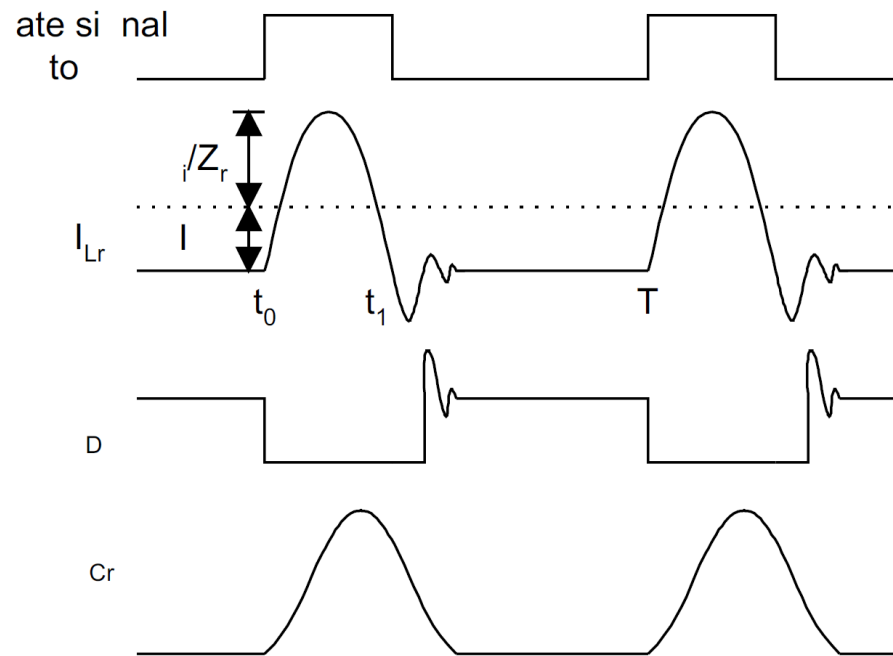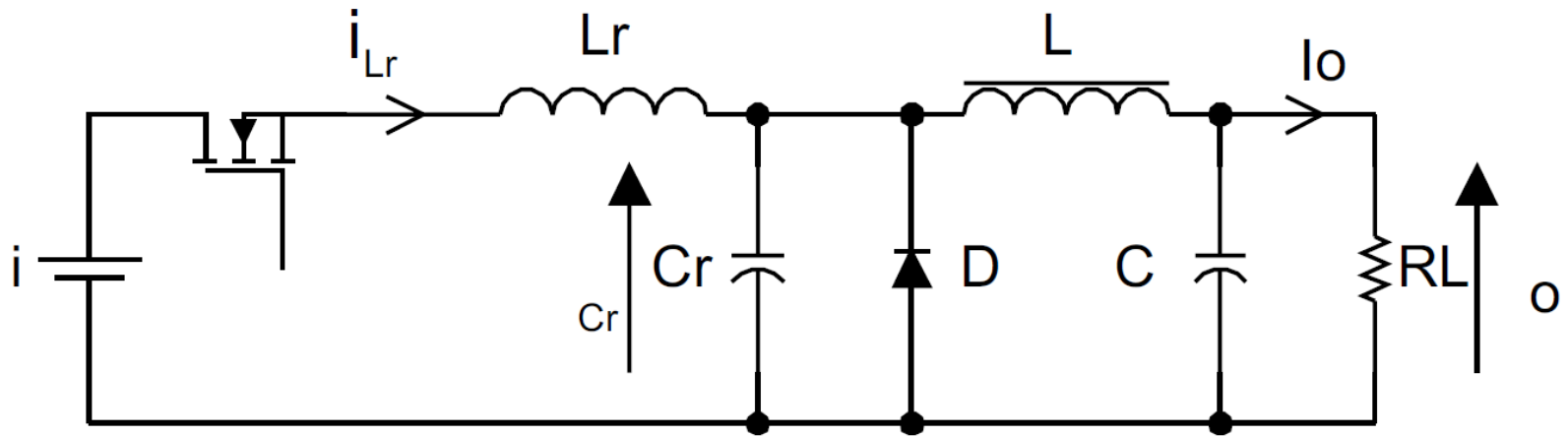

Quasi Resonant ZV


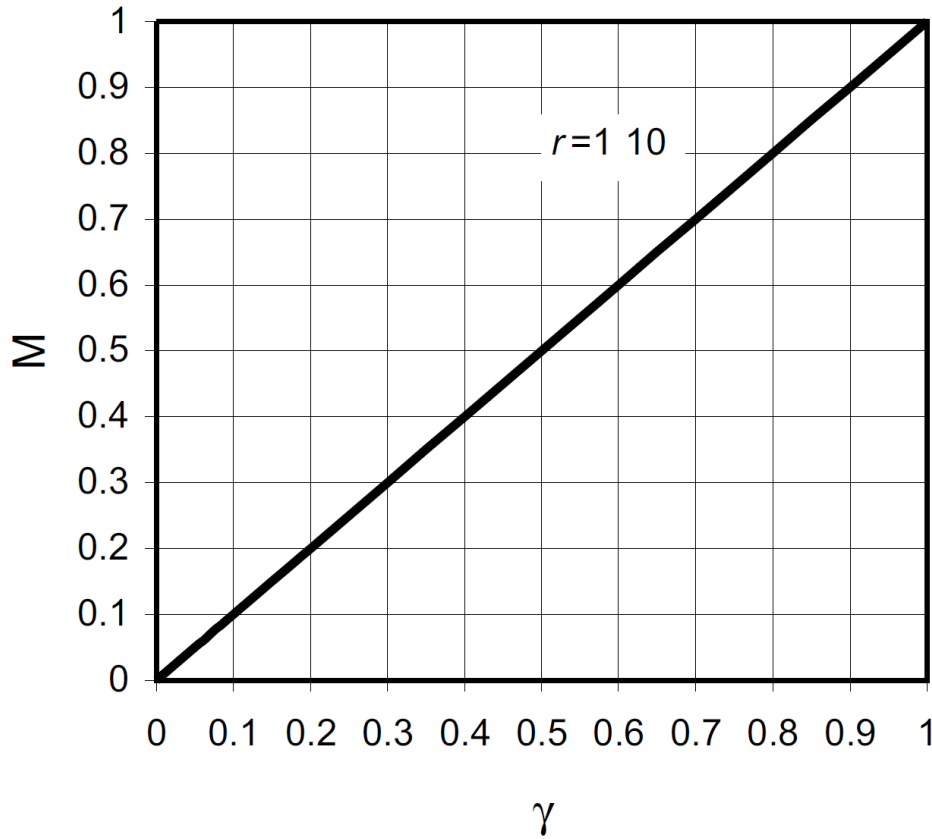


$$M = \frac{V_o}{V_i}$$




$$r = \frac{R_L}{Z_r}$$

$$\gamma = \frac{f_s}{f_r}$$



DC BUCK as Quasi Resonant ZCV

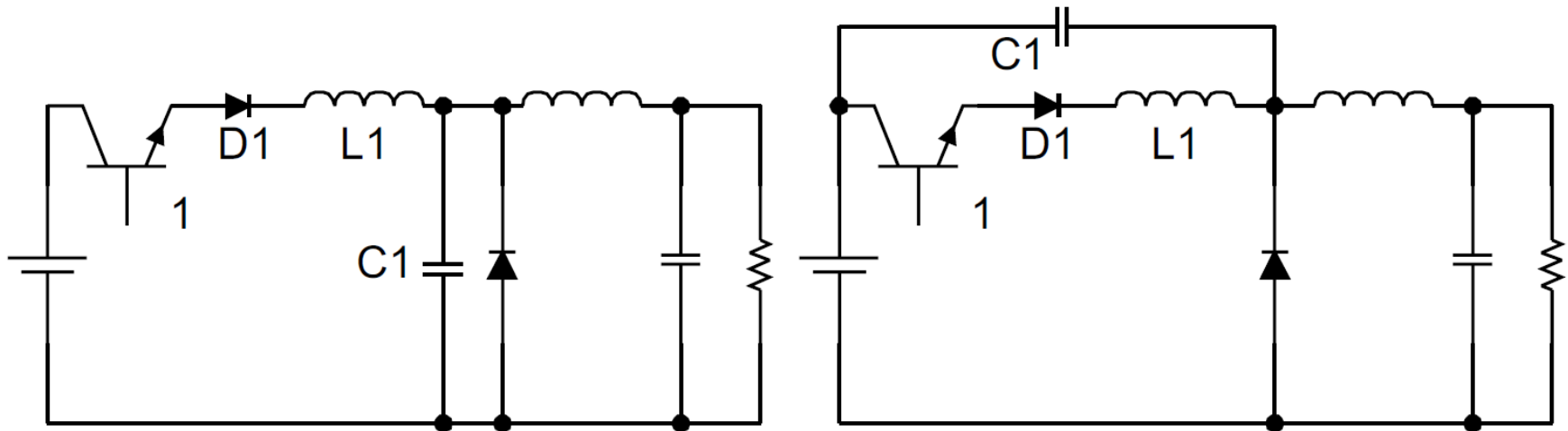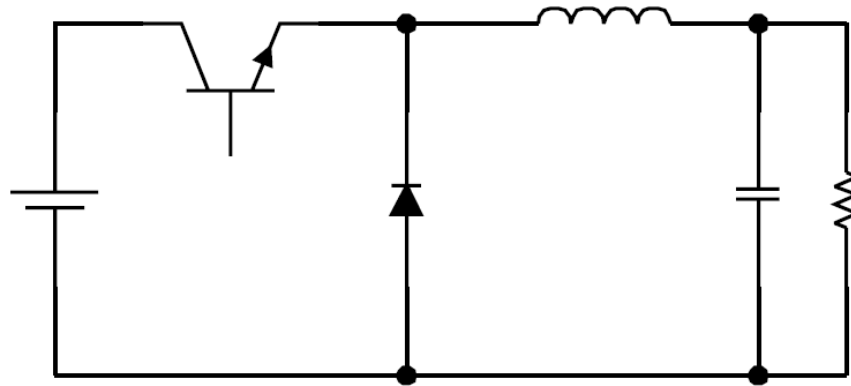



Boost as QR ZCV

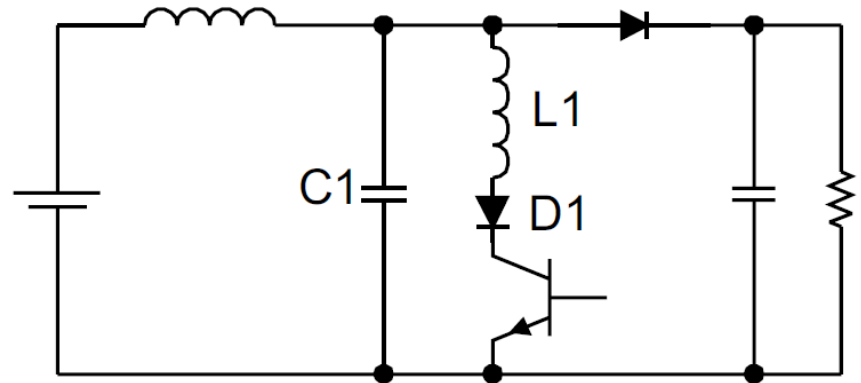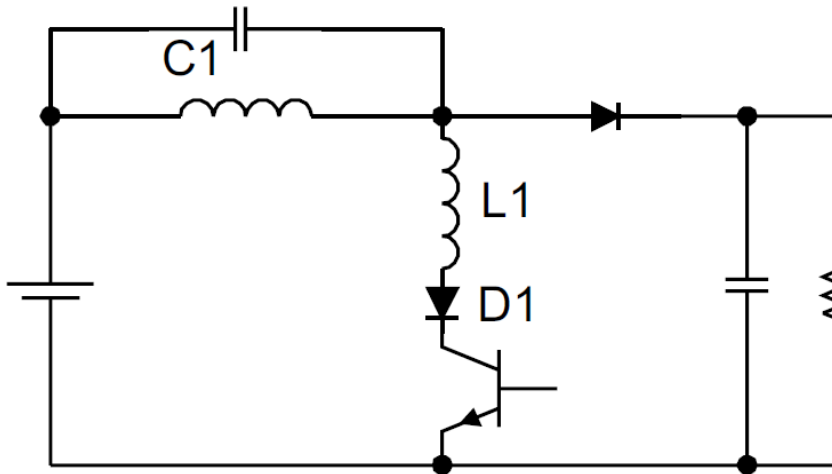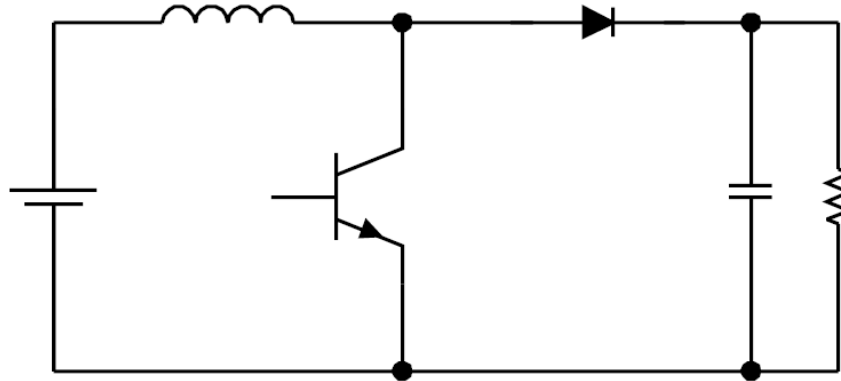



Buck-Boost as QR ZCV

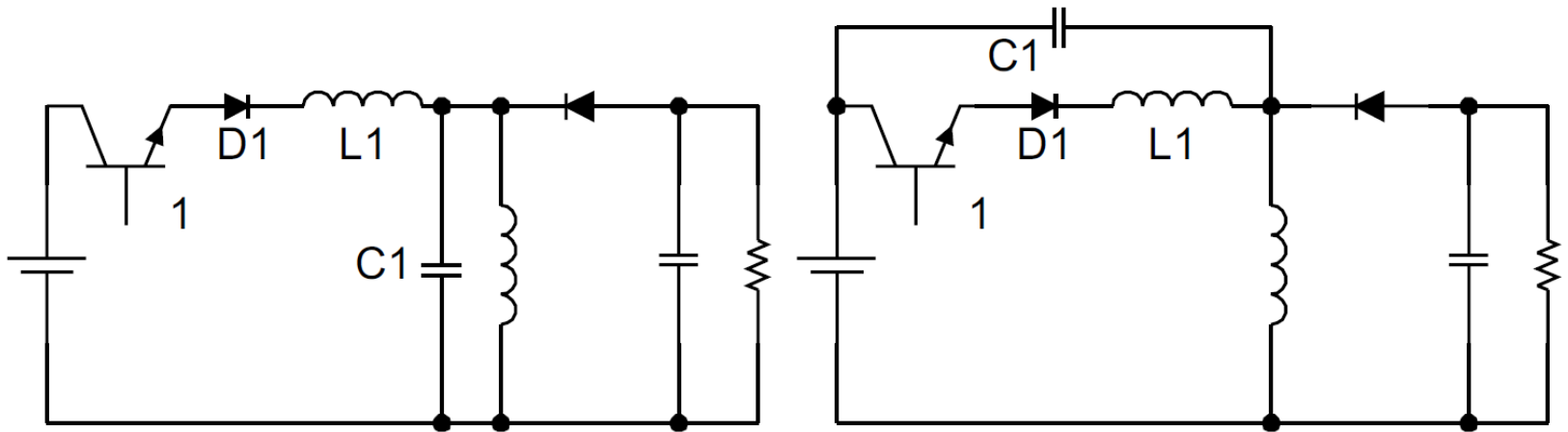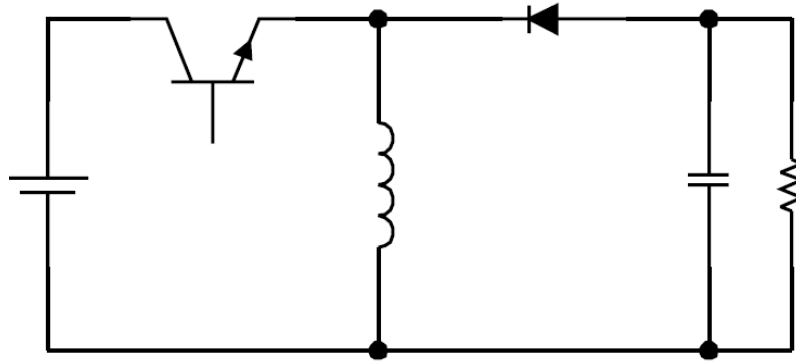




Ćuk as QR ZCV

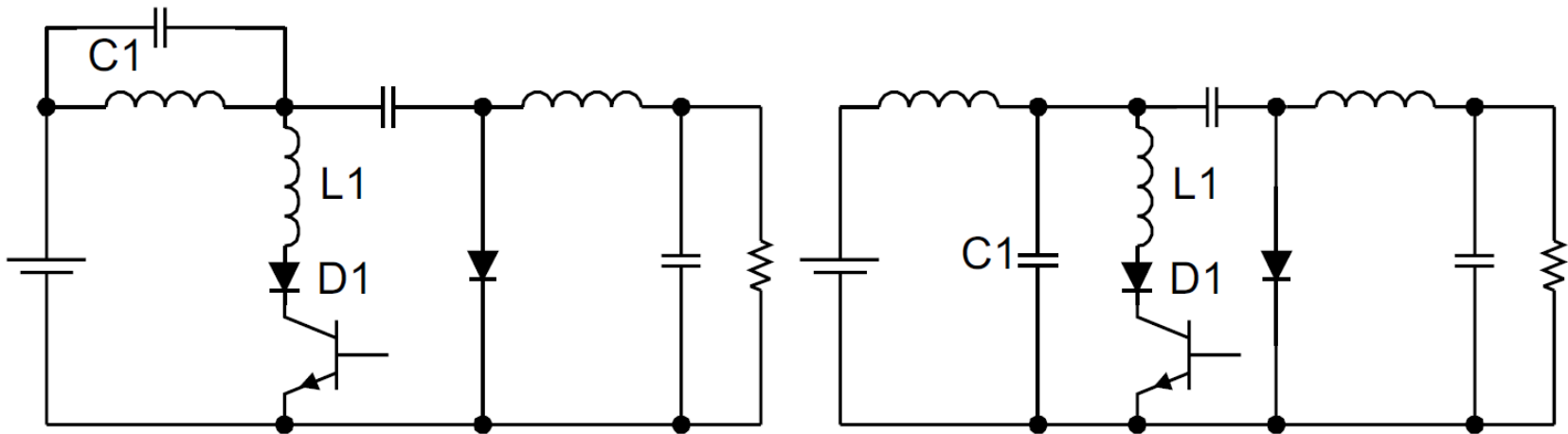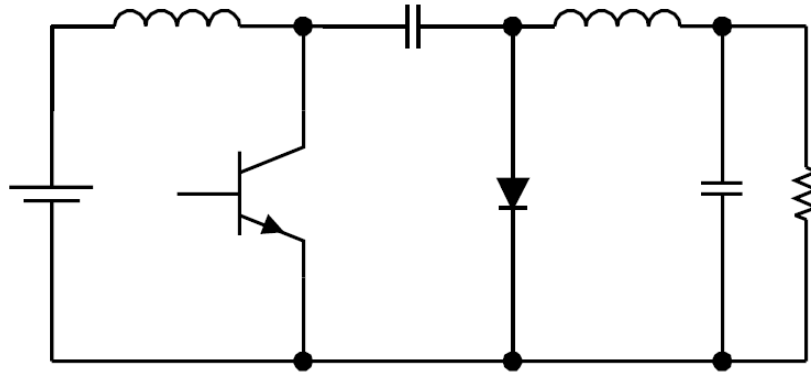


SEPIC as QR ZCV

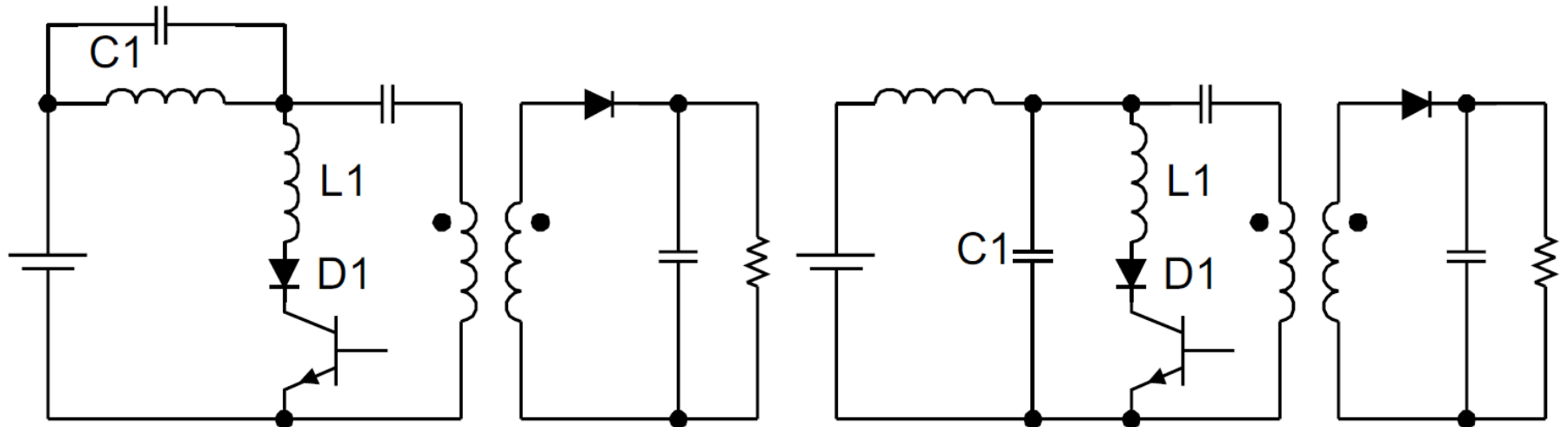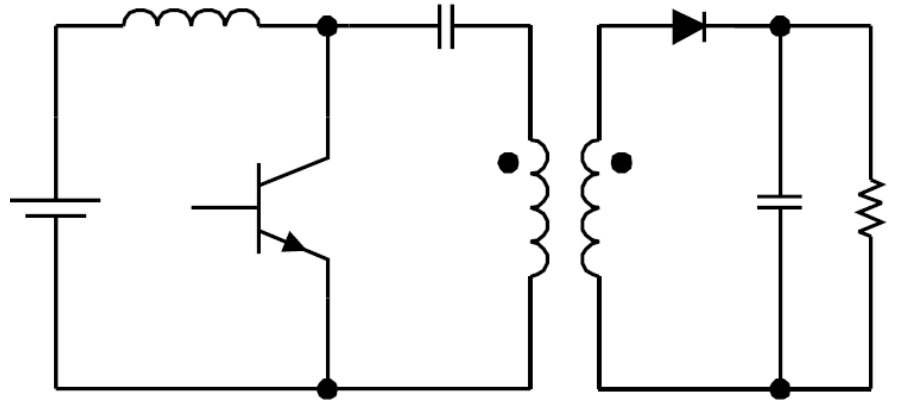





Flyback as QR ZCV

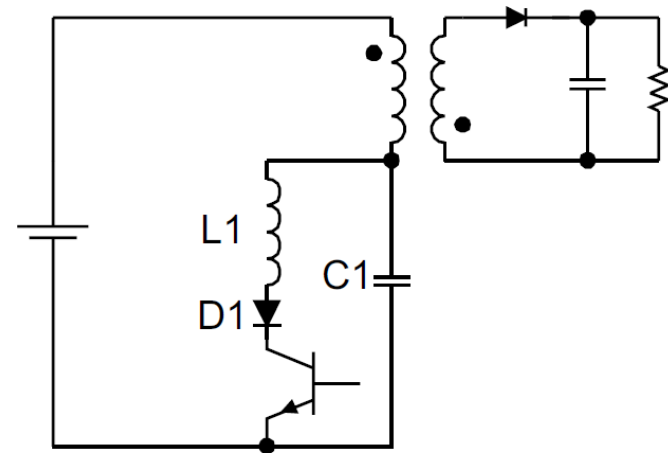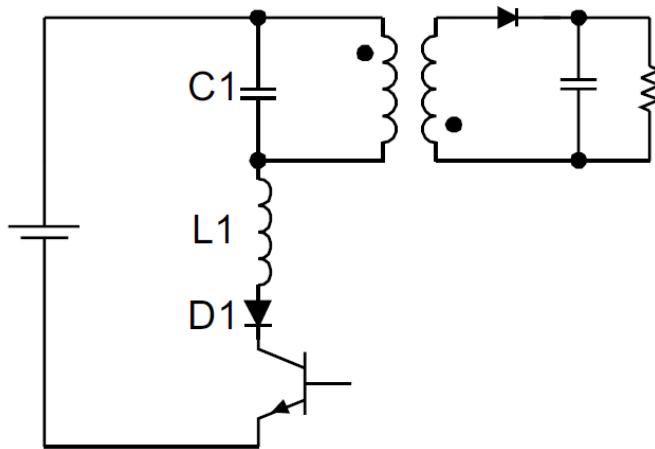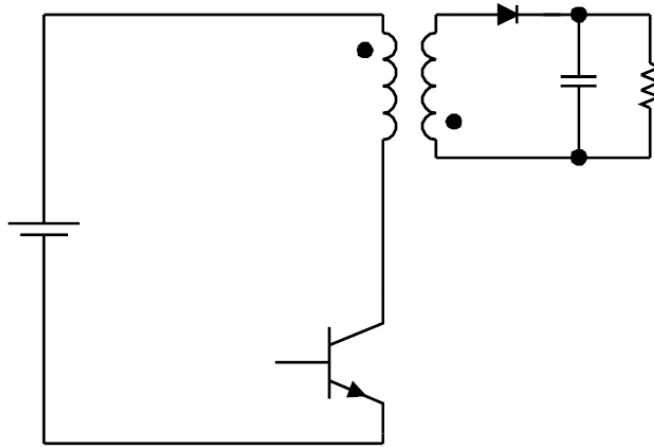





Forward as QR ZCV

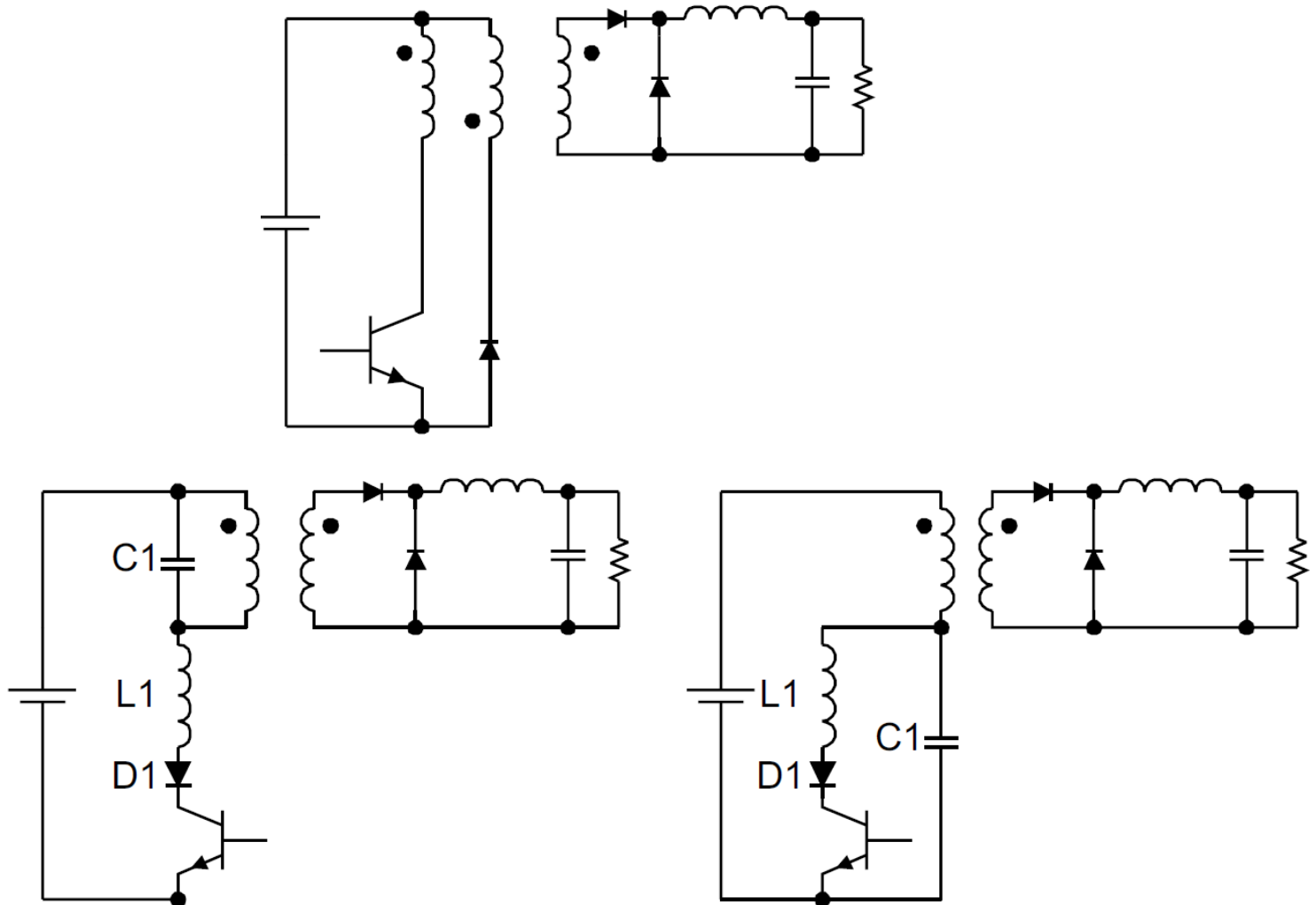





Buck/Boost QR Zero Voltage Switching

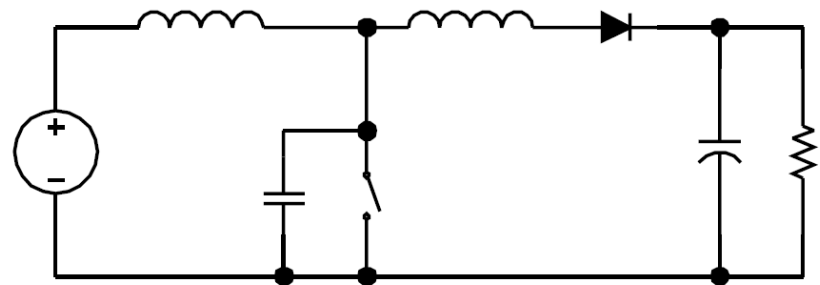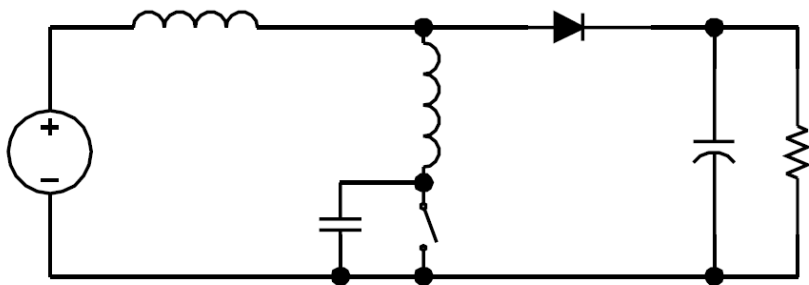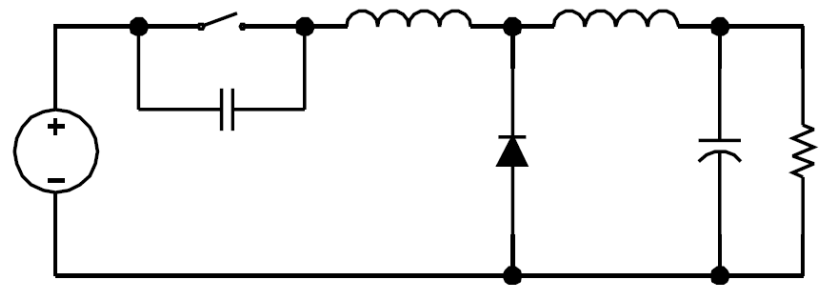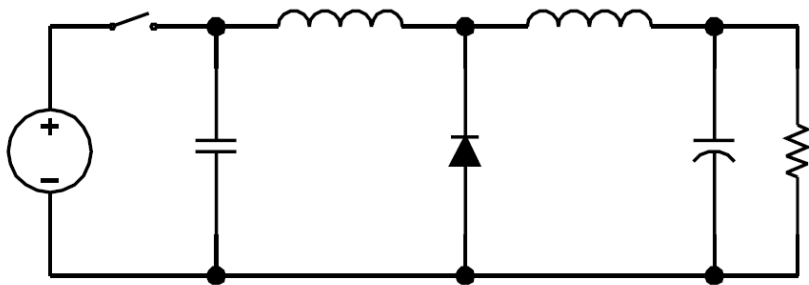


B-B Ćuk QR ZVS

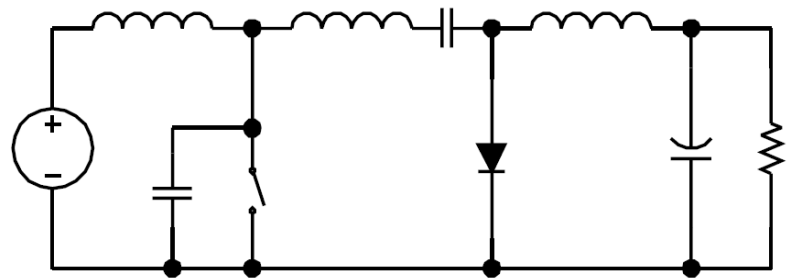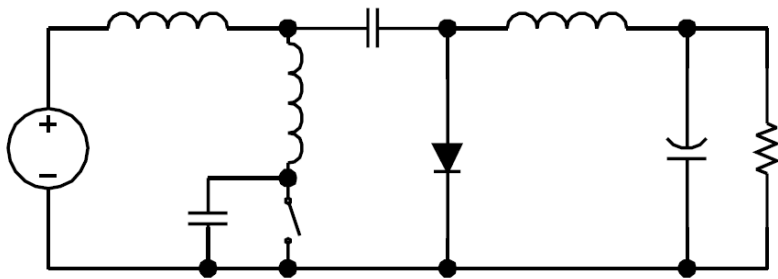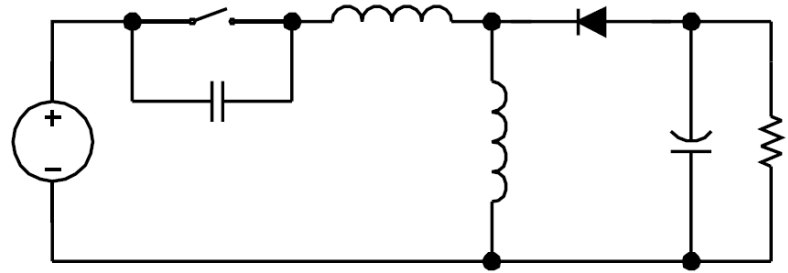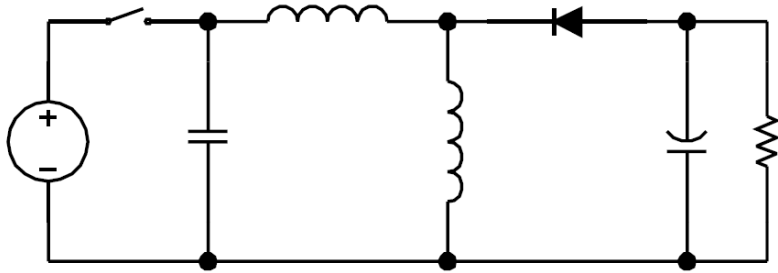







Flyback SEPIC QR ZVS

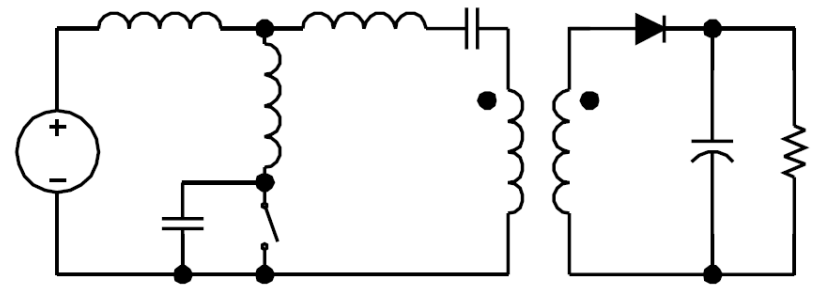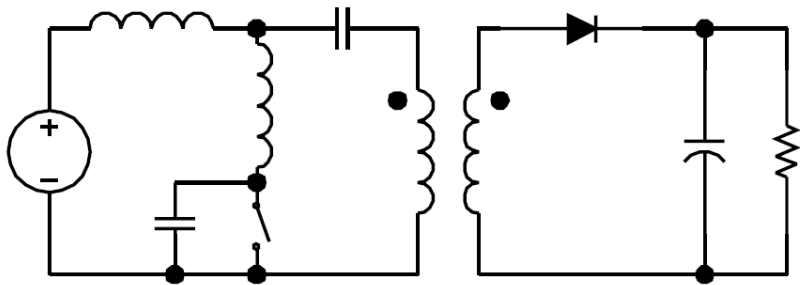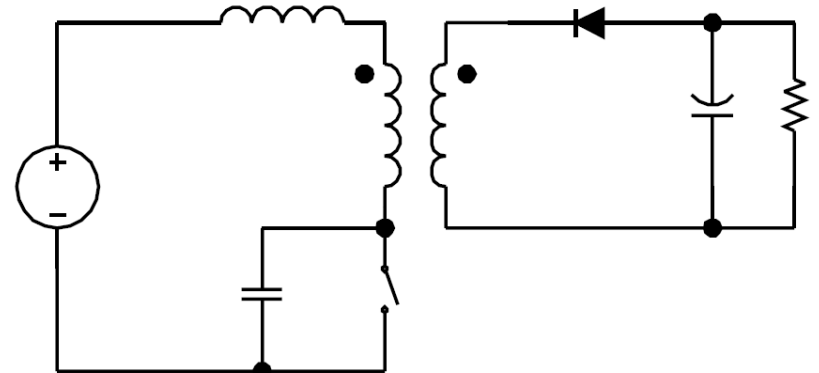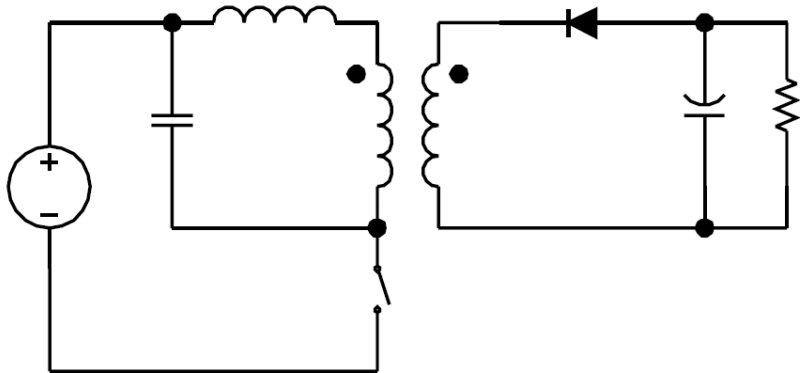

Resonant DC-DC converter

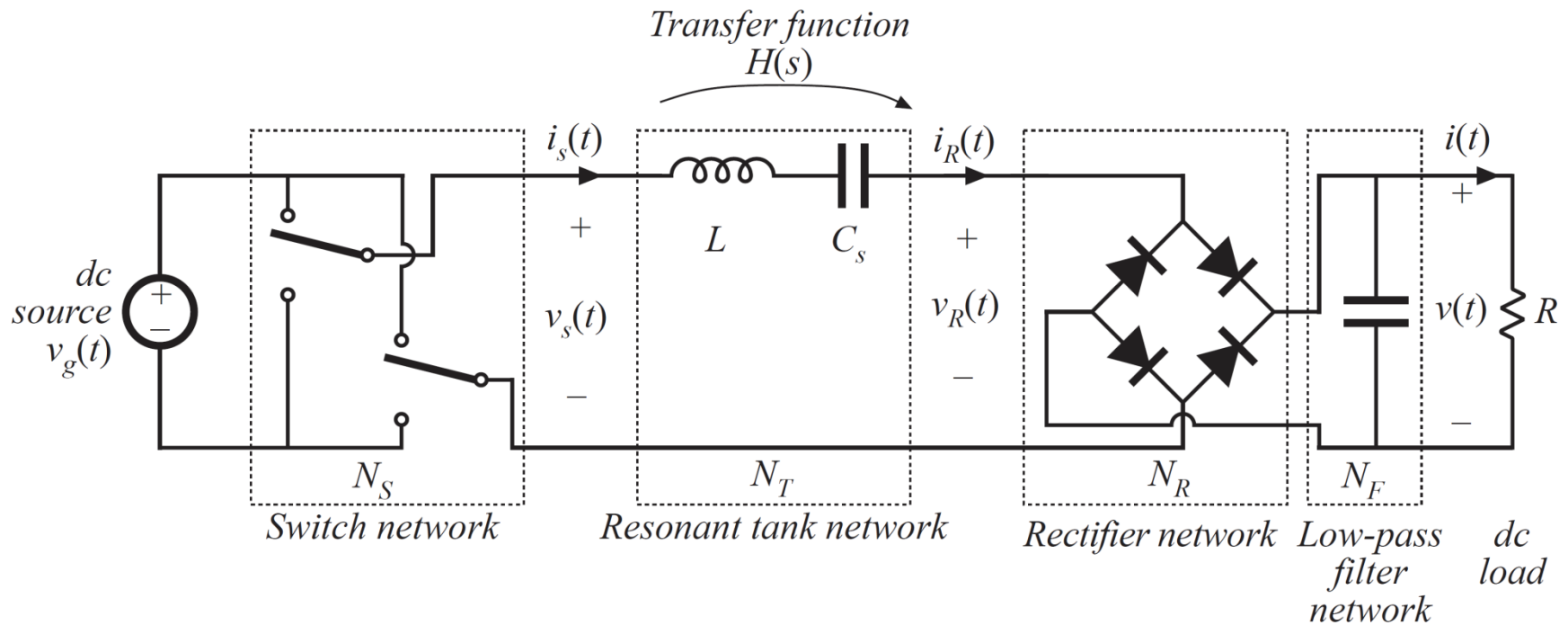


Tank network

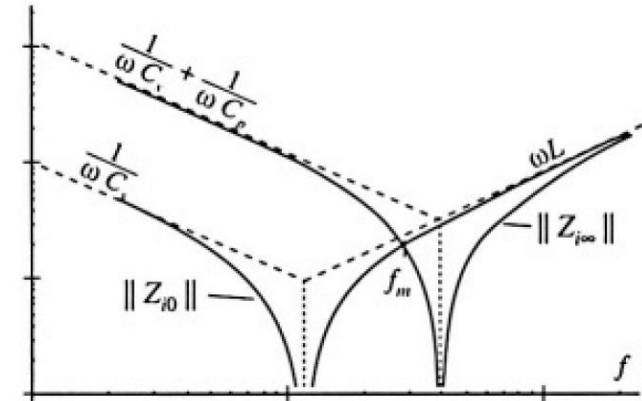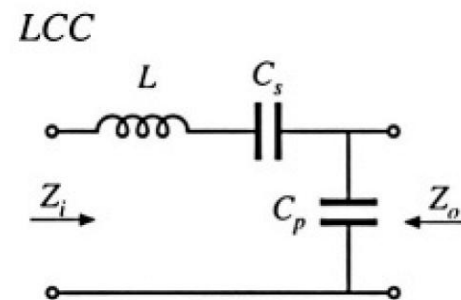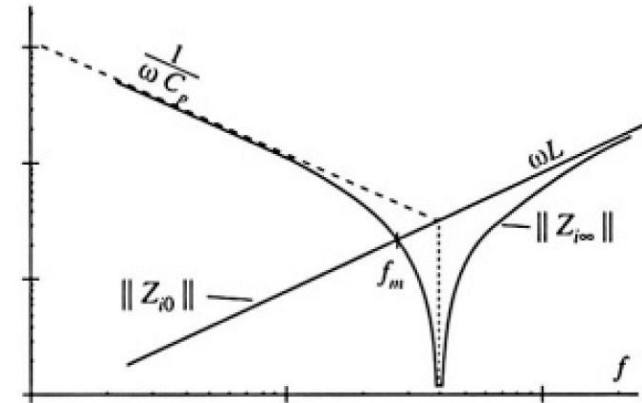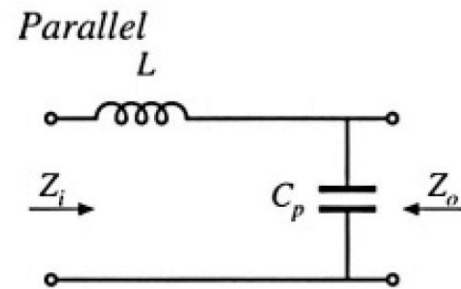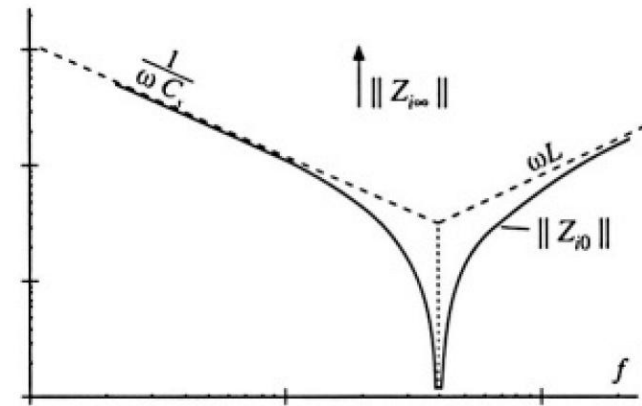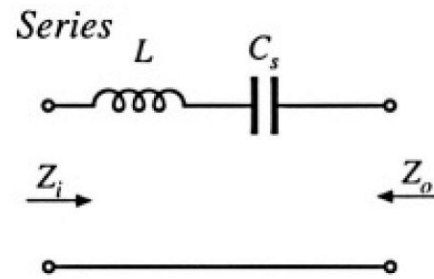


Switch networks


(a)

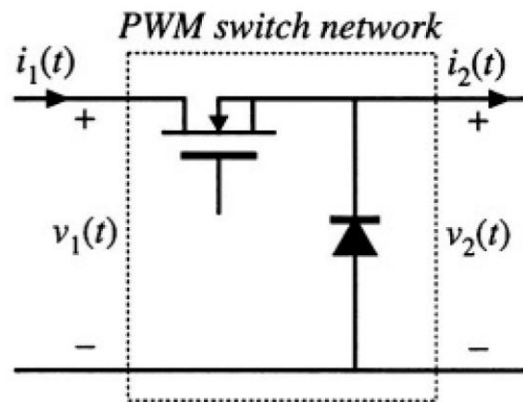


(b)

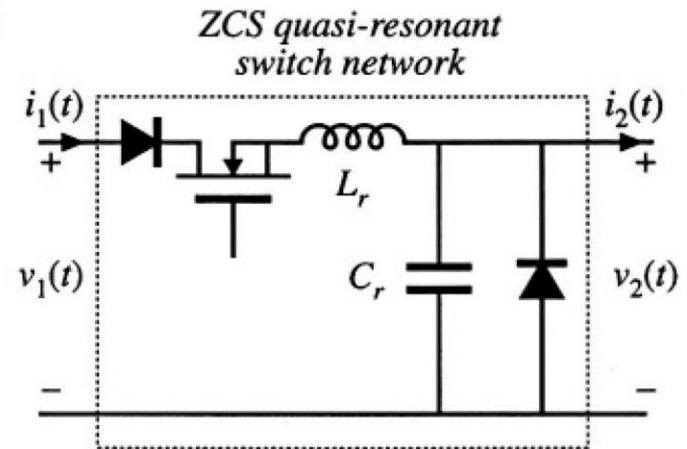





(c)

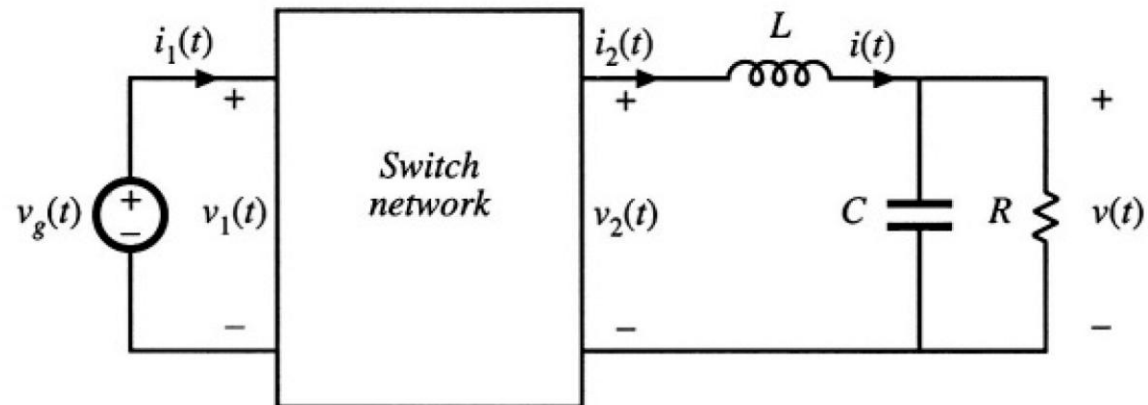



Series Resonant conv.

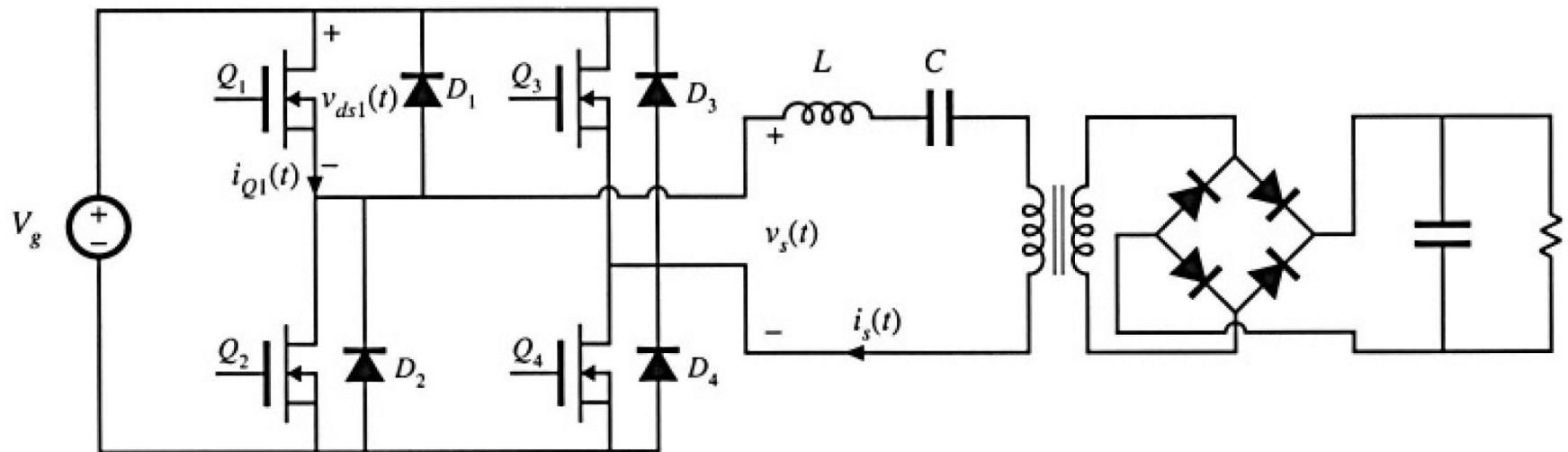

Resonant series operation

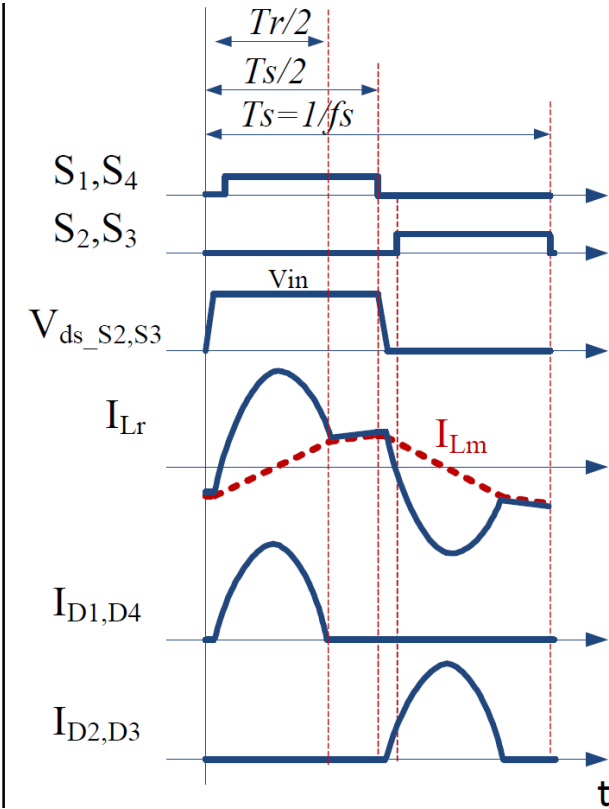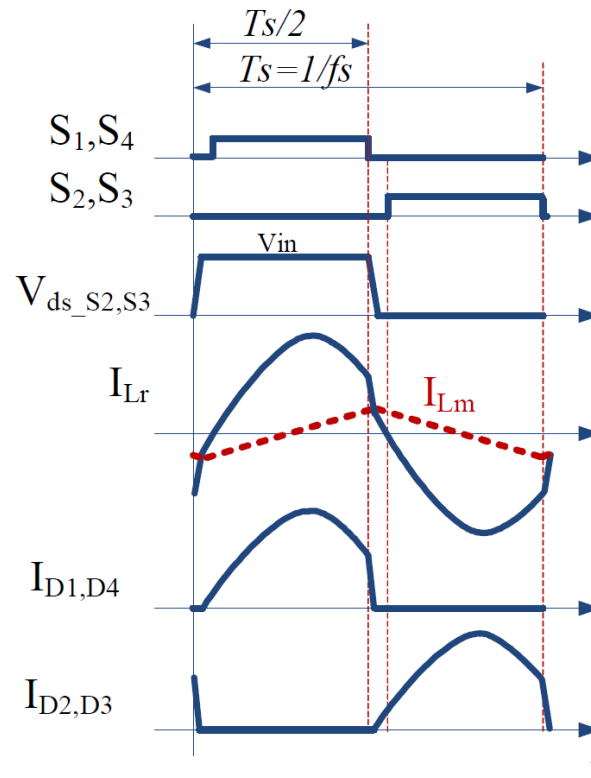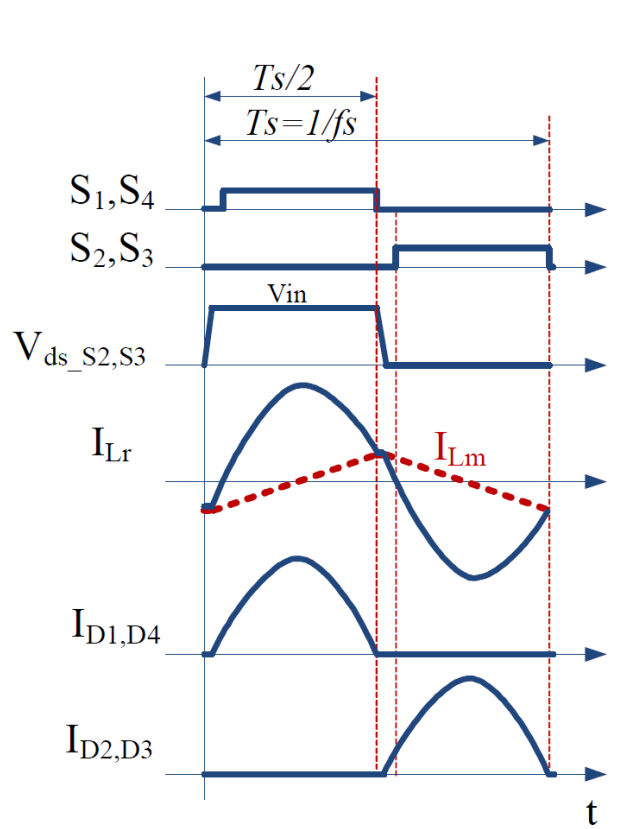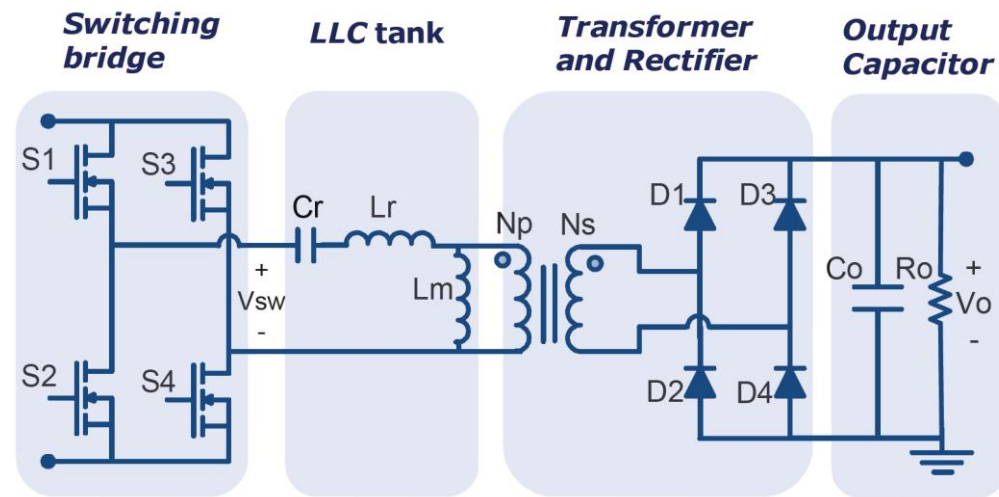


Resonant series region of oper.

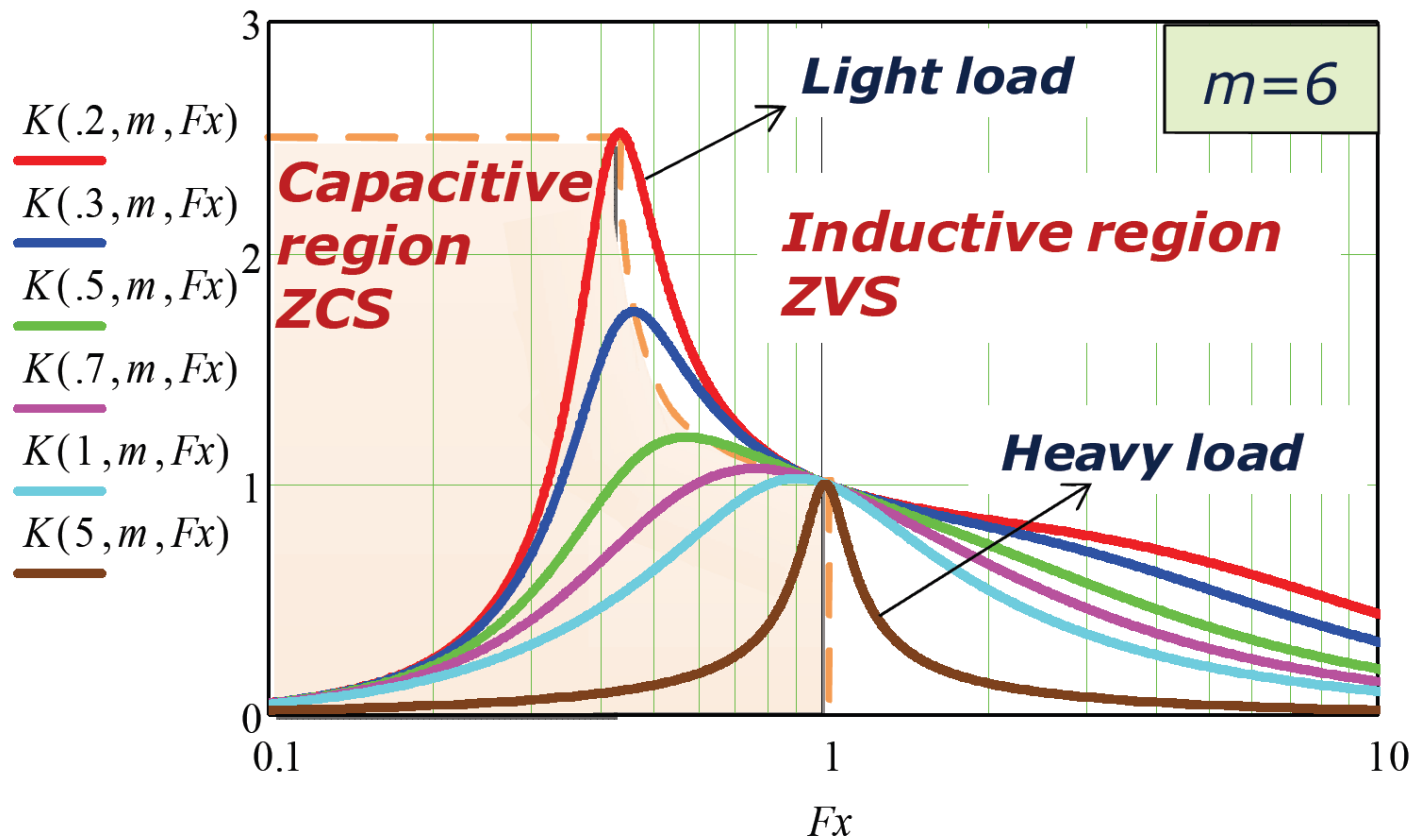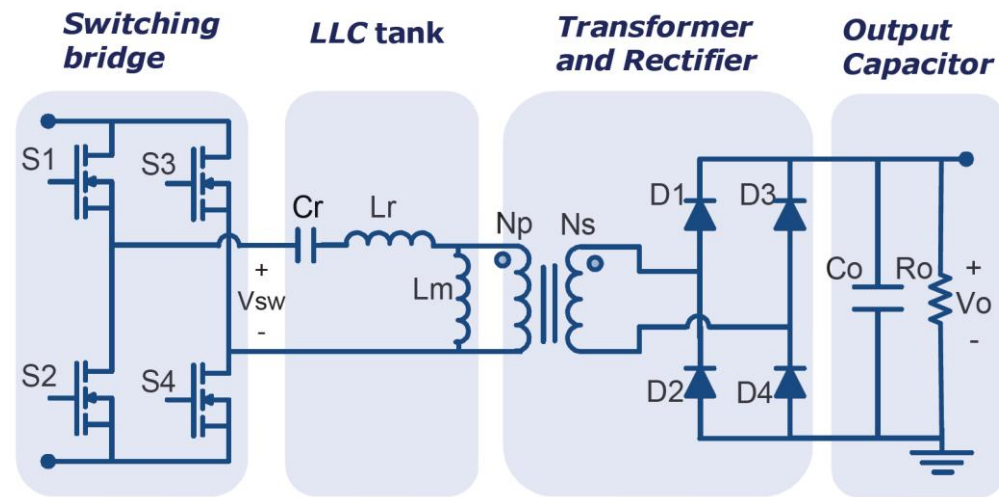

$$m = \frac{L_r + L_m}{L_r}$$

Half-bridge LCC ballast

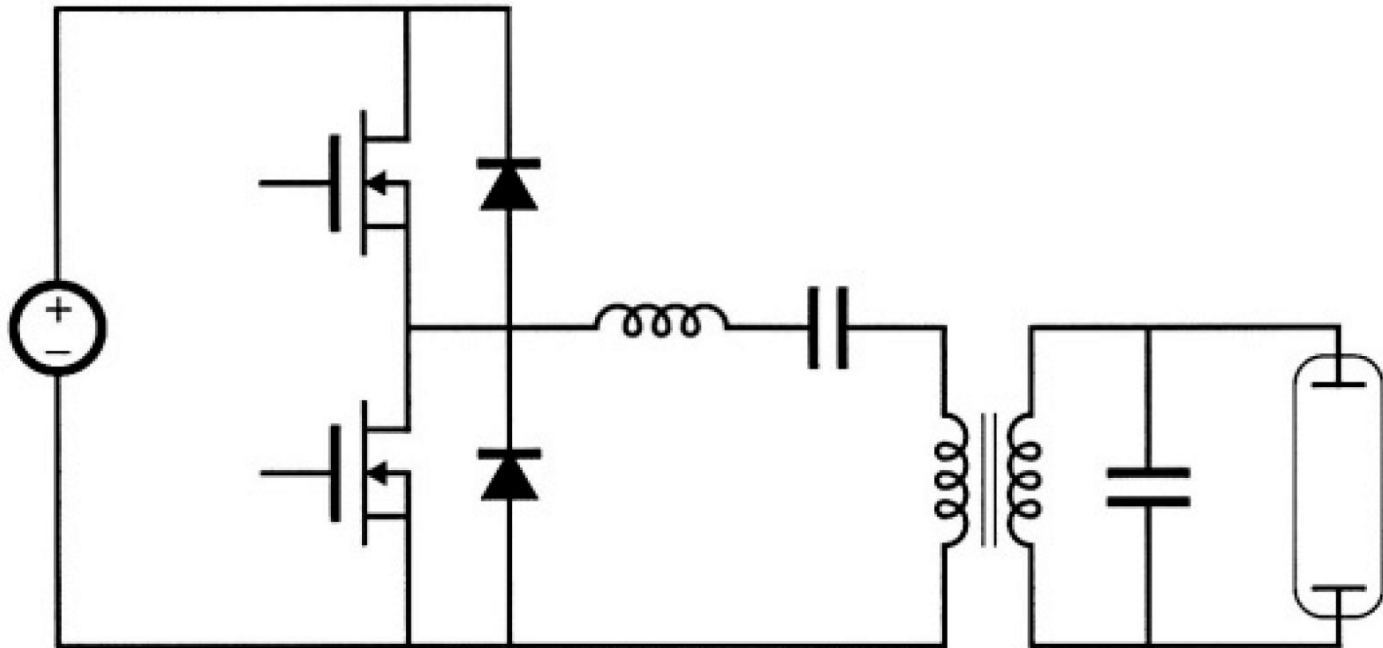

Homework

