

Energoelektronika

9. Switching DC Power Supplies



Plan

Power supplies

One of the most important applications of power electronics


- ▶ Linear power supplies
- ▶ Switching power supplies
- ▶ Electrical isolation
- ▶ Control of switched power supplies
- ▶ Power supply protection
- ▶ Electrical isolation and feedback loop

Linear Power Supplies

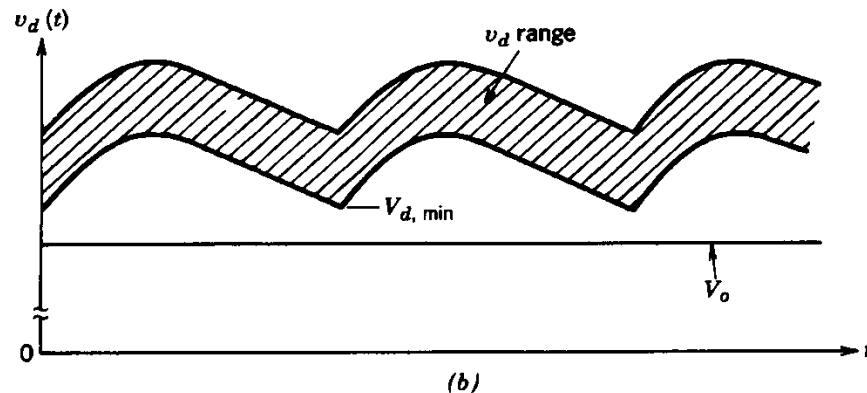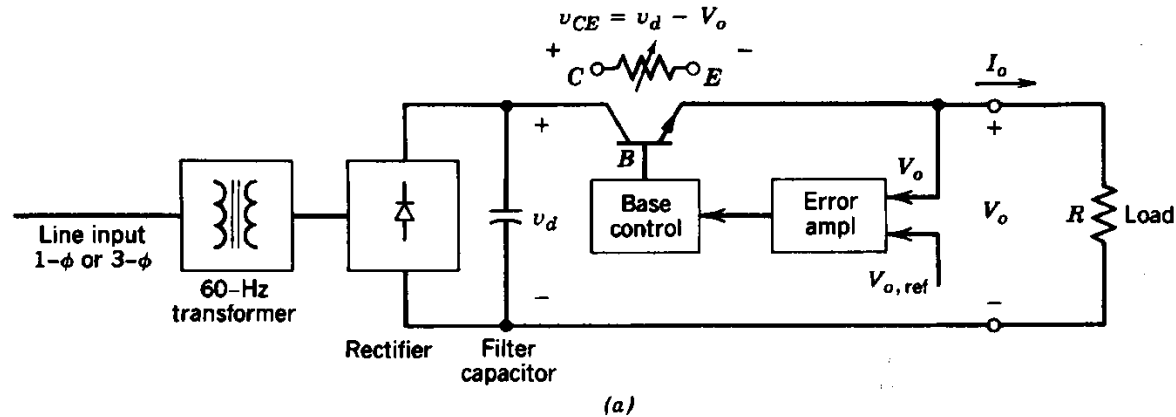

- Very poor efficiency and large weight and size


Switching DC Power Supply: Block Diagram

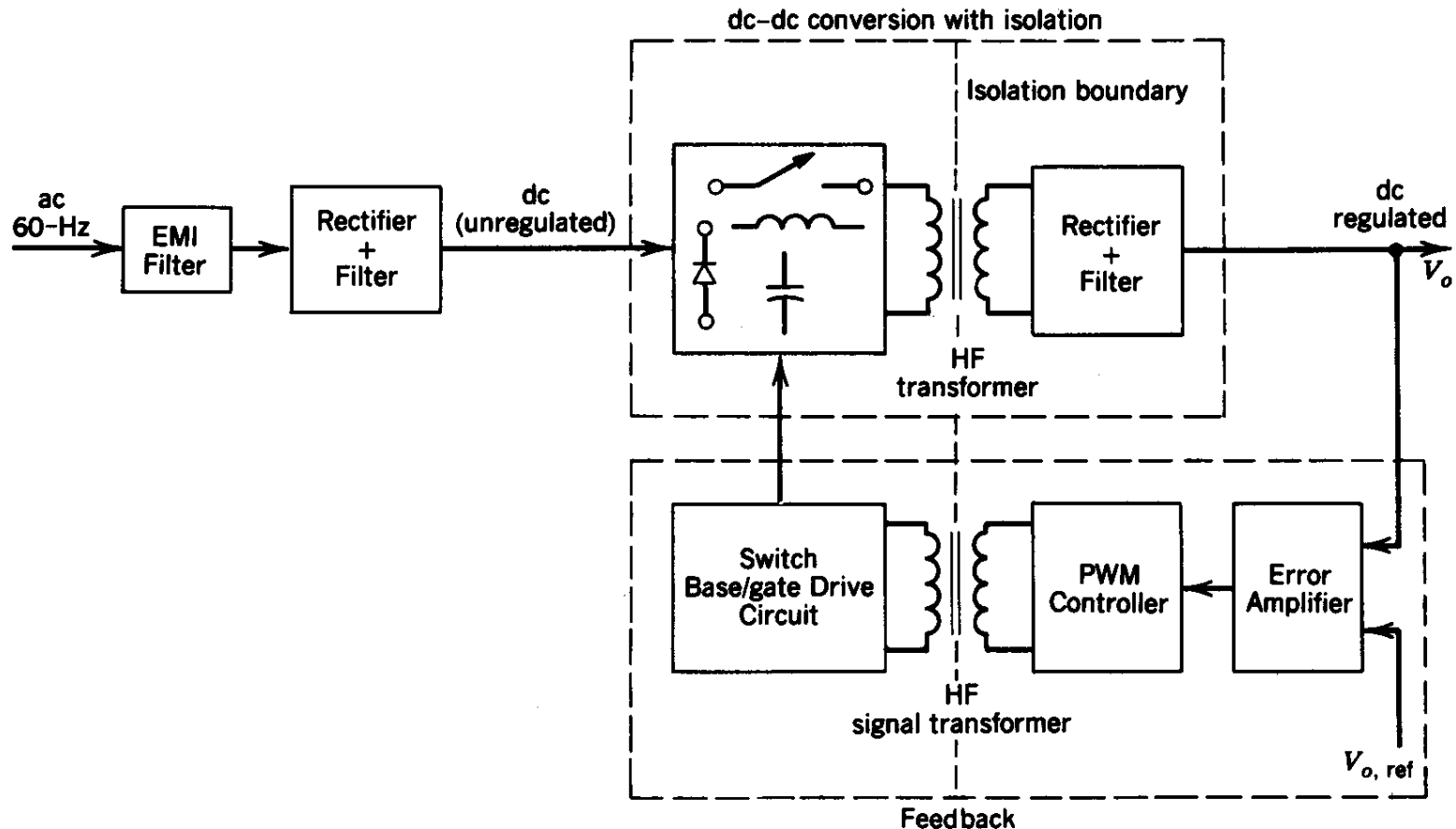

- High efficiency and small weight and size




Switching DC Power Supply

– Multiple Outputs

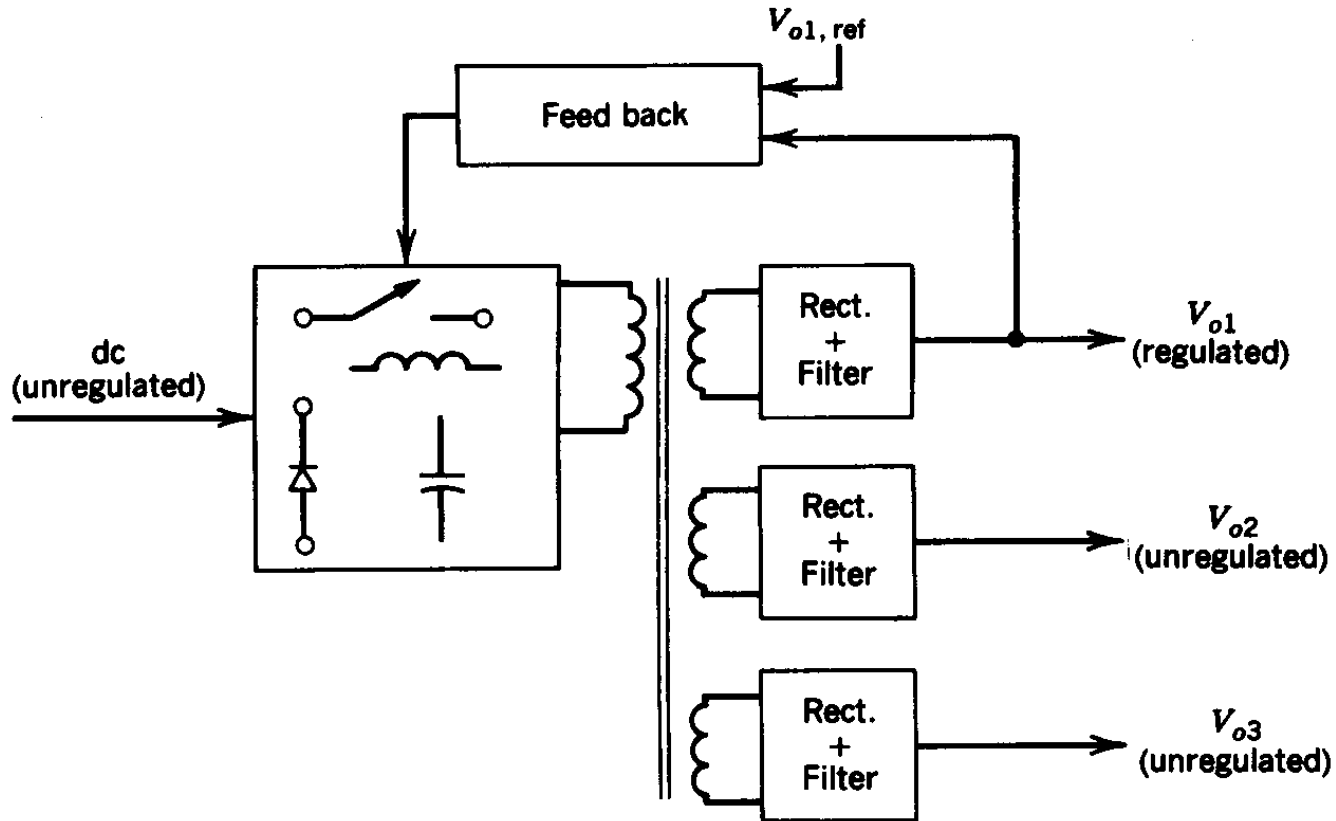



- ▶ In most applications, several dc voltages are required, possibly electrically isolated from each other

Transformer Analysis

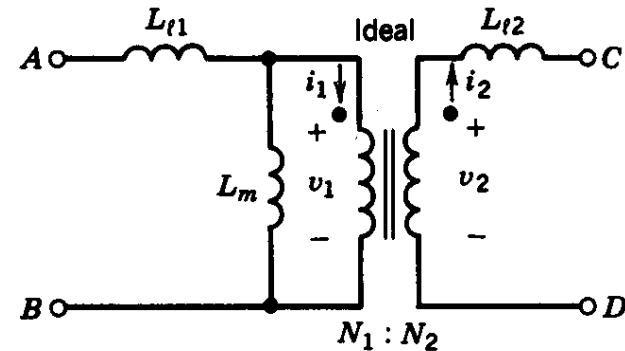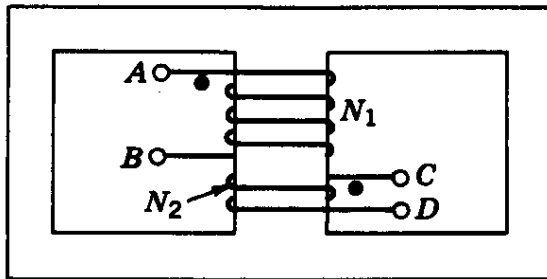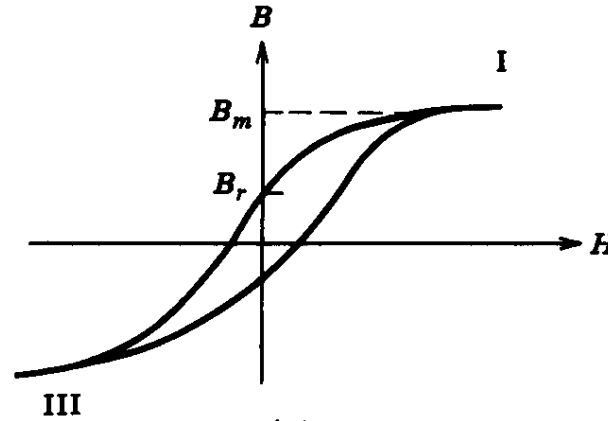



- ▶ Needed to discuss high-frequency isolated supplies

PWM to Regulate Output

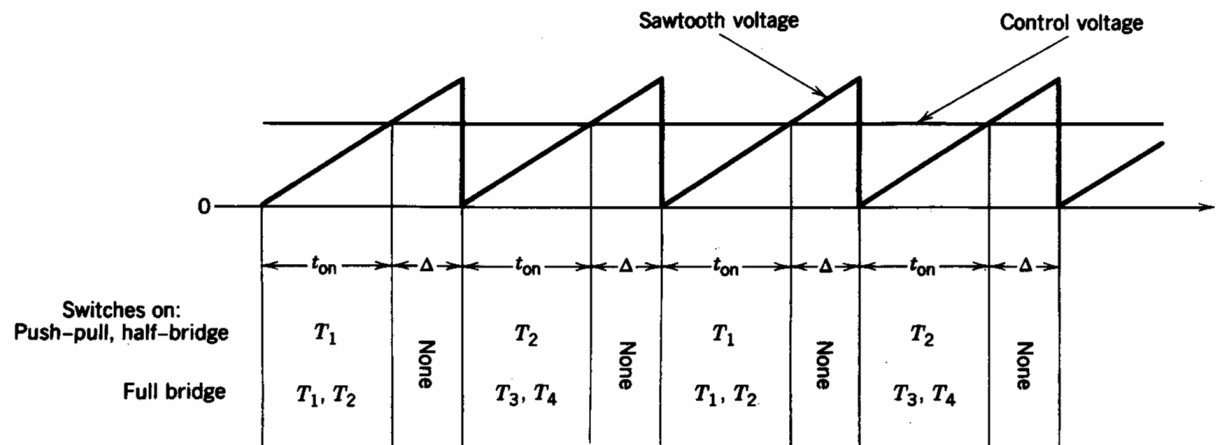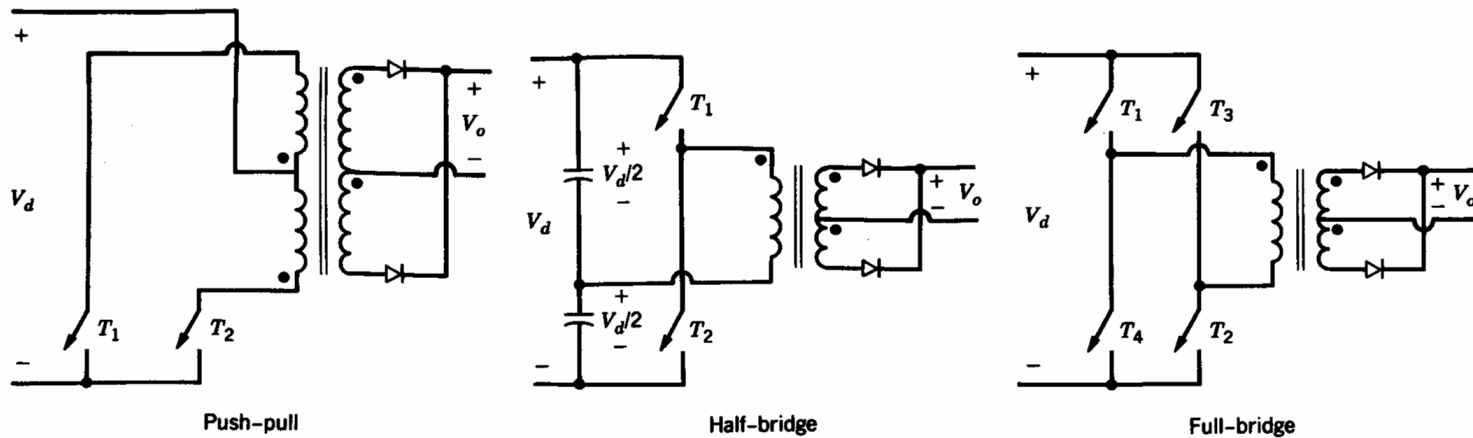

- Basic principle is the same as discussed in DC-AC Converter lecture

Flyback Converter

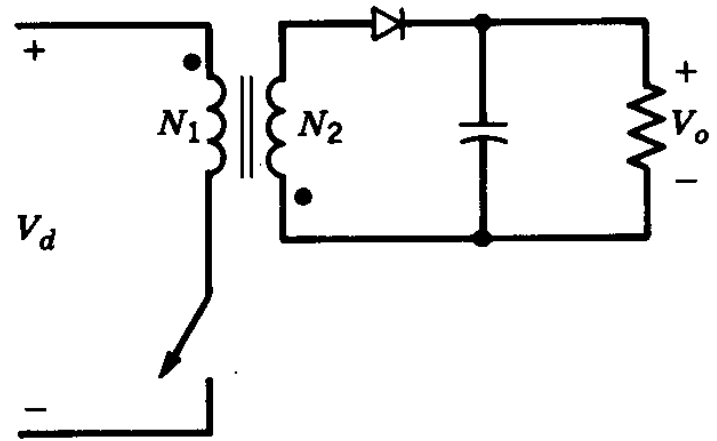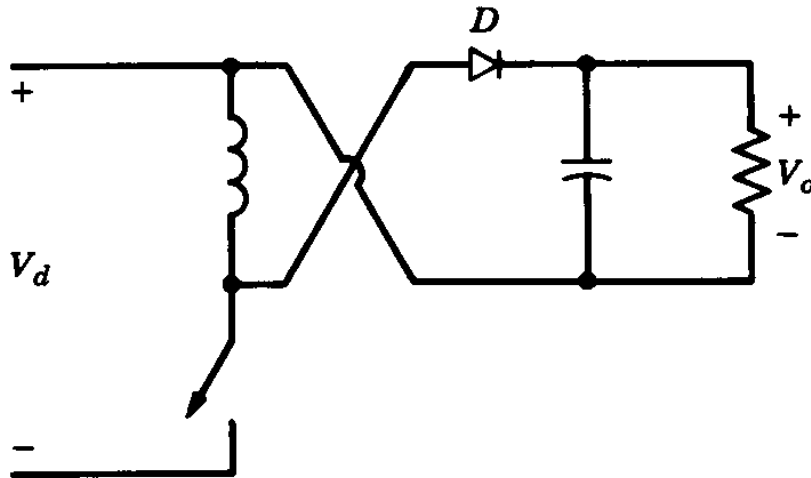

- ▶ Derived from buck-boost; very power at small power ($> 50\text{ W}$) power levels

Flyback Converter


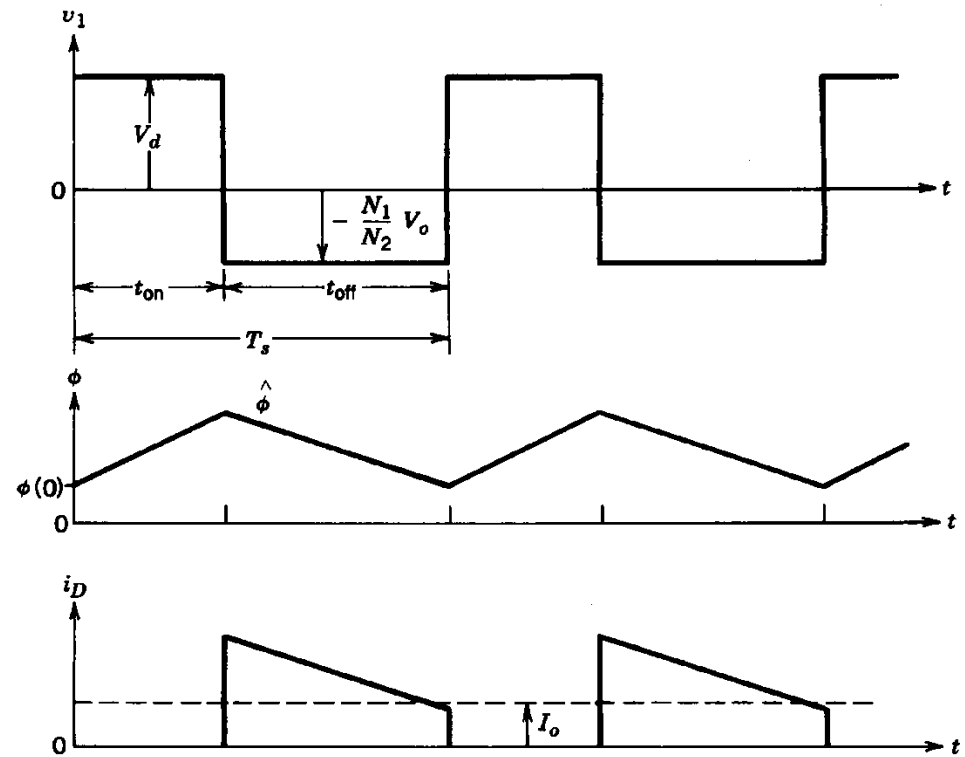
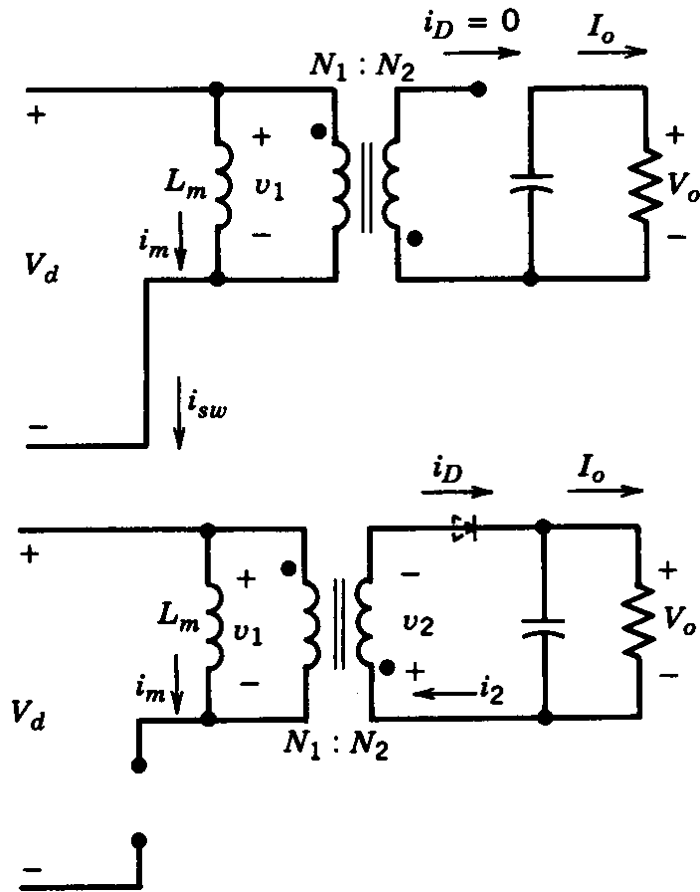
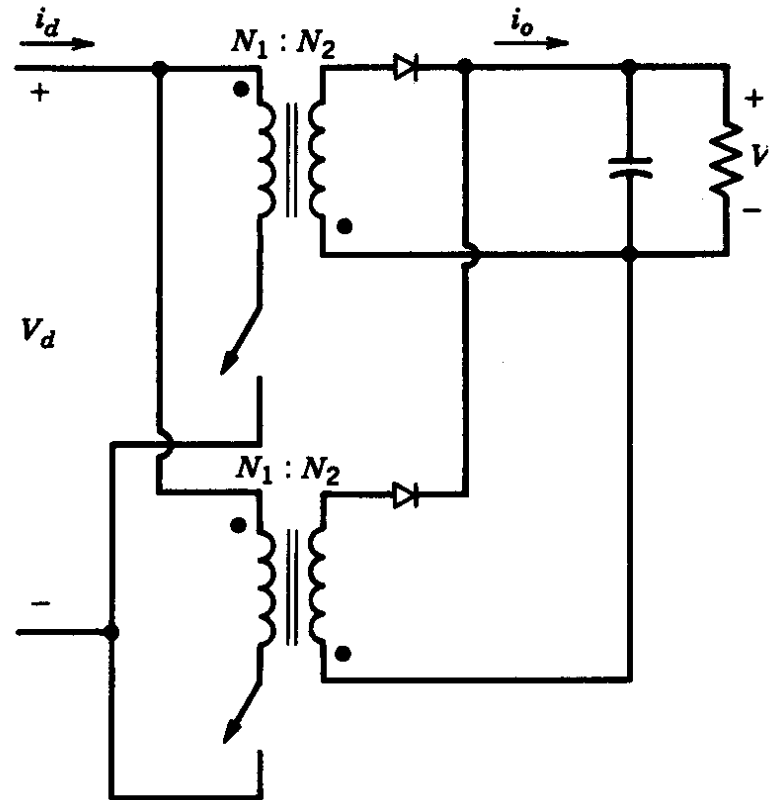


Figure 10-8 Flyback converter waveforms.


- Switch on and off states
(assuming incomplete core demagnetization)

Other Flyback Converter Topologies

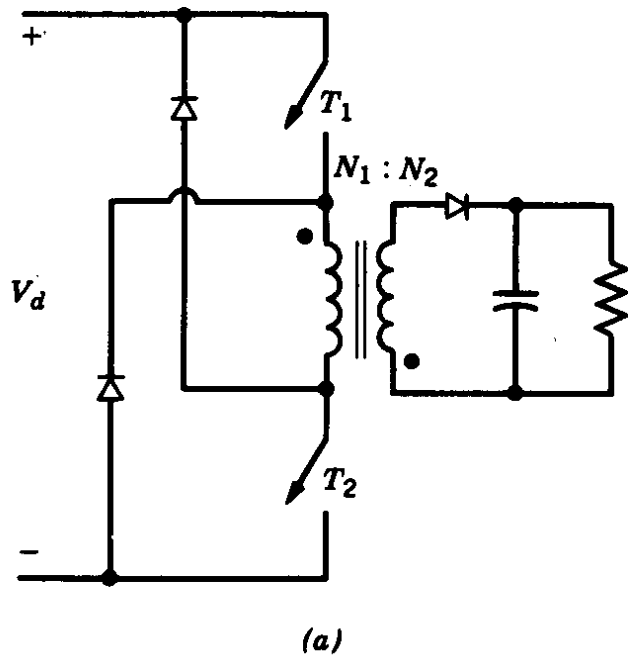

- ▶ Not commonly used



Forward Converter

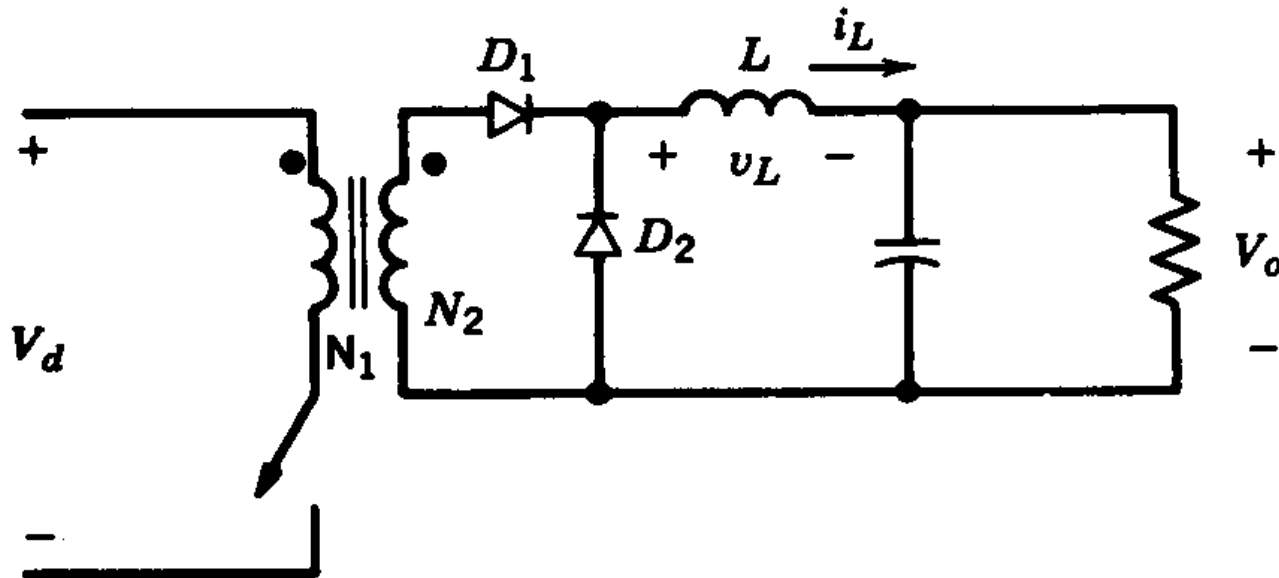



- ▶ Derived from Buck; idealized to assume that the transformer is ideal (not possible in practice)

Forward Converter

– in Practice

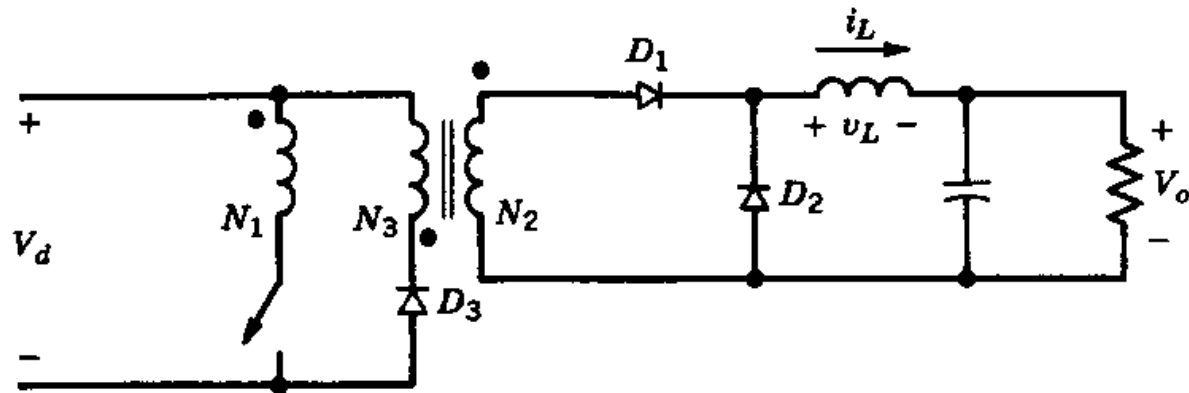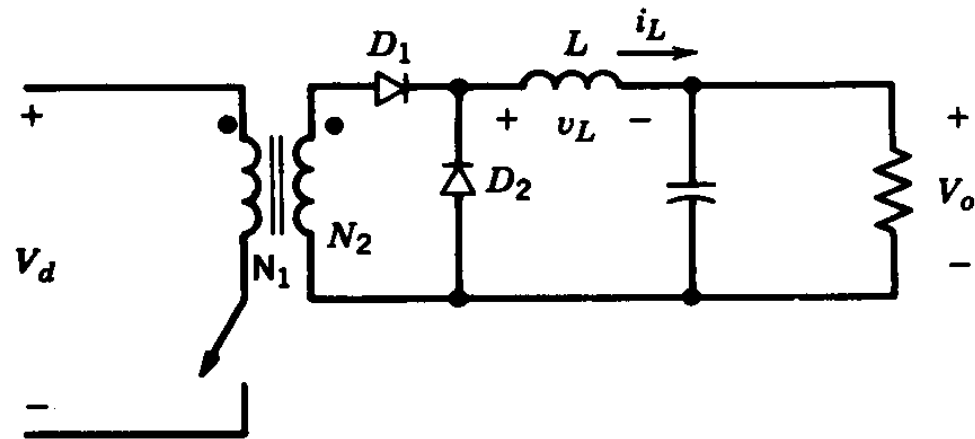



Practice Forward Converter Waveform

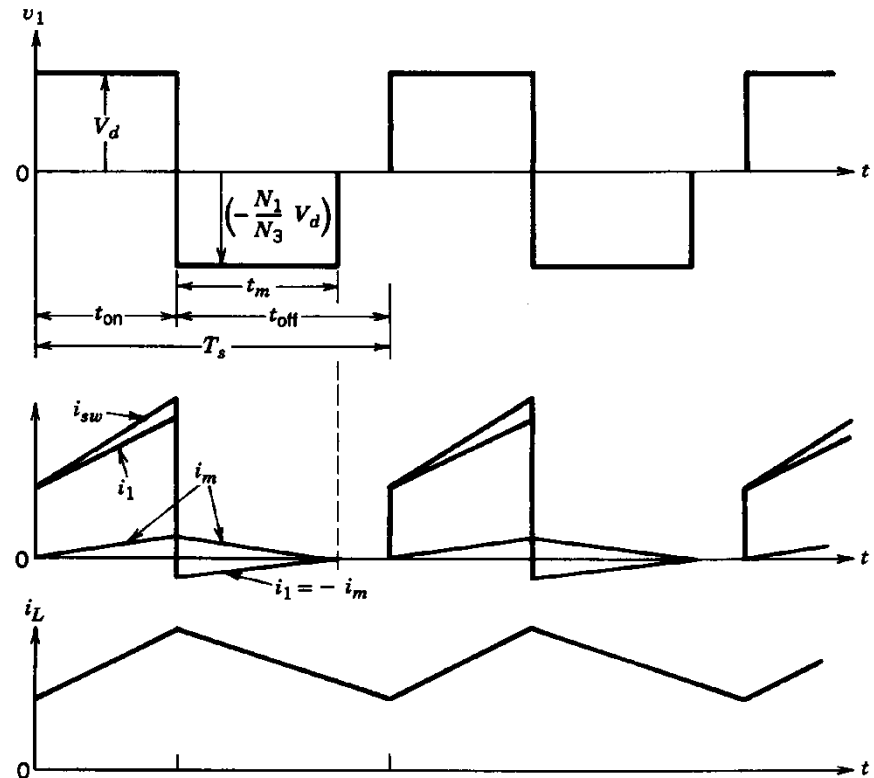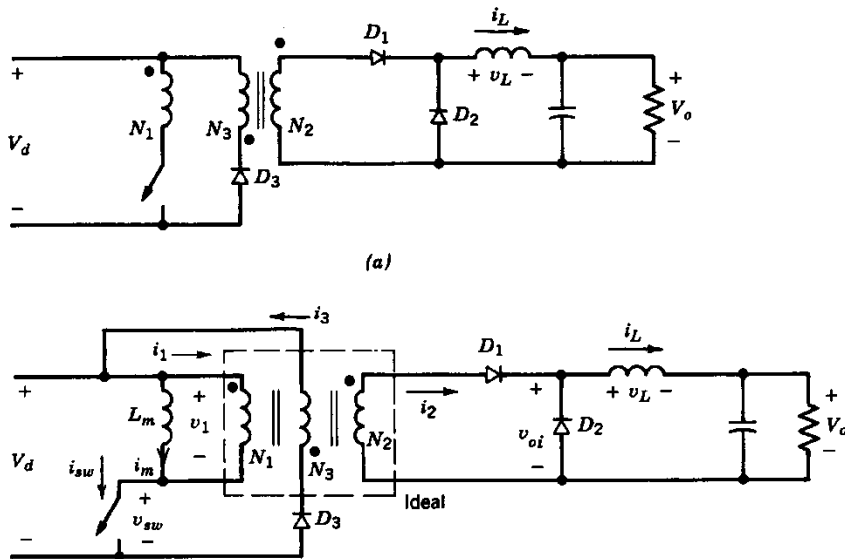

- Switching waveforms
(assuming incomplete core demagnetization)



Forward Converter

– Other Possible Topologies

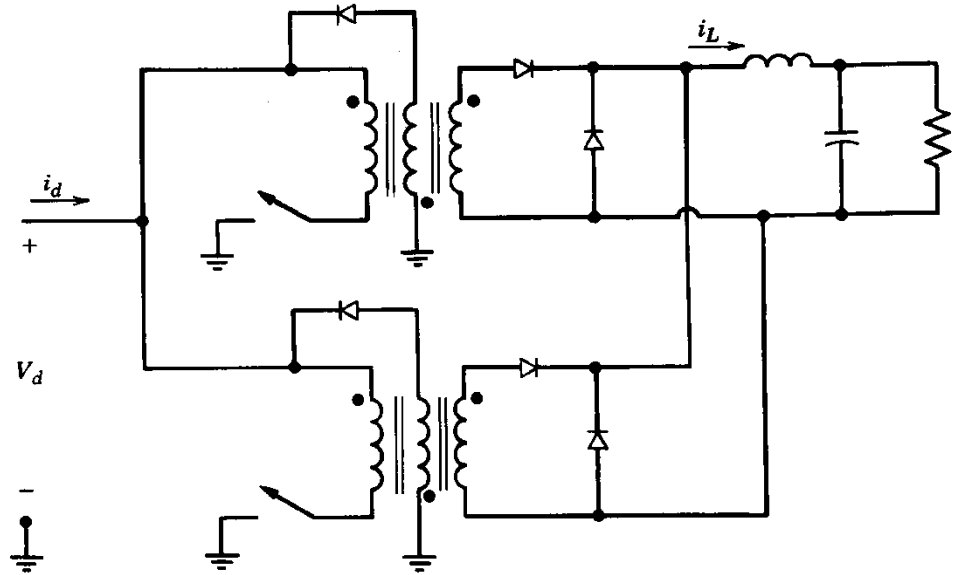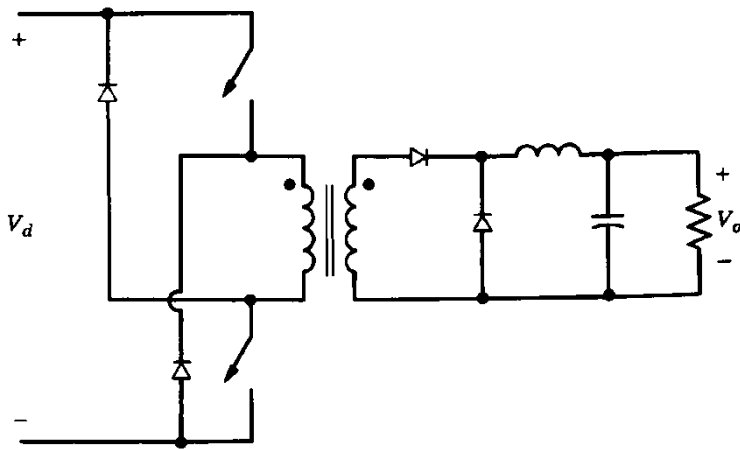



- ▶ Two-switch Forward converter is very commonly used

Push-Pull Inverter

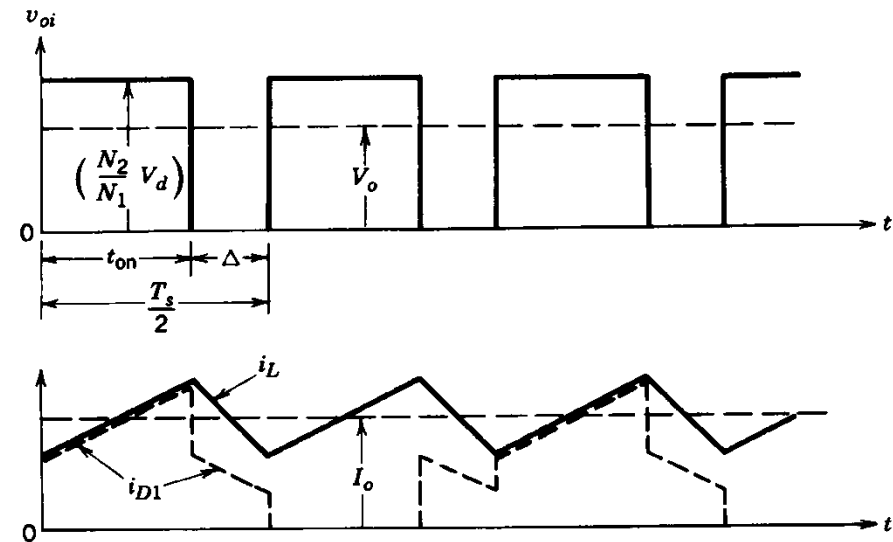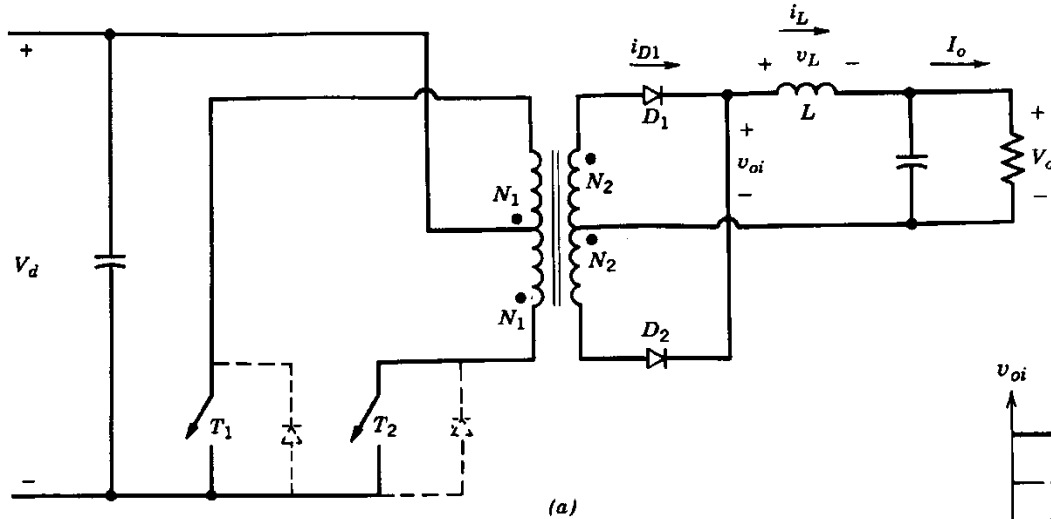


- ▶ Leakage inductances become a problem

Half-Bridge Converter

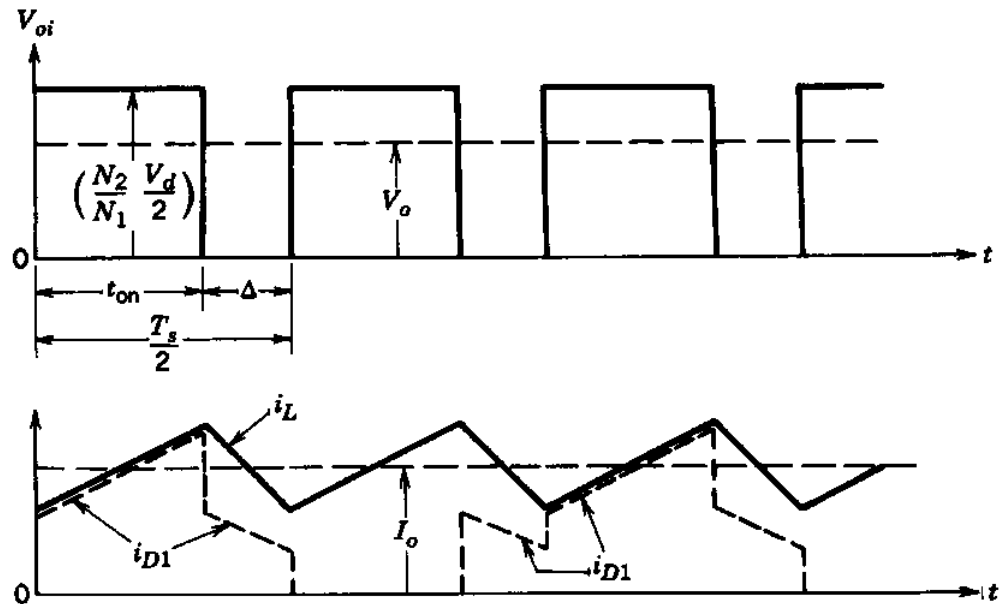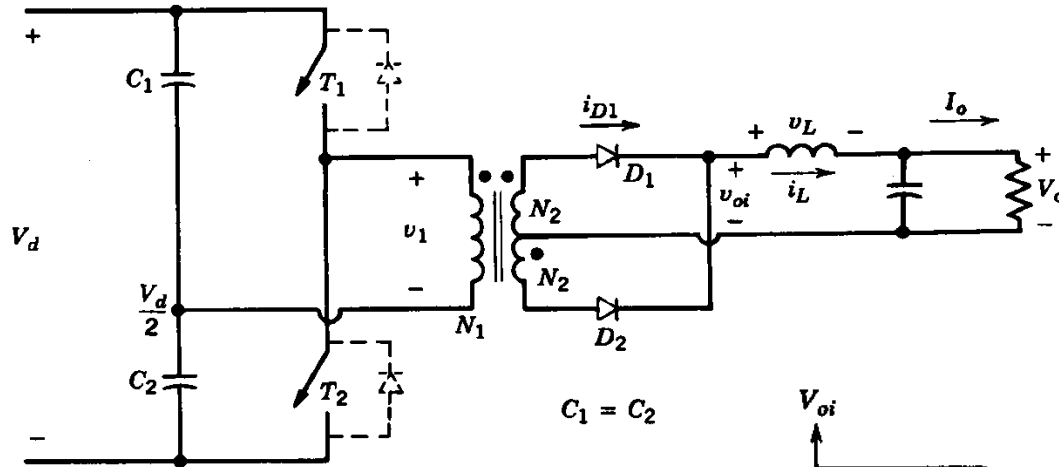


► Derived from Buck

Full-Bridge Converter

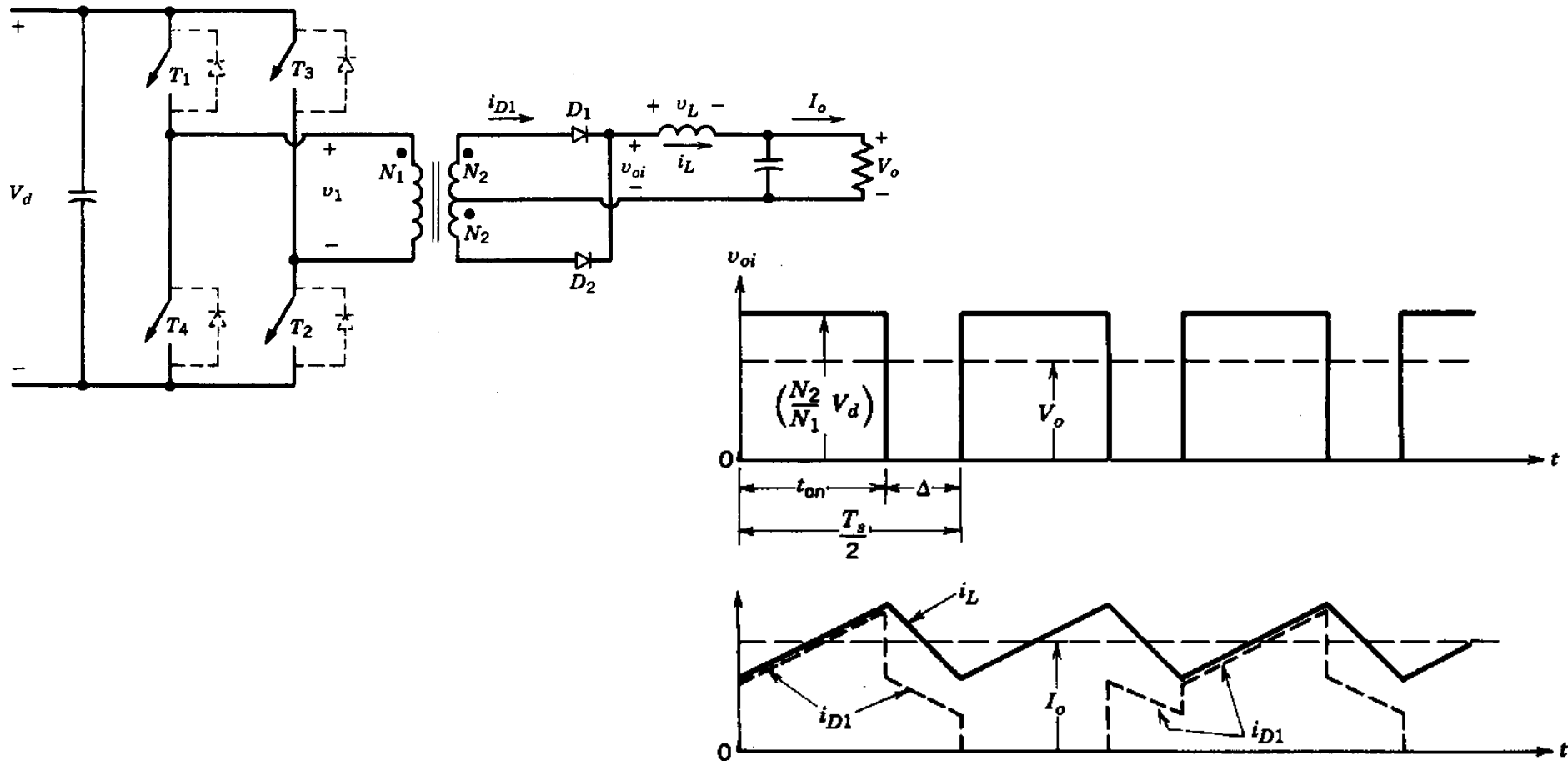



- Used at higher power levels ($> 0.5 \text{ kW}$)

Current-Source Converter

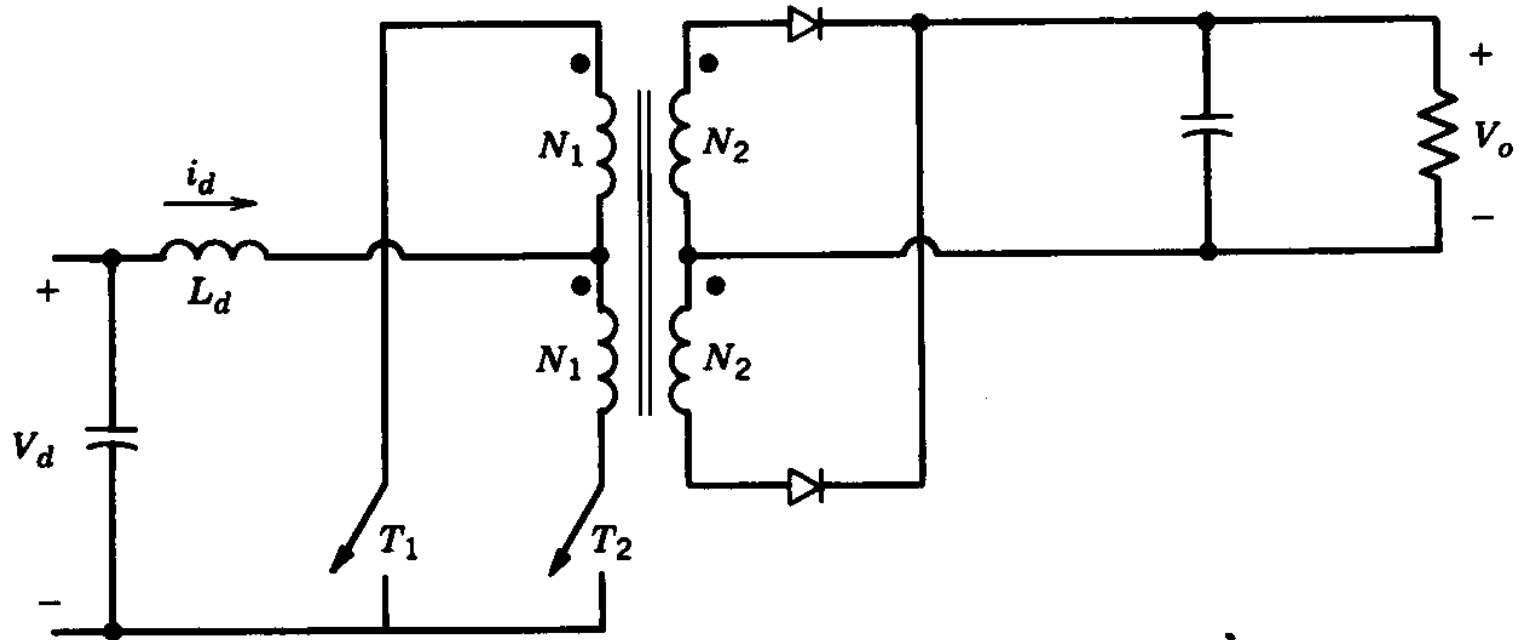



- ▶ More rugged (no shoot-through)
but both switches must not be open simultaneously

Ferrite Core Material

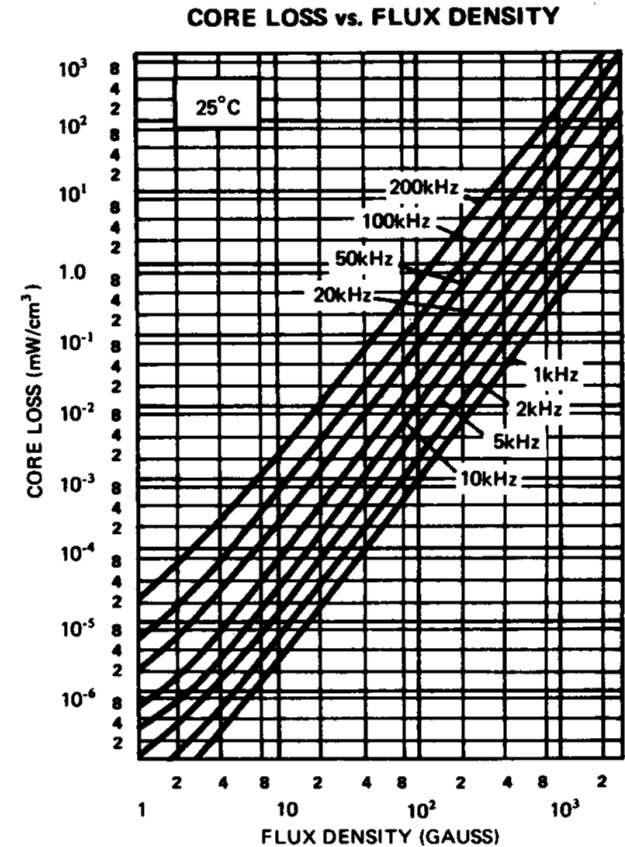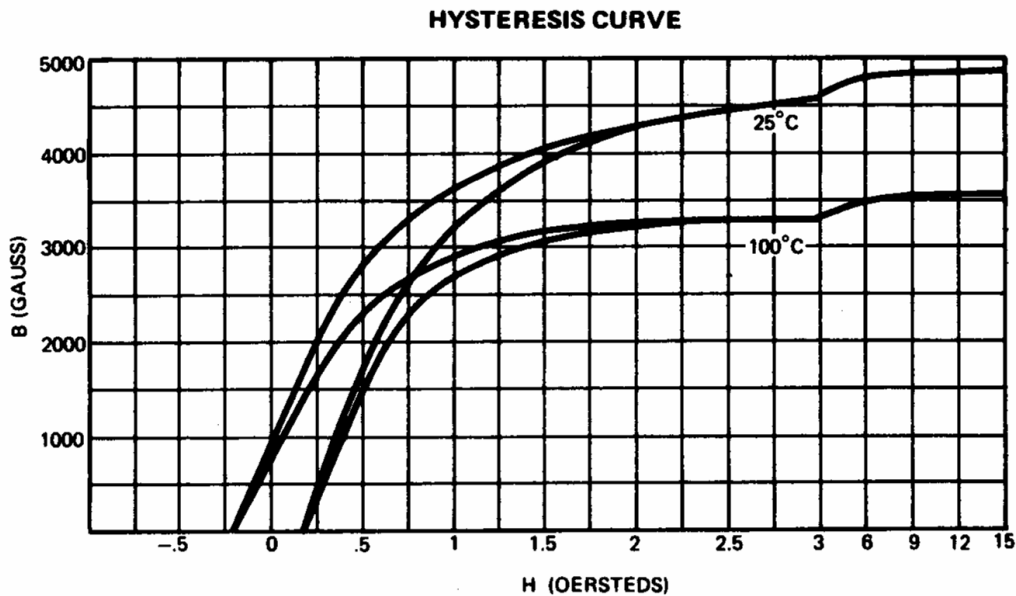



- ▶ Several materials to choose from based on applications

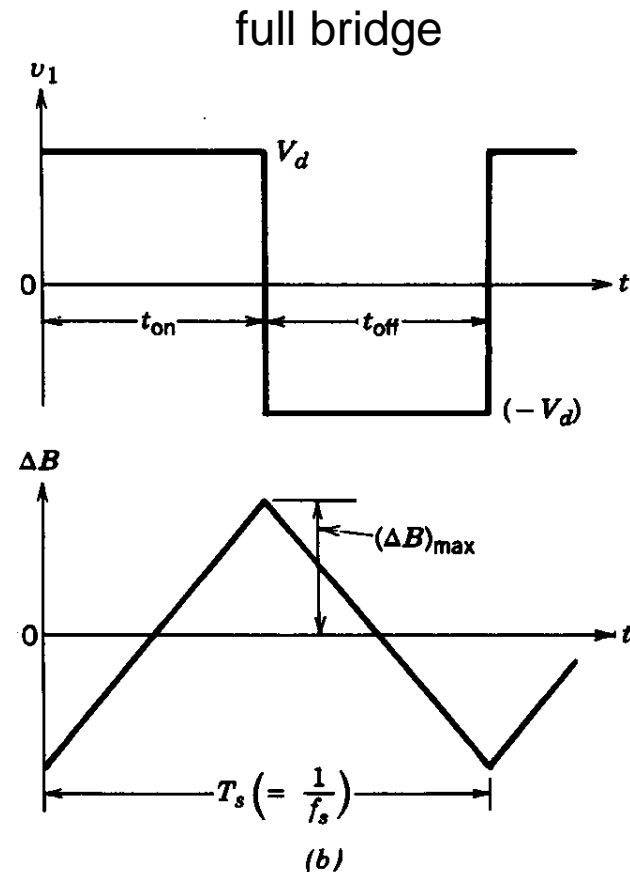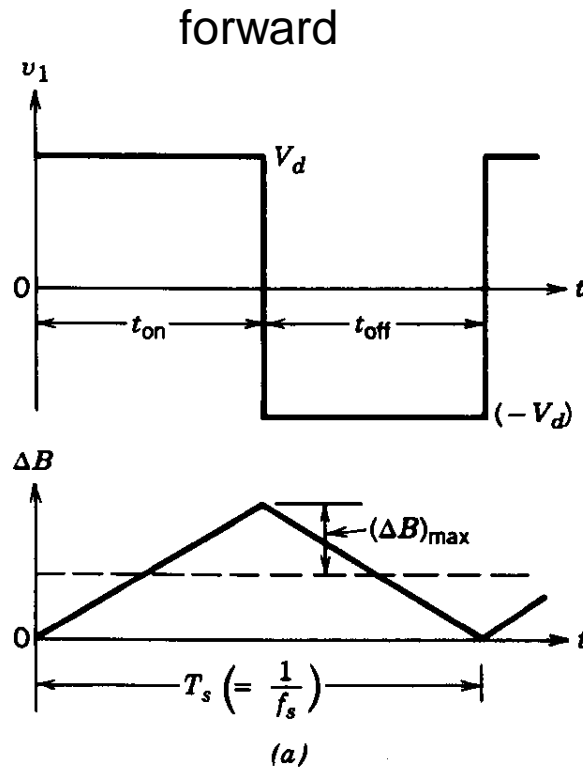Core Utilization in Various Converter Topologies



- ▶ At high switching frequencies, core losses limit excursion of flux density


Control to Regulate Voltage Output

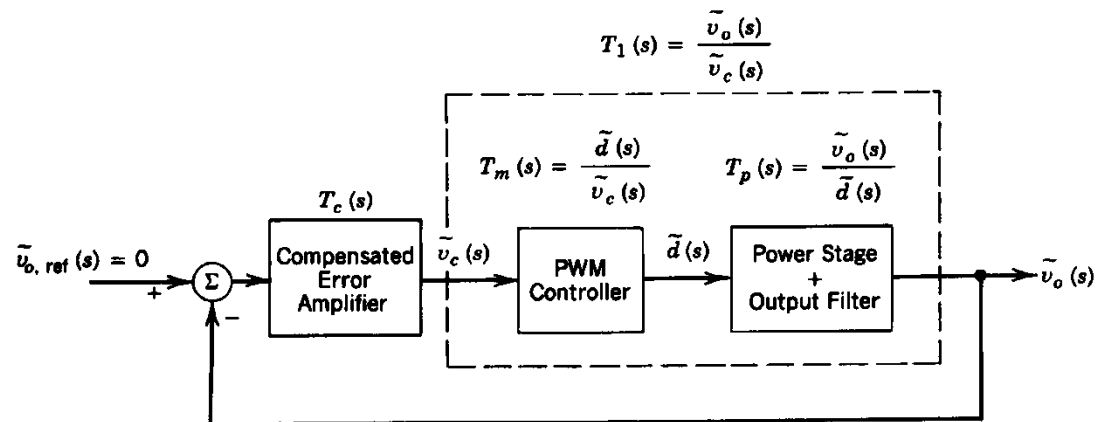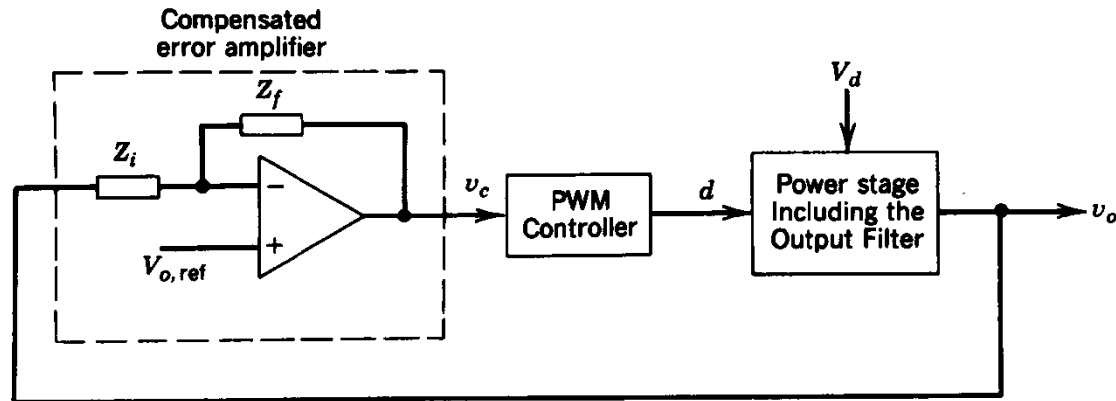



- ▶ Linearized representation of the feedback control system

Forward Converter

– An Example

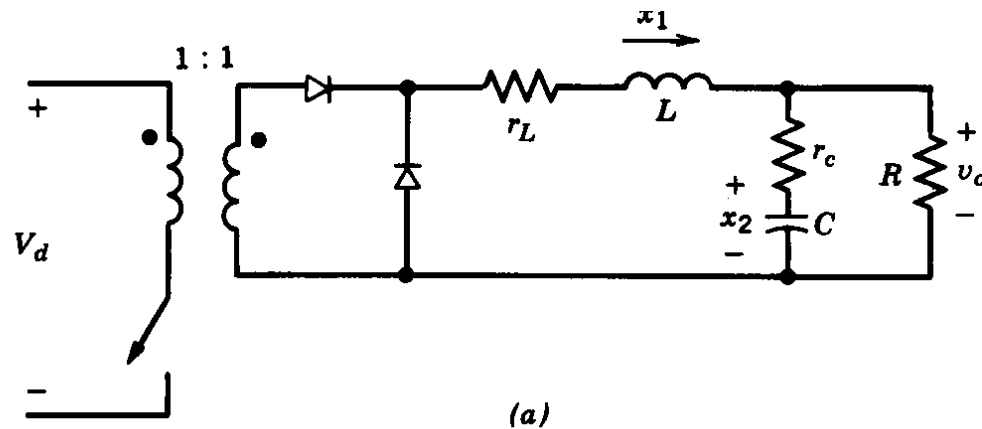

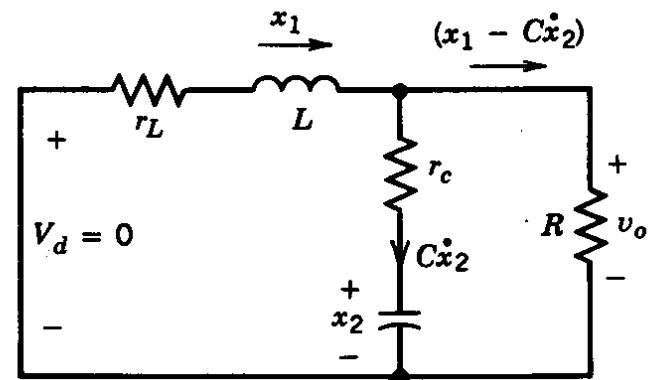
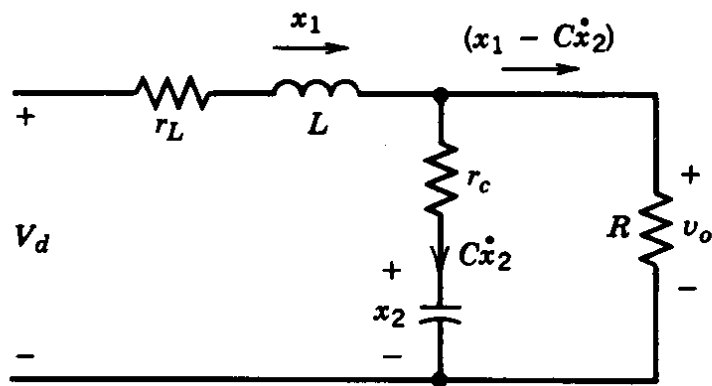
$$\begin{aligned} V_d &= 8 \text{ V} \\ V_o &= 5 \text{ V} \\ r_L &= 20 \text{ m}\Omega \\ L &= 5 \text{ }\mu\text{H} \\ r_c &= 10 \text{ m}\Omega \\ C &= 2,000 \text{ }\mu\text{F} \\ R &= 200 \text{ m}\Omega \\ f_s &= 200 \text{ kHz} \end{aligned}$$





- The switch and the diode are assumed to be ideal

Transfer Function Plots




► Forward converter

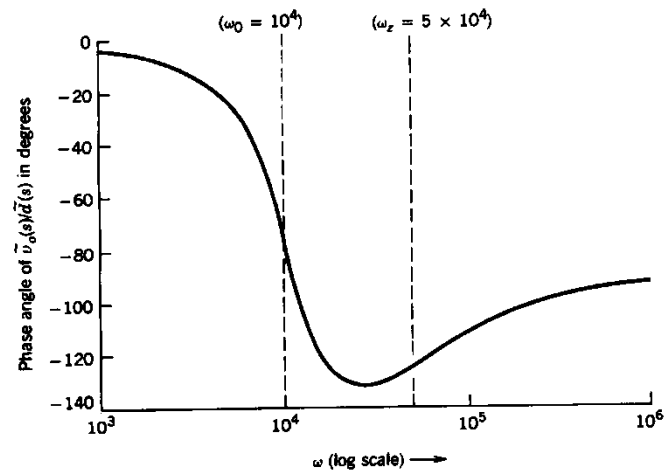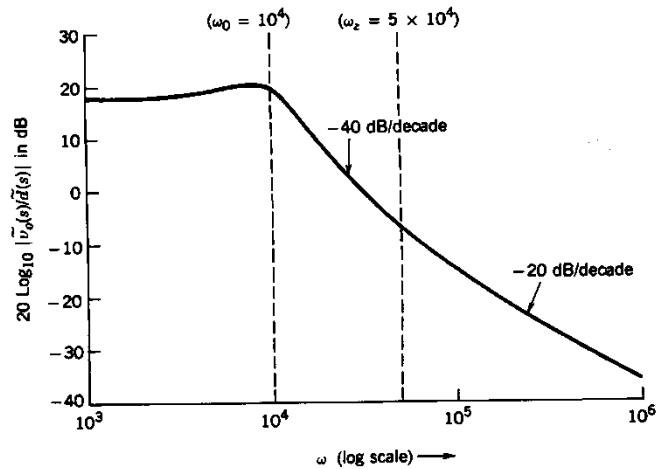

► Flyback converter

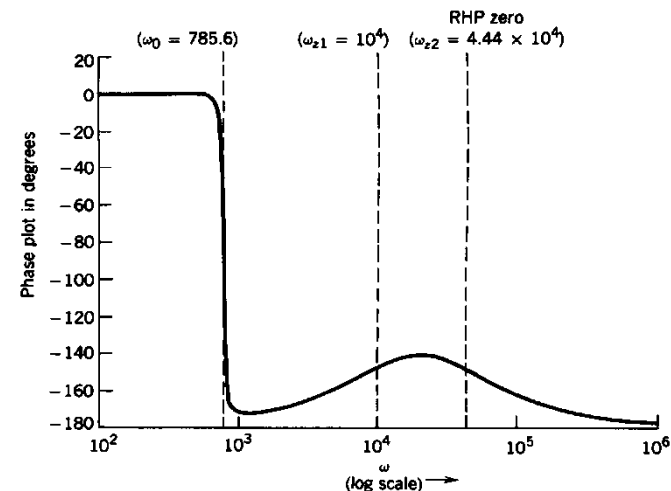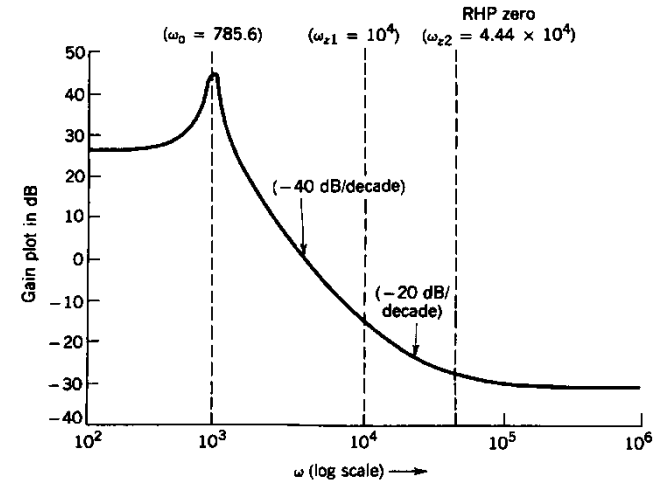


Linearizing the PWM Block

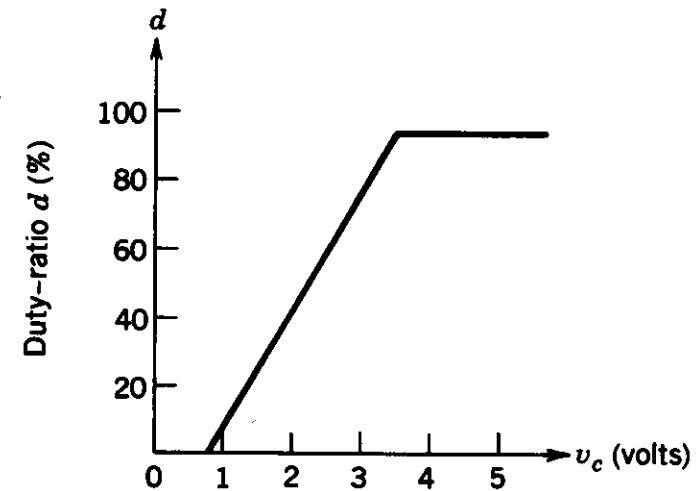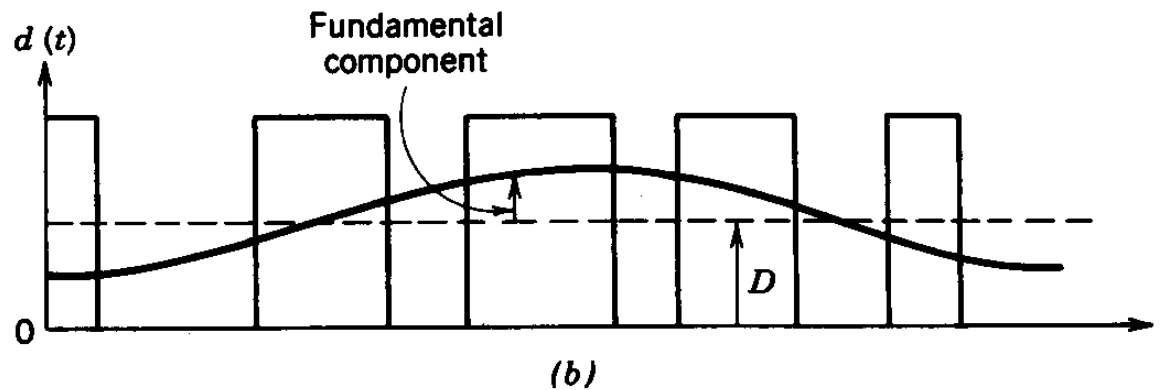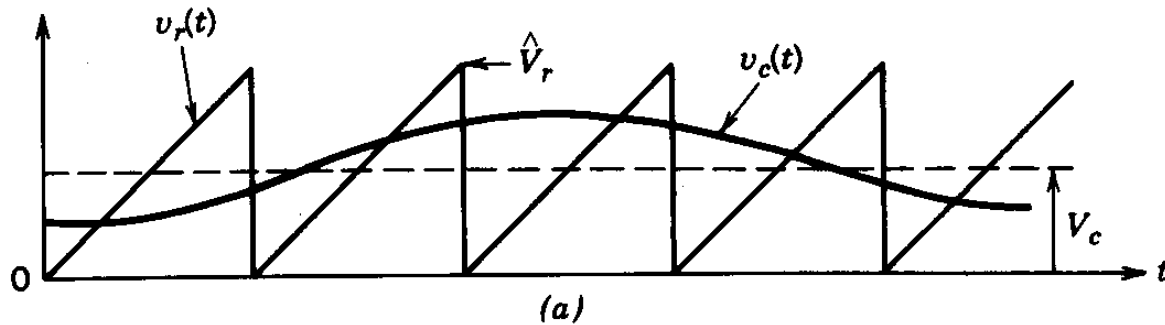



- ▶ The transfer function is essentially a constant with zero phase shift

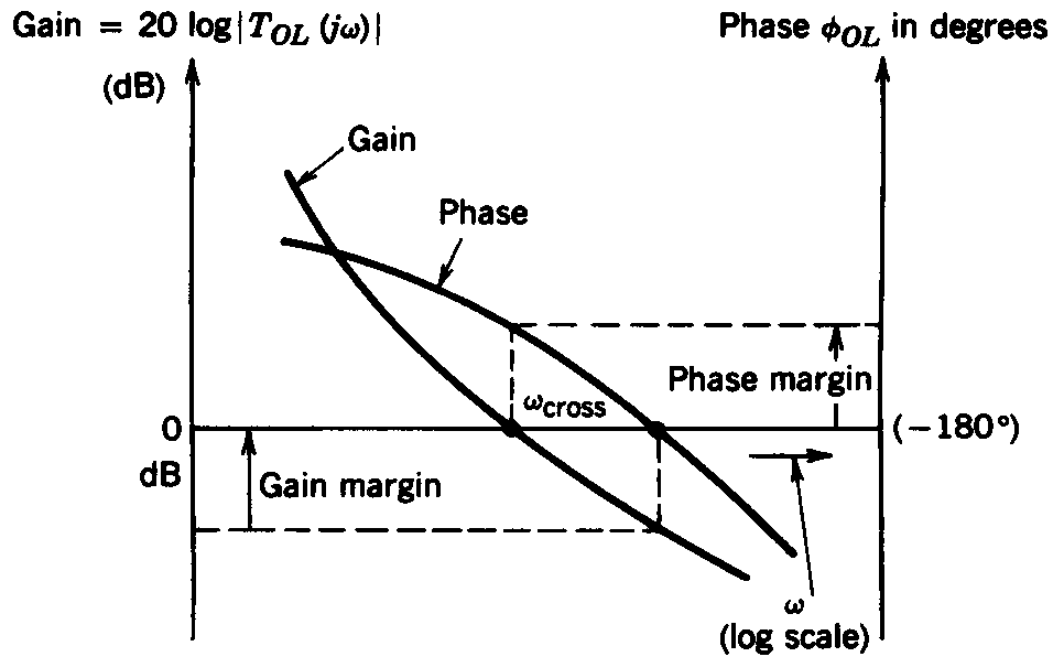Typical Gain and Phase Plots of the Open-Loop Transfer Function





- Definitions of the crossover frequency, phase and gain margins???

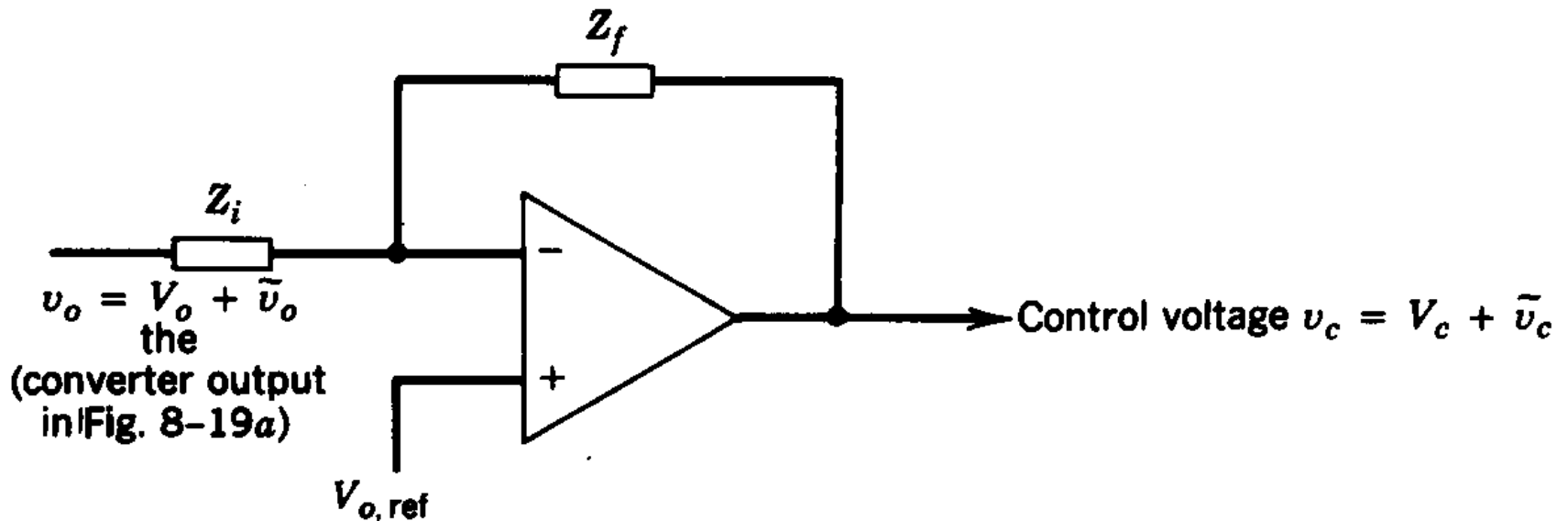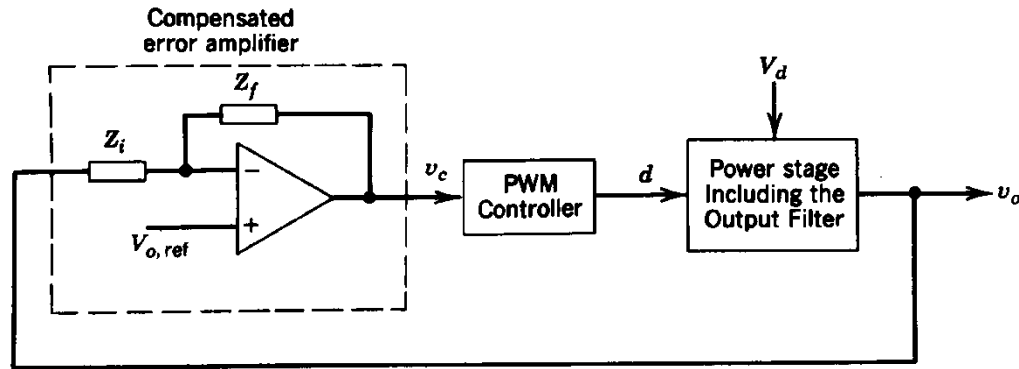A General Amplifier for Error Compensation




- Can be implemented using a single op-amp

Real type of error amplifier

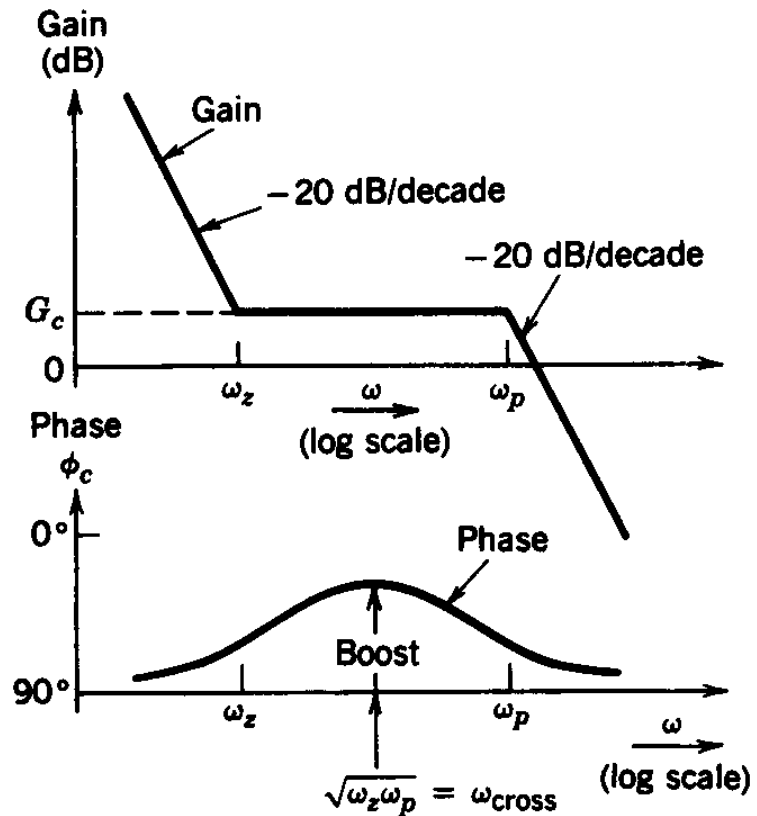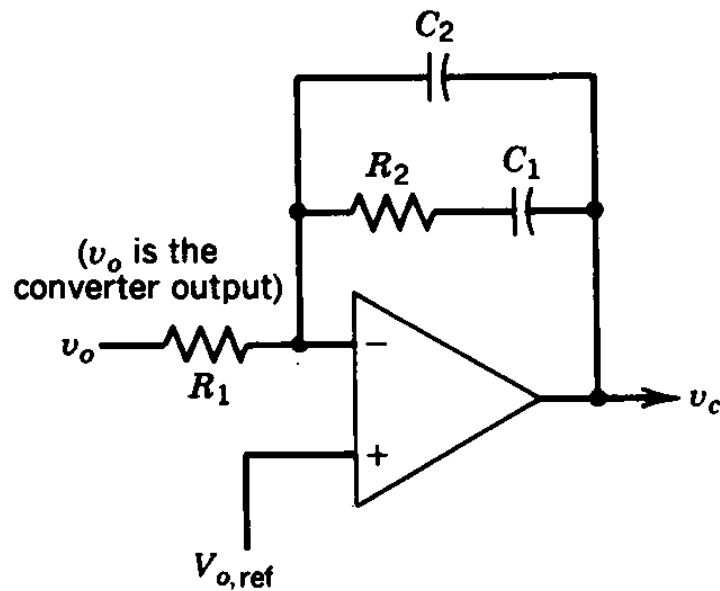


- Shows phase boost at the crossover frequency

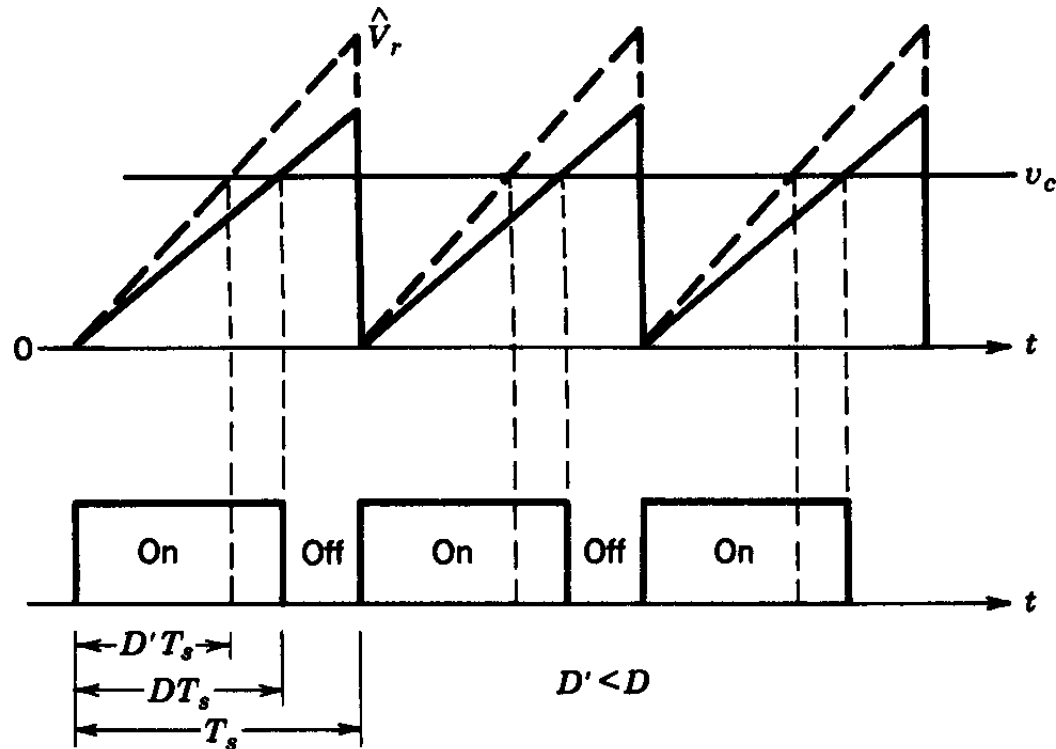Voltage Feed-Forward (when input voltage changes)




- Makes converter immune from input voltage variations

Voltage versus Current Mode Control

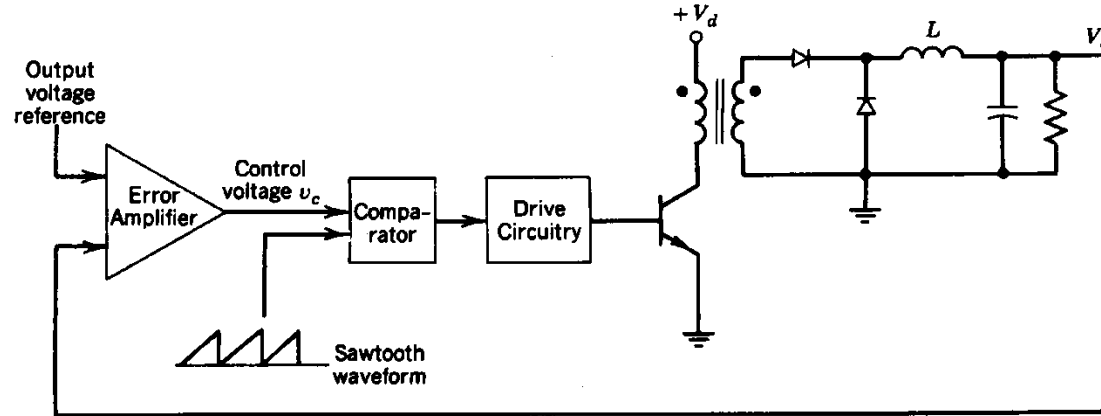




(a)

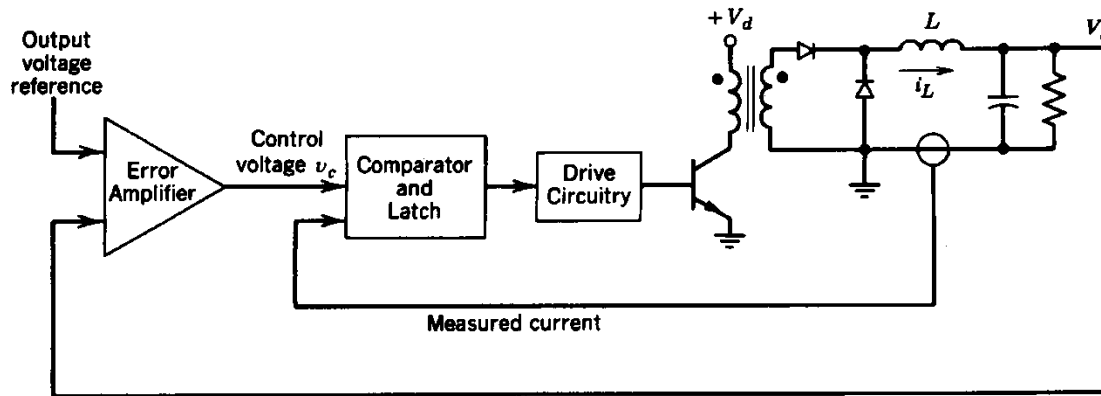

(b)


- ▶ Regulating the output voltage is the objective in both modes of control

Various Types of Current Mode Control

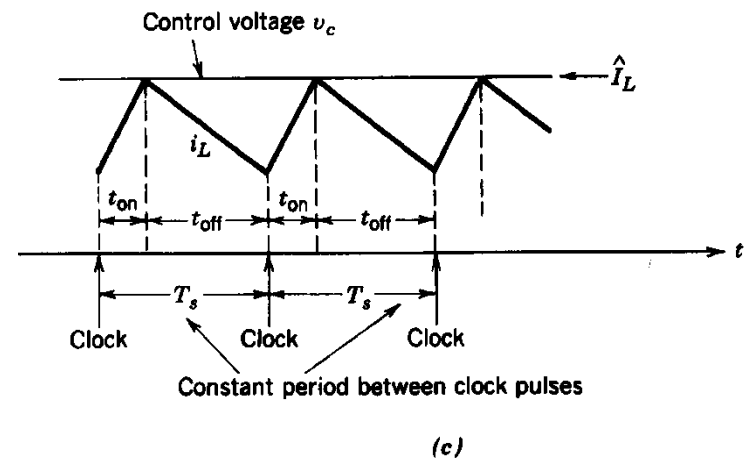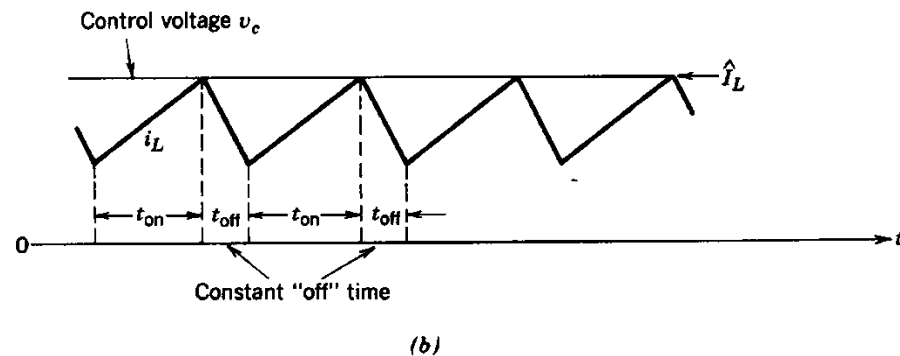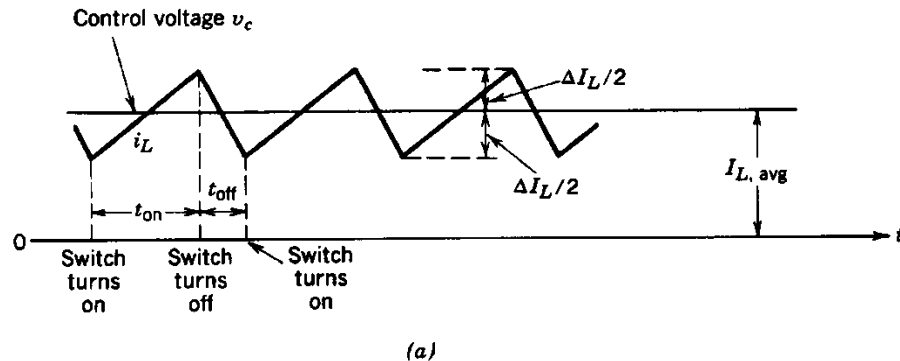

- ▶ a – tolerance band control, b – constant-off-time control, c – constant frequency with turn-on at clock time
- ▶ **Constant frequency, peak-current mode control is used most frequently**


Peak Current Mode Control

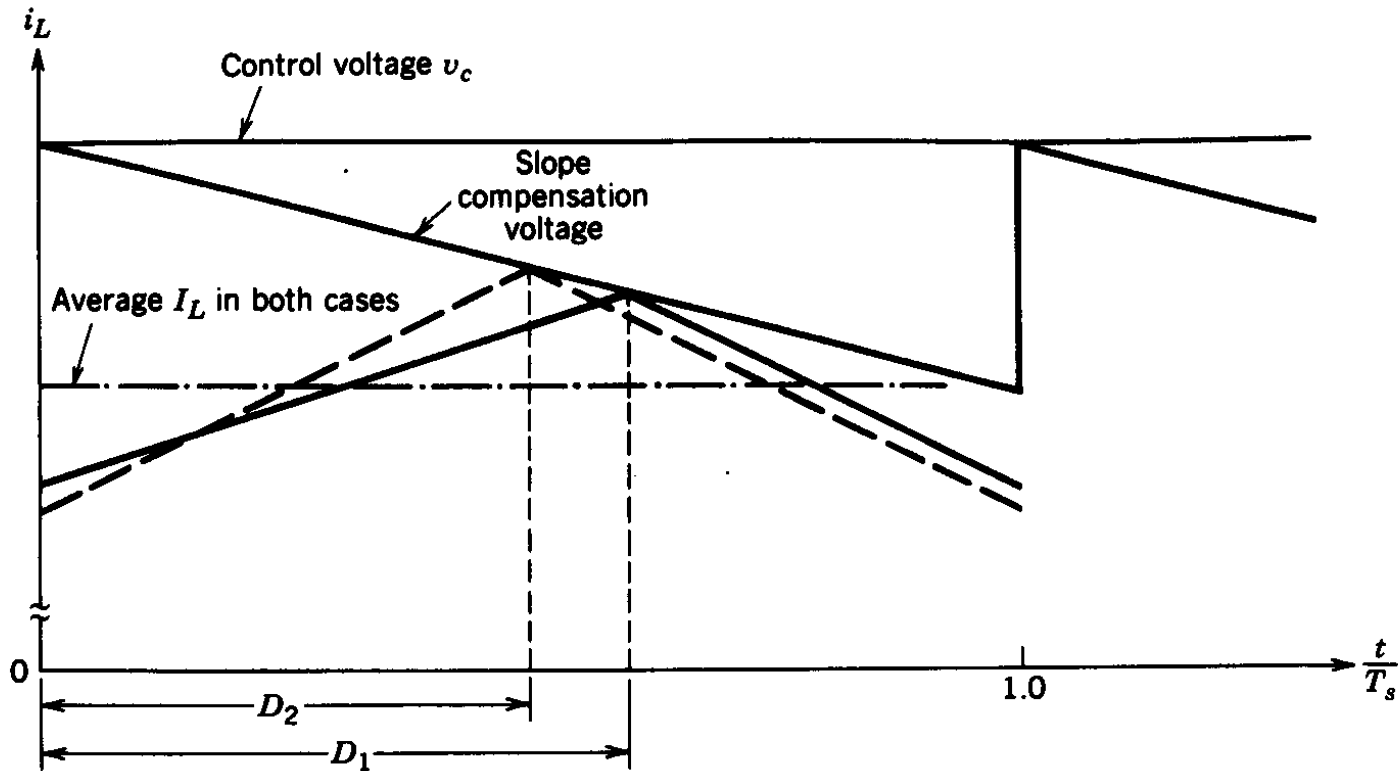


- Slope compensation is needed

A Typical PWM Control IC

BLOCK DIAGRAM

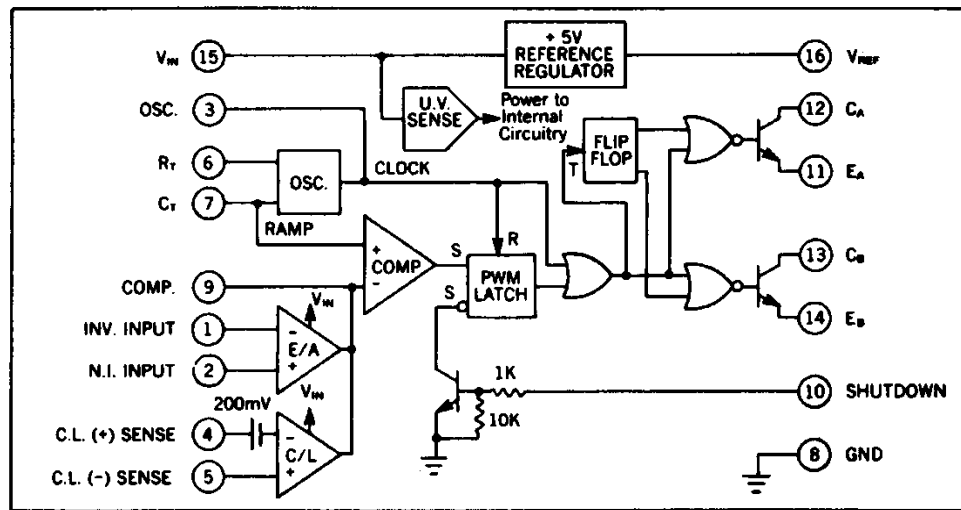


Pulse Width Modulator Transfer Function

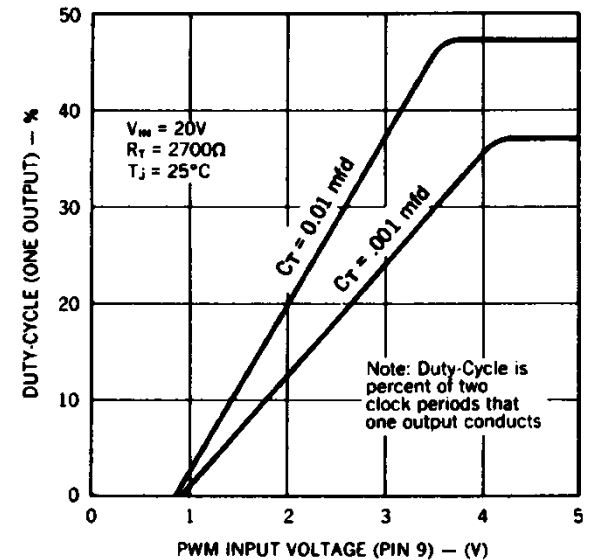

- Many safety control functions are built in


Current Limiting

- ▶ Constant current limiting


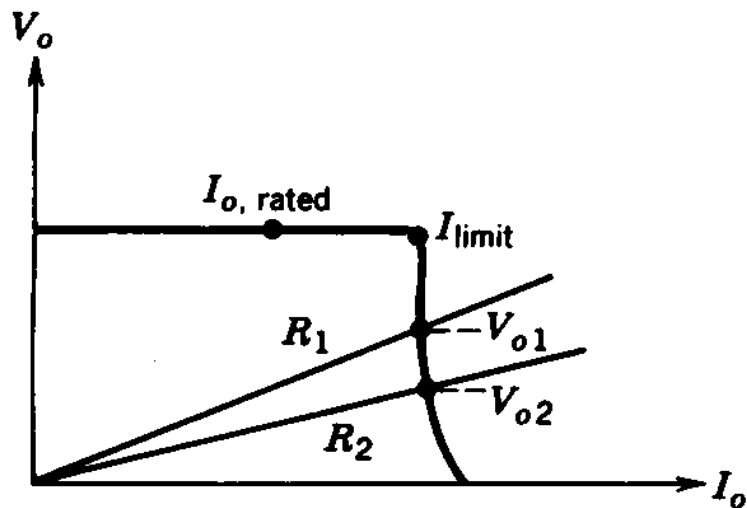


(a)


- ▶ Foldback current limiting

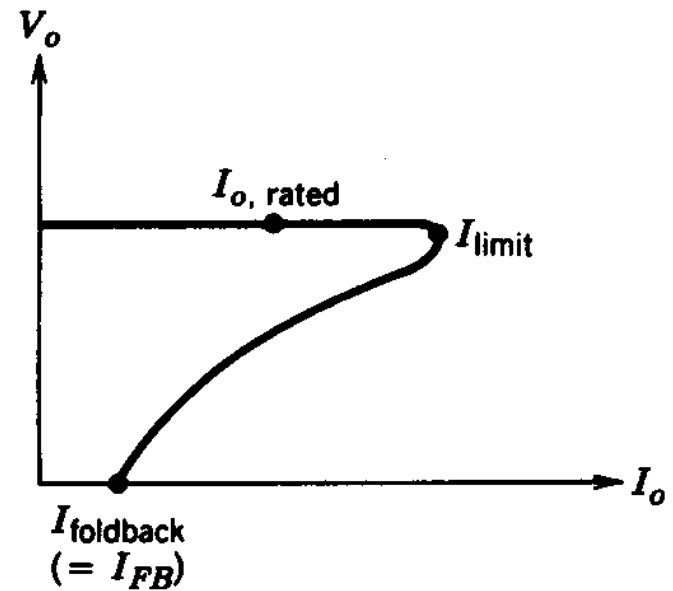

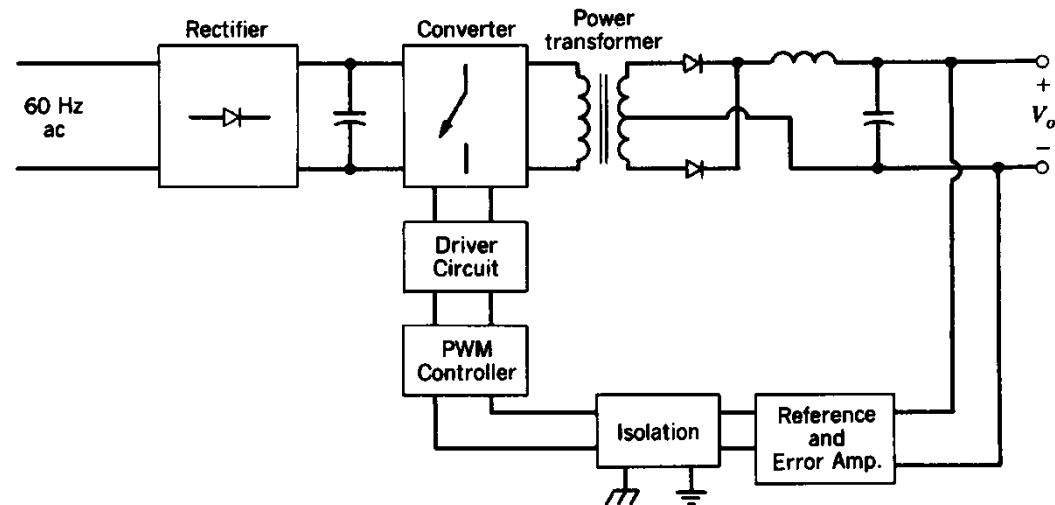
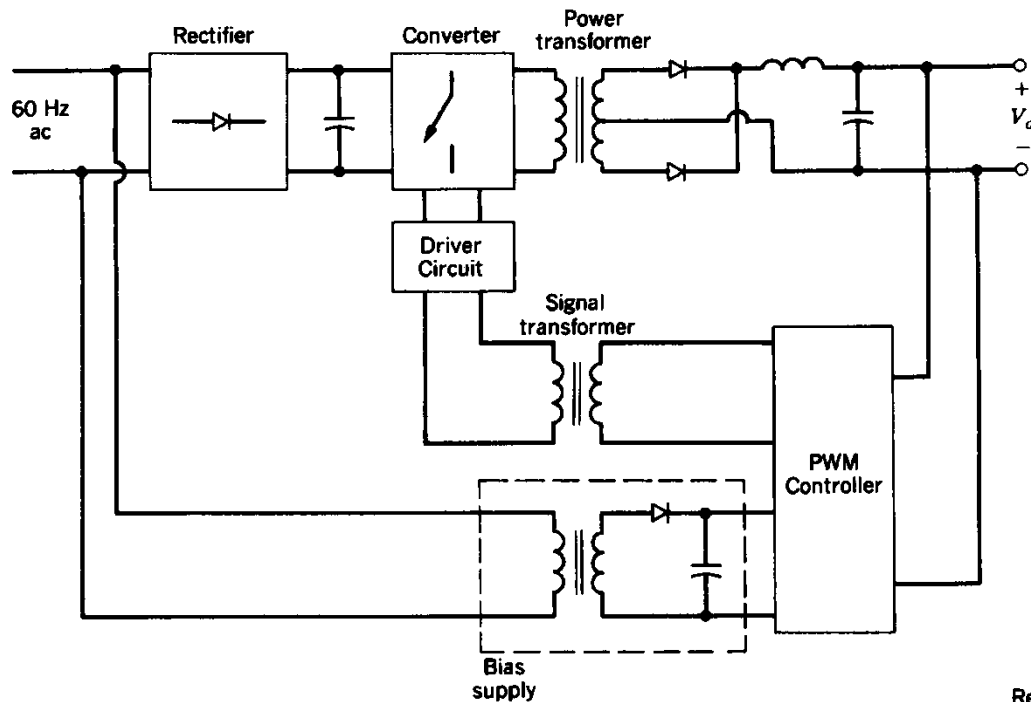
Implementing Electrical Isolation in the Feedback Loop



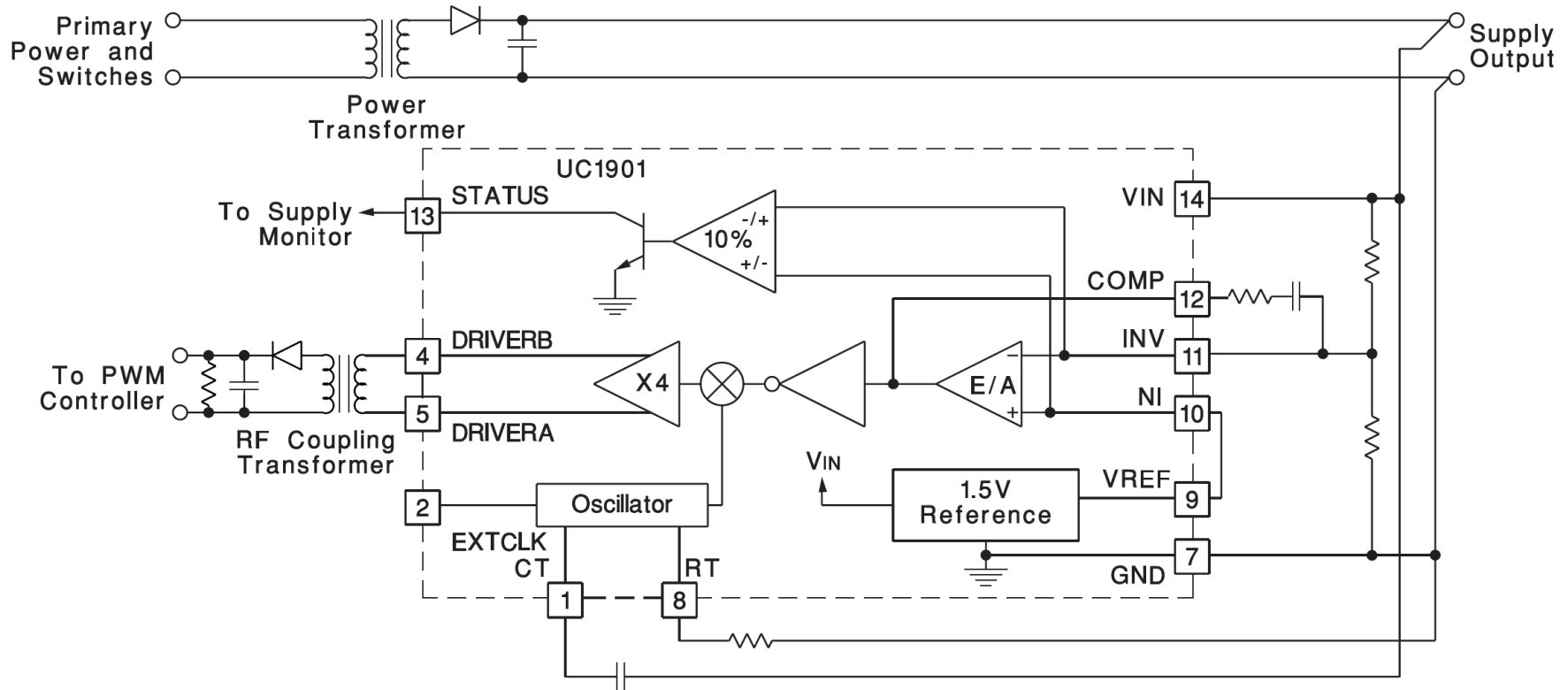Implementing Electrical Isolation in the Feedback Loop – practical approach UC1901




Input Filter

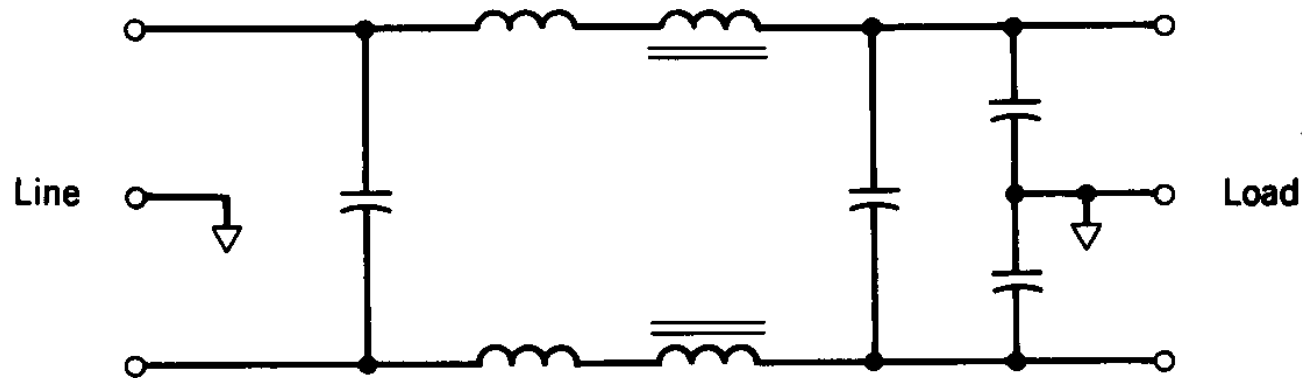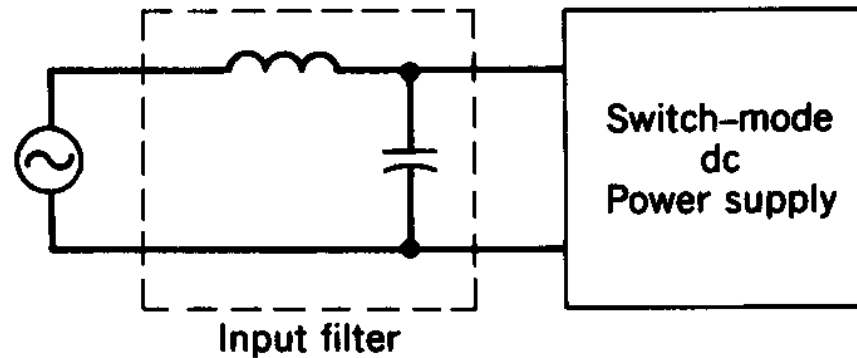



- ▶ Needed to comply with the EMI and harmonic limits


Viper22

fixed frequency off-line converter


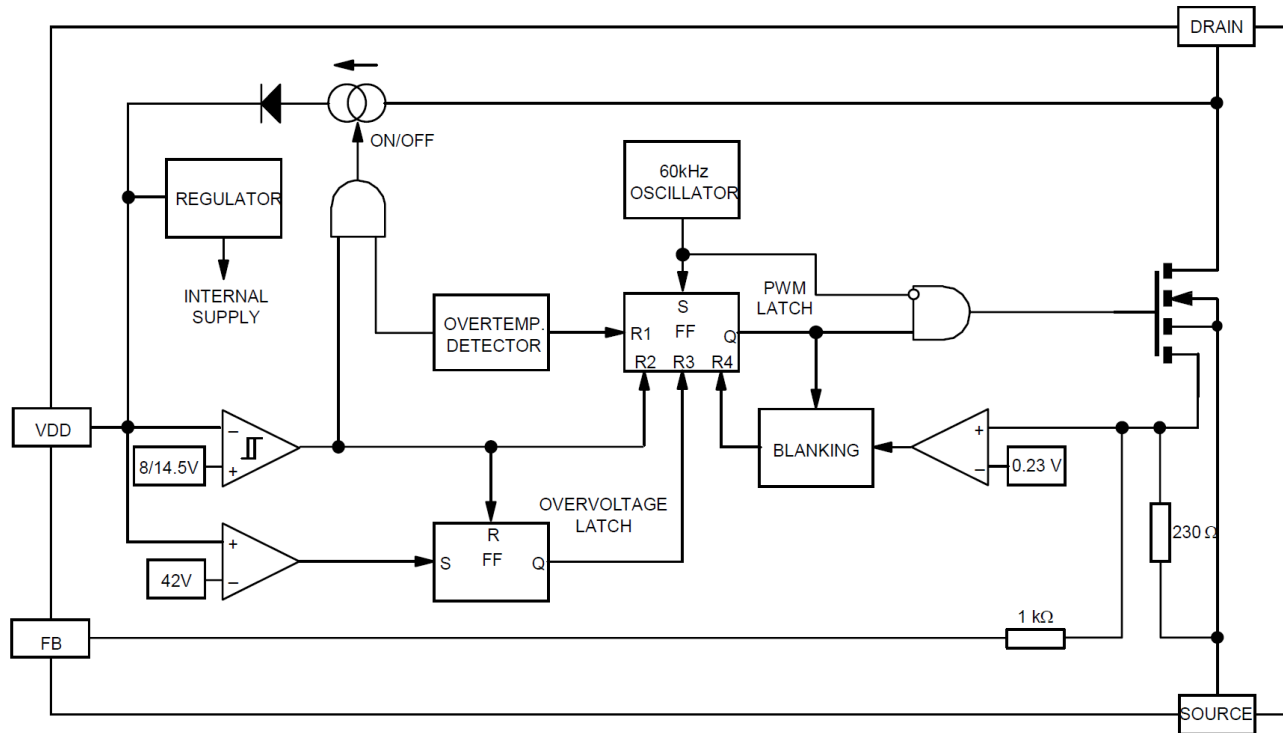


Viper simple nonisolated

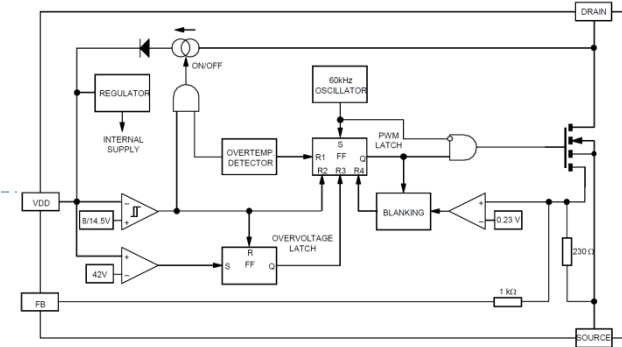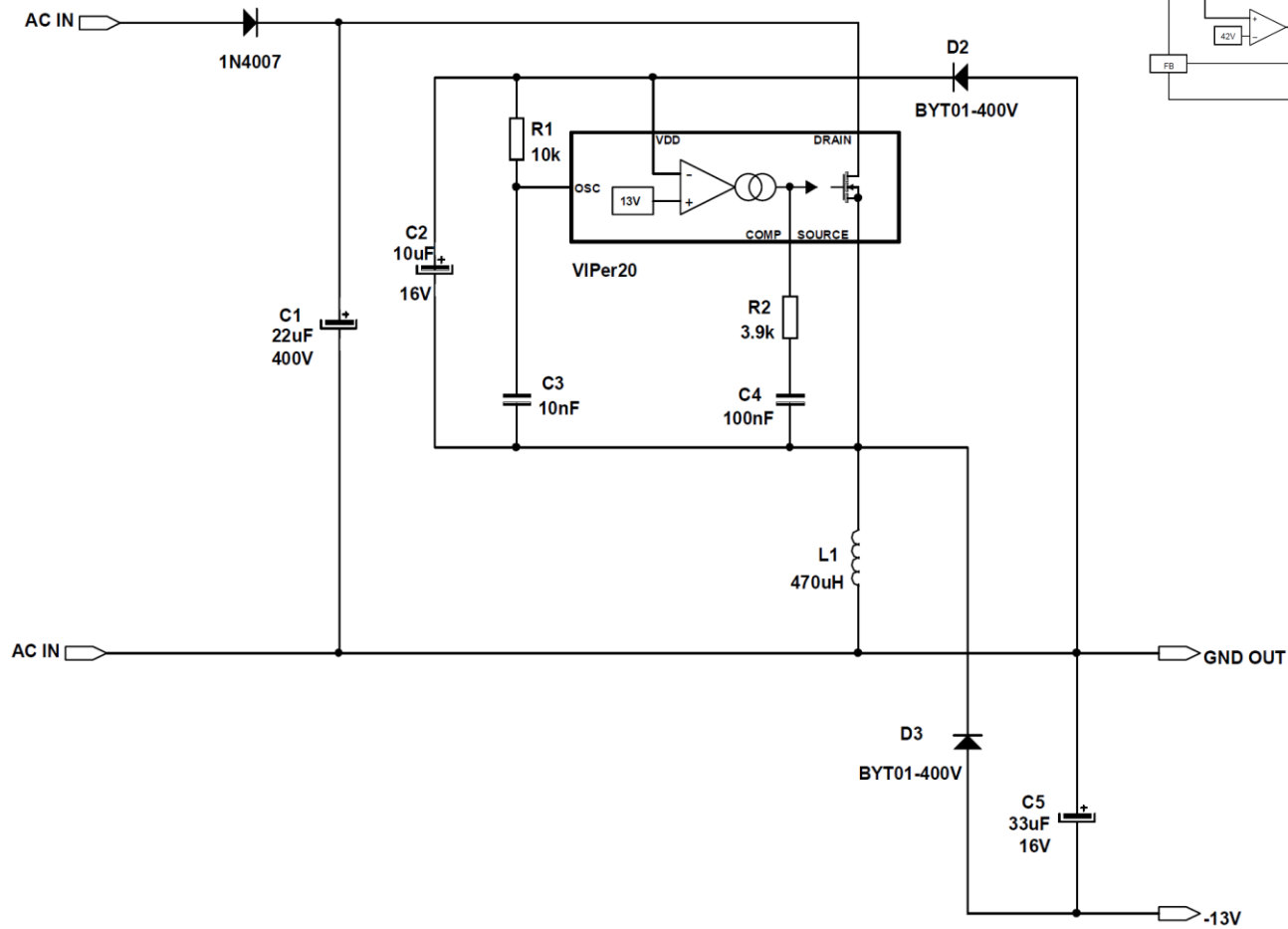

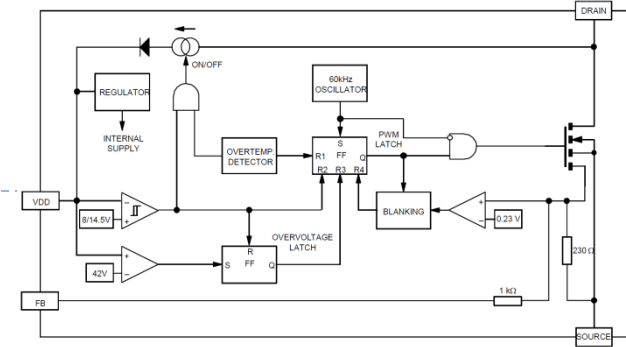

Viper simple

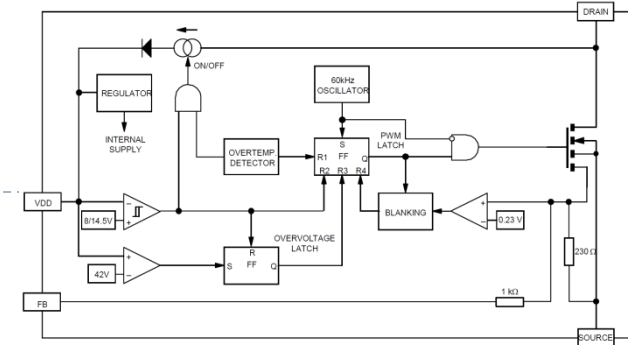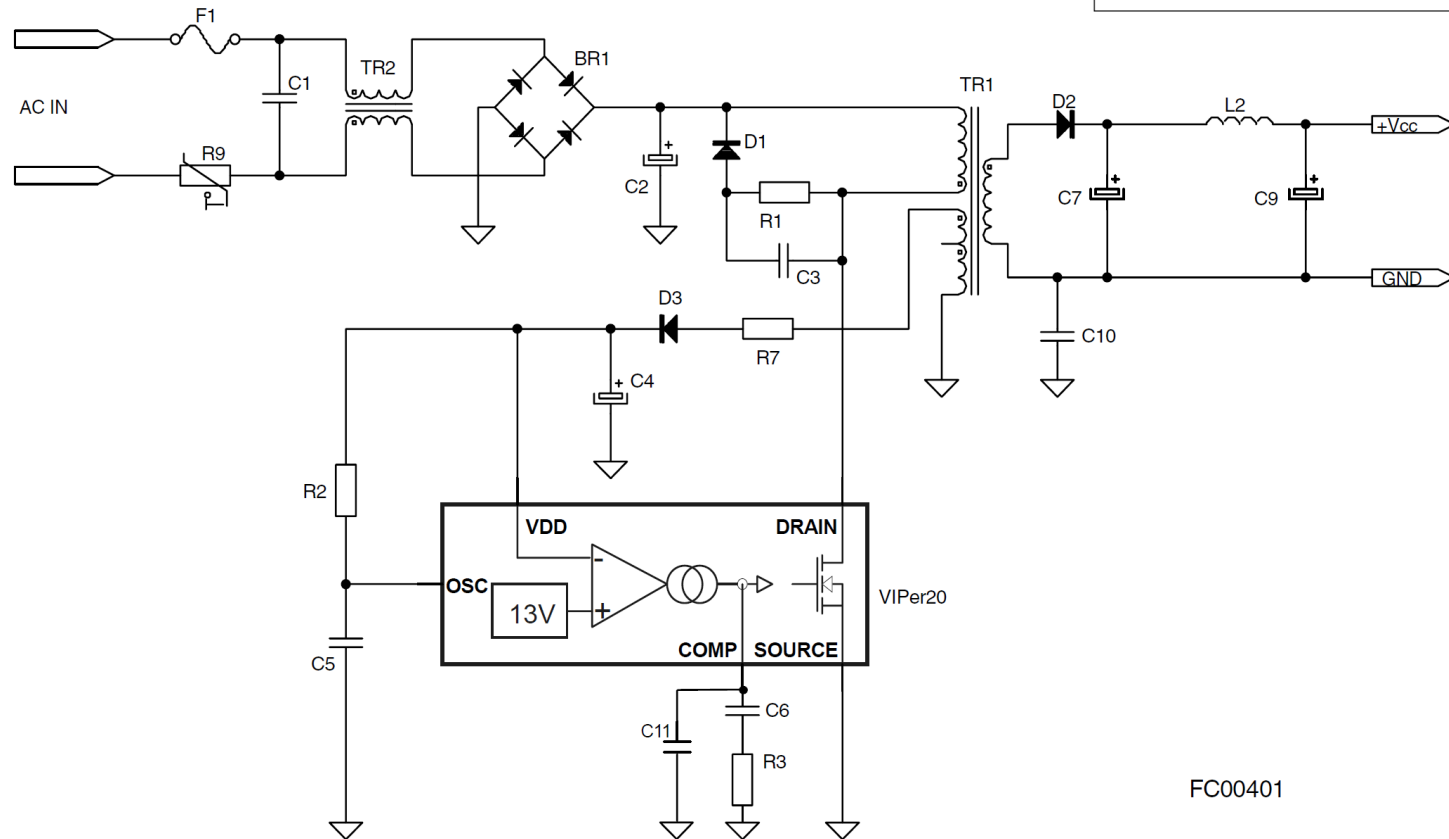

FC00401



Viper


low-cost universal DVD supply

Input	Output 1	Output 2	Output 3	Output 4	Output 5	Output 6
Universal line	5 V \pm 5% (1)	+12 V \pm 5% (1)	-12 V \pm 5% (1)	-26 V \pm 5% (1)	3.3 V \pm 5% (1)	5 V _{stb} \pm 5% (1)
Min. 85 V _{ac} Max. 265 V _{ac}	I _{min} . 20 mA I _{max} .1.5 A	I _{max} . 30 mA	I _{max} . 30 mA	I _{max} .50 mA	I _{max} . 150 mA	I _{max} .100 mA




Viper

low-cost universal DVD supply

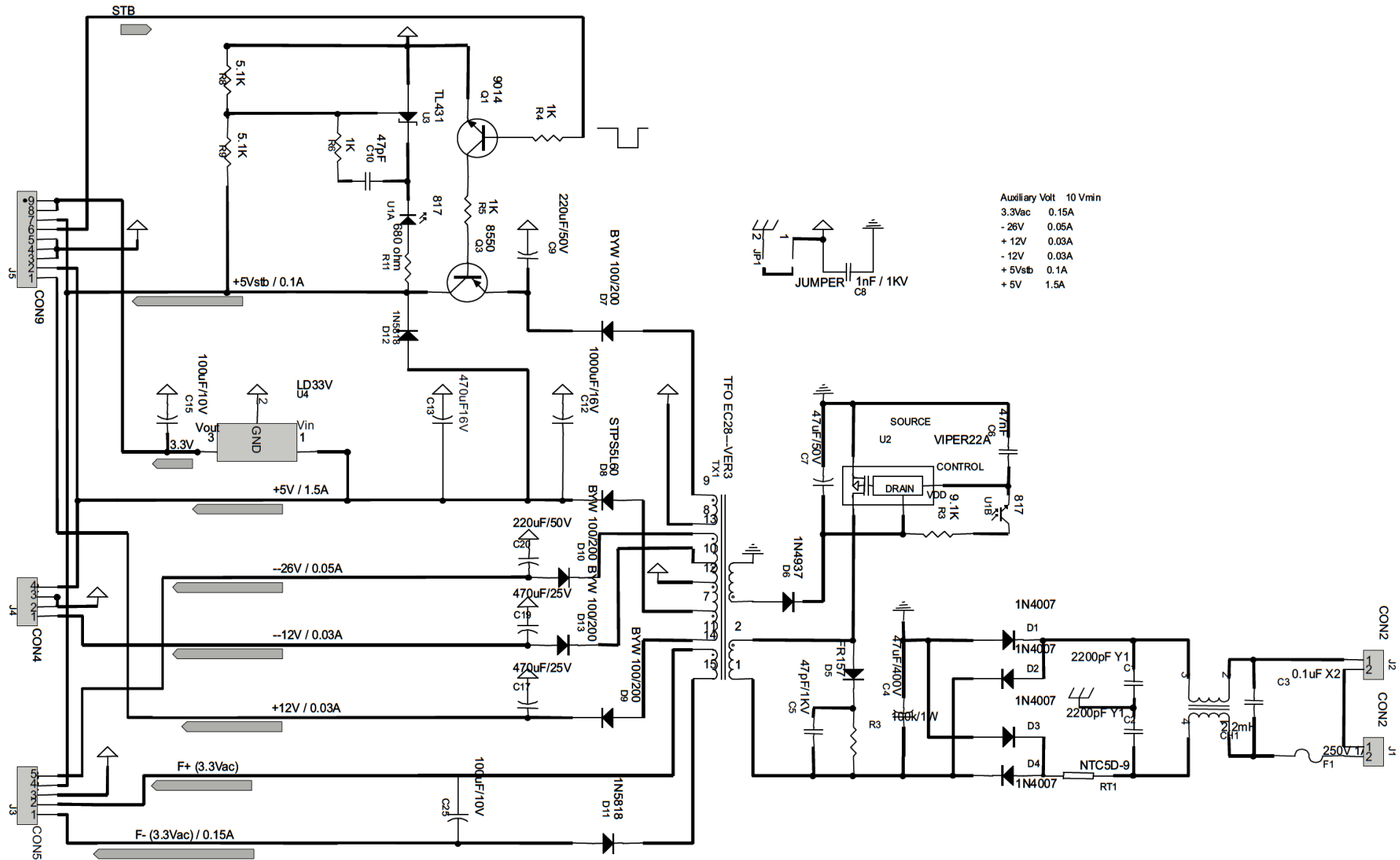

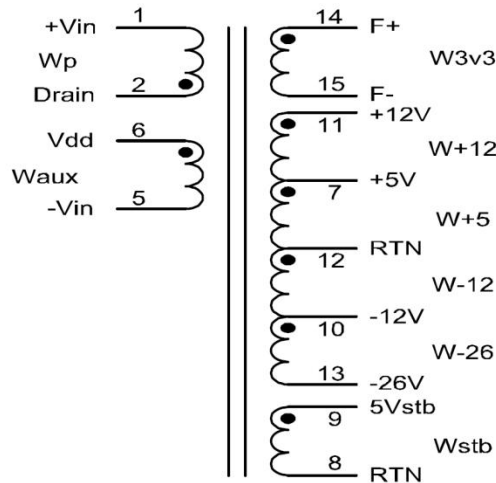Viper low-cost universal DVD supply – transformer





Primary inductance: $L_p = 2.8 \text{ mH}$ 1 kHz, 0.3V
Leakage inductance: $L_k < 28 \text{ uH}$ at secondary and auxiliary winding short (1 kHz, 0.3 V)
Core: EER28L
Bobbin: ER28 (6 + 9 pin)
Vendor: YuanDongDa electronics Co., Ltd

Layer description	Symbol	Start pin	End pin	Number of layers	Turns	Wire size (mm)
Primary	Wp	Pin 2	Pin 1	2	65	0.3
Out 1 (5 V/1.5 A)	W5	Pin 7	Pin 12	1	4	2*0.6
Out 2 (12 V/0.0 3 A)	W12	Pin 11	Pin 7	1	5	0.3
Out 3 (-12 V/0.0 3 A)	W-12	Pin 12	Pin 10	1	9	0.45
Out 4 (-26 V/0.05 A)	W-26	Pin 10	Pin 13	1	10	0.3
Out 5 (5 V _{stb} /0. 1 A)	Wstb	Pin 9	Pin 8	1	12	0.3
Out 6 (3. 3V/0.15 A)	W3v3	Pin 14	Pin 15	1	3	0.3
Auxiliary	Waux	Pin 6	Pin 5	1	24	0.3

Barrier (3 mm)									
		12	7	10	13	15	8	5	
Wp		W5	W12	W-12	W-26	W3v3	Wstb	Waux	
2	1	7	11	12	10	14	9	6	
Barrier (3 mm)									
Bobbin									

Viper low-cost universal DVD supply

– PCB layout

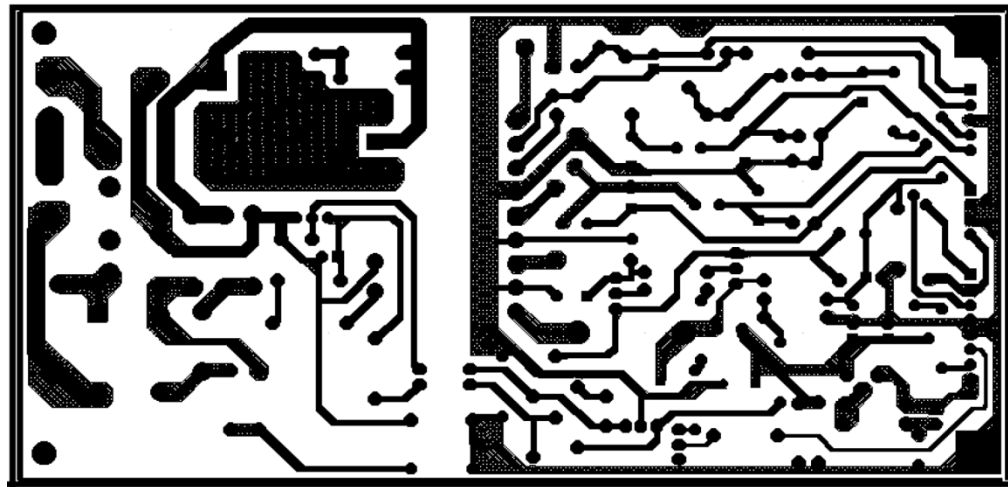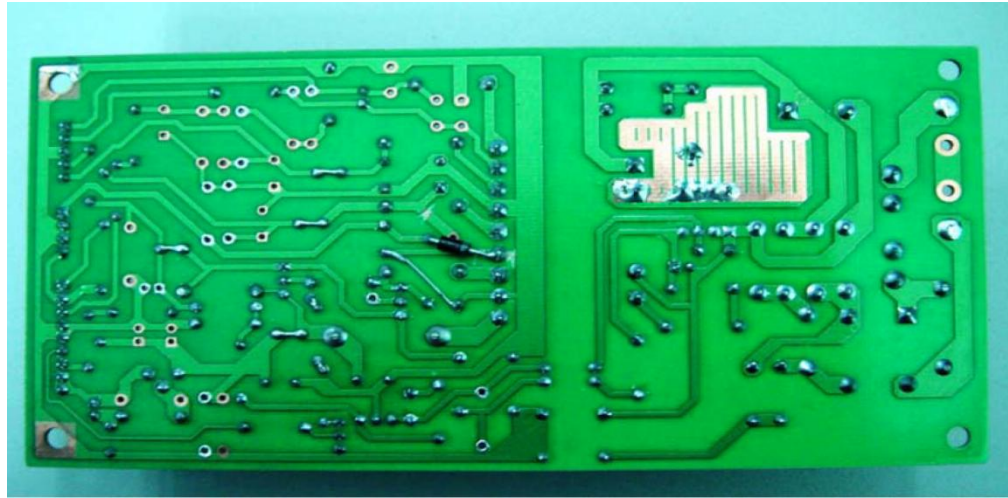

Homework

- ▶ Przeanalizować aplikacje
 - ▶ TOP221
 - ▶ MC33369