


Real Time Logic Simulator

Jari Komppa
March 27, 2008

Outline

- Development of the idea
- Development process
- The result

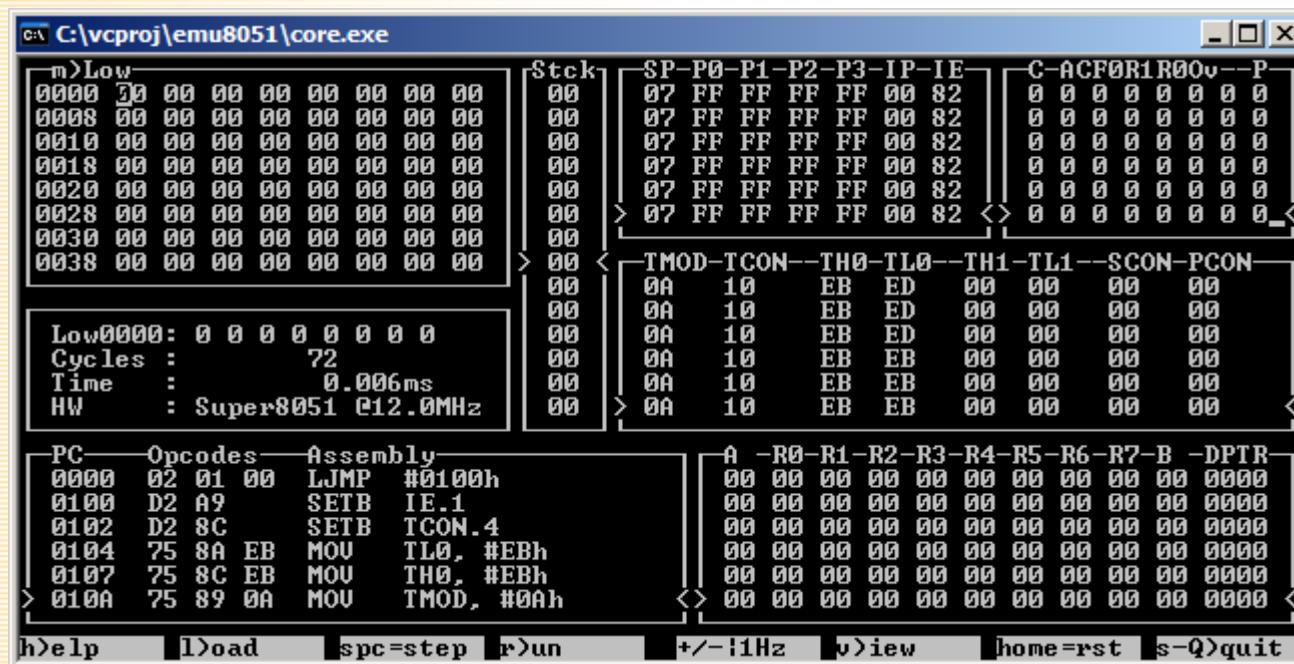- Original idea: graphical UI to my 8051 simulator (which is a console application)



- <http://iki.fi/sol/8051.html>

- The original simulator had a 'logic board' view – LEDs, buttons, other peripherals..

C:\vcproj\emu8051\core.exe

Logic board view


P0	1 2 3 4 5 6 7 8	P0.0/1: 00h	P2.0/1: 00h
*	* * * * * * *	P0.2/3: 00h	P2.2/3: 00h
0	0 0 0 0 0 0 0 0	P0.4/5: 00h	P2.4/5: 00h
P1	* * * * * * *	P0.6/7: 00h	P2.6/7: 00h
*	0 0 0 0 0 0 0 0	P1.0/1: 00h	P3.0/1: 00h
P2	* * * * * * *	P1.2/3: 00h	P3.2/3: 00h
*	0 0 0 0 0 0 0 0	P1.4/5: 00h	P3.4/5: 00h
P3	* * * * * * *	P1.6/7: 00h	P3.6/7: 00h
*	0 0 0 0 0 0 0 0		

->< 8bit shift registers >

h>elp l>oad s>pc=step r>un +/-1Hz v>iew h>ome=rst s-Q>quit




'Logic board' stole the show

```
C:\vcproj\emu8051\core.exe
m>Low
0000 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
0008 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
0010 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
0018 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
0020 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
0028 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
0030 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
0038 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
Low0000: 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0
Cycles : 72
Time : 0.006ms
HW : Super8051 @12.0MHz
PC Opcodes Assembly
0000 02 01 00 LJMP #0100h
0100 D2 A9 SETB IE.1
0102 D2 8C SETB TCON.4
0104 75 8A EB MOU TL0, #EBh
0107 75 8C EB MOU TH0, #EBh
010A 75 89 0A MOU TMOD, #0Ah
h>help l>load s>pc=step r>un +/-1Hz v>iew home=rst s-Q>quit
```

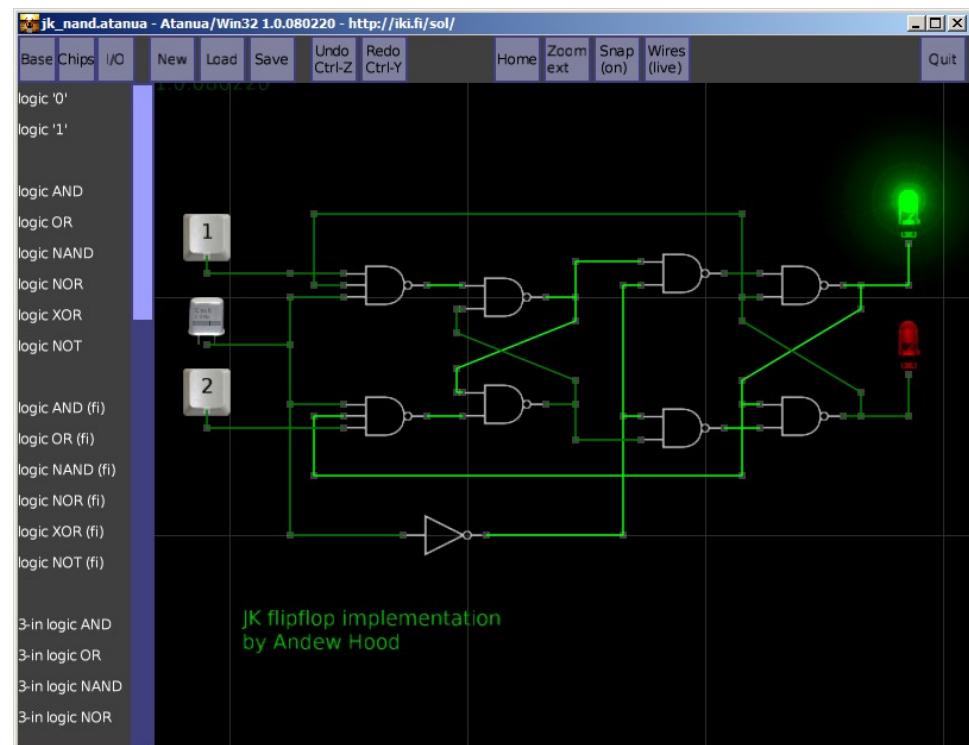


Atanua


Real time logic simulator

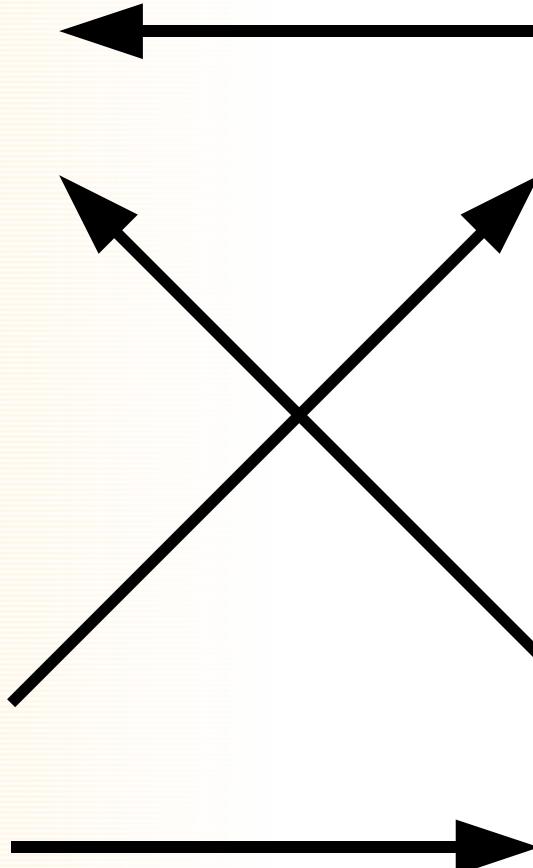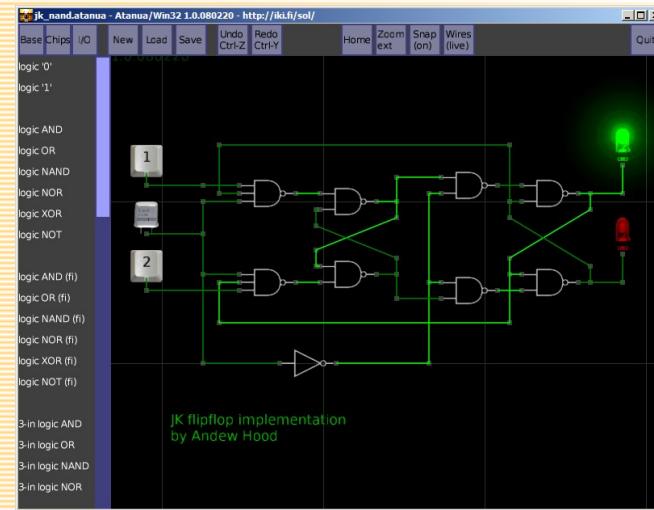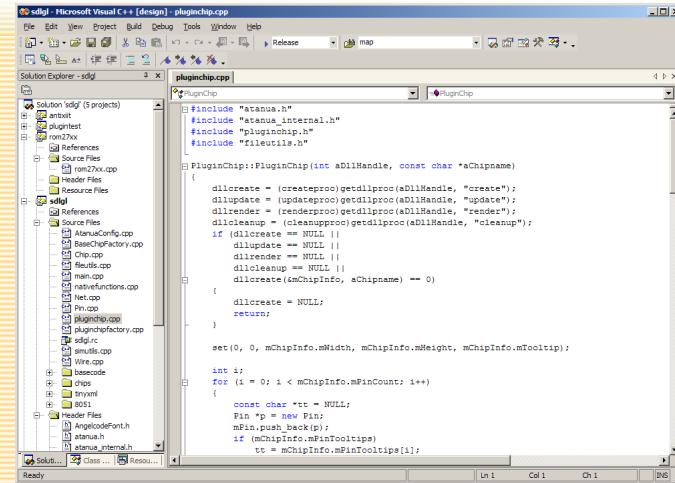



```
[screen 0:bash] jarikom@shell:~  
$ Ludum Dare - http://www.imitationpickles.org/ludum/ - LD11 - April 18-20 - Yaay!  
18:25 < fydo> drZool: rock on  
18:25 < drZool> yeah!  
18:26 < drZool> never done something like this before, scary and releeefing at  
        the same time  
18:33 !- mark [mark@e-71-231-111-167.hsd1.wa.comcast.net] has joined  
        #ludumdare  
18:33 !- mode/#ludumdare [+o mark] by X3  
18:38 !- hamumu [chatzilla#72-173-105-105.cust.wildblue.net] has joined  
        #ludumdare  
18:38 !- mode/#ludumdare [+o hamumu] by X3  
19:04 < X-Out> drzool: I have  
19:04 < X-Out> drzool: I ended up out of work :)  
19:10 < LoneStranger> :(  
19:26 < fydo> meow  
19:54 !- _kohai [_kohai567gar13-3-82-240-80-106.fbx.proxad.net] has joined  
        #ludumdare  
19:59 < Sol_HSA> say something funny, I'm going to take a screenshot of irc for  
        my presentation.. =)  
20:01 < _kohai> i love G.W. Bush !  
20:02 < _kohai> is it funny enough ? :)  
20:04 < Falkoni> something funny!  
[20:07] {Sol_HSA(+i)} {4:#ludumdare(+nst)} [Act: 3.5]  
[#ludumdare] green
```

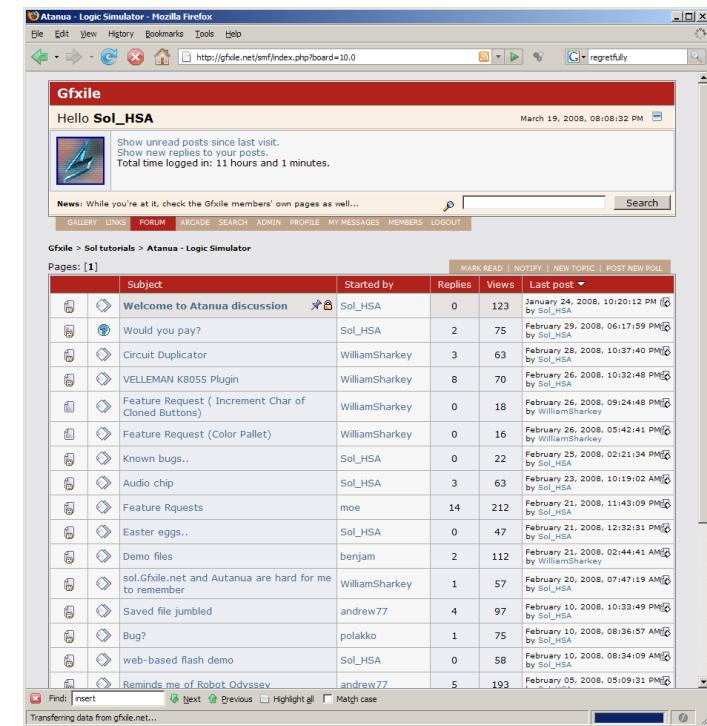


Simulated components

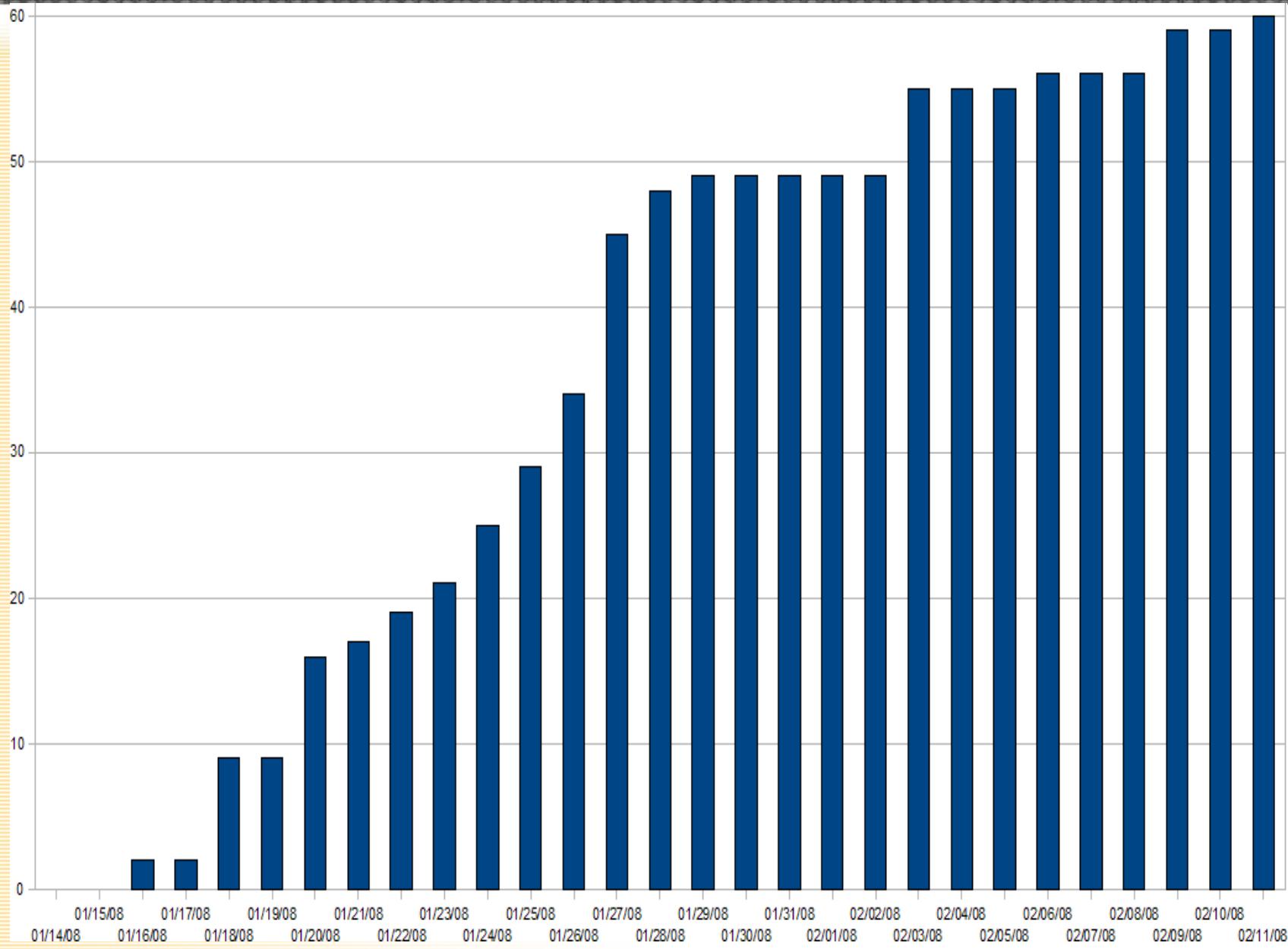


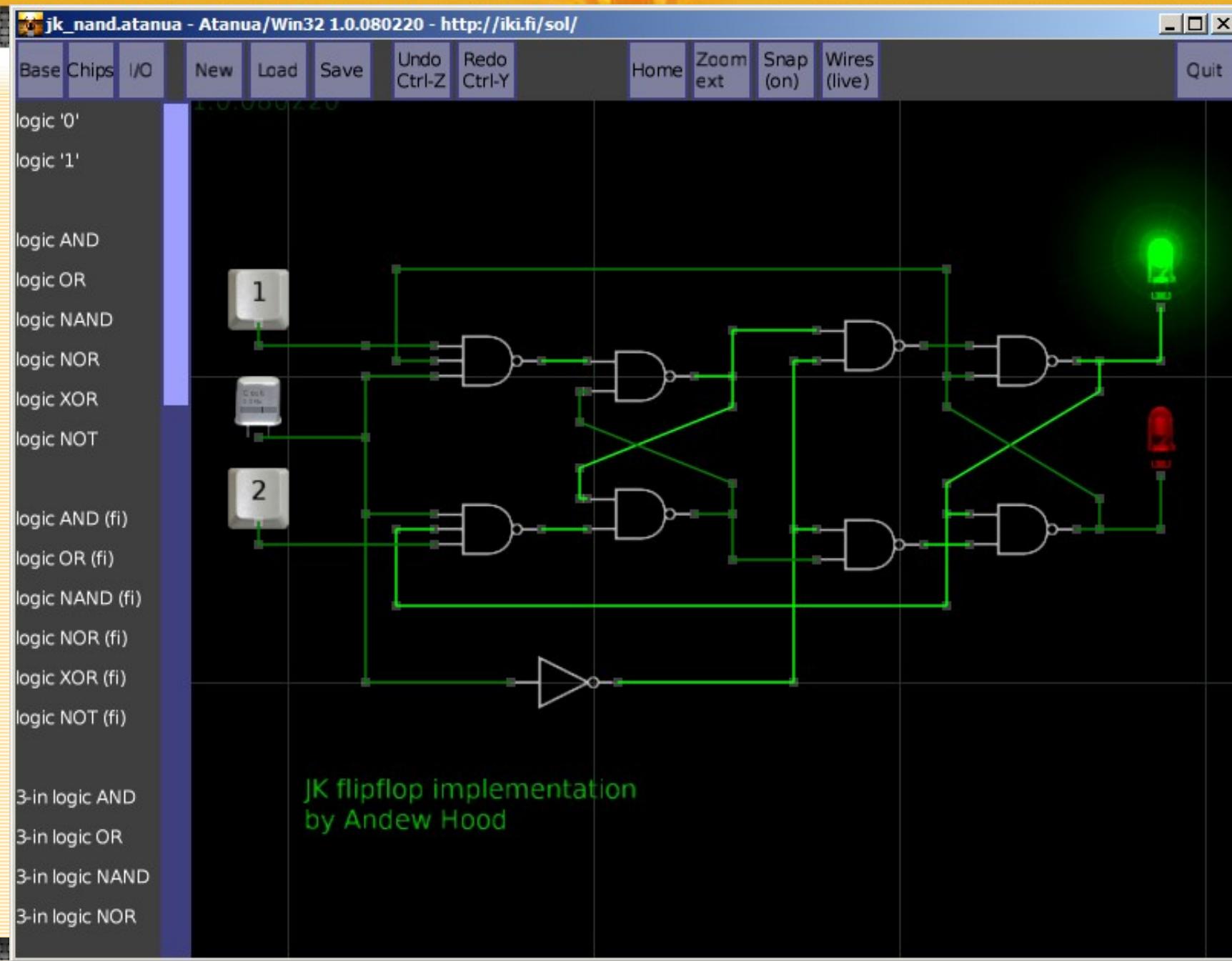

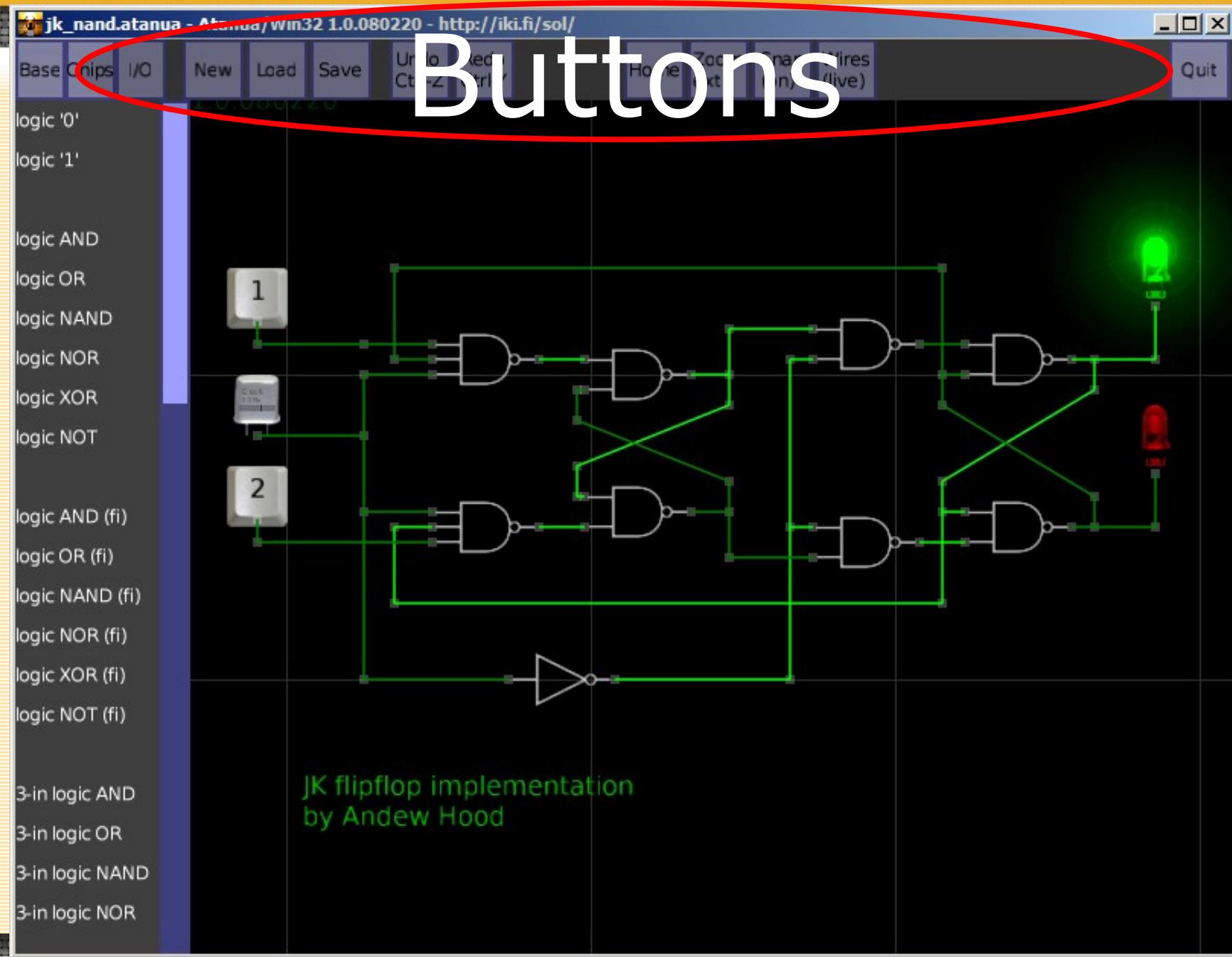

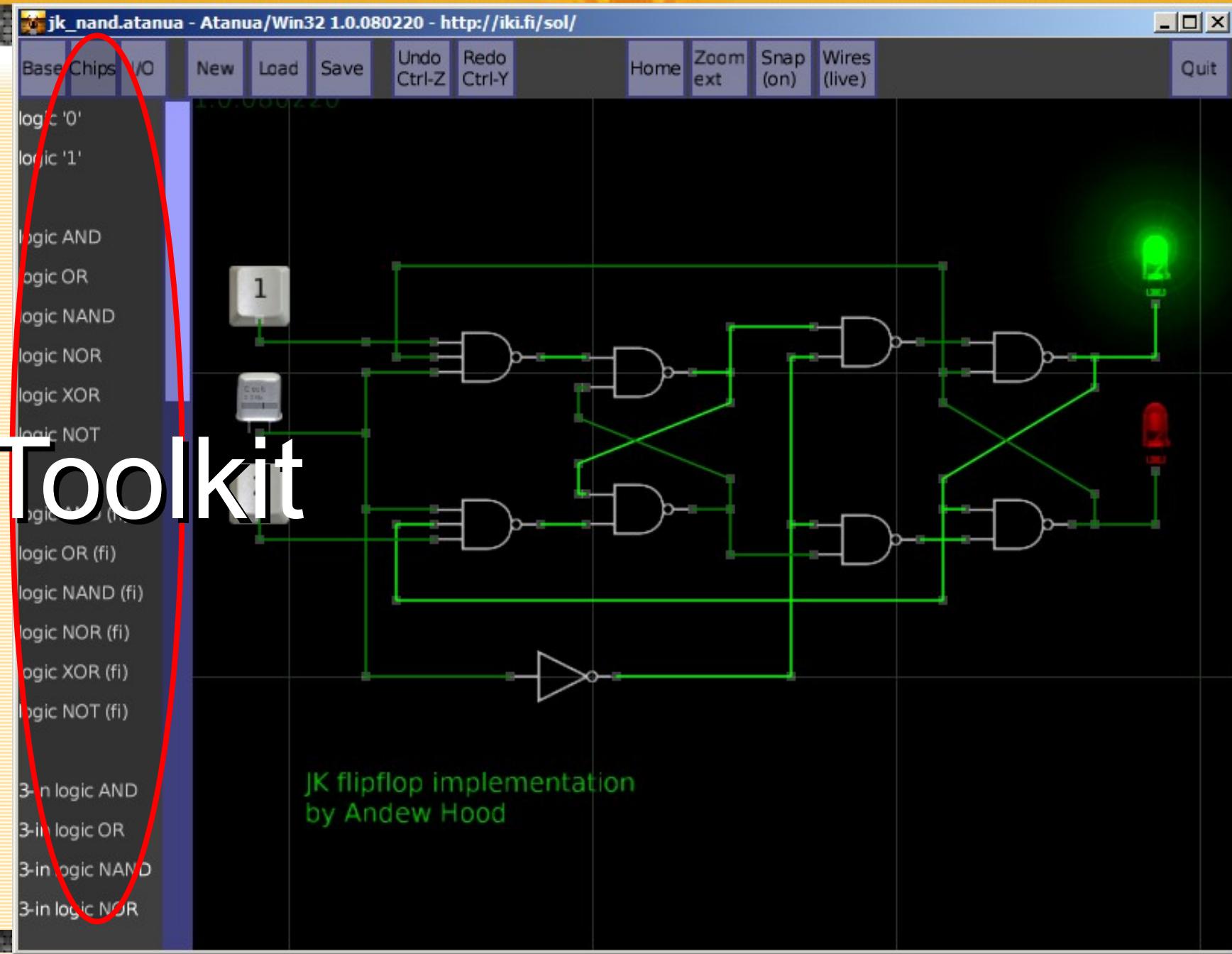

Toolkit

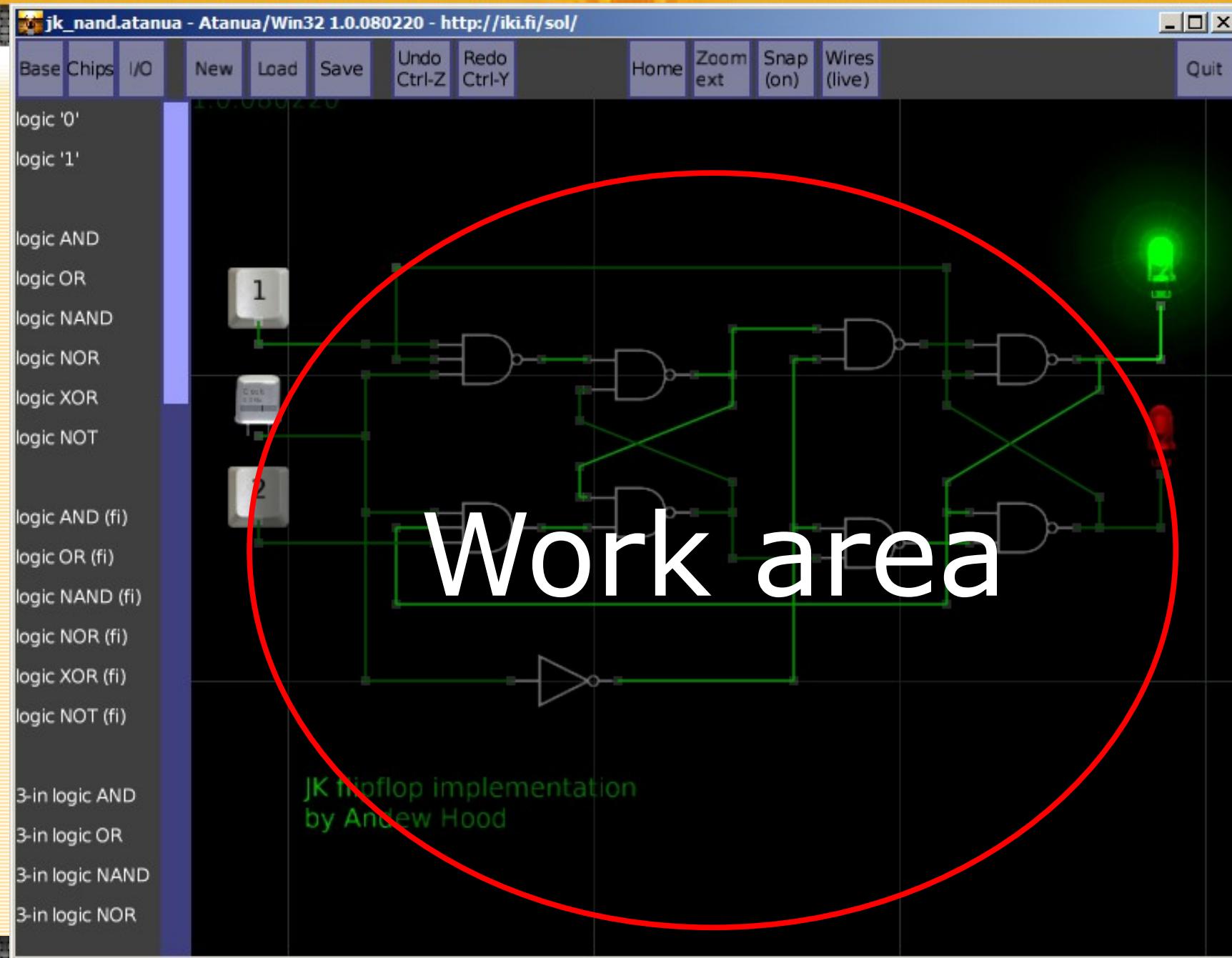



Demo..

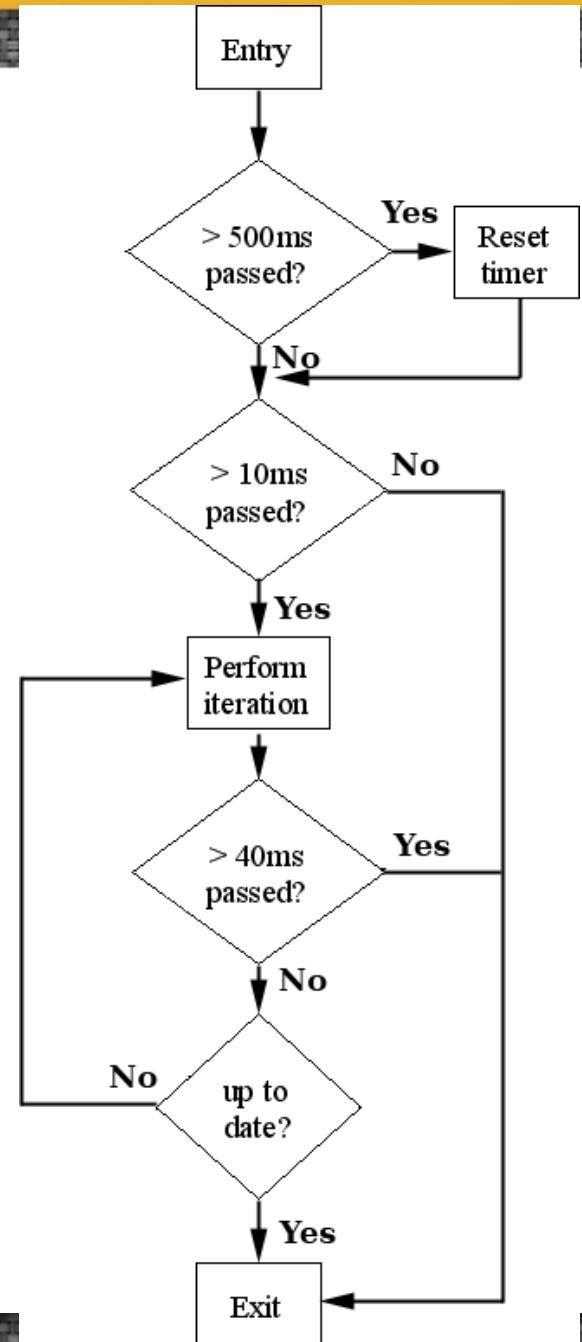Questions?

- Atanua: <http://www.atanua.org>
- My site: <http://iki.fi/sol/>
- 8051 emu: <http://iki.fi/sol/8051.html>

- Back-up slide:
Implementation of the
real-time logic simulation
- Logic simulation loop runs
at 1000Hz regardless of
graphics frame rate.



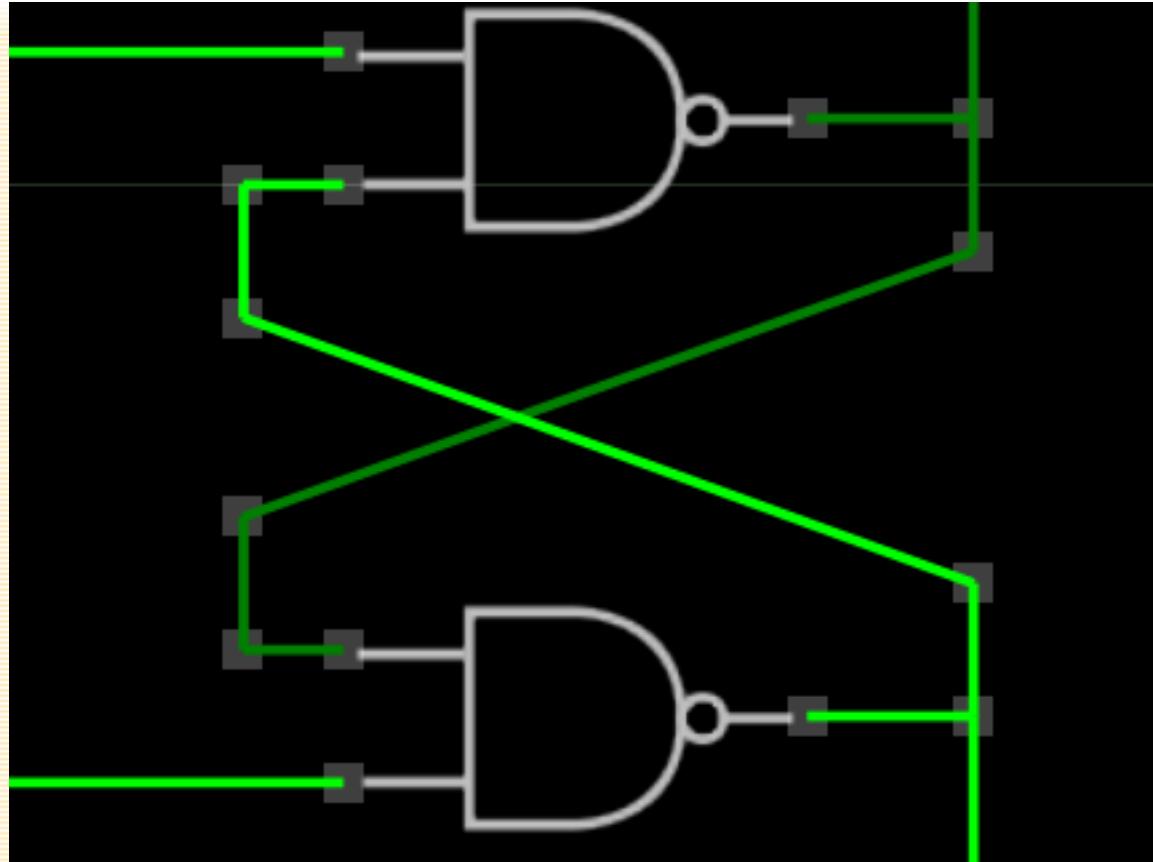

- Back-up slide:
Problematic cross-connections